


Quiz Average 7.60

Quiz High Score 10

PH 221

Quiz # 04 (10 pts)

Name Solution

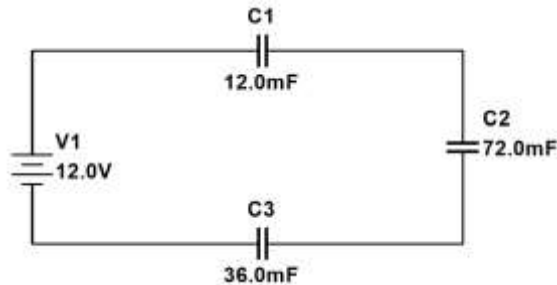

In the circuit on the left, what is the total capacitance attached to the power source?

- A. 120. mF B. 8.00 mF C. 0.125 mF D. 8.33 μ F


Capacitors in series!

$$\frac{1}{C_{Total}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} = \frac{1}{12.0 \text{ mF}} + \frac{1}{72.0 \text{ mF}} + \frac{1}{36.0 \text{ mF}} = \frac{6 + 1 + 2}{72.0 \text{ mF}} = \frac{9}{72.0 \text{ mF}}$$

$$C_{Total} = \frac{72.0 \text{ mF}}{9} = 8.00 \text{ mF}$$

So, the correct answer is B !

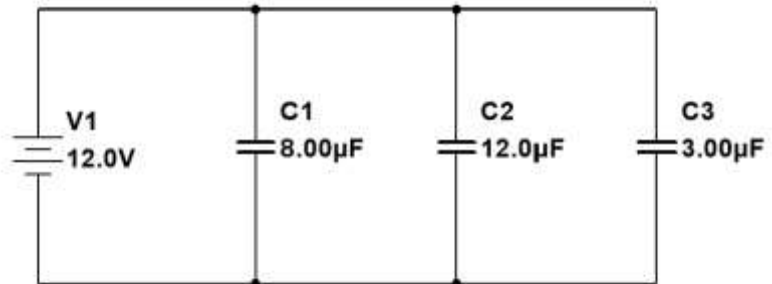In the circuit on the right, what is the charge found on Capacitor C_3 after the circuit has been connected for a long time?




- A. 276. μ C B. 22.2 μ C C. 4.00 μ C D. 36.0 μ C

Since this is a parallel circuit all capacitors have the same voltage across them, so the charge on C_3 is found from:

$$Q_3 = C_3 V_3 = (3.00 \mu\text{F})(12.0 \text{ V}) = 36.0 \mu\text{C}$$

So, the correct answer is D !

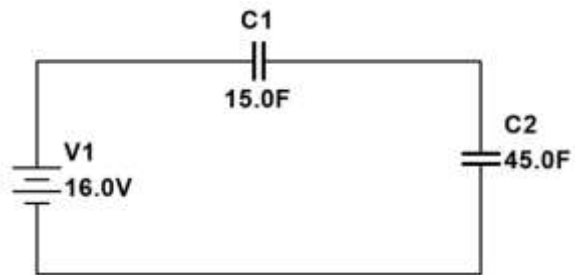Consider the circuit shown on the right. Assume the circuit has been connected for a long time so that the capacitors are fully charged. What is the energy stored in the capacitor C_2 ?



- A. 1080.J B. 360.J C. 1440.J D. 2.00 J

Energy stored in a capacitor can be found from:

$$U_{\text{Stored}} = \frac{Q^2}{2C}$$

Since the two capacitors are in series, the charge will be the same on both, so first find the effective capacitance of the pair in series

$$\frac{1}{C_{\text{Total Series}}} = \frac{1}{C_1} + \frac{1}{C_2} = \frac{1}{15.0 \text{ F}} + \frac{1}{45.0 \text{ F}} = \frac{3 + 1}{45.0 \text{ F}} = \frac{4}{45.0 \text{ F}}$$

$$C_{\text{Total Series}} = \frac{45.0}{4} \text{ F}$$

Now

$$Q_2 = Q_{\text{Total}} = C_{\text{Total}} V_S = \left(\frac{45.0}{4} \text{ F} \right) (16.0 \text{ V}) = 180. \text{ C}$$

Finding Energy

$$U_{\text{Stored}} = \frac{Q^2}{2C} = \frac{(180. \text{ C})^2}{2(45.0 \text{ F})} = \frac{32,400. \text{ C}^2}{90.0 \text{ F}} = 360. \text{ J}$$

So, the correct answer is B !

[Dr. Donovan's Classes](#)
[Page](#)

[Dr. Donovan's PH 221](#)
[Lecture Quiz & Exam](#)
[Solutions](#)

[NMU Physics](#)
[Department Web Page](#)

[NMU Main Page](#)

Please send any comments or questions about this page to ddonovan@nmu.edu

This page last updated on September 27, 2024

A.

B.

C.

D.

A.

C.

B.

D.

A.

B.

360.J

C.

D.