

$$P = iV = \frac{dq}{dt} \frac{dw}{dq} = \frac{dw}{dt}$$

Energy (W)

$$i = 4t^2 - t$$

$$V = 3$$

$$P = iV = 3(4t^2 - t) = 12t^2 - 3t$$

How much energy used in t_a

$$W = \int P dt = \int_0^{t_a} 12t^2 - 3t dt$$

$$W = 4t^3 - \frac{3}{2}t^2 \Big|_0^{t_a}$$

$$W = 4t_a^3 - \frac{3}{2}t_a^2$$

How much charge flowed in t_a ?

$$Q = \int_0^{T_a} i dt = \int_0^{T_a} (4t^2 - t) dt$$

$$Q = \left[\frac{4}{3} t^3 - \frac{1}{2} t^2 \right]_0^{T_a}$$


$$Q = \frac{4}{3} T_a^3 - \frac{1}{2} T_a^2$$

What is V Q Passed Through?

$$W = QV \Rightarrow V = \frac{W}{Q}$$


$$V = \frac{4T_a^3 - \frac{3}{2}T_a^2}{\frac{4}{3}T_a^3 - \frac{1}{2}T_a^2}$$

← Mess

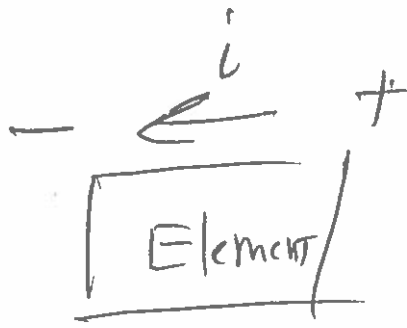


Absorbing
power

$$P < 0$$

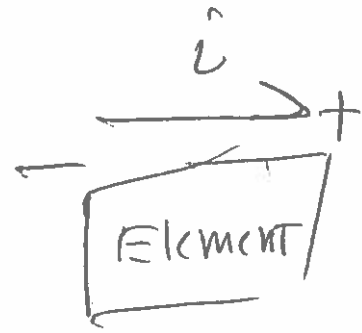

Power
supplied

$$P > 0$$

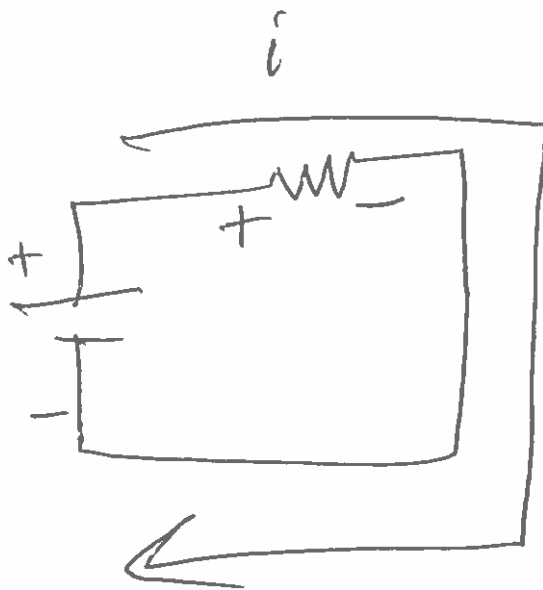

VOLTAGE Power Sources




V is fixed

i is whatever

external circuit
needs,

VOLTAGE source


CURRENT Power Sources

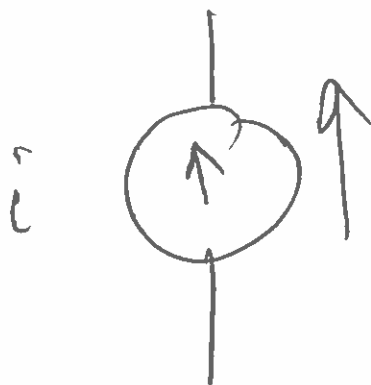

i is fixed

V is whatever is
needed by

external circuit,

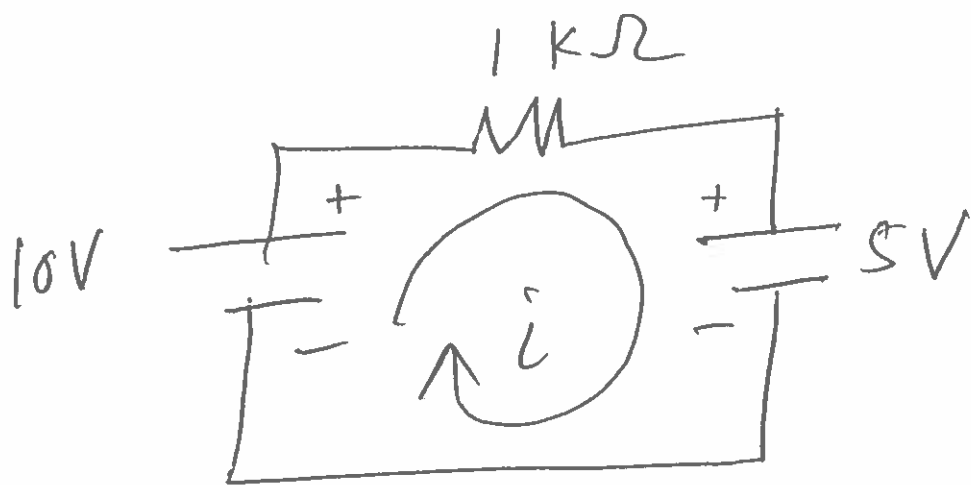

$$\hat{i} = 10\text{V} - i(1\text{k}\Omega) - 5\text{V} = 0$$

$$5\text{V} = i(1\text{k}\Omega)$$

$$i = \frac{5\text{V}}{1\text{k}\Omega} = \underline{5\text{mA}}$$


$$P_{10\text{V}} = 5\text{mA}(10\text{V}) = \overset{+}{50\text{mW}} \text{ Supplied}$$

$$P_{1\text{k}\Omega} = (5\text{mA})^2(1\text{k}\Omega) = \overset{-}{25\text{mW}}$$

Absorbed

$$P_{5\text{V}} = 5\text{mA}(-5\text{V}) = \overset{-}{25\text{mW}}$$

Absorbed

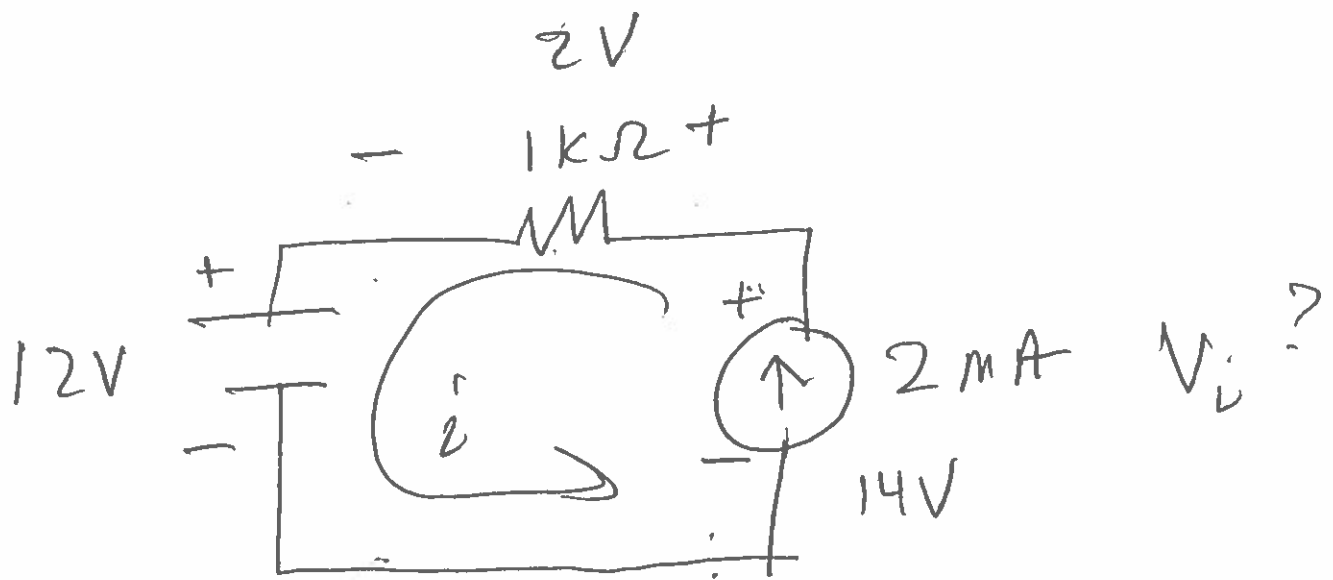

$$12V + 2V - V_i = 0$$

$$V_i = 14V$$

$$P_V = (-12V)(2mA) = -24 \text{ mW}$$

$$P_R = -(2mA)^2(1k\Omega) = -4 \text{ mW}$$

$$P_i = (2mA)(14V) = +28 \text{ mW}$$

0

Definition of a linear circuit

A linear circuit must satisfy Superposition
and Homogeneity

Superposition

$$\hat{i}_1 \rightarrow V_1 \quad \hat{i}_2 \rightarrow V_2$$

$$\text{Superposition} \Rightarrow (\hat{i}_1 + \hat{i}_2) \rightarrow (V_1 + V_2)$$

$$\hat{i}_1 = \frac{V_1}{R} \quad \hat{i}_2 = \frac{V_2}{R}$$

$$? = \frac{(V_1 + V_2)}{R} = \frac{V_1}{R} + \frac{V_2}{R} = \hat{i}_1 + \hat{i}_2$$

$$\hat{i} = \frac{V}{R} \quad \frac{V_1}{R} = \hat{i}_1$$

$$\frac{V_2^2}{R} = i_2$$

$$\frac{(V_1 + V_2)^2}{R} = \frac{V_1^2 + 2V_1V_2 + V_2^2}{R}$$

$$= i_1 + i_2 + \underbrace{\frac{2V_1V_2}{R}}_{i_{\text{mixed}}}$$

Homogeneity

$$i \rightarrow V$$

$$ki \rightarrow kV$$

k Parameter
for Transducers
Switches

$$i_1 = kV_1 \quad i_2 = kV_2$$

$$i_1 + i_2 = k(V_1 + V_2)$$

$$i = ke^V$$

$$k(e^{V_1} + e^{V_2})$$

$$\neq ke^{(V_1 + V_2)}$$

Ohm's Law

$$i = \frac{1}{R} V \quad \vec{J} = \sigma \vec{E}$$

$$\vec{J} = \frac{i}{A} \quad E = \frac{V}{d}$$

$$G = \frac{1}{R} \quad R = \frac{\rho L}{A} \quad \rho \text{ is resistivity}$$

$$G = \frac{\sigma A}{L} \quad \sigma = \frac{1}{\rho}$$

$$\rho = \rho_0 (1 + \alpha (T - T_0))$$