

$$R = \frac{\rho L}{A}$$

$\rho$  - resistivity it is  
Material Parameter

Units of  $\Omega m$

$$\rho = \rho_0 (1 + \alpha (T - T_0))$$



$\rho_0$  is resistivity @  $20^\circ C$

$T_0$  is  $20^\circ C$

for most materials  $\alpha > 0$

That means  $\rho \uparrow$  as  $T \uparrow$

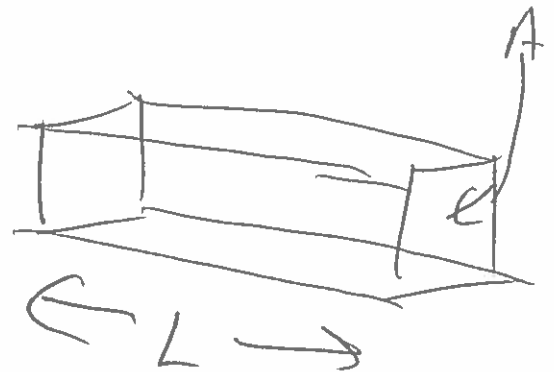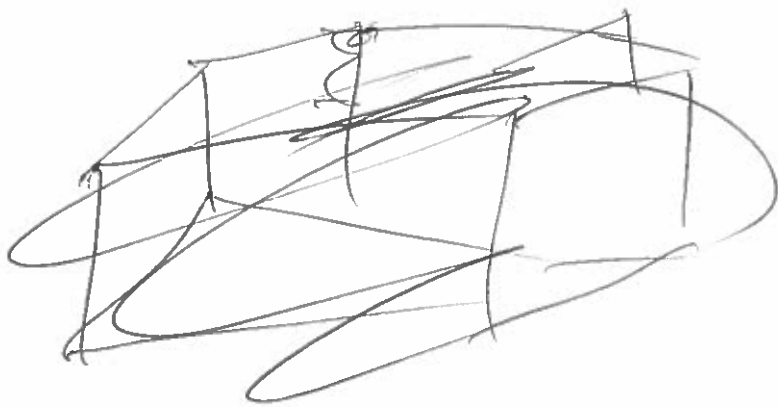$\alpha$  is Thermal factor ( $1/^\circ C$ )



$$\rho = 5 \times 10^{-6} \Omega m \quad A = 1 \times 10^{-6} m^2 \quad L = 1.0 m$$

$$R = \frac{(5 \times 10^{-6} \Omega m)(1.0 m)}{1 \times 10^{-6} m^2} = 5 \times 10^{-7} \Omega$$

Power is  $iV$

Ohm's Law  $i = \frac{V}{R}$  or  $V = iR$

$$P_{\text{resistor}} = i(iR) = i^2 R \quad \text{— Joule heating}$$

$$P_{\text{resistor}} = \frac{V}{R} V = \frac{V^2}{R}$$

$R_{\text{filament}}$  for 60W light bulb

$$\cancel{R} \quad P = \frac{V^2}{R} \quad R = \frac{V^2}{P}$$

$$R = \frac{(110V)^2}{60W} = 202 \Omega$$

$$P = iV \Rightarrow i = \frac{P}{V} = \frac{60W}{110V} = \underline{0.55A}$$

$$\hat{I} = \frac{1}{R} V$$

$$\hat{I} = G V$$

G is conductance

units S (Siemens)

$$G = \frac{\sigma A}{L}$$

$$R = \frac{\rho L}{A}$$

$$\sigma = \frac{1}{\rho}$$

$\sigma$  is conductivity

$\rho$  resistivity

Transducers are devices which have  
a physical property that changes due  
to an external system change.  
A rod expands as temperature increases

$$\dot{L} = K T$$


↑
↙
↘

Parameter                      Temperature

$$V = A F - \text{STress Transducer}$$




Switches

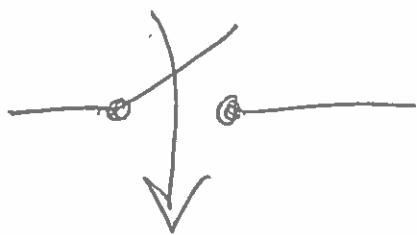


$$t = \tau_a$$

Switch closes  
 QT time  $\tau_a$

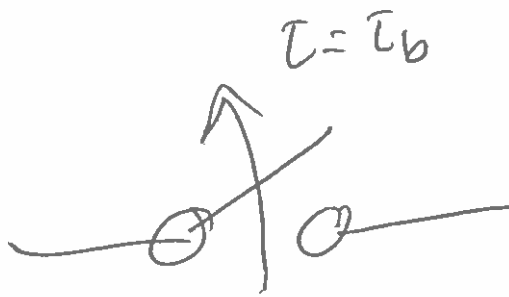


$$t = \tau_b$$


Switch opens  
 QT time  $\tau_b$

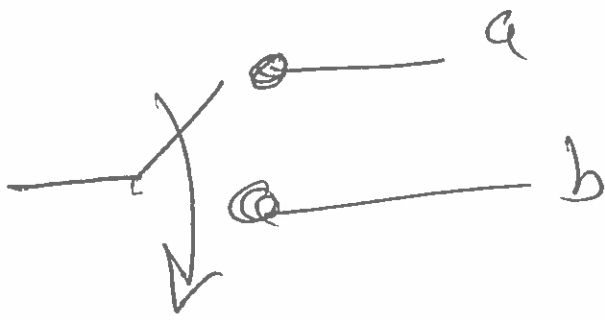

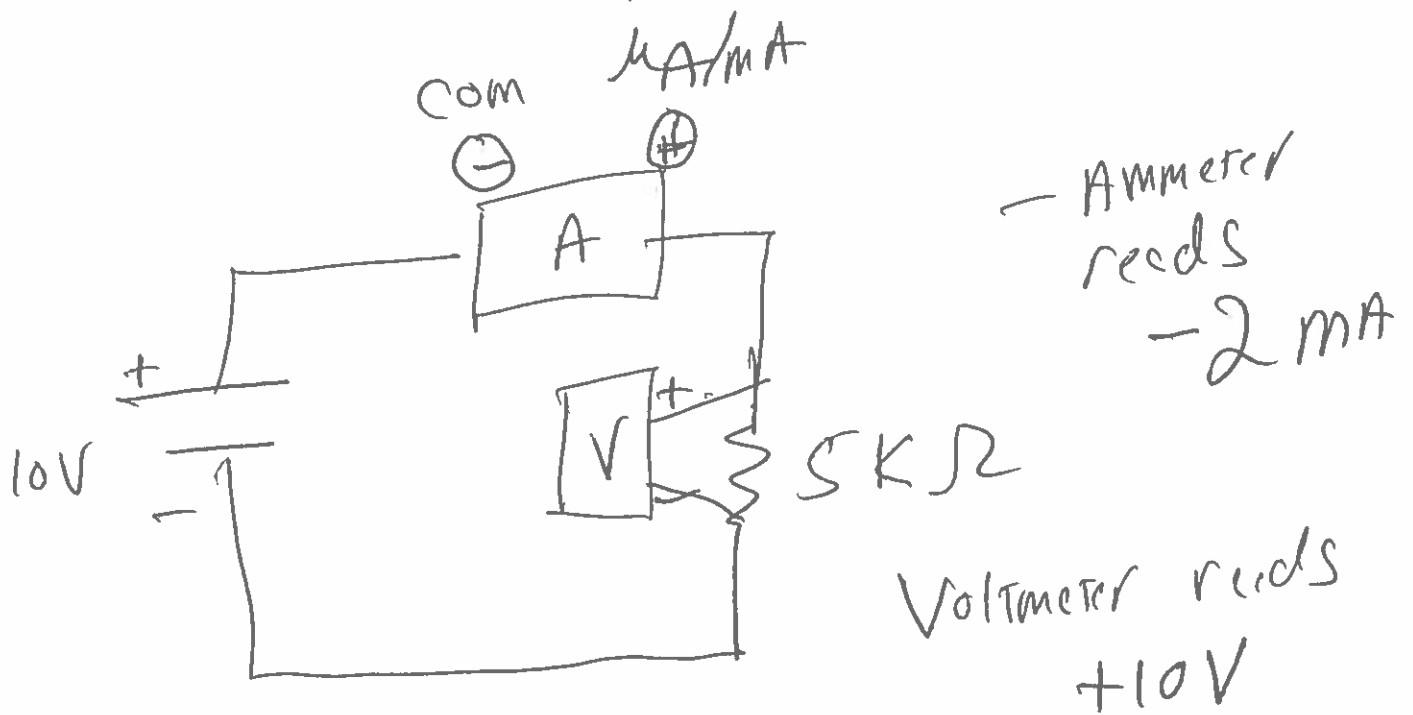$t = t_c$  Switch goes from line a  
to line b at  $t_c$


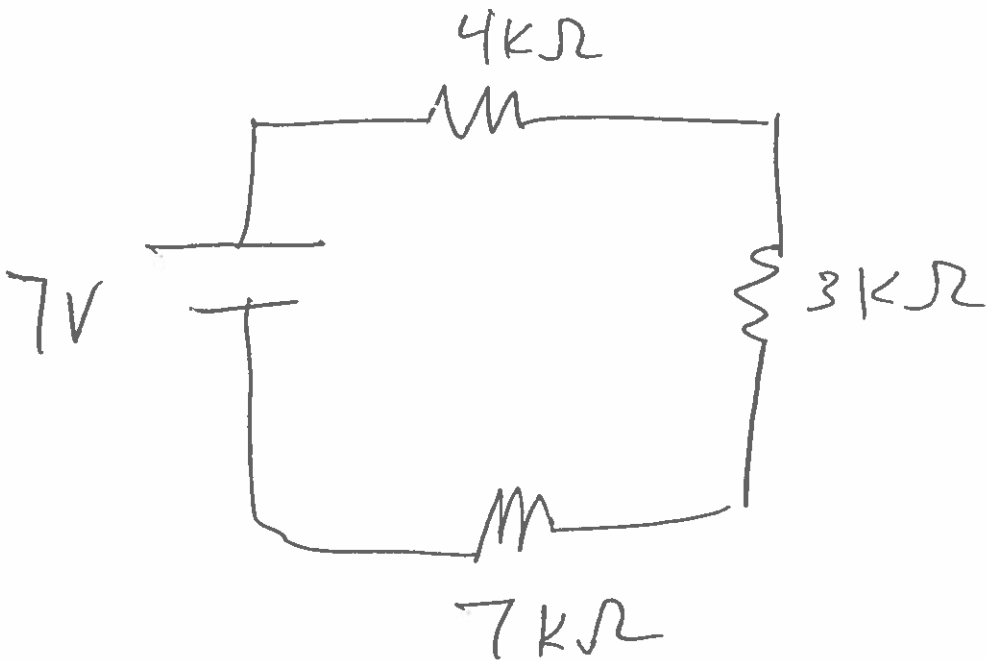
$$i = \frac{V}{R} = \frac{10V}{5K\Omega} = 2mA$$



$$\hat{i}_\phi = \frac{V_{TOT}}{R_{TOT}} = \frac{7V}{4k\Omega + 3k\Omega + 7k\Omega} = \frac{7V}{14k\Omega}$$

$$\hat{i} = 1.5 \text{ mA}$$

$$V_{4k\Omega} = 2V = \hat{i} R_{4k\Omega} = (1.5 \text{ mA})(4k\Omega)$$

2V

$$V_{3k\Omega} = 1.5V$$

$$V_{7k\Omega} = 3.5V$$


$$P_{7V} = (1.5 \text{ mA})(7V) = +3.5 \text{ mW}$$

$$P_{4k\Omega} = -(1.5 \text{ mA})^2 (4k\Omega) = -(1.5 \text{ mA})(2V) = -1.0 \text{ mW}$$

$$P_{3k\Omega} = -(1.5 \text{ mA})(1.5V) = -0.75 \text{ mW}$$

$$P_{7k\Omega} = -(1.5 \text{ mA})(3.5V) = -1.75 \text{ mW}$$

P, 2, 4-10

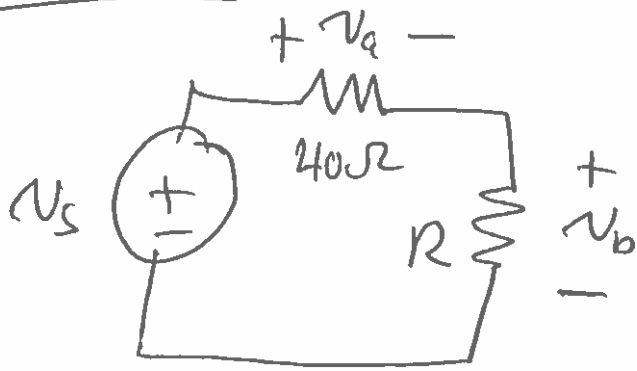

$v_a$ (V)	$v_b$ (V)
11.75	7.05
7.5	4.5
5.625	3.375
10	6
4.375	2.625

What is  $R$ ?

$$\hat{i} = \frac{v_a}{40\Omega} = \frac{v_b}{R}$$

$$v_b = \frac{R}{40\Omega} v_a \quad \text{--- EQUATION OF A LINE}$$

PLOT 5 POINTS FIND BEST SLOPE

$$\text{Slope} = \frac{R}{40\Omega} \Rightarrow R = 40\Omega (\text{SLOPE})$$

$$\text{MATLAB} \Rightarrow \text{slope} = 0.6 \Rightarrow R = 24\Omega$$