
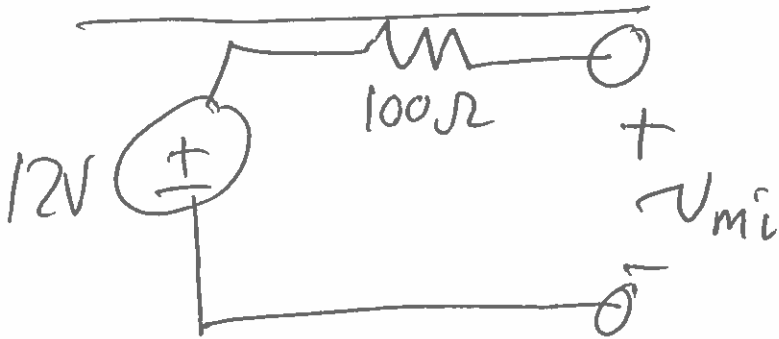


Ideal case

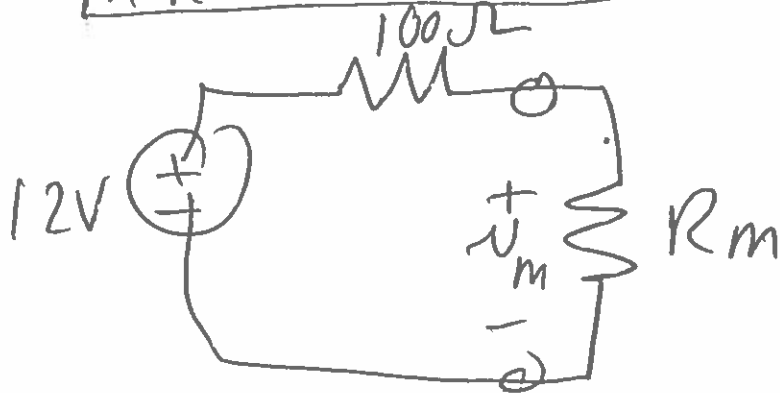

More realistic



$$V_m = \frac{R_m}{100\Omega + R_m} V_s = \frac{R_m}{100\Omega + R_m} (12V)$$

ideal case  $R_m \rightarrow \infty$  Open circuit

$$V_m \rightarrow 12V$$

when  $R_m < \infty$  not ideal

$$V_m < V_{mi} = \underbrace{12V}_{\text{ideal}}$$

What is error if  $R_m = 900\Omega$

$$\% \text{ error} = \frac{V_{mi} - V_m}{V_{mi}} \times 100\% = 1 - \frac{V_m}{V_{mi}}$$

$$V_m = \frac{R_m}{100\Omega + R_m} (12V) = \left( \frac{900\Omega}{100\Omega + 900\Omega} \right) (12V)$$

$$V_m = 0.9(12V)$$

$$\% \text{ error} = \frac{12V - 0.9(12V)}{12V} \times 100\% = 1 - 0.9 \times 100\%$$

$$\% \text{ error} = \boxed{0.1} \times 100\% = 10\%$$

What should  $R_m$  be for 2% error

$$\% \text{ error} = \frac{V_{mi} - V_m}{V_{mi}} \times 100\%$$

$$2\% = 1 - \frac{V_m}{V_{mi}} \times 100\%$$

$$1,02 = 1 - \frac{V_m}{V_{mi}}$$

$$\frac{V_m}{V_{mi}} = 1 - 1,02 = 0,98$$

$$V_m = \frac{R_m}{100\Omega + R_m} (12V) \quad V_{mi} = 12V$$

$$\frac{R_m}{100\Omega + R_m} = 0,98 \quad R_m = 0,98(100\Omega + R_m)$$

$$0,02 R_m = 0,98(100\Omega)$$

$$R_m = \frac{98\Omega}{0,02} = \boxed{4,900\Omega}$$

# Complex Circuits

---

## MOST BASIC Kirchhoff's Laws

TWO


1) JUNCTION RULE  $\sum i_{in} = \sum i_{out}$

QT JUNCTION  $\Rightarrow$  CONSERVATION OF CHARGE.

2) LOOP RULE  $\sum V_i$  around a

closed loop MUST = 0.

$\Rightarrow$  CONSERVATION OF ENERGY.

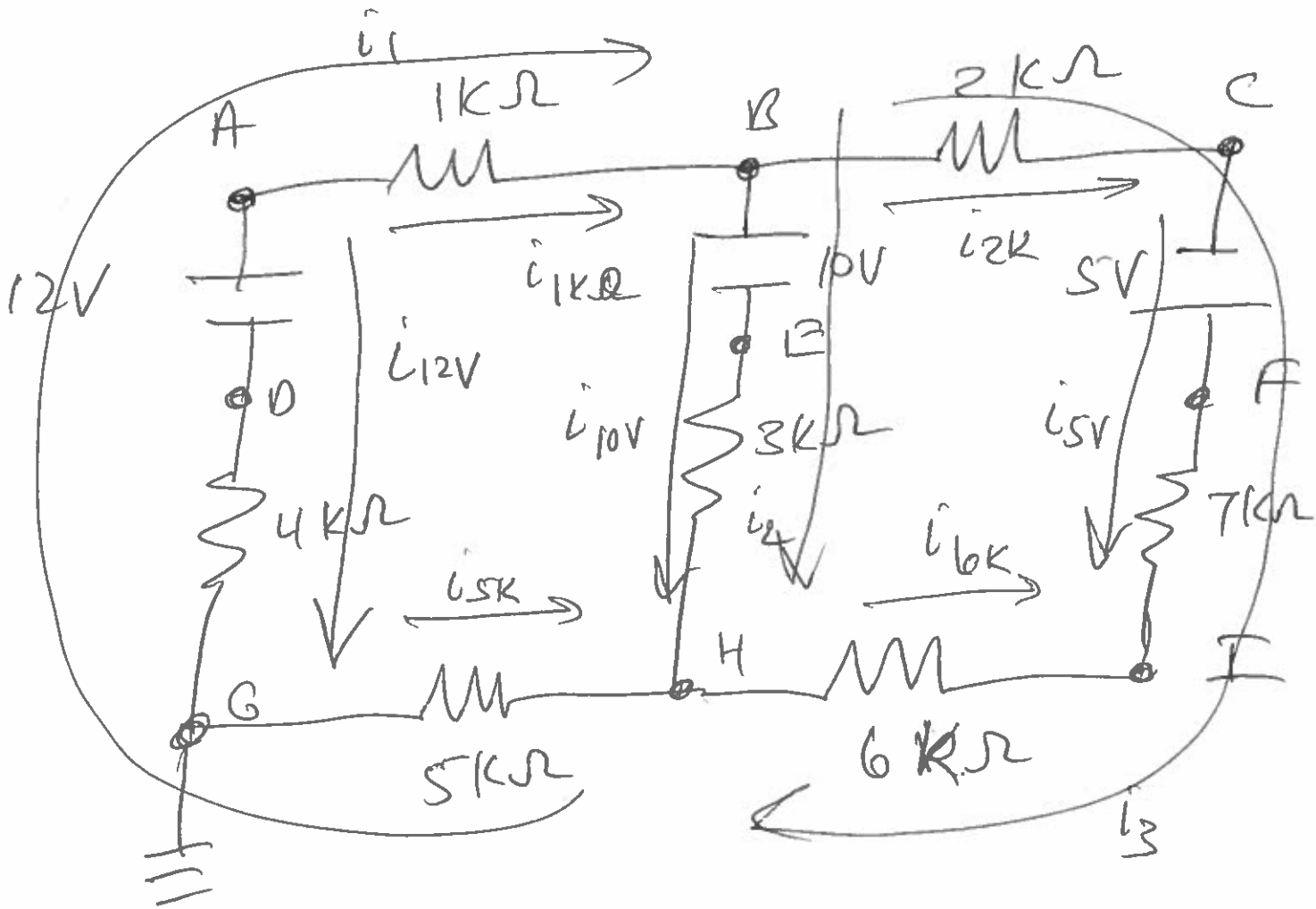

Currents to right or Down Assumed  $> 0$   
 Currents to left or UP Assumed  $< 0$

$$\dot{i}_{1k\Omega} = -\dot{i}_{12V} = -\dot{i}_{5k} = \dot{i}_1$$

$$\dot{i}_{2k\Omega} = \dot{i}_{5V} = -\dot{i}_{6k} = \dot{i}_3$$

$$\dot{i}_{10V} = \dot{i}_2$$

Need ( Junction 2 loops

$$\text{JUNCTION AT POINT B} \Rightarrow \underline{\hat{i}_1 = \hat{i}_2 + \hat{i}_3}$$

Left loop Go clockwise start at A

$$- \hat{i}_1 (1k\Omega) - 10V - \hat{i}_2 (3k\Omega)$$

$$\hat{i}_1 (5k\Omega) \hat{i}_1 (4k\Omega)$$