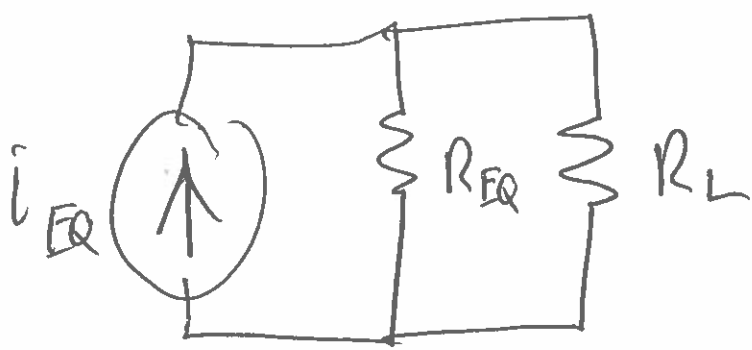


Equivalent circuits



Load resistance
 V_{RL}, i_L
is unchanged





1) Simplify Series resistances
and Parallel resistances




$$R_{\text{series}} = R_1 + R_2 + \dots + R_n$$

$$R_{\text{parallel}} \Rightarrow \frac{1}{R_{\text{parallel}}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}$$


Adding components to simplify circuits

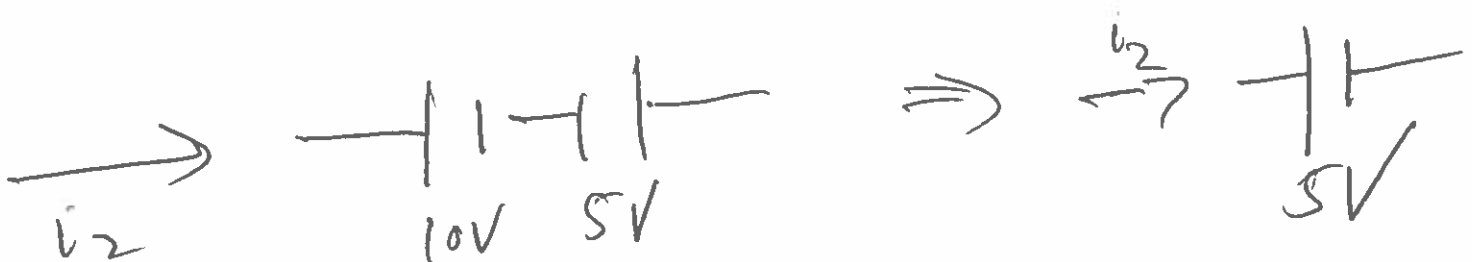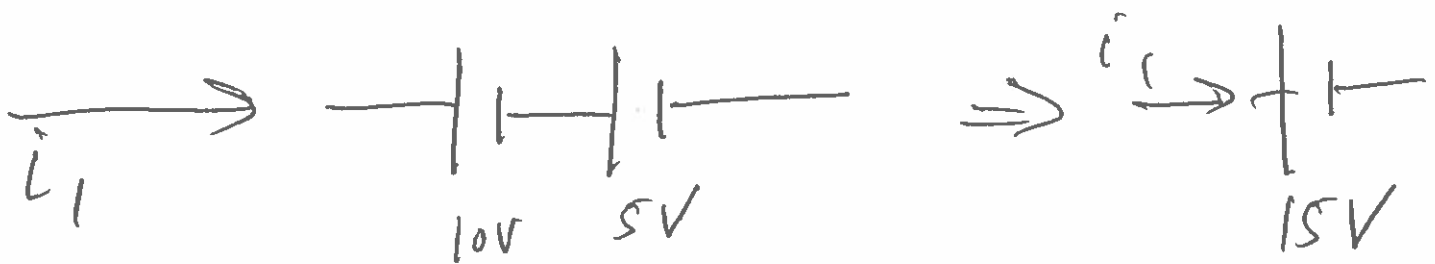
1) if current is common you can
Voltage components observing Polarity



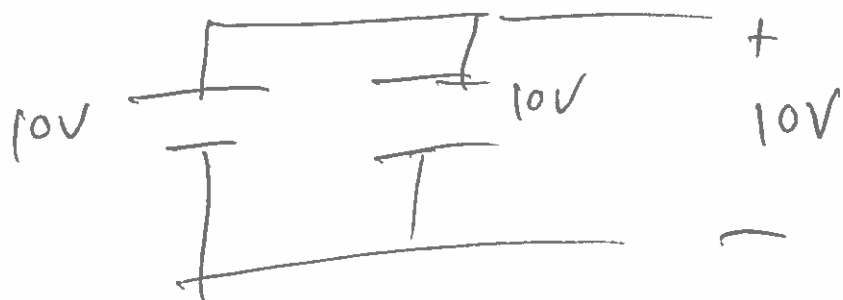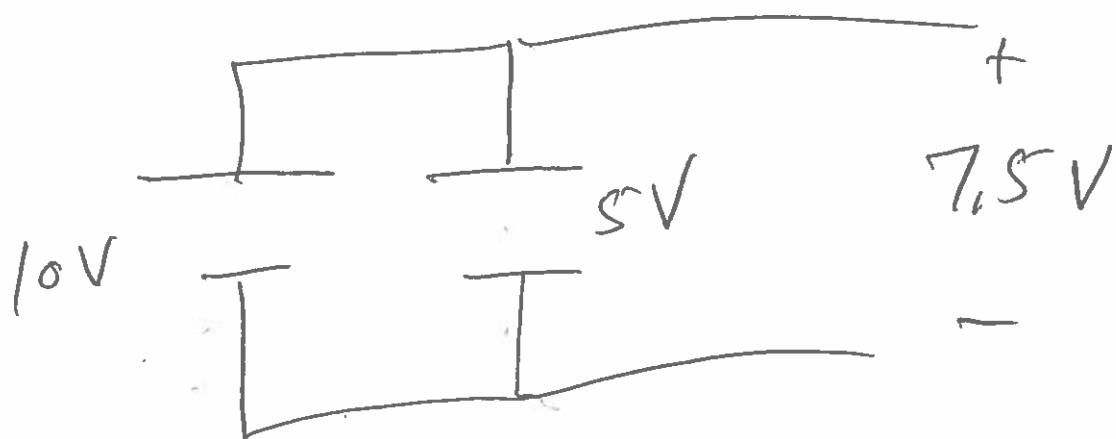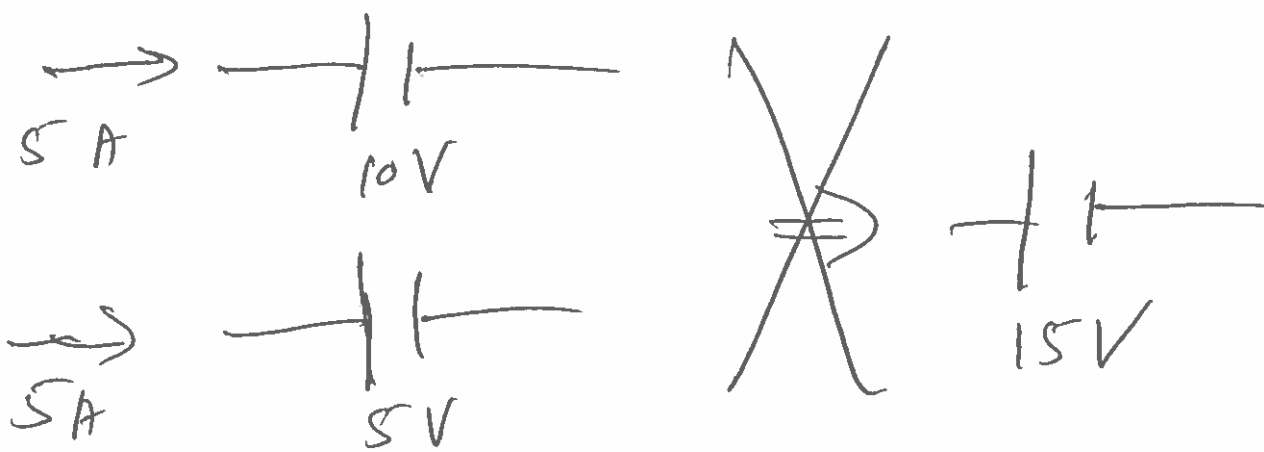

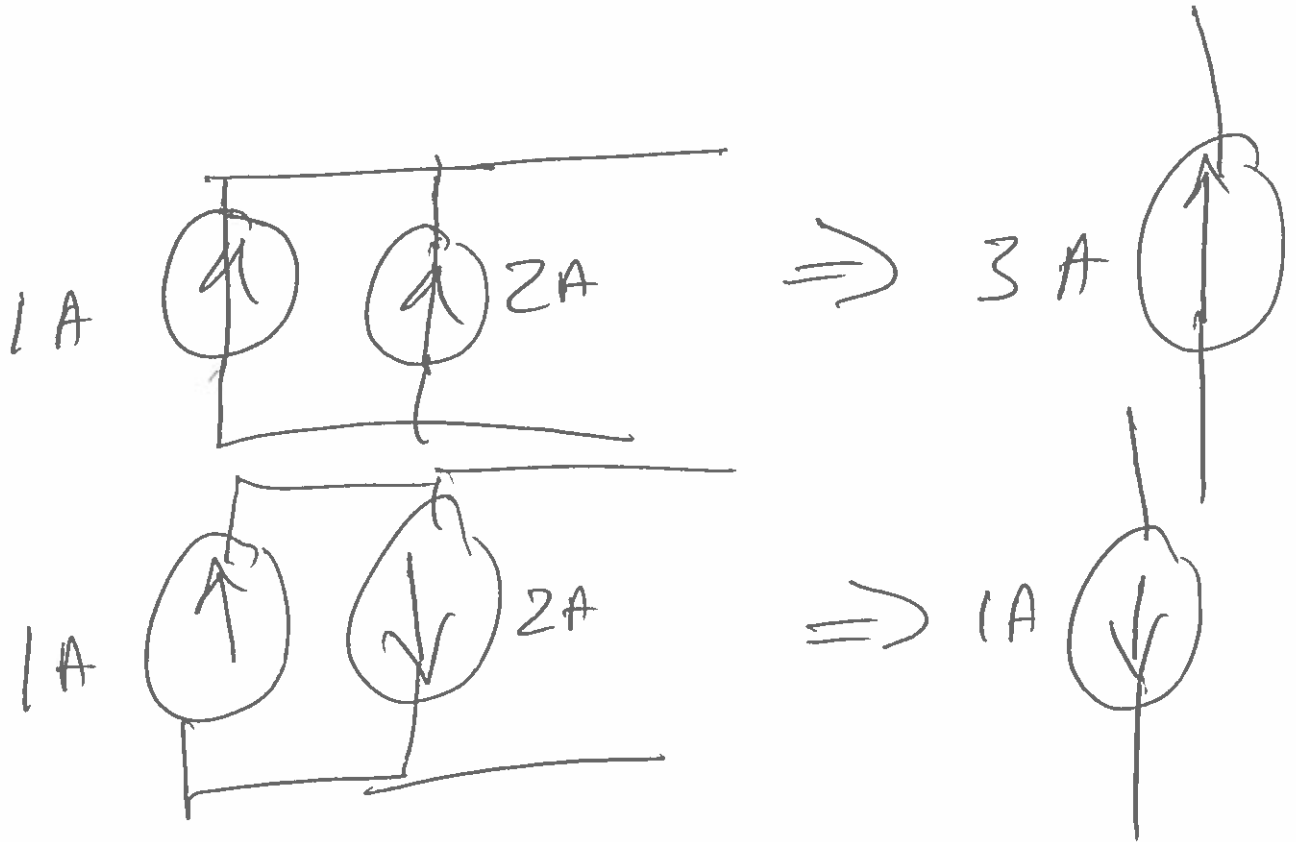2) current ~~objects~~ objects can be added
in parallel if voltage across
is same



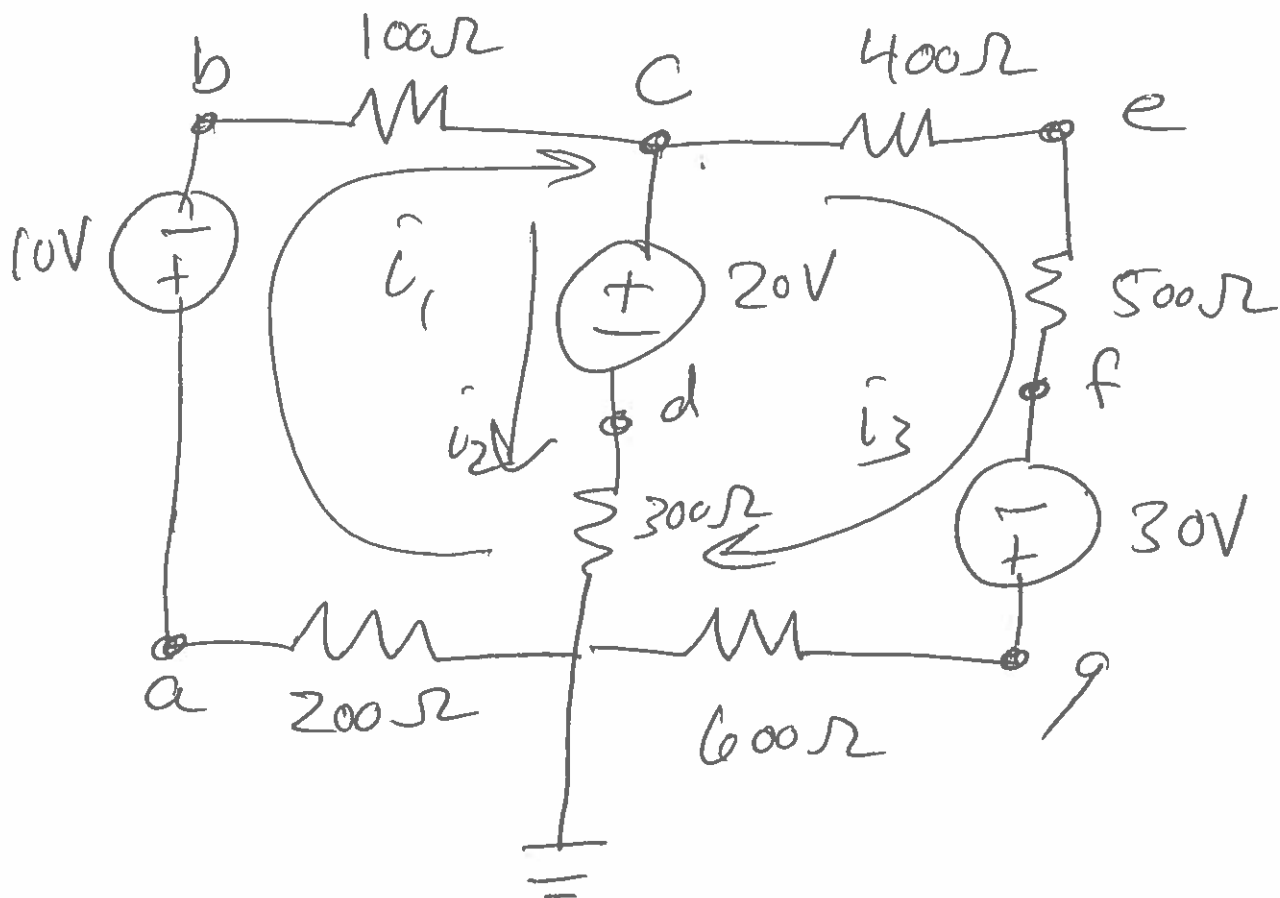

at c

$$i_1 = i_2 + i_3$$

Left Loop start a clockwise

$$-10V - i_1(100\Omega) - 20V - i_2(300\Omega) - i_1(200\Omega) = 0$$

Right loop start c clockwise

$$-i_3(400\Omega) - i_3(500\Omega) + 30V - i_3(600\Omega) + i_2(300\Omega) + 20V = 0$$

$$\hat{i}_1 - \hat{i}_2 - \hat{i}_3 = 0$$

$$\hat{i}_1 (200\Omega + 100\Omega) + \hat{i}_2 (300\Omega) = - (20V + 10V)$$


$$\hat{i}_2 (300\Omega) - \hat{i}_3 (400\Omega + 500\Omega + 600\Omega) =$$

~~$- (10V + 20V)$~~
 ~~$- (30V + 20V)$~~

$$\hat{i}_1 = -0.039394 \text{ A} = -39.4 \text{ mA}$$

$$\hat{i}_2 = -0.060606 \text{ A} = -60.6 \text{ mA}$$
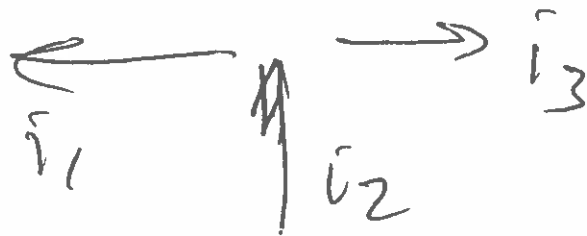
$$\hat{i}_3 = +0.021212 \text{ A} = +21.2 \text{ mA}$$



$$V_{ac} = -10V - \hat{i}_1 (100\Omega)$$

$$= -10V - (-0.0394 \text{ A}) (100\Omega)$$

$$= -10V + 3.94 \text{ V} = -6.06 \text{ V}$$

$$V_{a \rightarrow c_2} = + \hat{i}_1 (200 \Omega) + \hat{i}_2 (300 \Omega) + 20V$$

$$= (-0.0394 \text{ A}) (200 \Omega) + (-\cancel{0.0606}^{0.0606} \text{ A}) (300 \Omega) + 20V$$

$$= -7.8 \text{ V} - 18.18 \text{ V} + 20 \text{ V}$$

$$= -6.02 \text{ V}$$