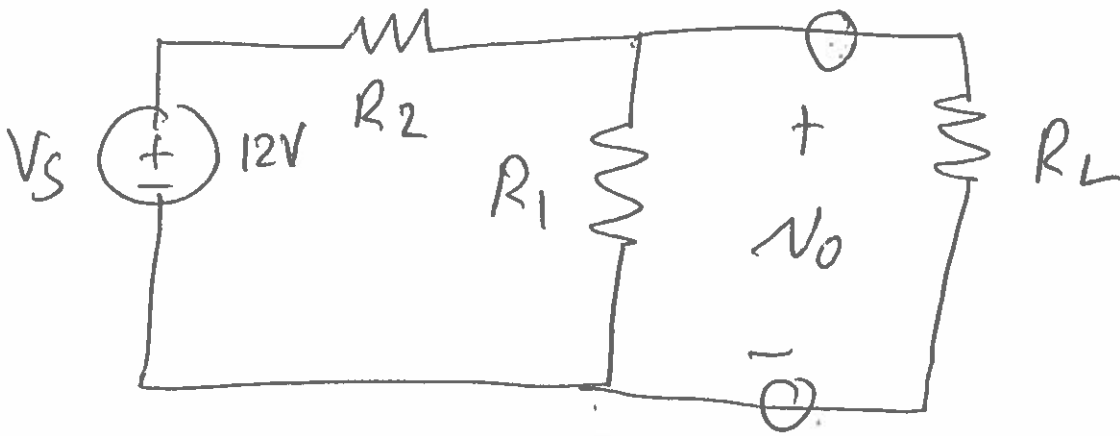


DP 3-2.



$$R_L = 200\Omega \pm 5\% \Rightarrow 190\Omega \leq R_L \leq 210\Omega$$

$$V_S = 12V \pm 1\% \quad \text{Provide } 5W$$


Design circuit using 5%  $\frac{1}{8}W$  resistors

$$R_1 \text{ and } R_2 \text{ so that } V_0 = 4V \pm 10\%$$

5%  $\frac{1}{8}W$   $100\Omega$  would have resistance  
between  $95\Omega$  and  $105\Omega$  and  
can safely dissipate  $\frac{1}{8}W = 0.125W$

Let's simplify by making  $R_1 = \infty$

Open circuit Use No  $R_1$

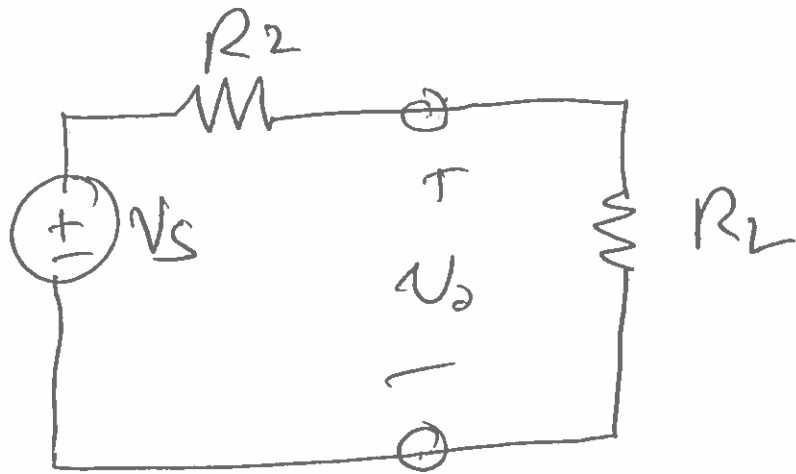

$R_2$  should be  $400\Omega$

$$\text{Then } V_o = \frac{V_s R_L}{R_2 + R_L}$$


$$V_o = \frac{(12V)(200\Omega)}{400\Omega + 200\Omega} = \frac{200\Omega (12V)}{600\Omega} = 4V \checkmark$$

$$P_{R_2} \Rightarrow I = \frac{V_{TOT}}{R_{TOT}} = \frac{12V}{600\Omega} = 0.02A$$

$$P_{R_2} = I^2 R_2 = (0.02A)^2 (400\Omega) = 0.16W > 1W$$

Make  $400\Omega$  by 2  $200\Omega$  resistors
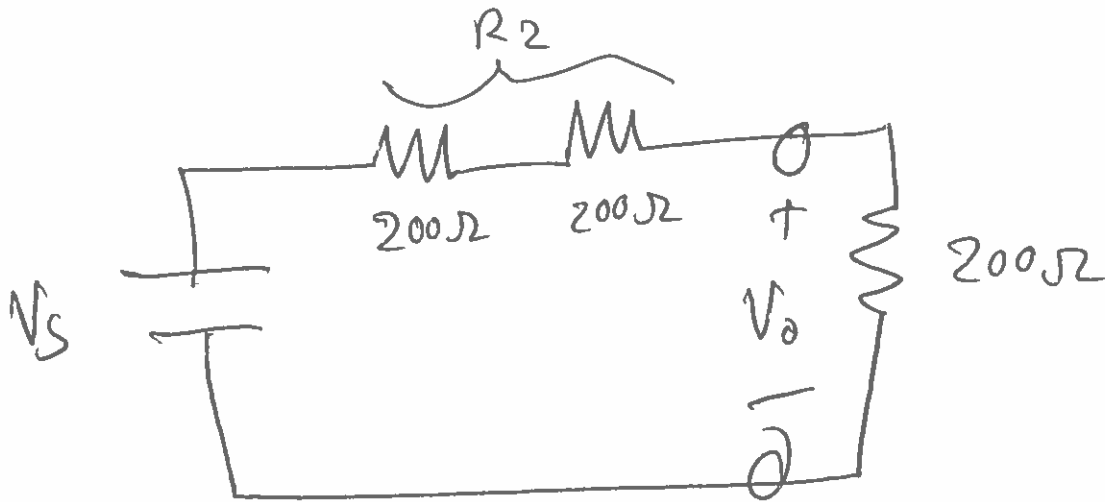
$$P_{200\Omega} = i^2 R = (0.02A)^2 (200\Omega) = 0.08W < 0.125W$$



$$P_{200\Omega} = 0.08W \times 2 = 0.16W$$

$$P_{200\Omega} = 0.08W \quad \frac{0.08W}{2} = 0.04W < 0.125W$$

is  $V_0 = 4V \pm 10\%$   $3.6V \Rightarrow 4.4V$

Largest  $V_0 \Rightarrow R_L$  is  $R_L + 5\% = 210\Omega$

$$R_{200\Omega} = 190\Omega \quad R_{200} - 5\%$$

$$V_S = 12V + 1\% \quad \text{~~12.1V~~ ~~12.2V~~ 12.1V$$

$$V_o = \frac{V_s R_L}{R_L + R_2}$$

$$V_o = \frac{(12.12\text{V})(210\Omega)}{(210\Omega + 2(190\Omega))} = \frac{12.12\text{V}(210\Omega)}{590\Omega}$$

$$V_o = 4.314\text{V} < 4.4\text{V} \checkmark$$

Smallest  $V_o$       $R_L = R_L - 5\% \Rightarrow 190\Omega$


$$R_{200\Omega} = R_{200} + 5\% \Rightarrow 210\Omega$$

$$V_s = V_o - 17\% = 11.88\text{V}$$

$$V_o = \frac{(11.88\text{V})(190\Omega)}{190\Omega + 2(210\Omega)} = \frac{(11.88\text{V})(190\Omega)}{610\Omega}$$

$$V_o = 3.70\text{V} > 3.6\text{V} \checkmark$$
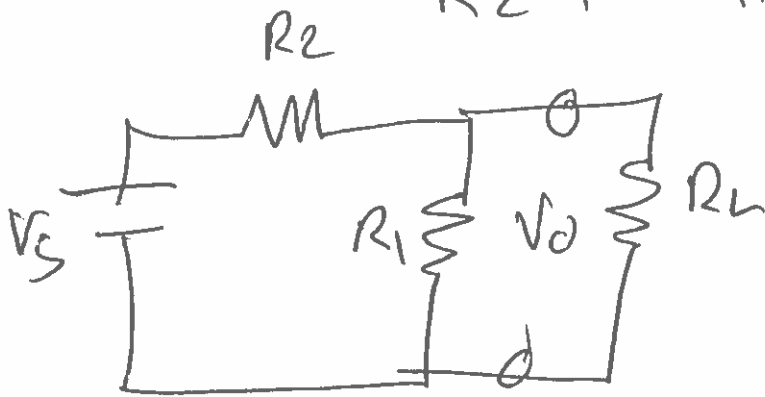
$$V_o = \frac{V_s R_{eff}}{R_2 + R_{eff}}$$



$$R_{eff} = \frac{R_L R_1}{R_L + R_1}$$

$$V_o = \frac{V_s R_L R_1}{(R_L + R_1) \left( R_2 + \frac{R_L R_1}{R_L + R_1} \right)}$$

# Complex D.C. Circuits

## Two Basic Circuit Types

- ① Planar — Circuit can be drawn on a plane without any wire crossings.
- ② Non-Planar — Circuit is more 3d wires have to cross over or "leave" the plane.


## 2 Techniques

- ① Node Voltages — can do either circuit usually mostly constant current sources.
- ② Mesh currents — can only do planar usually mostly constant voltage sources.

In reality both are specialized ways of  
 doing Kirchhoff equations,  
 but you do less thinking and they are very  
 easy to put into MATLAB,

Voltage nodes are points between two or  
 more circuit elements.

consider

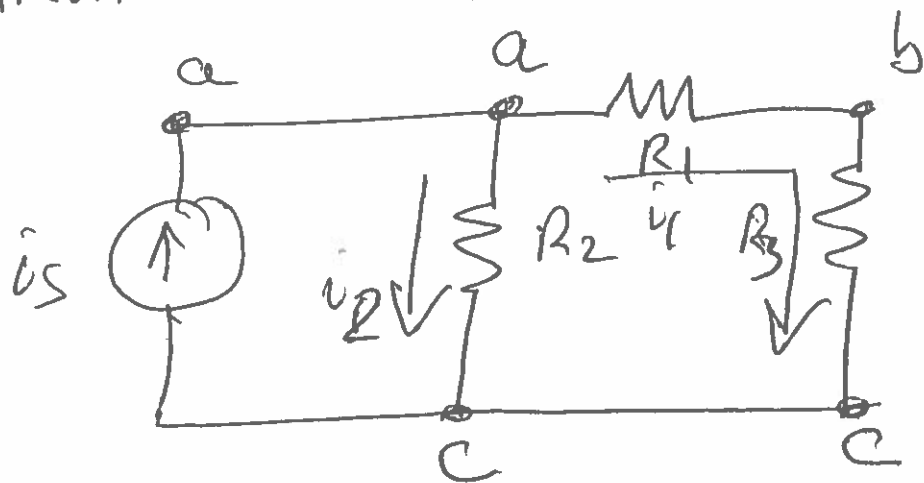

$$V_c = 0 \Rightarrow \text{Ground point}$$

$$\text{at } a \quad \hat{I}_s = \hat{I}_1 + \hat{I}_2$$

$$\hat{I}_1 = \frac{V_a - V_b}{R_1} = \frac{V_b}{R_3} \quad \hat{I}_2 = \frac{V_a}{R_2}$$