

$$a/ \quad -3 \text{ mA} = V_a \left( \frac{1}{10 \text{ k}\Omega} \right)$$

$$b/ \quad +3 \text{ mA} = V_b \left( \frac{1}{22 \text{ k}\Omega} \right) - V_c \left( \frac{1}{22 \text{ k}\Omega} \right)$$

$$c/ \quad +6 \text{ mA} = V_c \left( \frac{1}{22 \text{ k}\Omega} + \frac{1}{15 \text{ k}\Omega} \right) - V_b \left( \frac{1}{22 \text{ k}\Omega} \right) - V_d \left( \frac{1}{15 \text{ k}\Omega} \right)$$


$$d/ \quad 0 = V_d \left( \frac{1}{5 \text{ k}\Omega} + \frac{1}{15 \text{ k}\Omega} + \frac{1}{36 \text{ k}\Omega} \right) - V_g \left( \frac{1}{5 \text{ k}\Omega} \right) - V_c \left( \frac{1}{15 \text{ k}\Omega} \right)$$

$$e / +2\text{mA} - 6\text{mA} = v_d \left( \frac{1}{12\text{k}\Omega} \right) - v_i \left( \frac{1}{12\text{k}\Omega} \right)$$

$$f / -2\text{mA} = v_f \left( \frac{1}{6\text{k}\Omega} \right) - v_g \left( \frac{1}{6\text{k}\Omega} \right)$$

$$g / 0 = v_g \left( \frac{1}{6\text{k}\Omega} + \frac{1}{5\text{k}\Omega} + \frac{1}{2\text{k}\Omega} \right) - v_f \left( \frac{1}{6\text{k}\Omega} \right) \\ - v_d \left( \frac{1}{5\text{k}\Omega} \right) - v_h \left( \frac{1}{2\text{k}\Omega} \right)$$

### Voltage Node Example #4

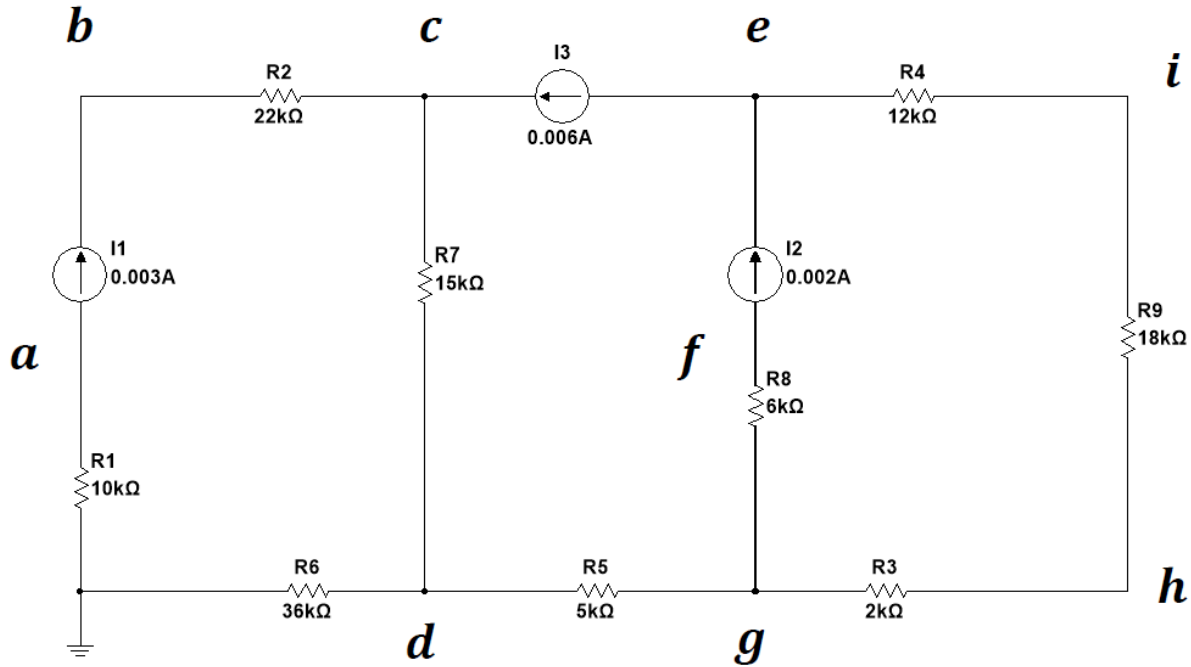

### Voltage Node Equations

At node a:

$$-3 \text{ mA} = V_a \left( \frac{1}{10 \text{ k}\Omega} \right)$$

At node b:

$$+3 \text{ mA} = V_b \left( \frac{1}{22 \text{ k}\Omega} \right) - V_c \left( \frac{1}{22 \text{ k}\Omega} \right)$$

At node c:

$$+6 \text{ mA} = V_c \left( \frac{1}{22 \text{ k}\Omega} + \frac{1}{15 \text{ k}\Omega} \right) - V_b \left( \frac{1}{22 \text{ k}\Omega} \right) - V_d \left( \frac{1}{15 \text{ k}\Omega} \right)$$

At node d:

$$0 = V_d \left( \frac{1}{5 \text{ k}\Omega} + \frac{1}{15 \text{ k}\Omega} + \frac{1}{36 \text{ k}\Omega} \right) - V_g \left( \frac{1}{5 \text{ k}\Omega} \right) - V_c \left( \frac{1}{15 \text{ k}\Omega} \right)$$

At node e:

$$+2 \text{ mA} - 6 \text{ mA} = V_e \left( \frac{1}{12 \text{ k}\Omega} \right) - V_i \left( \frac{1}{12 \text{ k}\Omega} \right)$$

At node f:

$$-2 \text{ mA} = V_f \left( \frac{1}{6 \text{ k}\Omega} \right) - V_g \left( \frac{1}{6 \text{ k}\Omega} \right)$$

At node g:

$$0 = V_g \left( \frac{1}{6 \text{ k}\Omega} + \frac{1}{5 \text{ k}\Omega} + \frac{1}{2 \text{ k}\Omega} \right) - V_f \left( \frac{1}{6 \text{ k}\Omega} \right) - V_d \left( \frac{1}{5 \text{ k}\Omega} \right) - V_h \left( \frac{1}{2 \text{ k}\Omega} \right)$$

At node h:

$$0 = V_h \left( \frac{1}{2 \text{ k}\Omega} + \frac{1}{18 \text{ k}\Omega} \right) - V_g \left( \frac{1}{2 \text{ k}\Omega} \right) - V_i \left( \frac{1}{18 \text{ k}\Omega} \right)$$

At node i:

$$0 = V_i \left( \frac{1}{12 \text{ k}\Omega} + \frac{1}{18 \text{ k}\Omega} \right) - V_e \left( \frac{1}{12 \text{ k}\Omega} \right) - V_h \left( \frac{1}{18 \text{ k}\Omega} \right)$$

Rewriting to make entering into MATLAB easier:

$$\begin{aligned} -3 \text{ mA} &= V_a \left( \frac{1}{10 \text{ k}\Omega} \right) \\ +3 \text{ mA} &= V_b \left( \frac{1}{22 \text{ k}\Omega} \right) - V_c \left( \frac{1}{22 \text{ k}\Omega} \right) \\ +6 \text{ mA} &= -V_b \left( \frac{1}{22 \text{ k}\Omega} \right) + V_c \left( \frac{1}{22 \text{ k}\Omega} + \frac{1}{15 \text{ k}\Omega} \right) - V_d \left( \frac{1}{15 \text{ k}\Omega} \right) \\ 0 &= -V_c \left( \frac{1}{15 \text{ k}\Omega} \right) + V_d \left( \frac{1}{5 \text{ k}\Omega} + \frac{1}{15 \text{ k}\Omega} + \frac{1}{36 \text{ k}\Omega} \right) - V_g \left( \frac{1}{5 \text{ k}\Omega} \right) \\ +2 \text{ mA} - 6 \text{ mA} &= V_e \left( \frac{1}{12 \text{ k}\Omega} \right) - V_i \left( \frac{1}{12 \text{ k}\Omega} \right) \\ -2 \text{ mA} &= V_f \left( \frac{1}{6 \text{ k}\Omega} \right) - V_g \left( \frac{1}{6 \text{ k}\Omega} \right) \\ 0 &= -V_d \left( \frac{1}{5 \text{ k}\Omega} \right) - V_f \left( \frac{1}{6 \text{ k}\Omega} \right) + V_g \left( \frac{1}{6 \text{ k}\Omega} + \frac{1}{5 \text{ k}\Omega} + \frac{1}{2 \text{ k}\Omega} \right) - V_h \left( \frac{1}{2 \text{ k}\Omega} \right) \\ 0 &= -V_g \left( \frac{1}{2 \text{ k}\Omega} \right) + V_h \left( \frac{1}{2 \text{ k}\Omega} + \frac{1}{18 \text{ k}\Omega} \right) - V_i \left( \frac{1}{18 \text{ k}\Omega} \right) \\ 0 &= -V_e \left( \frac{1}{12 \text{ k}\Omega} \right) - V_h \left( \frac{1}{18 \text{ k}\Omega} \right) + V_i \left( \frac{1}{12 \text{ k}\Omega} + \frac{1}{18 \text{ k}\Omega} \right) \end{aligned}$$

From MATLAB the Voltage nodes are found to be:

Node	Voltage (V)
a	-30.
b	309.
c	243.
d	108
e	-50.
f	66.
g	78.
h	70.
i	-2.0

### MATLAB Code

```
%lecture example of Voltage nodes with constant Current sources
%large circuit. Example 4
%version 2021-02-12 DW Donovan
```

```

clear all;

%Voltage Node Method
G=[(1/10) 0 0 0 0 0 0 0 0;
    0 (1/22) (-1/22) 0 0 0 0 0 0;
    0 (-1/22) (1/22 + 1/15) (-1/15) 0 0 0 0 0;
    0 0 (-1/15) (1/5 + 1/15 + 1/36) 0 0 (-1/5) 0 0;
    0 0 0 0 (1/12) 0 0 0 (-1/12);
    0 0 0 0 0 (1/6) (-1/6) 0 0;
    0 0 0 (-1/5) 0 (-1/6) (1/5 + 1/6 + 1/2) (-1/2) 0;
    0 0 0 0 0 0 (-1/2) (1/2 + 1/18) (-1/18);
    0 0 0 0 (-1/12) 0 0 (-1/18) (1/12 + 1/18)];
ii=[-3 3 6 0 (2-6) -2 0 0 0]';
V=G\ii;
va=V(1);
vb=V(2);
vc=V(3);
vd=V(4);
ve=V(5);
vf=V(6);
vg=V(7);
vh=V(8);
vi=V(9);

ANS={'Node' 'Voltage (V)';
    'va' va;
    'vb' vb;
    'vc' vc;
    'vd' vd;
    've' ve;
    'vf' vf;
    'vg' vg;
    'vh' vh;
    'vi' vi};
ANS

```

```

%{
ANS =
    'Node'      'Voltage (V)'
    'va'        [      -30]
    'vb'        [  309.0000]
    'vc'        [  243.0000]
    'vd'        [  108.0000]
    've'        [  -50.0000]
    'vf'        [   66.0000]
    'vg'        [   78.0000]
    'vh'        [   70.0000]
    'vi'        [   -2.0000]
%}

```

```
%Double Check
```

```

i1 = 3;
i2 = -6;
i3 = -4;
vac = -i1*10;
vbc = +i1*36+(i1-i2)*15+i1*22;
vcc = +i1*36+(i1-i2)*15;
vdc = +i1*36;
vec = +i1*36+i2*5+i3*2+i3*18+i3*12;
vfc = +i1*36+i2*5+(i2-i3)*6;
vgc = +i1*36+i2*5;
vhc = +i1*36+i2*5+i3*2;
vic = +i1*36+i2*5+i3*2+i3*18;

```

```

Ans2 = {'Node' 'Voltage (V)' 'Check Voltage (V)'};
    'va' va vac;
    'vb' vb vbc;
    'vc' vc vcc;
    'vd' vd vdc;
    've' ve vec;
    'vf' vf vfc;
    'vg' vg vgc;
    'vh' vh vhc;
    'vi' vi vic};

```


```
Ans2
```



```
%{
```





```
Ans2 =
```

'Node'	'Voltage (V)'	'Check Voltage (V)'
'va'	[ -30]	[ -30]
'vb'	[ 309.0000]	[ 309]
'vc'	[ 243.0000]	[ 243]
'vd'	[ 108.0000]	[ 108]
've'	[ -50.0000]	[ -50]
'vf'	[ 66.0000]	[ 66]
'vg'	[ 78.0000]	[ 78]
'vh'	[ 70.0000]	[ 70]
'vi'	[ -2.0000]	[ -2]

```
%}
```

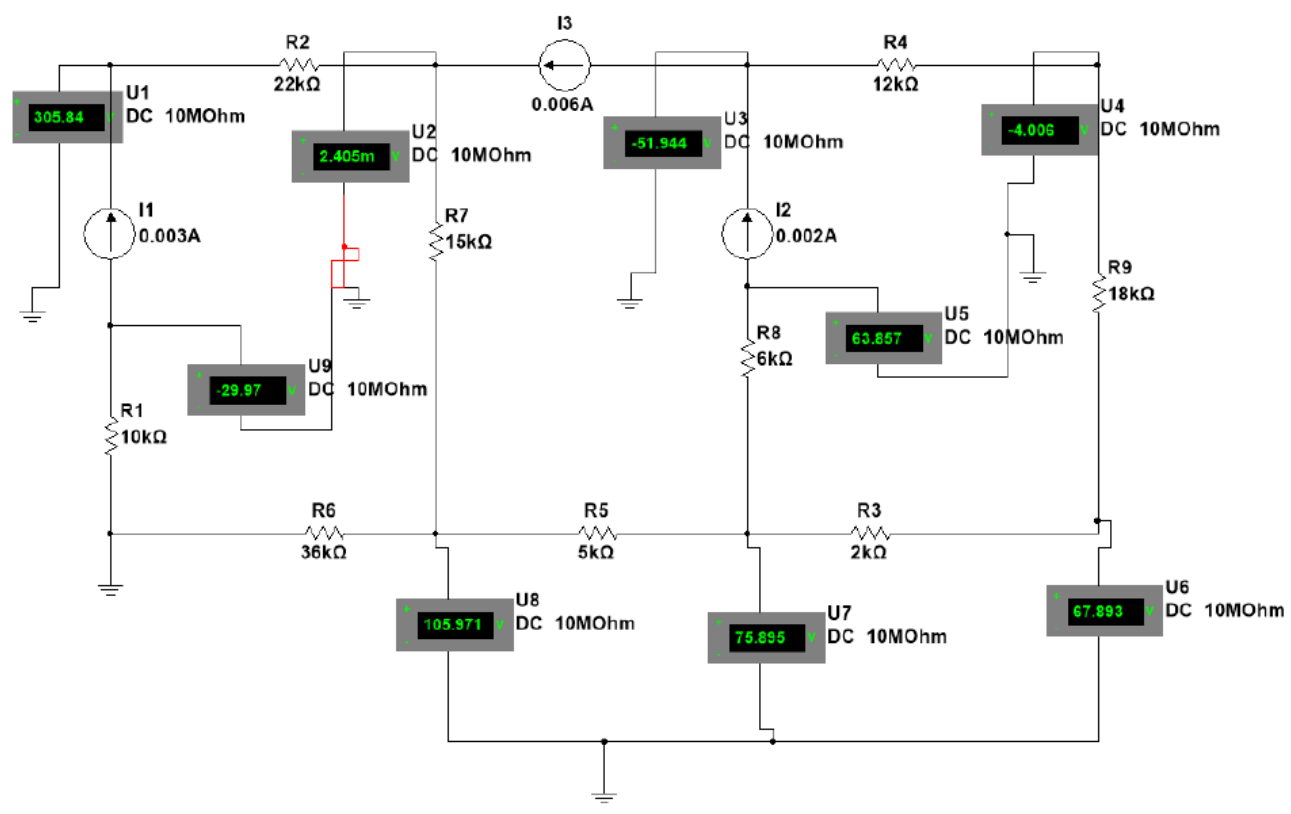


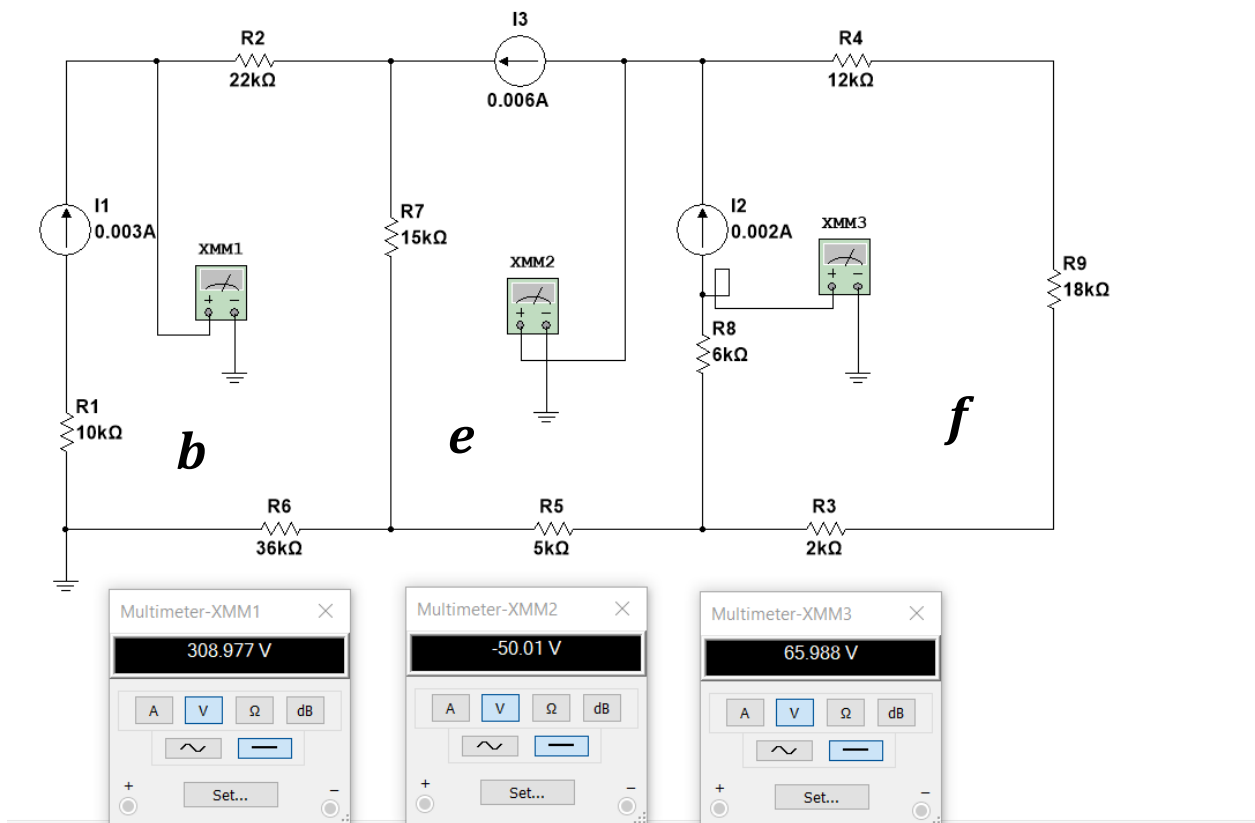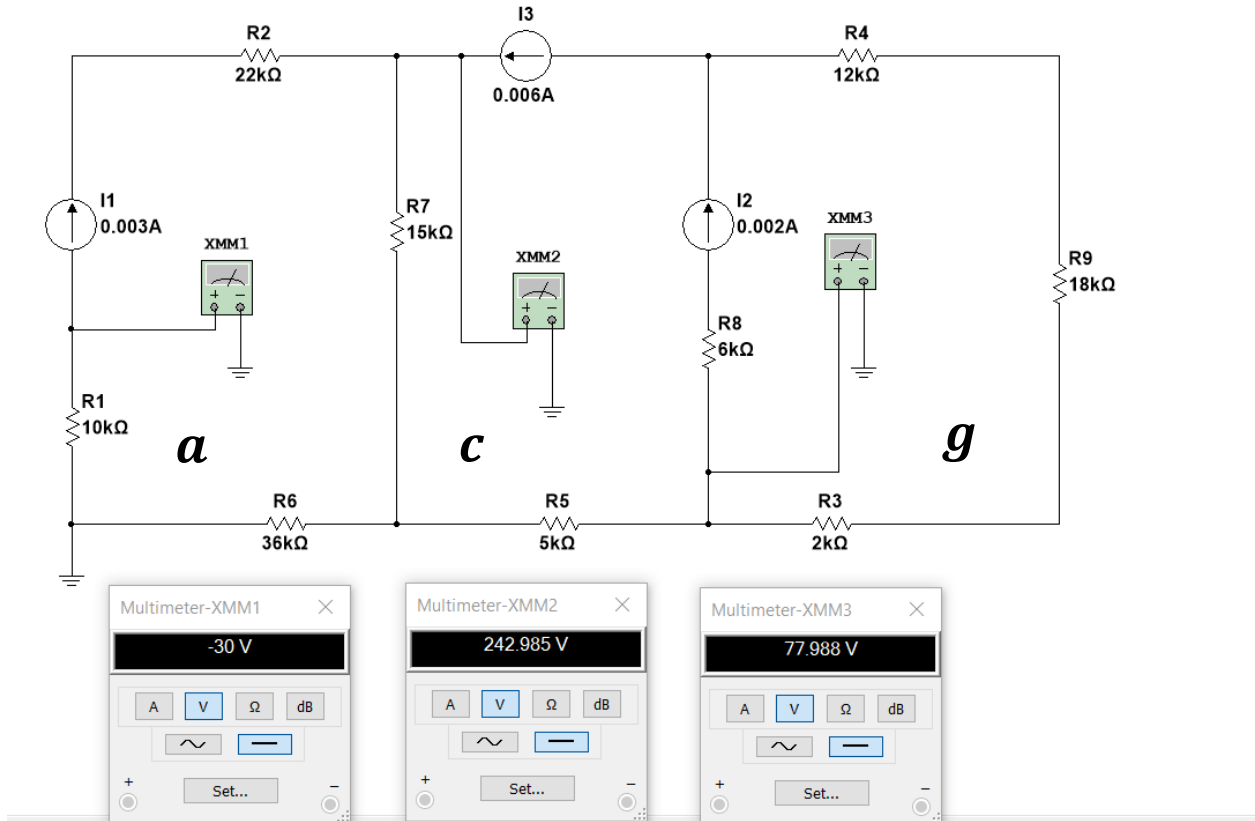

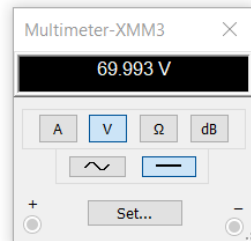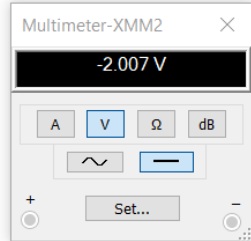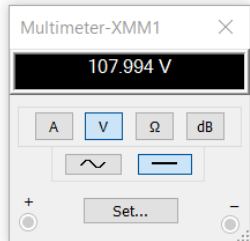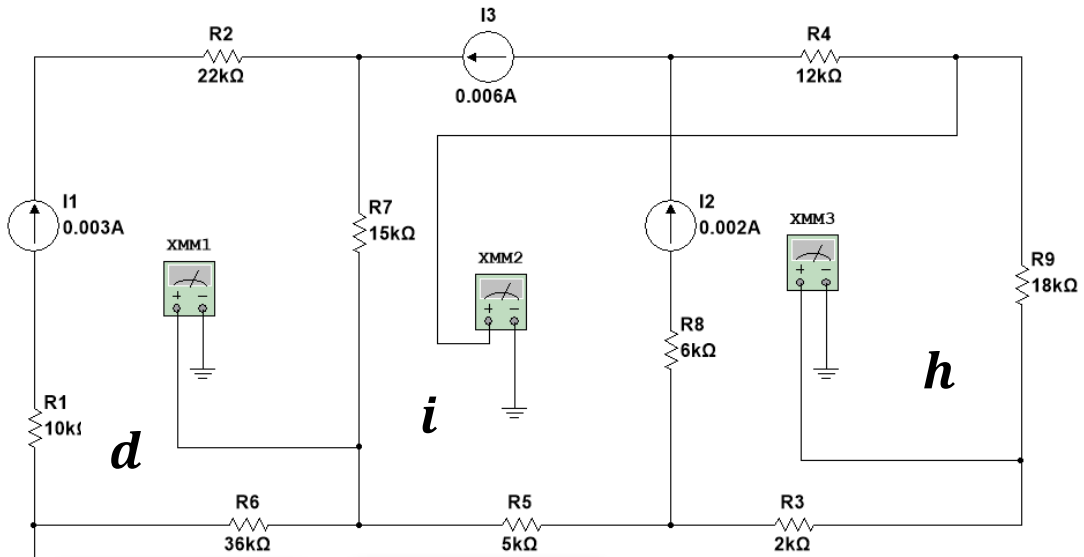


VOLTAGE Node When Voltage Sources Present.

Two Possibilities

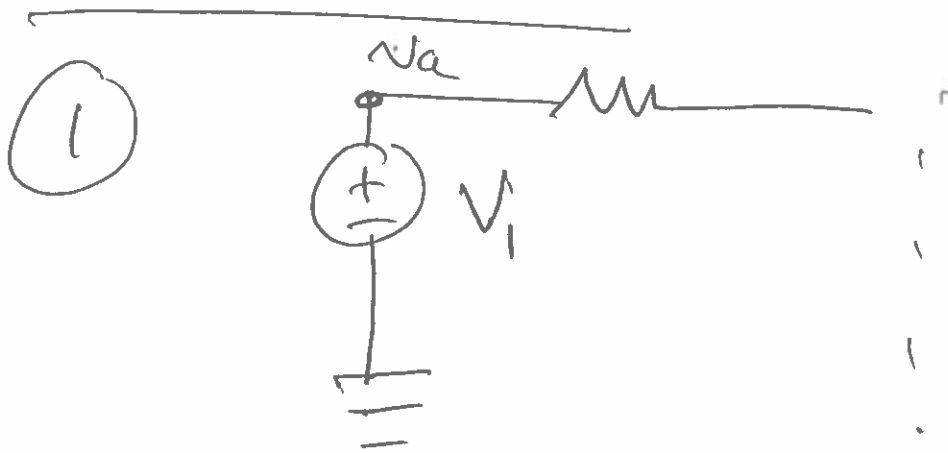

$$V_a = V_1$$

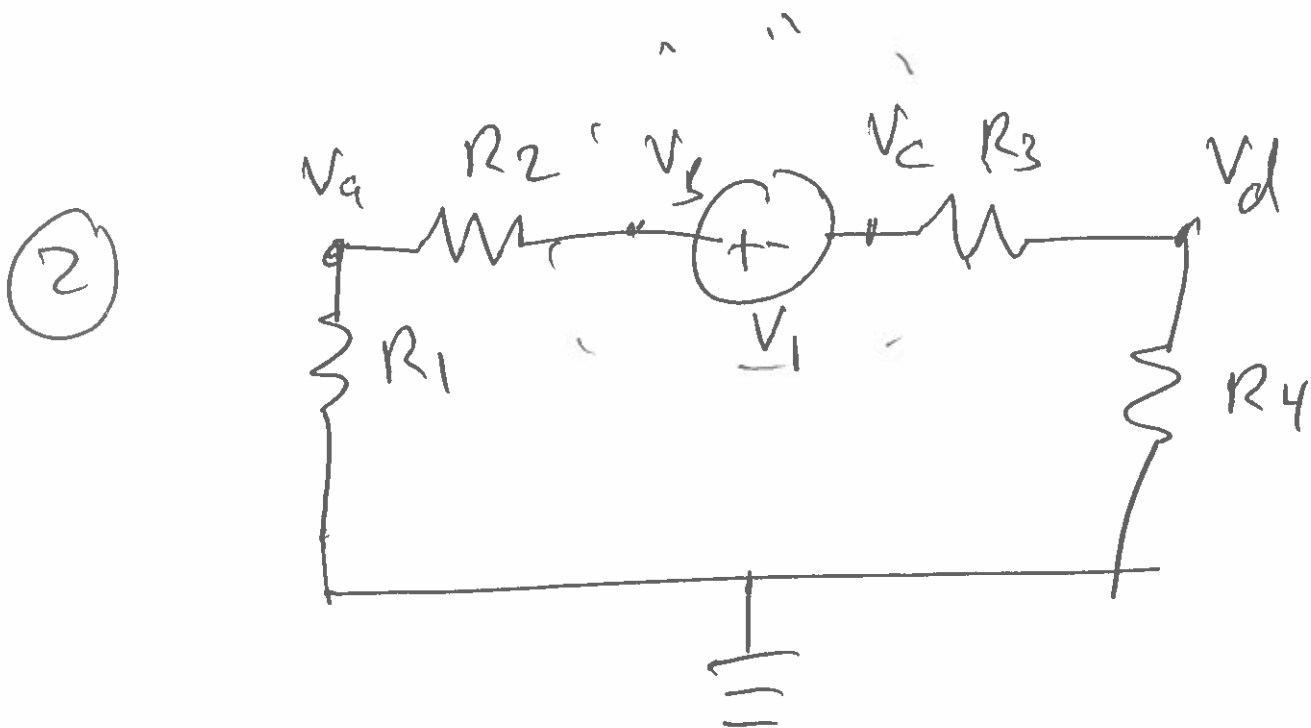

Super node B-C

2 equations

$$\textcircled{1} \rightarrow V_B = V_C + V_1$$

$\textcircled{2}$  Treat both  $V_B$  and  $V_C$  as positive

$$\rightarrow 0 = V_B \left( \frac{1}{R_2} \right) + V_C \left( \frac{1}{R_3} \right) - V_A \left( \frac{1}{R_2} \right) - V_D \left( \frac{1}{R_3} \right)$$


rest

~~$$0 = V_A \left( \frac{1}{R_2} \right) - V_B \left( \frac{1}{R_2} \right)$$~~

~~$$0 = V_D \left( \frac{1}{R_3} \right) - V_C \left( \frac{1}{R_3} \right)$$~~

$$\rightarrow 0 = V_A \left( \frac{1}{R_1} + \frac{1}{R_2} \right) - V_B \left( \frac{1}{R_2} \right)$$
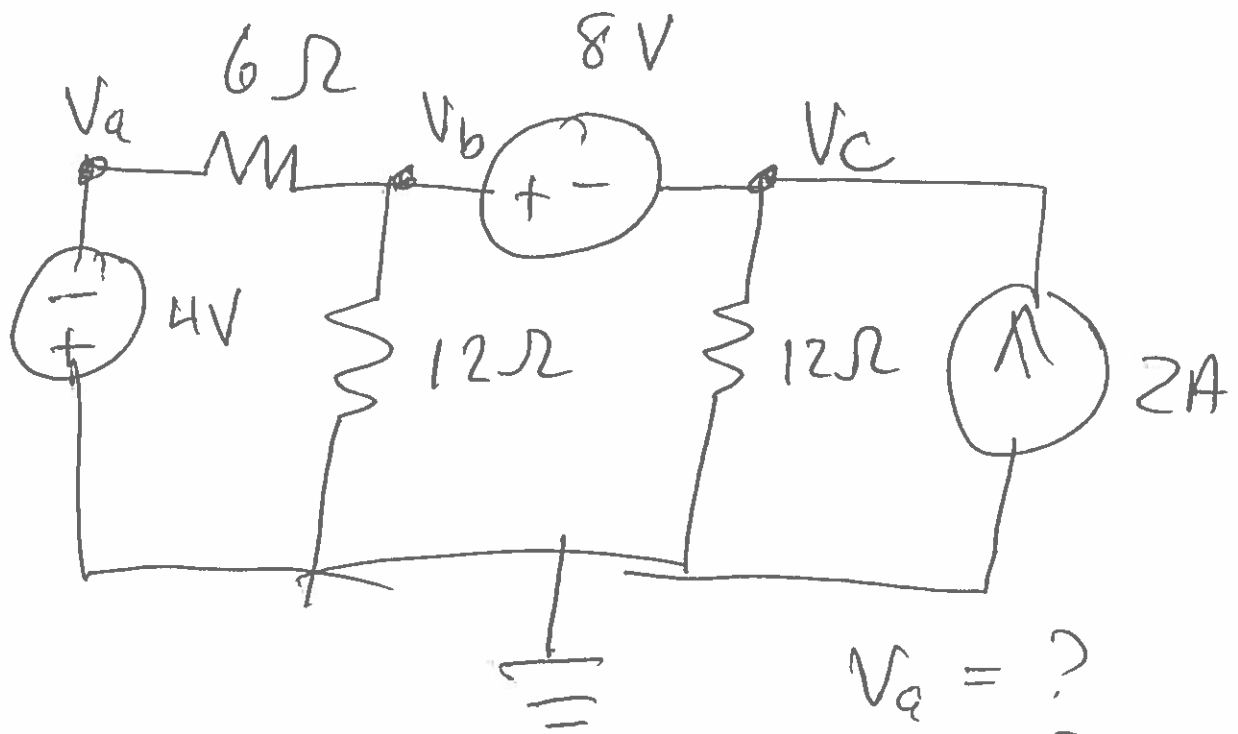
$$\rightarrow 0 = V_D \left( \frac{1}{R_3} + \frac{1}{R_4} \right) - V_C \left( \frac{1}{R_3} \right)$$



$V_a = ?$   
 $V_b = ?$   
 $V_c = ?$

$$V_a = -4V$$

Super node  $\Rightarrow V_b = V_c + 8V$

$$2A = V_b \left( \frac{1}{6\Omega} + \frac{1}{12\Omega} \right) + V_c \left( \frac{1}{12\Omega} \right) - V_a \left( \frac{1}{6\Omega} \right)$$


$$2A = (V_c + 8V) \left( \frac{2+1}{12\Omega} \right) + V_c \left( \frac{1}{12\Omega} \right) - (-4V) \frac{2}{12\Omega}$$

$$\cancel{24V} - 8V = 3V_C + \cancel{24V} + V_C$$

$$-8V = 4V_C \Rightarrow \boxed{V_C = -2V}$$

$$V_B = V_C + 8V = -2V + 8V = \underline{6V}$$
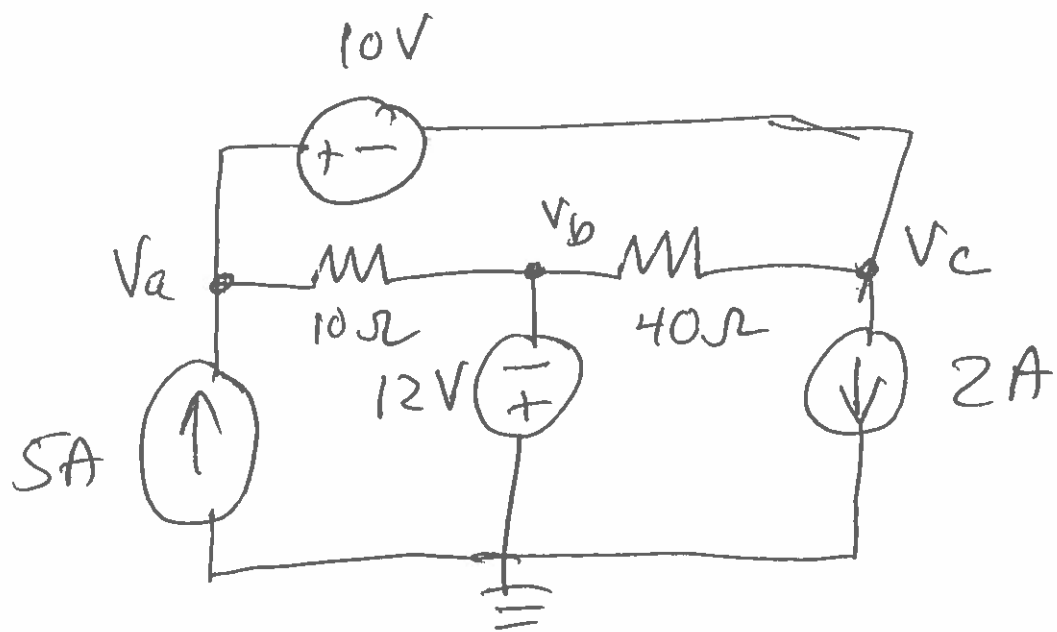
$$\boxed{V_A = -4V, V_B = +6V, V_C = -2V}$$



$$V_b = -12V$$

Supernode

$$V_a = V_c + 10V$$

$$5A - 2A = V_a \left( \frac{1}{10\Omega} \right) + V_c \left( \frac{1}{40\Omega} \right) - V_b \left( \frac{1}{10\Omega} + \frac{1}{40\Omega} \right)$$

$$3A = (V_c + 10V) \left( \frac{1}{10\Omega} \right) + V_c \left( \frac{1}{40\Omega} \right) - (-12V) \left( \frac{4+1}{40\Omega} \right)$$

$$120V = 4V_c + 40V + V_c + 60V$$

$$20V = 5V_c \Rightarrow V_c = 4V$$

$$V_a = V_c + 10V = 4V + 10V$$

$$V_a = 14V$$

$$V_b = -12V$$

$$V_c = 4V$$


# Mesh Currents

- must be planar circuits.

A mesh is a loop which does not contain any other loops within it.

Convention is all mesh currents go clockwise.

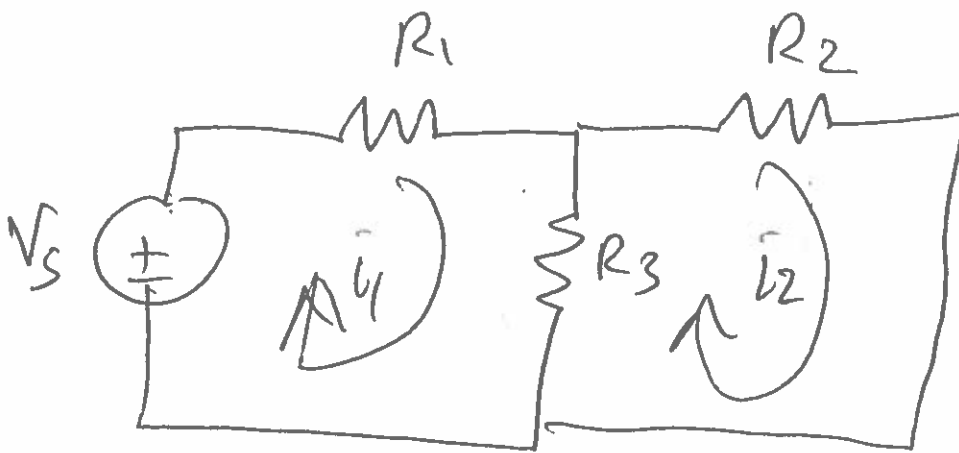This is primarily another way of using Kirchhoff's Loop Rule.



$$\text{Left loop } +V_s - i_1 R_1 - (i_1 - i_2) R_3 = 0$$

$$\text{Right loop } \cancel{(i_1 - i_2)} R_3 - i_2 R_2 = 0$$

$(i_1 - i_2)$

$$V_S = \hat{I}_1 (R_1 + R_3) - \hat{I}_2 R_3$$

$$0 = -\hat{I}_1 (R_3) + \hat{I}_2 (R_3 + R_2)$$