

$$i = ?$$

$$i = i_2 - i_1$$

$$i_1 / -28V = i_1 (6\Omega + 2\Omega) - i_2 (2\Omega)$$

$$i_2 / -8V = i_2 (2\Omega + 4\Omega) - i_3 (4\Omega) - i_1 (2\Omega)$$

$$i_3 / 0 = i_3 (4\Omega + 12\Omega) - i_2 (4\Omega)$$

$$i_1(6\Omega + 2\Omega) - i_2(2\Omega) = -28V$$

$$-i_1(2\Omega) + i_2(2\Omega + 4\Omega) - i_3(4\Omega) = -8V$$

$$-i_2(4\Omega) + i_3(4\Omega + 12\Omega) = 0$$

$$R = \begin{bmatrix} (6+2) & -2 & 0 \\ -2 & (2+4) & -4 \\ 0 & -4 & (4+12) \end{bmatrix}$$

$$V = \begin{bmatrix} 28 \\ -8 \\ 0 \end{bmatrix}$$

$$i\hat{i} = R \setminus V$$

$$\hat{i}_1 = i\hat{i}(1)$$

$$\hat{i}_1 = -4.33A$$

$$\hat{i}_2 = i\hat{i}(2)$$


$$\hat{i}_2 = -3.33A$$

$$\hat{i}_3 = i\hat{i}(3)$$

$$\hat{i}_3 = -0.833A$$

$$\hat{i} = \hat{i}_2 - \hat{i}_1 = -3.33A - (-4.33A)$$

$$\hat{i} = 1.0A$$

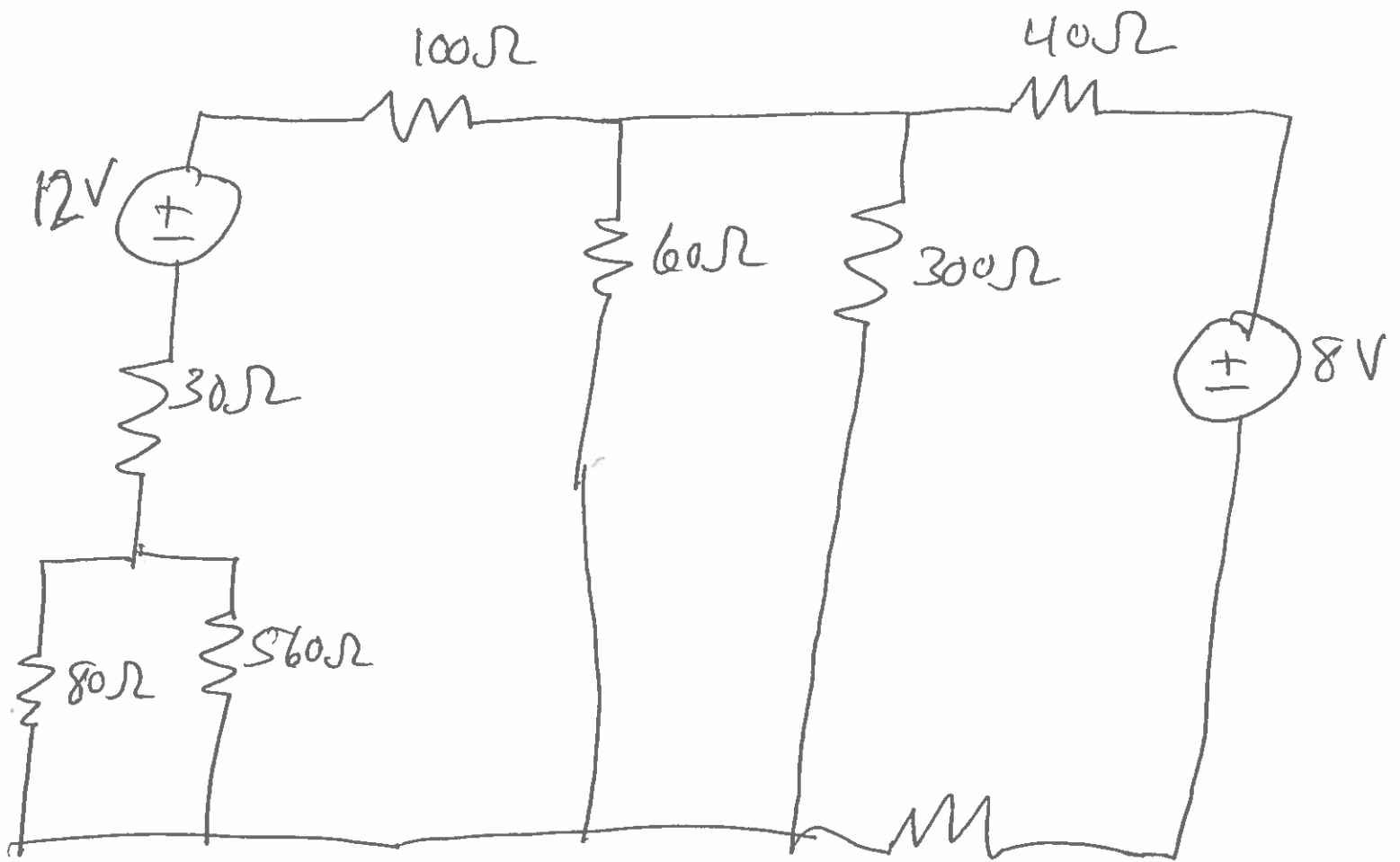


$$P_{12\text{V}} = ?$$

$$P_{8\text{V}} = ?$$

$$P_{30\Omega} = ?$$

$$\frac{1}{80\Omega} + \frac{1}{560\Omega} = \frac{8}{560\Omega} \Rightarrow R_{\text{ref}} = 70\Omega$$
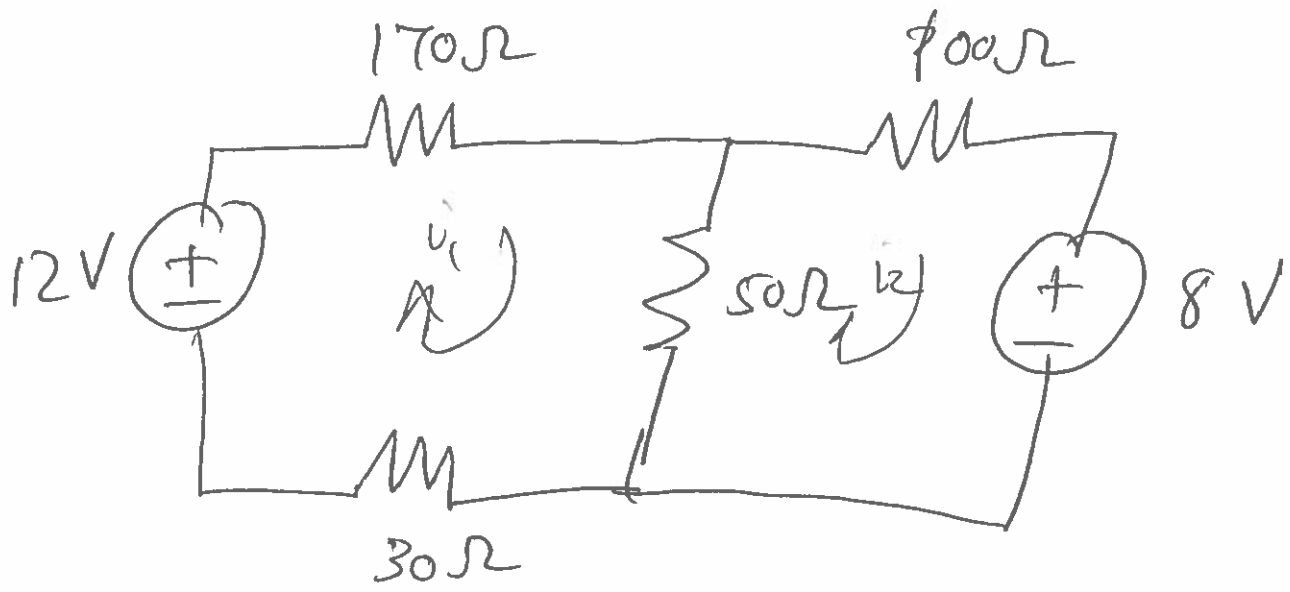
$$60\Omega / 300\Omega \Rightarrow 50\Omega$$



$$+12V = i_1 (30\Omega + 170\Omega + 50\Omega) - i_2 (50\Omega)$$

$$\textcircled{\times} -8V = i_2 (100\Omega + 50\Omega) - i_1 (50\Omega)$$

$$12V = 250\Omega i_1 - 50\Omega i_2$$

$$-8V = -50\Omega i_1 + 150\Omega i_2$$

$$36V = 750\Omega i_1 - 150\Omega i_2$$

$$-8V = -50\Omega i_1 + 150\Omega i_2$$

$$\textcircled{\times} 28V = 700\Omega i_1 \rightarrow i_1 = 0.04A$$

$$i_2 = \frac{i_1(250\Omega) - 12V}{50\Omega} = -0.04A$$

$$P_{12V} = i_1 V = (0.04A) 12V$$

$$P_{12V} = +0.48W$$


$$P_{8V} = -i_2 V = -(-0.04A) 8V$$

$$P_{8V} = +0.32W$$

$$P_{30\Omega} = -i_1^2 R_{30}$$

$$= -(0.04A)^2 (30\Omega)$$

$$P_{30\Omega} = -0.048W$$

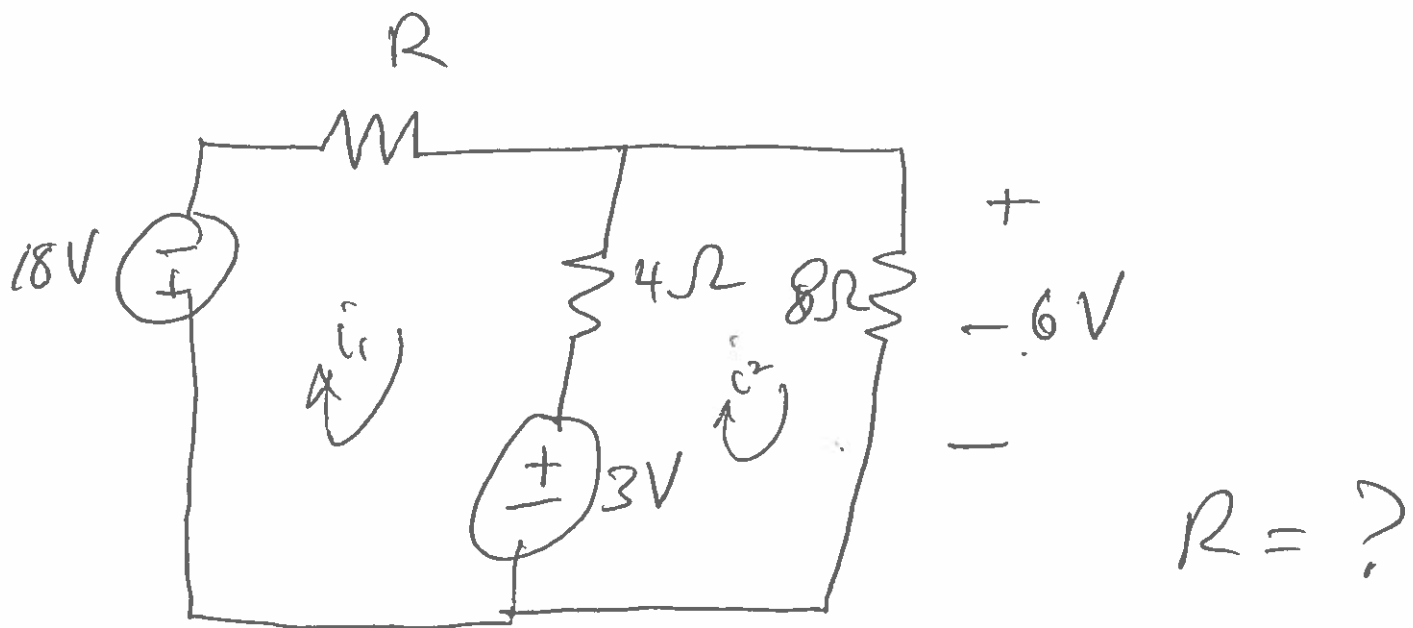

$$i_1 / -18V = i_1 (R + 4\Omega) - i_2 (4\Omega) - 3V$$

$$i_2 \quad 3V = i_2 (4\Omega + 8\Omega) - i_1 (4\Omega)$$

$$-21V = i_1 (R + 4\Omega) - i_2 (4\Omega)$$

$$3V = -i_1 (4\Omega) + i_2 (4\Omega + 8\Omega)$$

$$i_2 = \frac{V}{R} = \frac{-6V}{8\Omega} = -0.75A$$

$$-21V = \hat{i}_1 (R + 4\Omega) - (-1.75A)(4\Omega)$$

$$+3V = -\hat{i}_1 (4\Omega) + (-1.75A)(4\Omega + 8\Omega)$$

$$\frac{3}{4} \times 23 = -9V$$

$$3V + 9V = -\hat{i}_1 (4\Omega)$$


$$\hat{i}_1 = \frac{-12V}{4\Omega} = -3A$$

$$-21V = (-3A)(R + 4\Omega) - (-1.75A)(4\Omega) - 3V$$

$$\frac{-24V}{-3A} = R + 4\Omega$$

$$8\Omega = R + 4\Omega$$

$$\Rightarrow R = 4\Omega$$

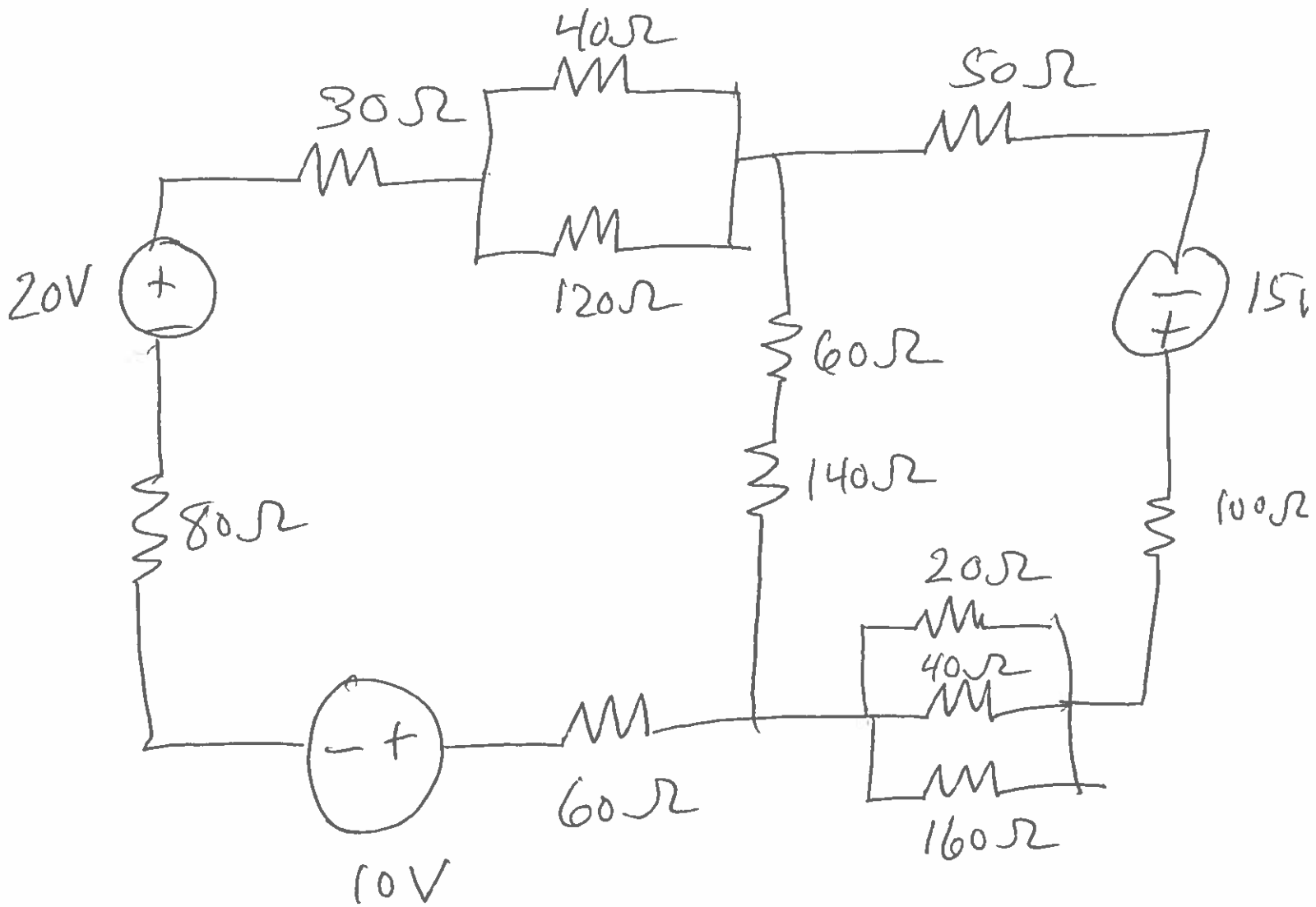

$$P_{140\Omega} = ?$$

$$\frac{1}{40\Omega} + \frac{1}{120\Omega} = \frac{3+1}{120\Omega} = \frac{4}{120\Omega} = \frac{1}{30\Omega}$$

$$\frac{1}{20\Omega} + \frac{1}{40\Omega} + \frac{1}{160\Omega} = \frac{8+4+1}{160} = \frac{13}{160\Omega}$$

$$\frac{160}{13} \Omega + 150\Omega = 162.3$$

