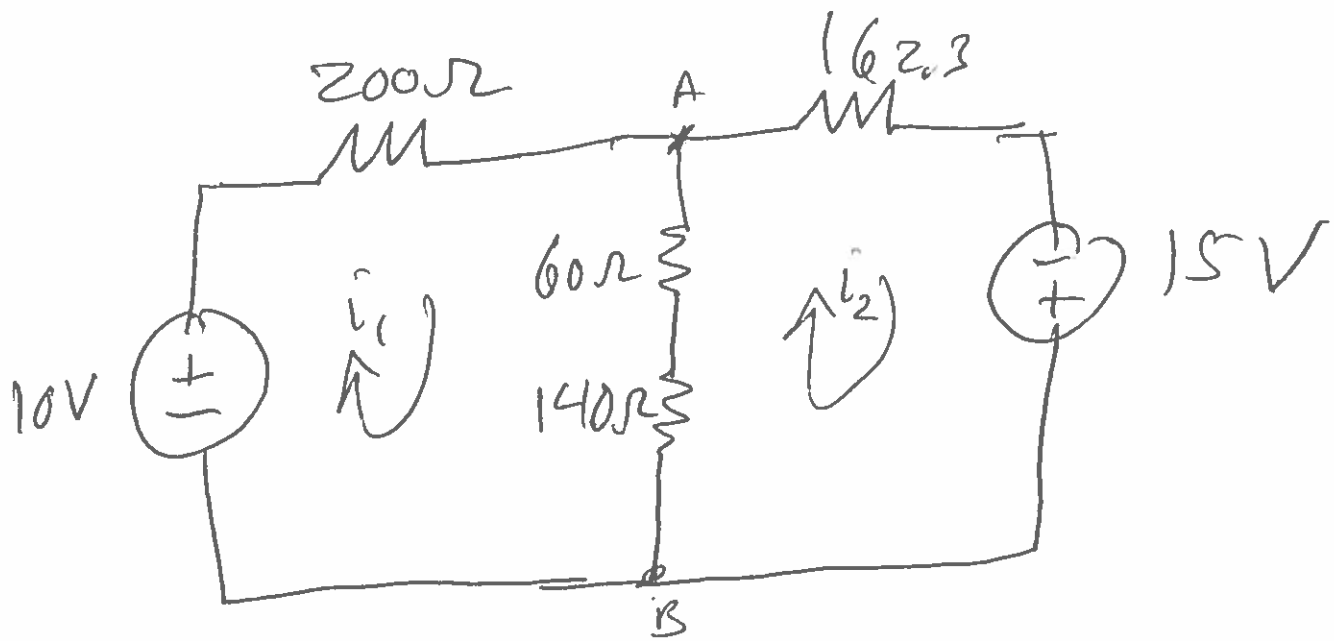


$P_{140\Omega} = ?$

$$\frac{1}{40\Omega} + \frac{1}{120\Omega} = \frac{3+1}{120\Omega} = \frac{4}{120\Omega} = \frac{1}{30\Omega}$$

$$\frac{1}{20\Omega} + \frac{1}{40\Omega} + \frac{1}{160\Omega} = \frac{8+4+1}{160} = \frac{13}{160\Omega}$$

$$\frac{160}{13} \Omega + 150\Omega = 162.3$$



$$+10V = \hat{i}_1 (200\Omega + 60\Omega + 140\Omega) - \hat{i}_2 (60\Omega + 140\Omega)$$

$$+15V = \hat{i}_2 (140\Omega + 60\Omega + 162.3\Omega) - \hat{i}_1 (60\Omega + 140\Omega)$$

$$- \hat{i}_1 (60\Omega + 140\Omega)$$

$$10V = \hat{i}_1 (400\Omega) - \hat{i}_2 (200\Omega)$$

$$15V = -\hat{i}_1 (200\Omega) + \hat{i}_2 (362.3\Omega)$$

$$10V = \hat{i}_1 (400\Omega) - \hat{i}_2 (200\Omega)$$

$$30V = -\hat{i}_1 (400\Omega) + \hat{i}_2 (\cancel{200\Omega} + 724,6\Omega)$$

$$40V = 524,6\Omega \hat{i}_2$$

$$\hat{i}_2 = \frac{40V}{524,6\Omega} = 0,0762A$$

$$\hat{i}_1 = \frac{10V + (0,0762A)(200\Omega)}{400\Omega}$$

$$\hat{i}_1 = 0,0631A$$

$$P_{140\Omega} = i^2 R$$

$$\hat{i} = \hat{i}_2 - \hat{i}_1$$

$$\hat{i} = 0,0762A - 0,0631A$$

$$P_{140\Omega} = (0,0131A)^2 (140\Omega) \quad \hat{i} = 0,0131A$$

$$P = 0,240W$$

$$\Delta V_{A \rightarrow B} = 60 \Omega (-\hat{i}_1 + \hat{i}_2) + 140 \Omega (-\hat{i}_1 + \hat{i}_2)$$

$$= 200 \Omega (\hat{i}_2 - \hat{i}_1)$$


$$= 200 \Omega (0.0131 \text{ A}) = +2.62$$

$\Rightarrow B$ is higher potential

How to handle current sources in mesh analysis?

again 2 cases

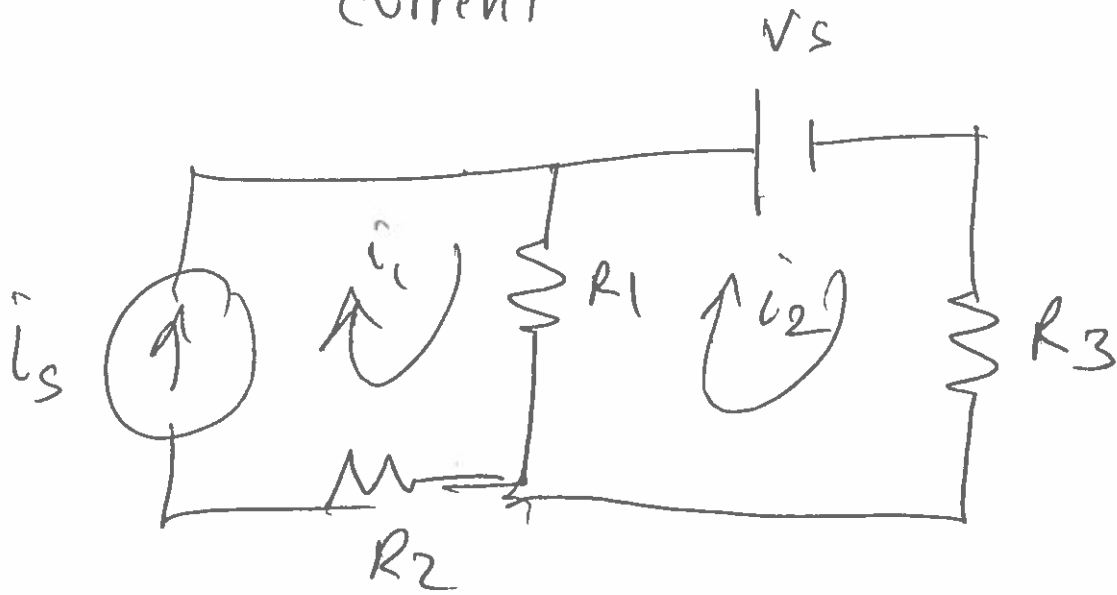① current source only involves 1 mesh current



$$\hat{i}_1 = \hat{i}_s$$


$$-V_s = \hat{i}_2(R_1 + R_3) - \hat{i}_1 R_1$$

$$\hat{i}_2(R_1 + R_3) = \hat{i}_s R_1 - V_s$$

$$\hat{i}_2 = \frac{\hat{i}_s R_1 - V_s}{R_1 + R_3}$$

2 case current source involves


2 meshes \Rightarrow super mesh

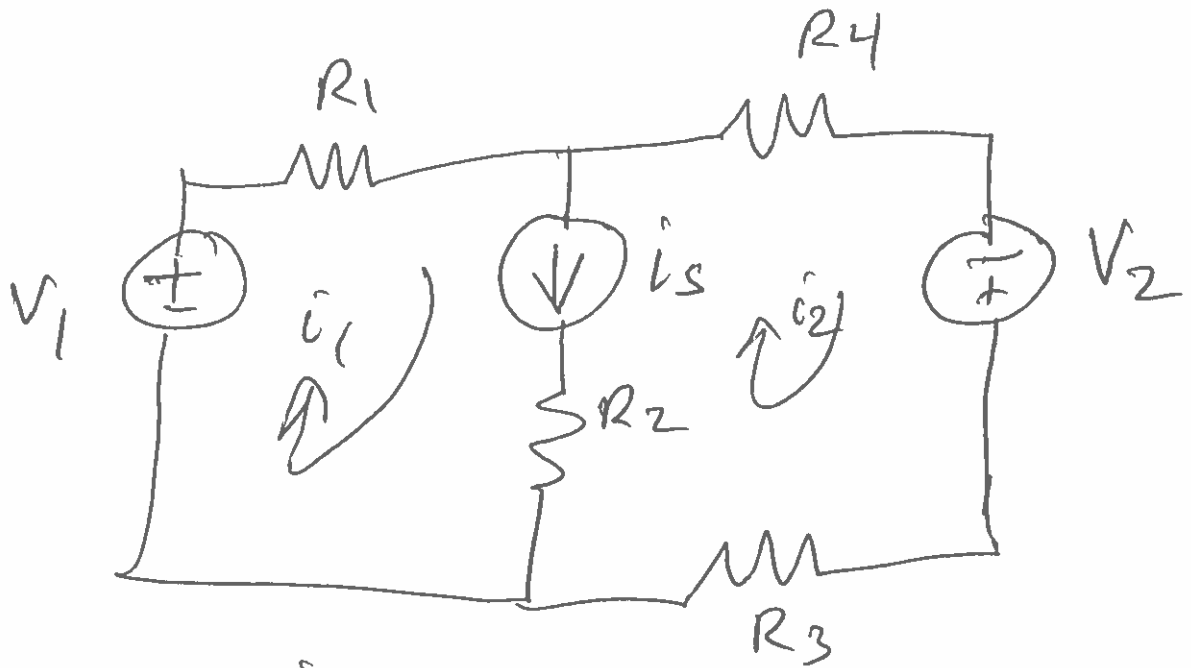

$$\dot{i}_1 - \dot{i}_2 = +i_s \quad 1 \text{ eqn}$$

$$V_1 + V_2 = \dot{i}_1 (R_1) \cancel{+ R_2} + \dot{i}_2 (R_4 + R_3)$$

example 1

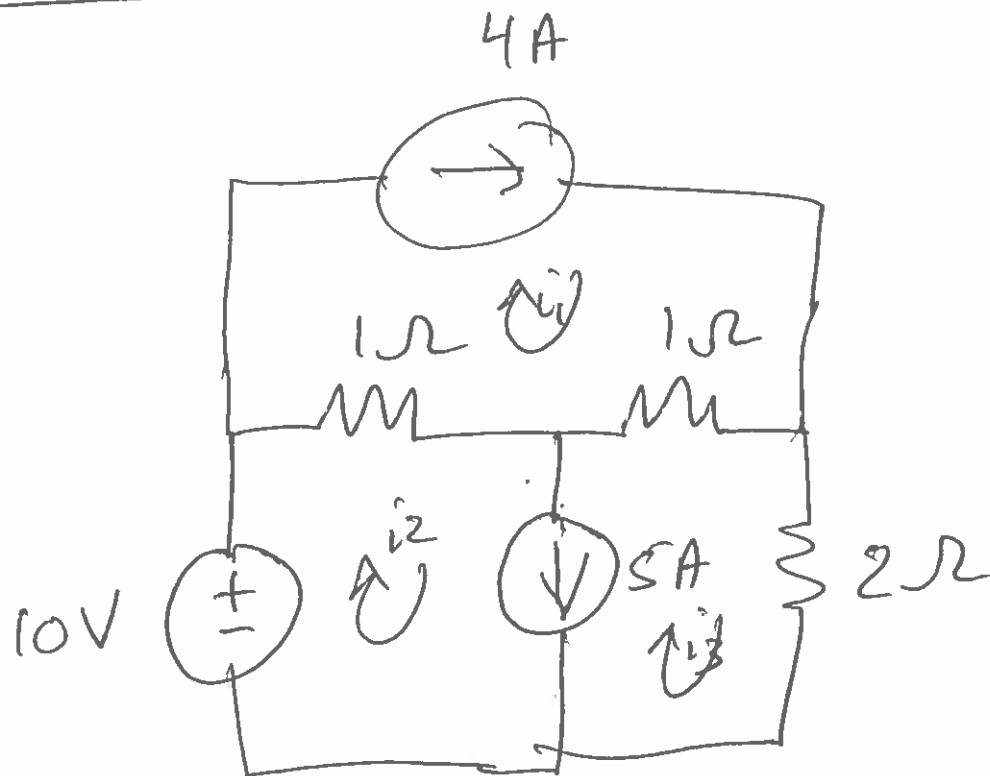

Find $i_1, i_2, i_3 \Rightarrow i_1 = 4A$

$$i_2 - i_3 = 5A$$

$$10V = i_2(1\Omega) + i_3(1\Omega + 2\Omega)$$

$$- i_1(1\Omega + 1\Omega)$$

$$10V + (4A)(2\Omega) = i_2(1\Omega) + i_3(3\Omega)$$

$$\underbrace{18V}_{18V} = (5A + i_3)(1\Omega) + i_3(3\Omega)$$


$$13V = i_3 (4\Omega)$$

$$\hat{i}_3 = \frac{13}{4} A$$

$$\hat{i}_2 = 5A + \hat{i}_3 = \frac{33}{4} A$$

$$\hat{i}_1 = 4A \quad \hat{i}_3 = 3.25A \quad \hat{i}_2 = 8.25A$$

WHAT IS VOLTAGE ACROSS 5A SOURCE ?

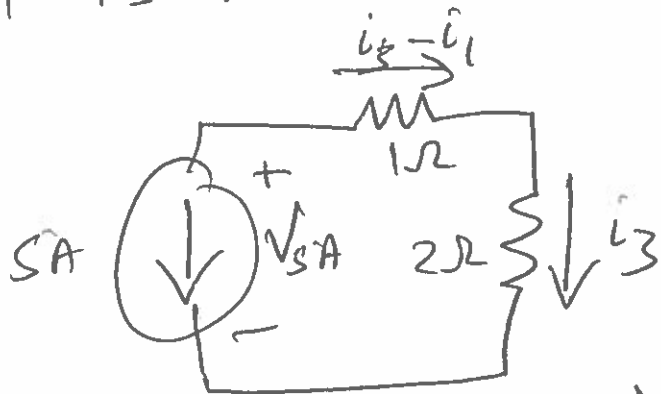


$$V_{SA} - (i_2 - i_1)(1\Omega) - i_3(2\Omega) = 0$$

$$V_{SA} = i_3(2\Omega) - i_1(1\Omega)$$

$$V_{SA} = \left(\frac{13}{4} \cdot 2\right) V - (4A)(1\Omega)$$

$$9.75V - 4V$$

$$= +5.75V$$

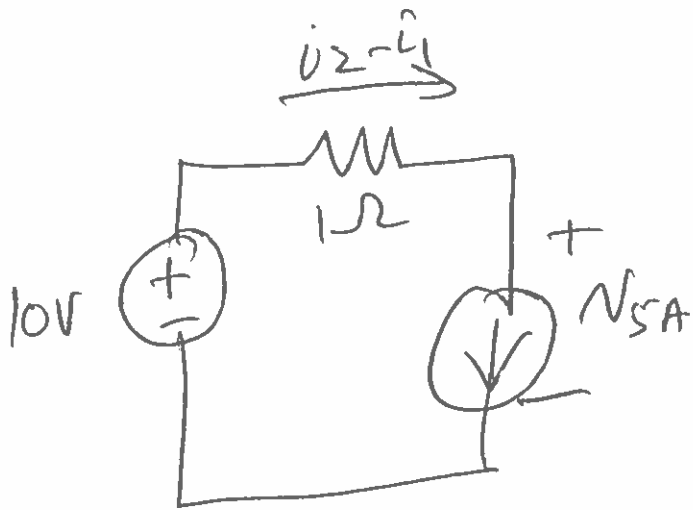


$$10V - (i_2 - i_1)(1\Omega) - V_{SA} = 0$$

$$V_{SA} = 10V - (8.25A - 4A)(1\Omega)$$

$$= 10V - 4.25A = 5.75V$$

ex 2

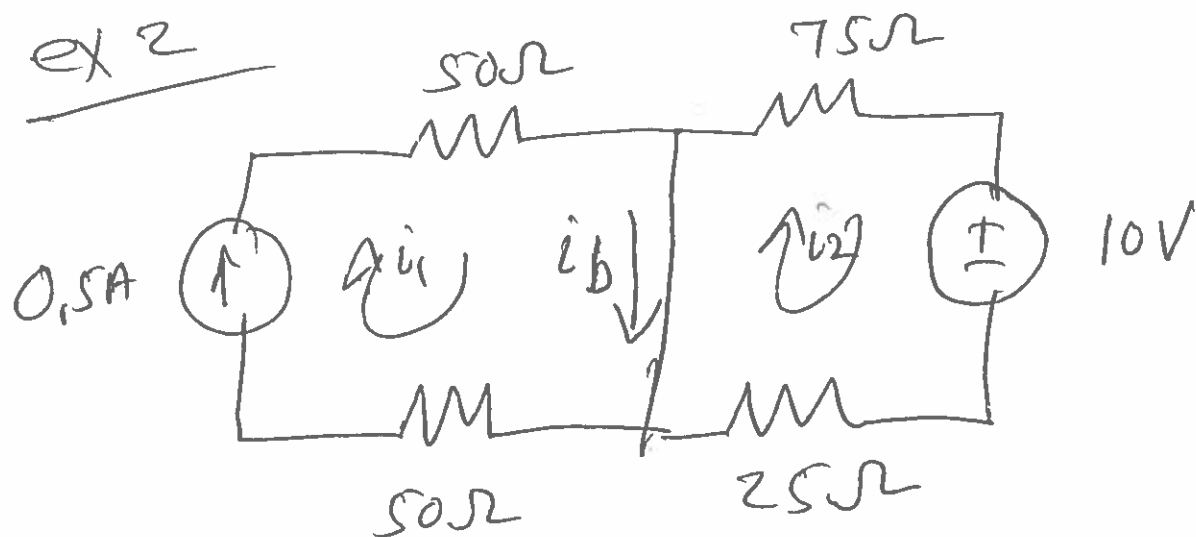


$$i_b = i_1 - i_2$$

$$i_1 = 0.5 \text{ A}$$

$$\text{for } i_2 \Rightarrow -10 \text{ V} = i_2 (75 \Omega + 25 \Omega)$$

$$i_2 = \frac{-10 \text{ V}}{100 \Omega} = -0.1 \text{ A}$$
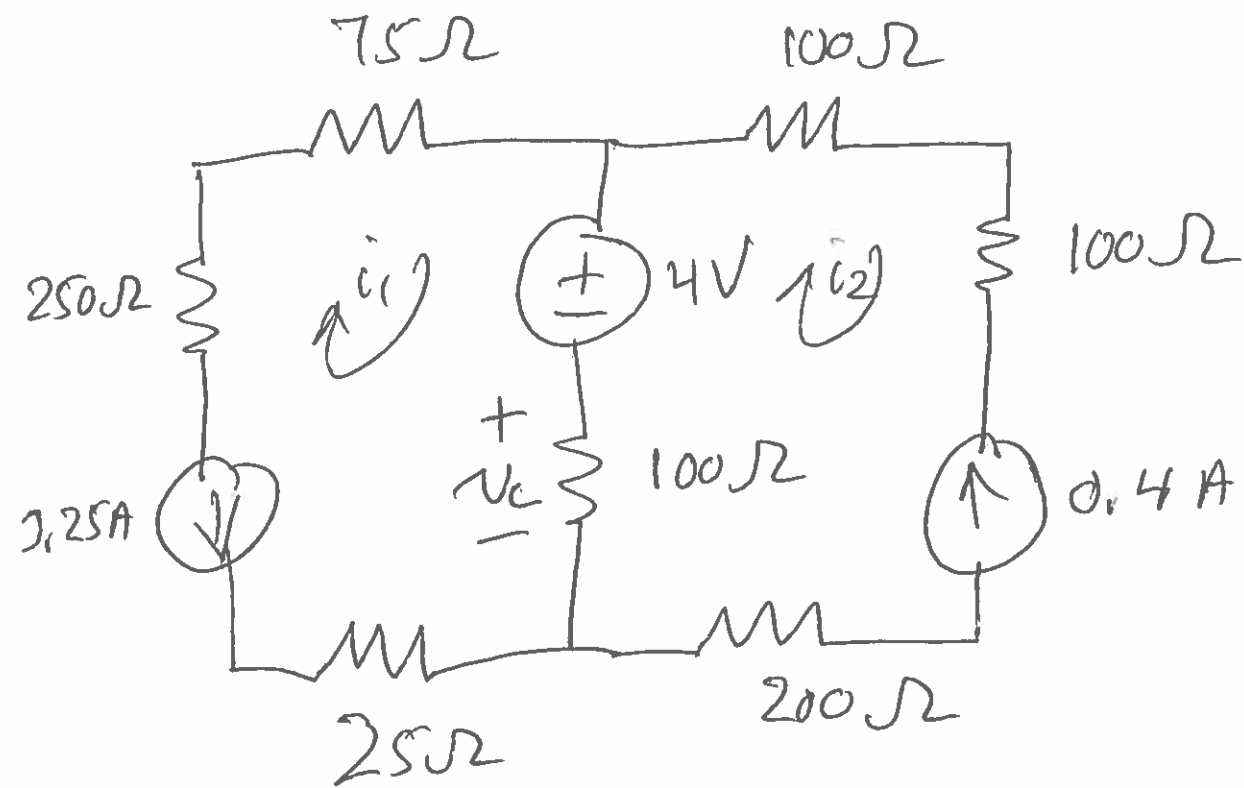
$$i_b = 0.5 \text{ A} - (-0.1 \text{ A}) = \underline{0.6 \text{ A}}$$



$$V_c = ?$$

$$\hat{i}_1 = -0.25 \text{ A}$$

$$\hat{i}_2 = -0.40 \text{ A}$$


$$V_c = (\hat{i}_1 - \hat{i}_2) 100 \Omega$$

$$V_c = (-0.25 \text{ A} - (-0.40 \text{ A})) 100 \Omega$$

$$= +0.15 \text{ A} (100 \Omega)$$

$$= +15 \text{ V}$$



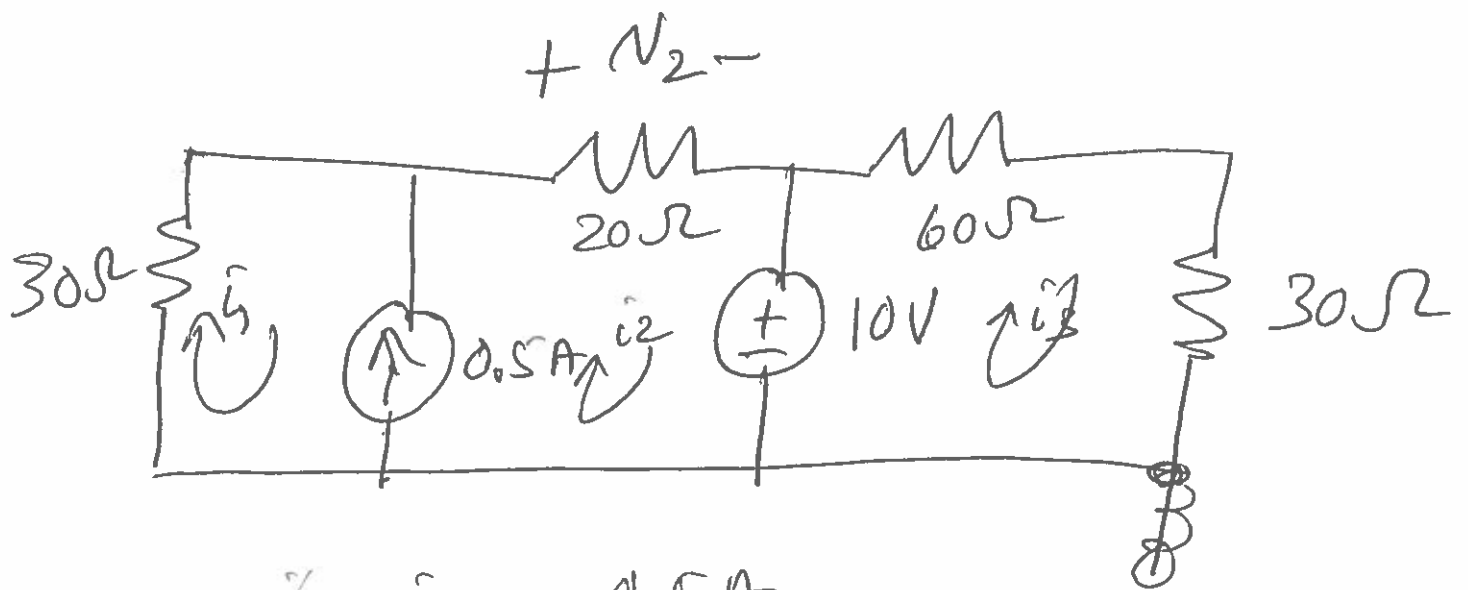

$$i_2 - i_1 = 0.5 \text{ A}$$

$$-10 \text{ V} = i_1 (30 \Omega) + i_2 (20 \Omega)$$

$$-10 \text{ V} = i_1 (30 \Omega) + (0.5 \text{ A} + i_1) (20 \Omega)$$

$$-10 \text{ V} = i_1 (50 \Omega) + 10 \text{ V}$$

$$i_1 = \frac{-20 \text{ V}}{50 \Omega} = -0.4 \text{ A}$$

~~$$V_2 = (-0.4 \text{ A})(20 \Omega) = -8 \text{ V}$$~~