
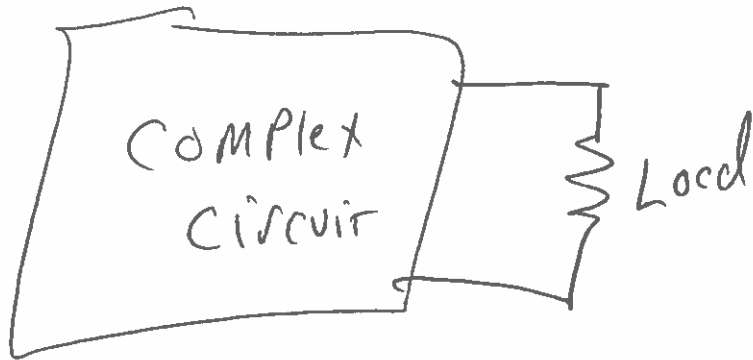

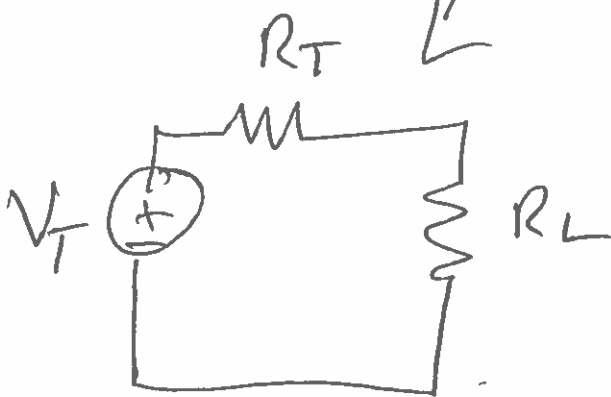
# BASIC Idea of chapter 5

All circuits can be reduced to 1 of 2 types



or






Thevenin  
Equivalent  
circuit



Norton  
Equivalent  
~~circuit~~  
circuit


# Source Transformation

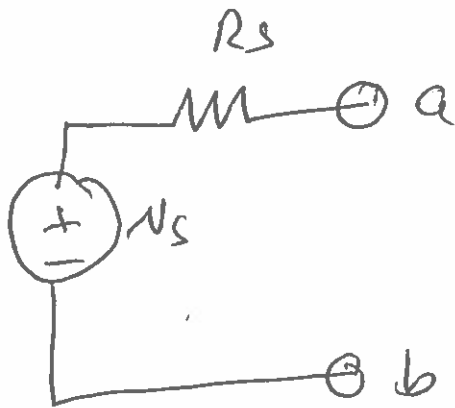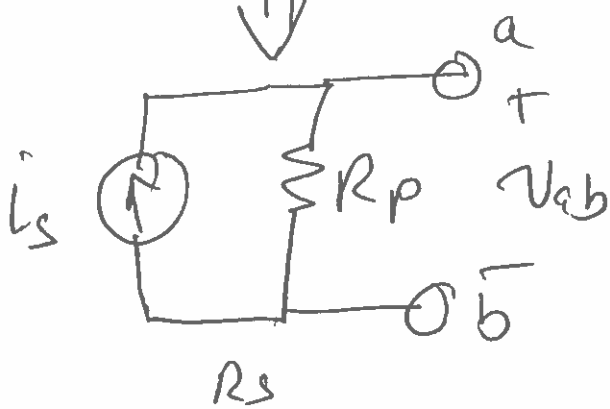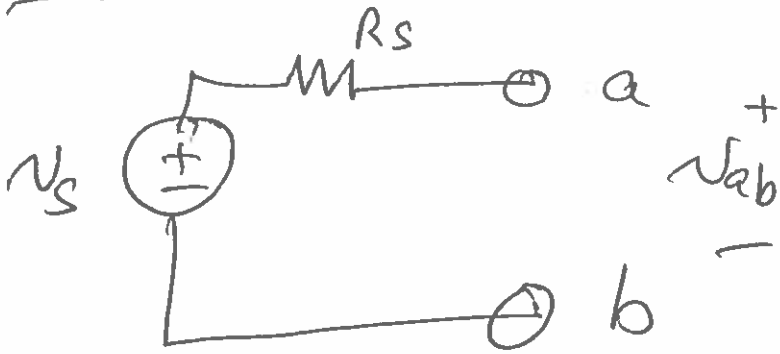

$$V_{ab} = V_S$$

Open circuit no voltage dropped across  $R_S$

$$V_{ab} = V_S$$

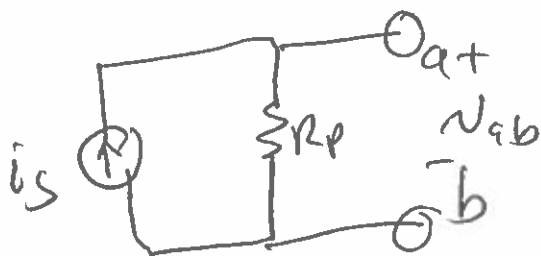



$$V_{ab} = i_S R_P$$

To be equivalent circuits

$$V_{ab} = V_{ab}$$

$$V_S = \hat{I}_S R_P$$

$$\hat{I}_S = \frac{V_S}{R_P}$$

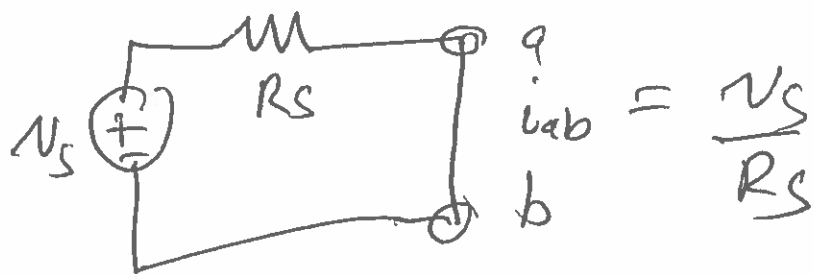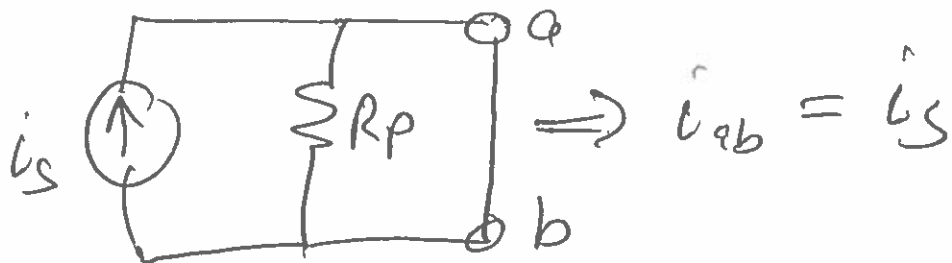

$$\hat{I}_{ab} = I_{ab}$$


$$\hat{I}_S = \frac{V_S}{R_S}$$

$$V_S = \hat{I}_S R_P$$



$$\hat{I}_S = \frac{V_S}{R_S}$$

$$\Rightarrow R_P = R_S$$


# Two Sources are equivalent

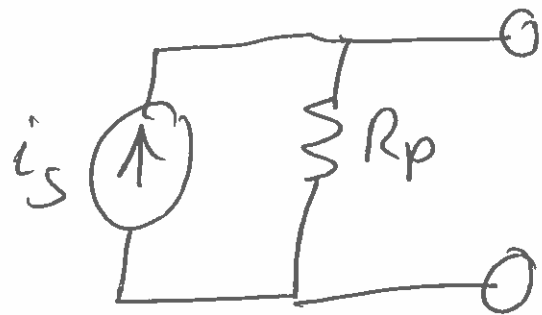

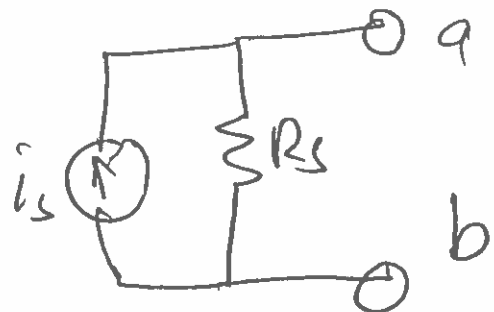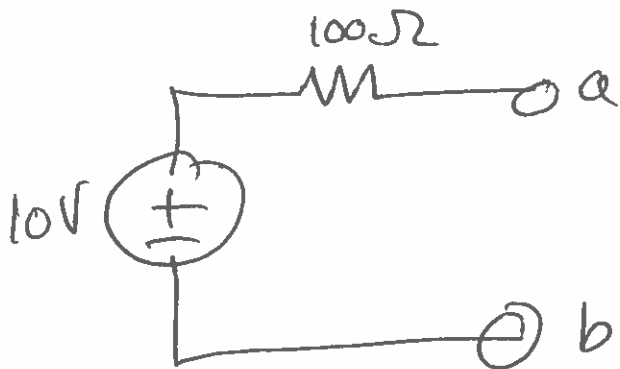
if  $R_p = R_s$  and  $i_s = \frac{V_s}{R_s}$  or  $V_s = i_s R_s$




$$i_s = \frac{10V}{100\Omega} = 0.10A$$

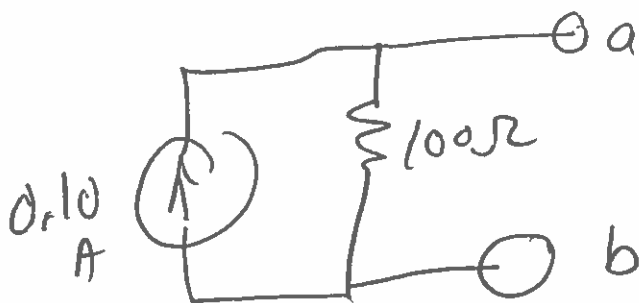

Let's TEST

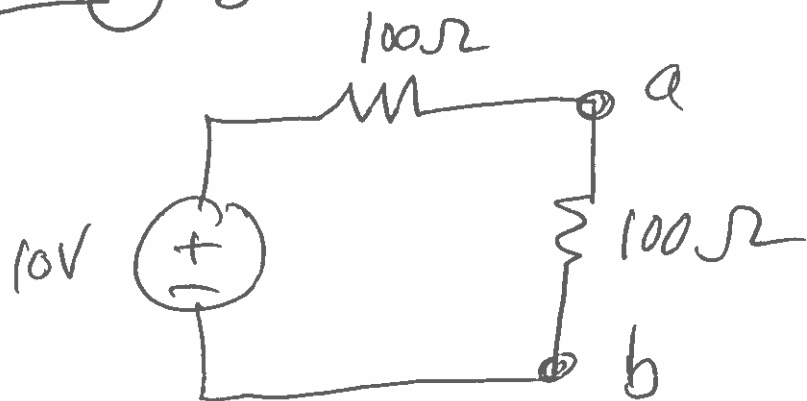

$$V_{ab} = 5V$$

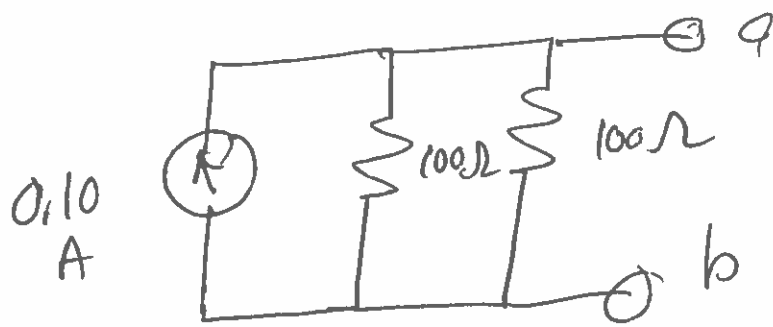



$$V_{ab} = I_{ab} (100\Omega)$$

$$I_{ab} = 0.05 \text{ A}$$


$$V_{ab} = (0.05 \text{ A})(100\Omega) = 5 \text{ V} \quad \checkmark$$
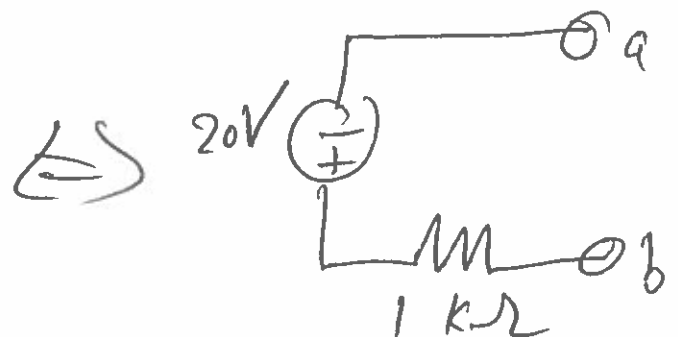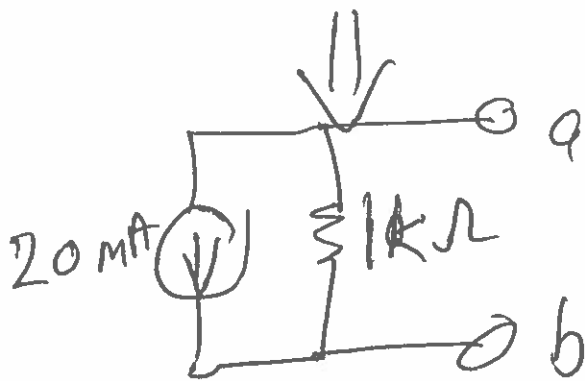
### Dual Circuits

Dual circuits are circuits where an equivalent circuit is obtained by replacing  $V$  sources with  $i$ -sources and  $R$  by  $G (\frac{1}{R})$




ex



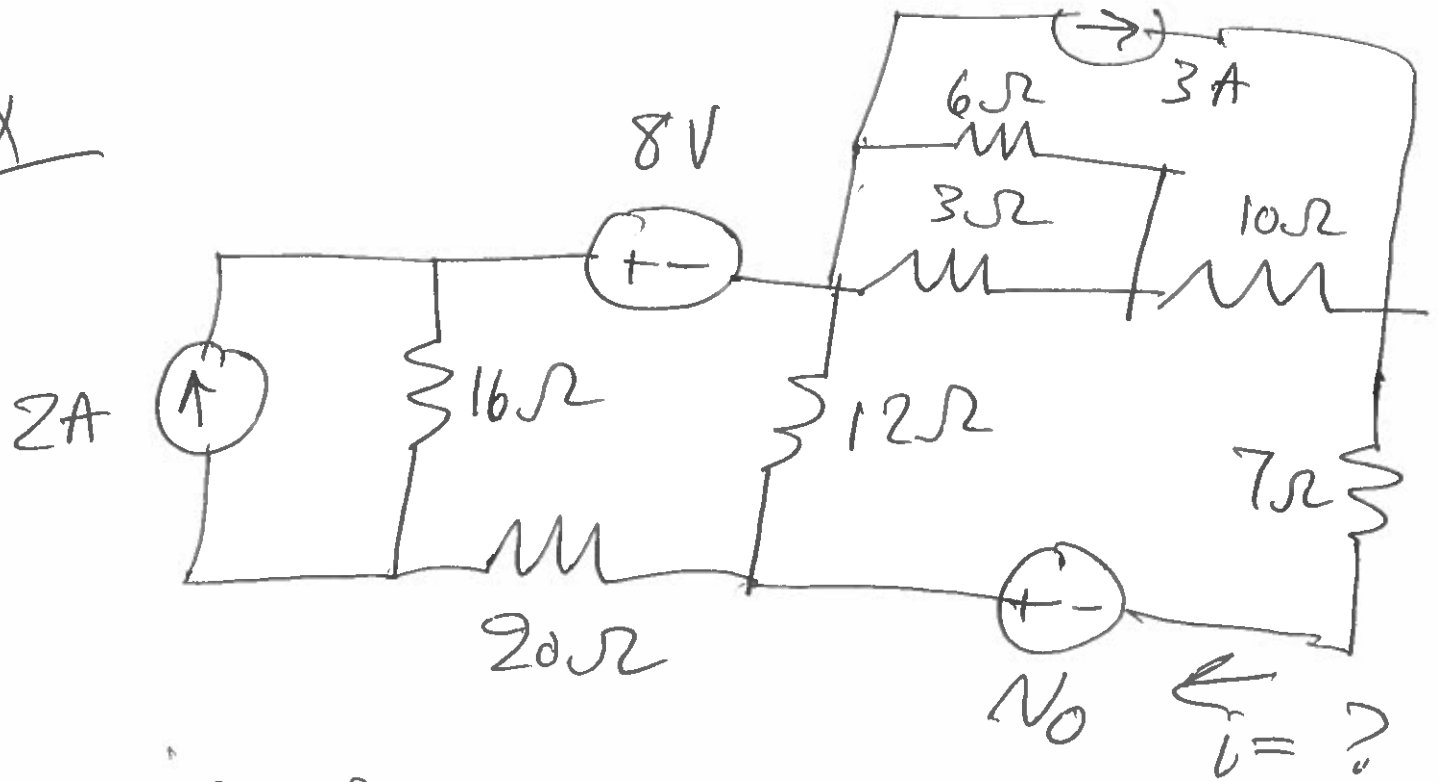




LF  $i = \frac{5}{2} A$   $V_o = ?$

$$\frac{1}{6\Omega} + \frac{1}{3\Omega} = \frac{1+2}{6\Omega} = \frac{3}{6\Omega} = \frac{1}{2\Omega} \Rightarrow 2\Omega$$

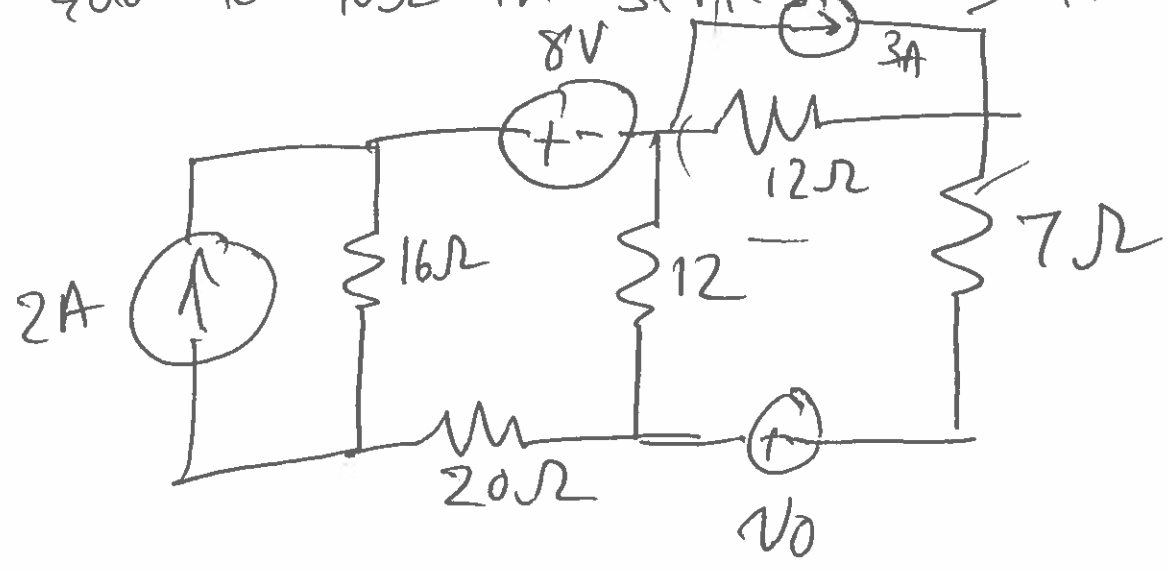add to 10Ω in series  $\Rightarrow 12\Omega$




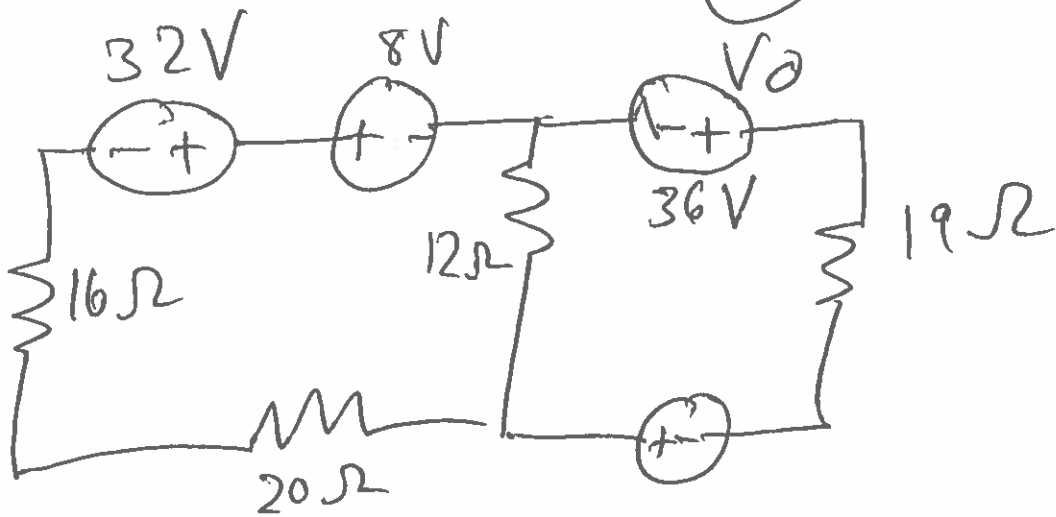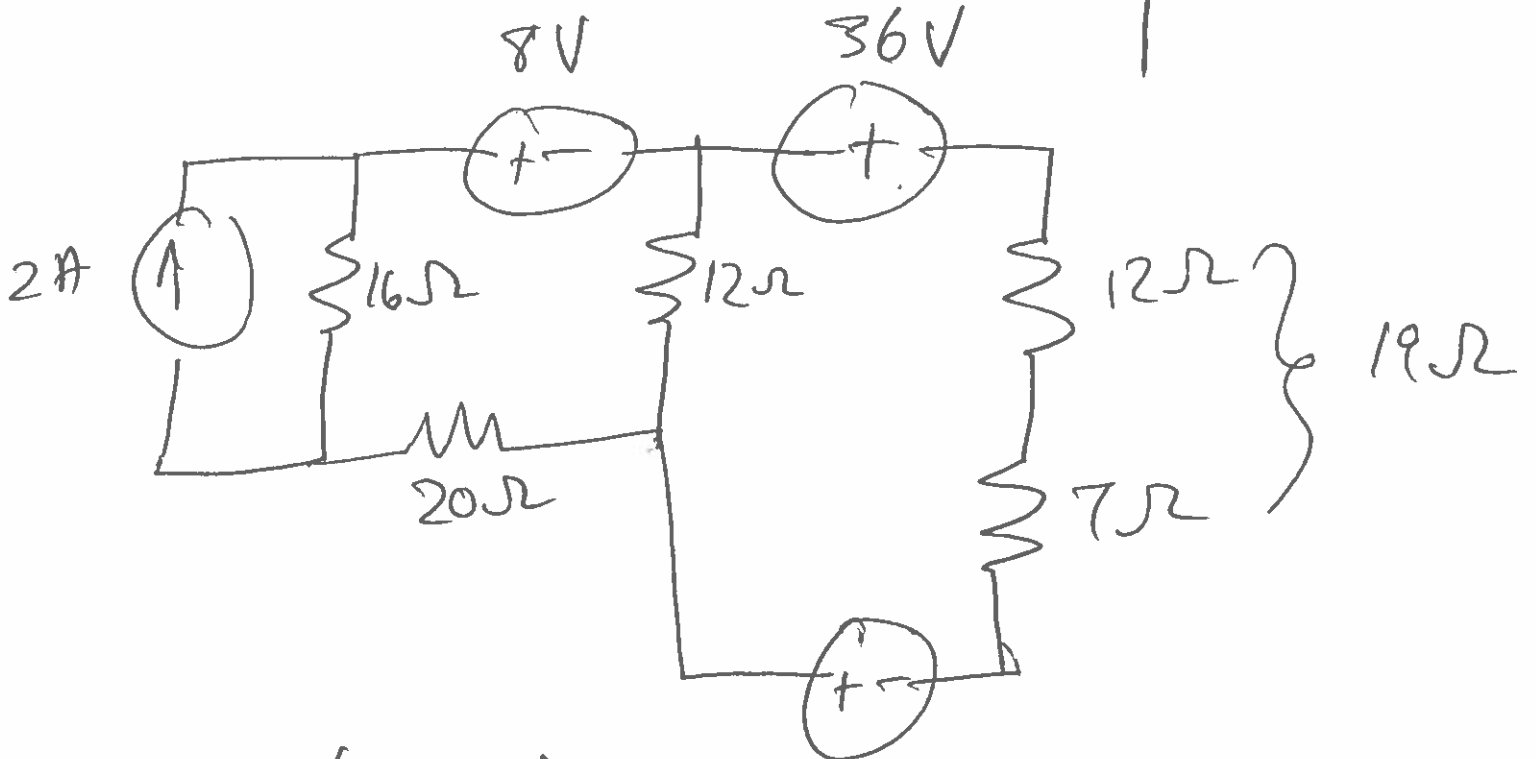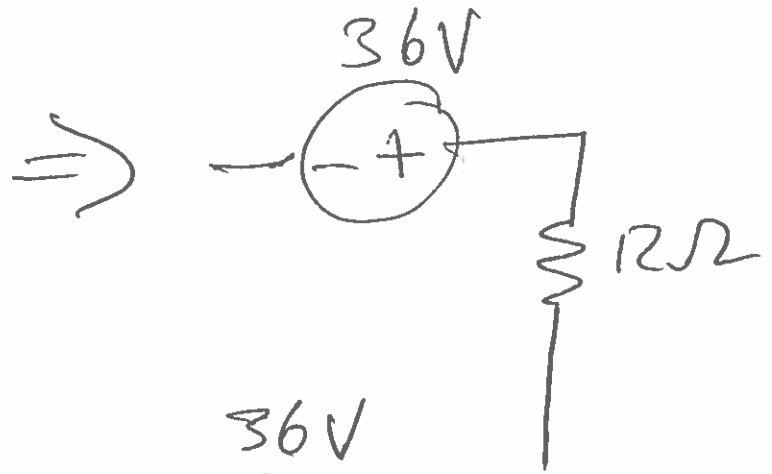


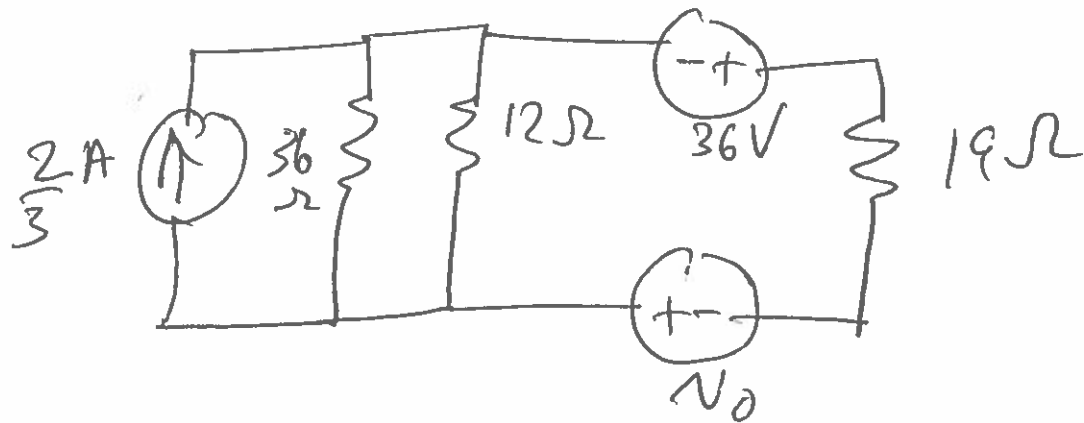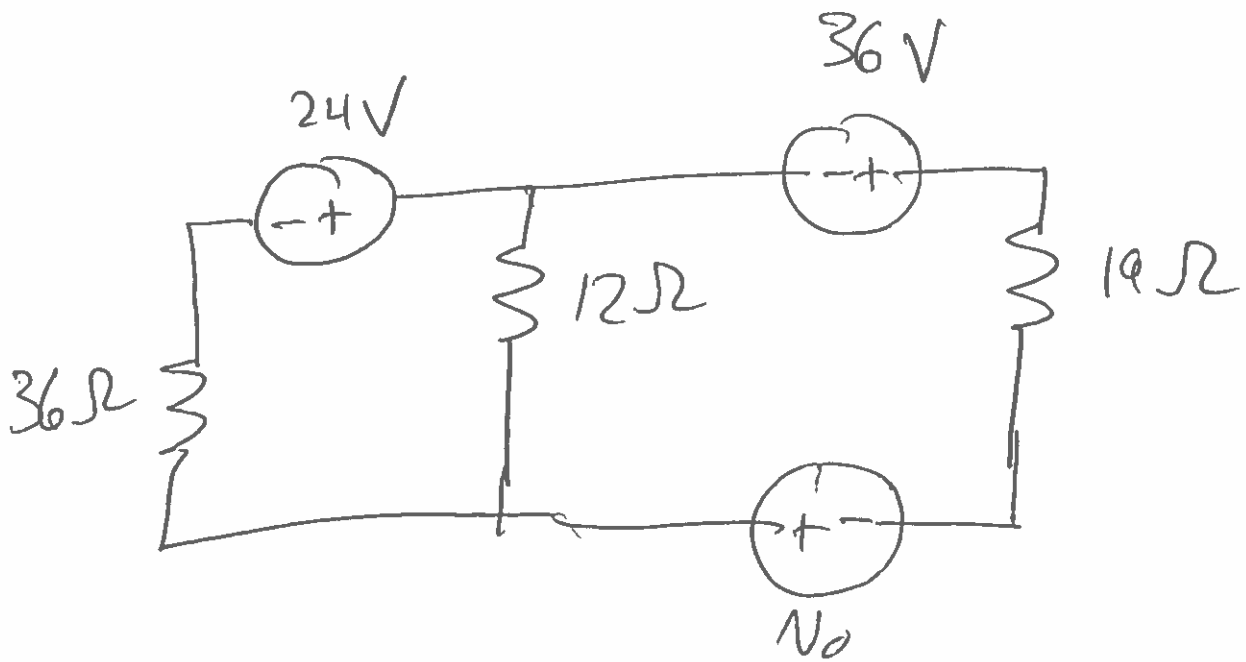

$$\frac{1}{36\Omega} + \frac{1}{12\Omega} = \frac{1+3}{36\Omega} = \frac{4}{36\Omega} = \frac{1}{9\Omega}$$

$$R \Rightarrow 9\Omega$$

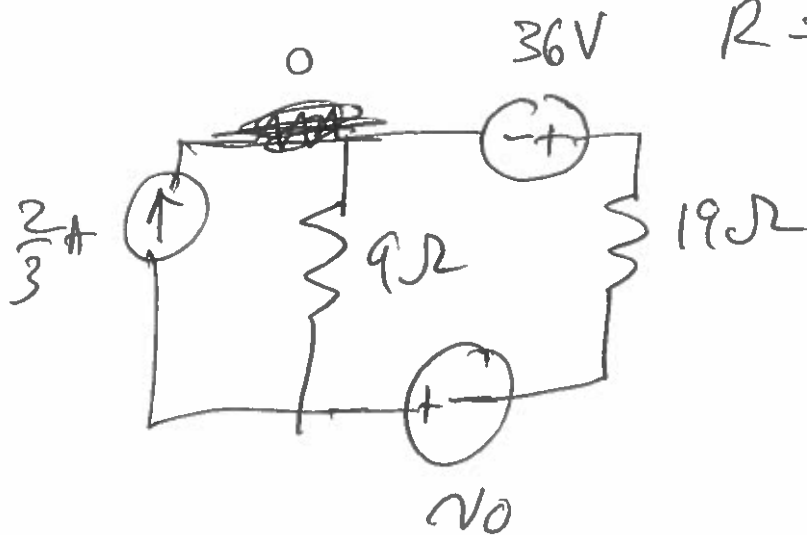

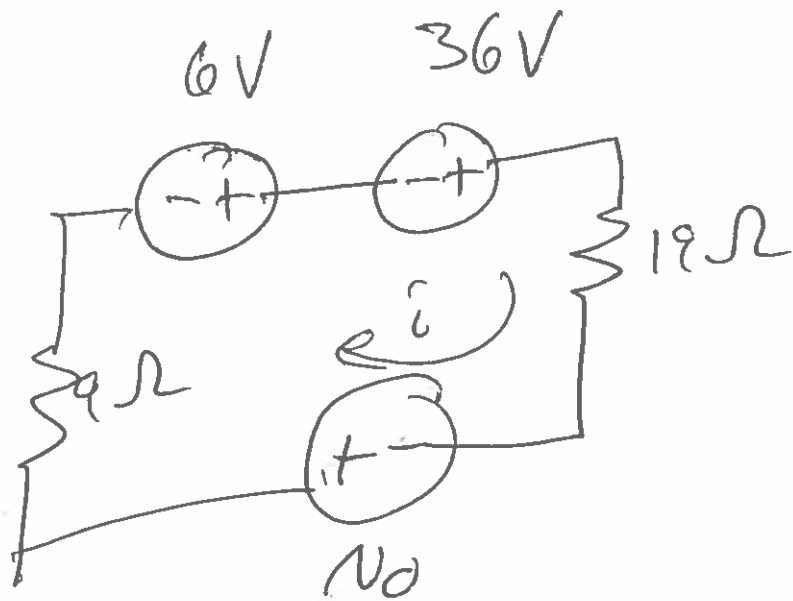


$$i = \frac{V_o + 42V}{28\Omega} = \frac{5}{2} A$$




$$V_o = -42V + 28\Omega \left(\frac{5}{2} A\right)$$

$$V_o = 70V - 42V = \boxed{+28V}$$

ex

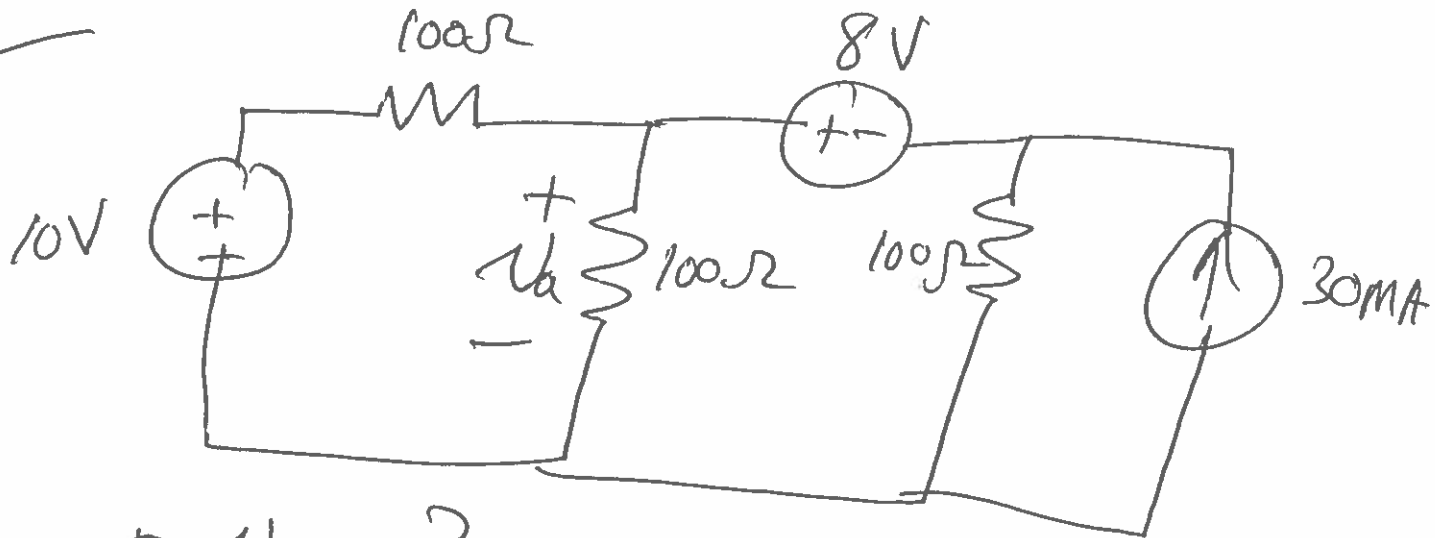

$U_a = ?$

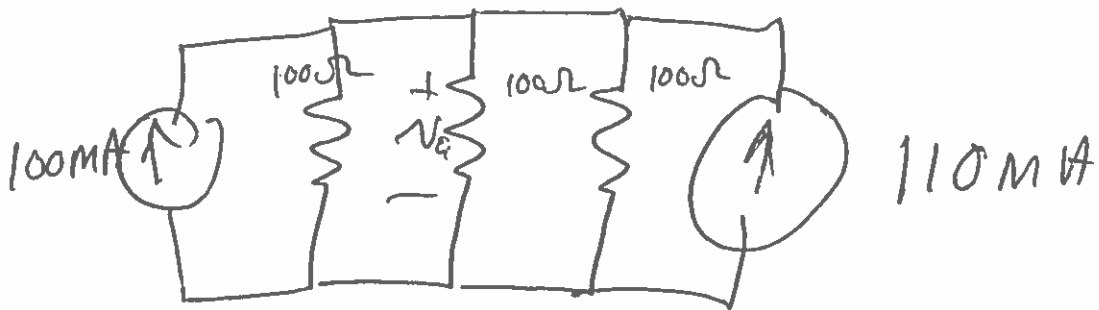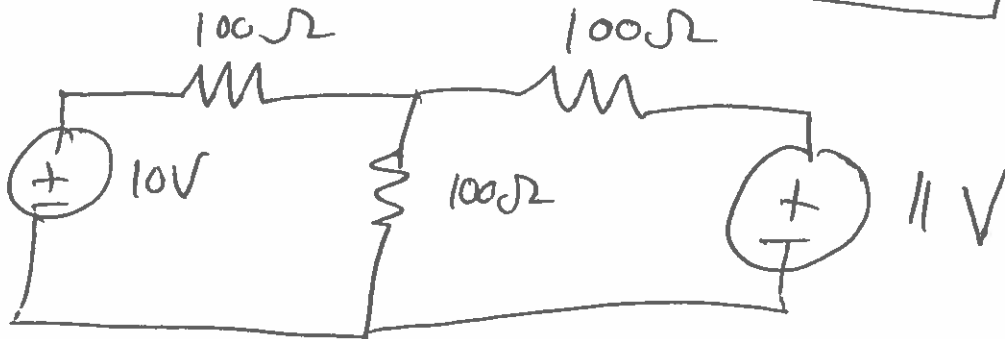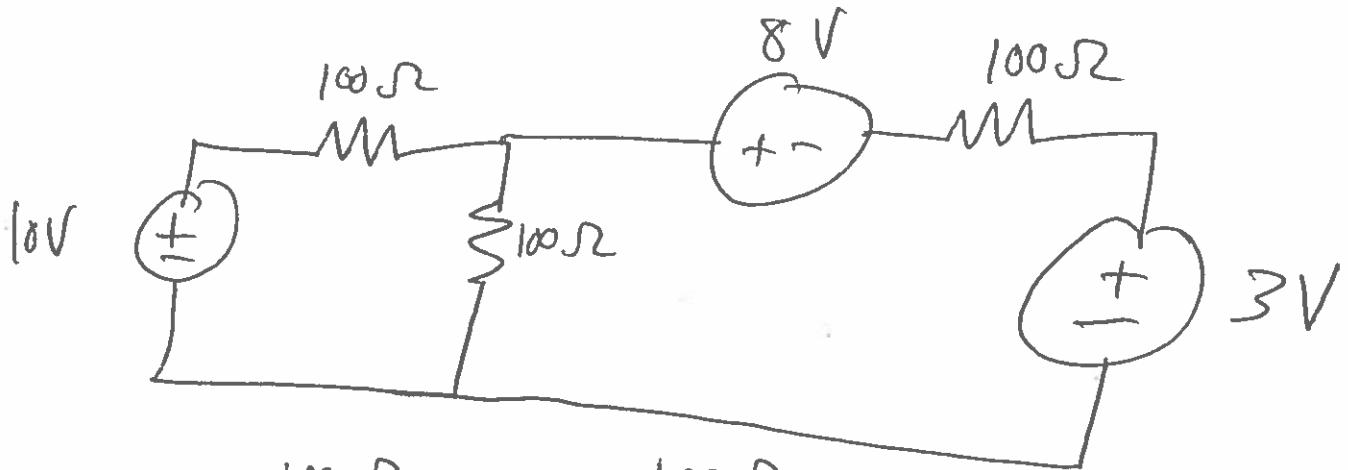



$$i_{100\Omega} = \frac{1}{3}(210 \text{ mA}) = 70 \text{ mA}$$

$$U_q = (70 \text{ mA})(100 \Omega) = 7 \text{ V}$$