

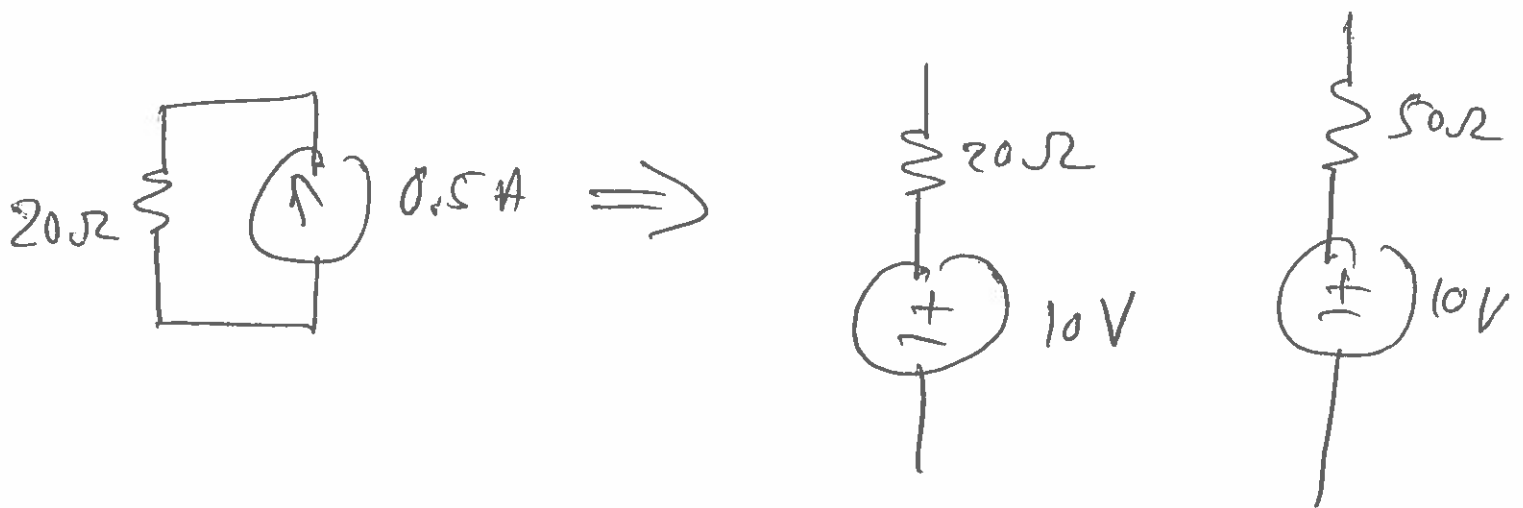



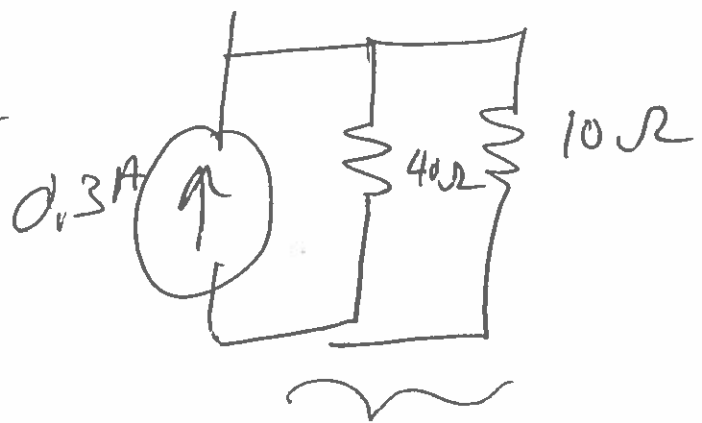
What is power supplied by 3 Power sources



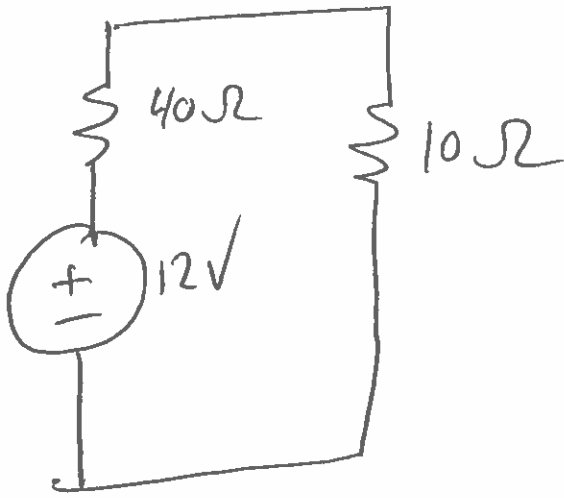

$$\frac{1}{40\Omega} + \frac{1}{10\Omega} = \frac{1+4}{40\Omega}$$

$$\Rightarrow 8\Omega$$

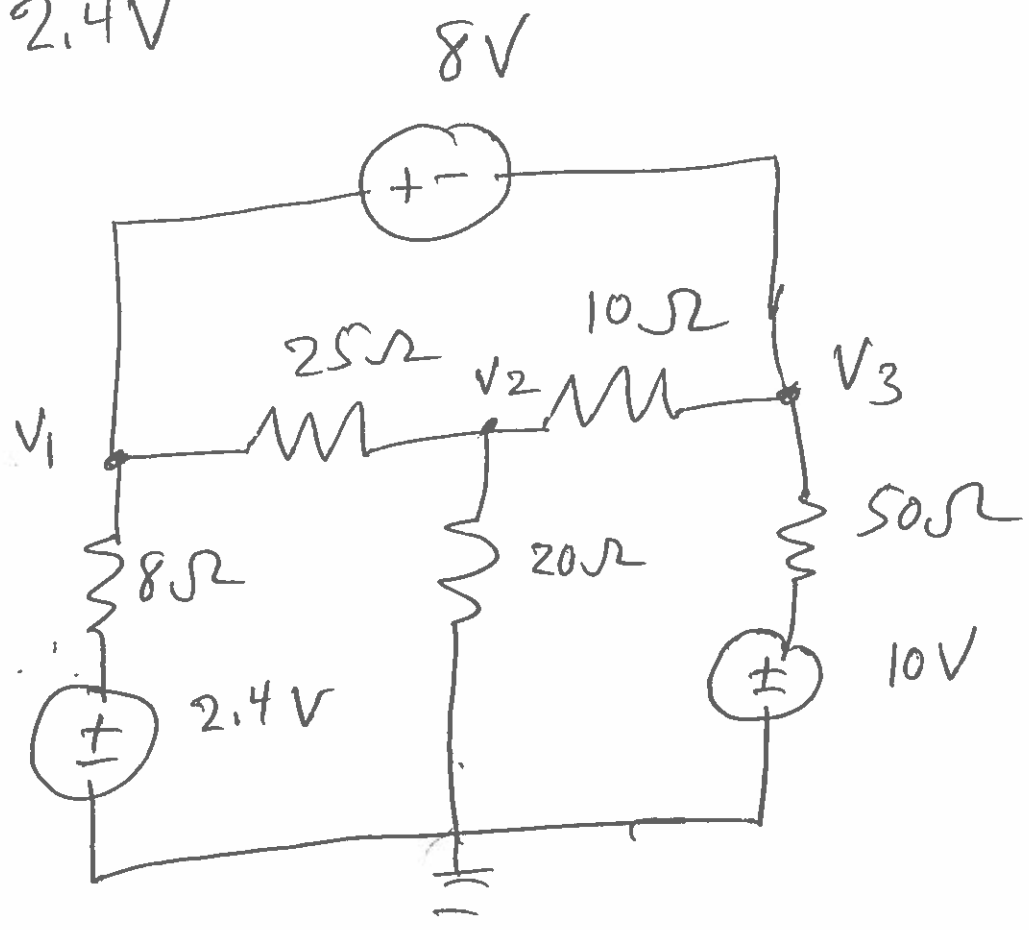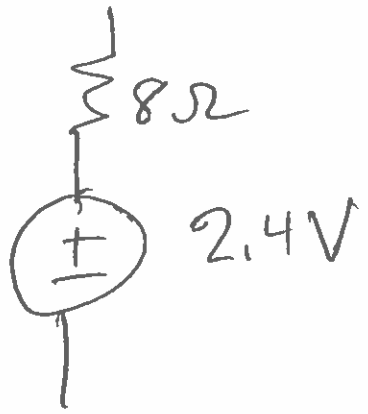

Node analysis

Super node

$$V_1 = V_3 + 8V$$

$$0 = V_1 \left(\frac{1}{8V} + \frac{1}{25\Omega} \right) + V_3 \left(\frac{1}{10\Omega} + \frac{1}{5\Omega} \right)$$

$$- V_2 \left(\frac{1}{25\Omega} + \frac{1}{10\Omega} \right) - \frac{2.4V}{8\Omega} - \frac{10V}{5\Omega}$$

V_2 node

$$0 = V_2 \left(\frac{1}{25\Omega} + \frac{1}{20\Omega} + \frac{1}{10\Omega} \right) - 0.3A - 0$$

$$- V_1 \left(\frac{1}{25\Omega} \right) - V_3 \left(\frac{1}{10\Omega} \right)$$

GOTO MATLAB

$$V_1 = 4.79V$$

$$V_2 = -0.68V$$

$$V_3 = 3.21V$$

```
%Program to solve PH 320 Class Example 2021 02 26 DW  
Donovan
```

```
clear all;
```

```
R = [1 0 -1;  
     (1/8 + 1/25) -(1/25 + 1/10) (1/10 + 1/50);  
     -(1/25) (1/25 + 1/20 + 1/10) -(1/10)];
```

```
ii = [8 0.5 0]';
```

```
V = R\ii;
```

```
V1 = V(1)
```

```
V2 = V(2)
```

```
V3 = V(3)
```

```
%{
```

```
V1 =
```

```
4.7873
```

```
V2 =
```

```
-0.6831
```

```
V3 =
```

```
-3.2127
```


```
%}
```

$$i_{50} = \frac{10V - (-3.21V)}{50\Omega} = +0.264A \uparrow$$

$$i_8 = \frac{4.79V - 2.40V}{8\Omega} = +0.299A \downarrow$$

$$i_{10} = \frac{-0.68V - (-3.21V)}{10\Omega} = +0.253A \rightarrow$$
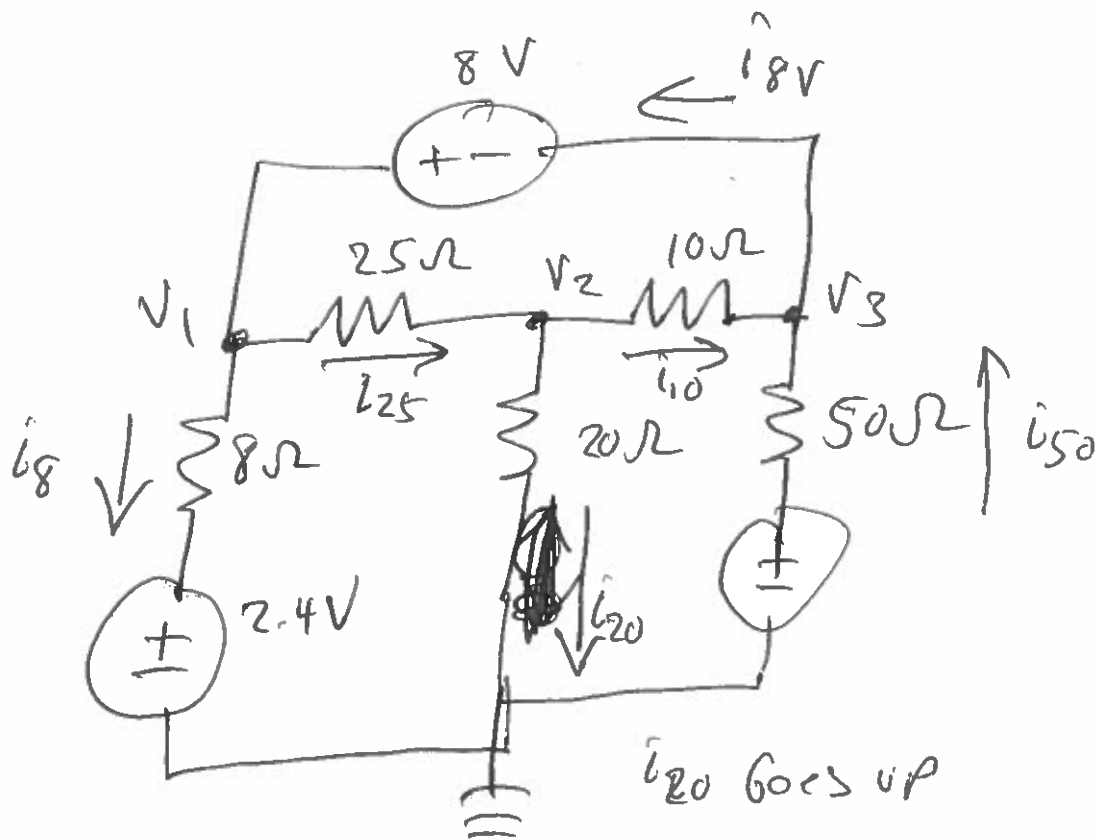
$$i_{25} = \frac{4.79V - (-0.68V)}{25\Omega} = +0.219A \rightarrow$$




$$i_{20} = i_{25} - i_{10} = 0.219A - 0.253A = -0.034A$$

$$\hat{i}_{8V} = \hat{i}_{10} + \hat{i}_{50} = 0.264A + 0.253A \\ = 0.517A$$

$$\text{or } \hat{i}_{8V} = \hat{i}_8 + \hat{i}_{25} = 0.299A + 0.219A \\ = 0.518A \checkmark$$


$$P_{8V} = 8V(0.5175A) = \boxed{4.14W}$$

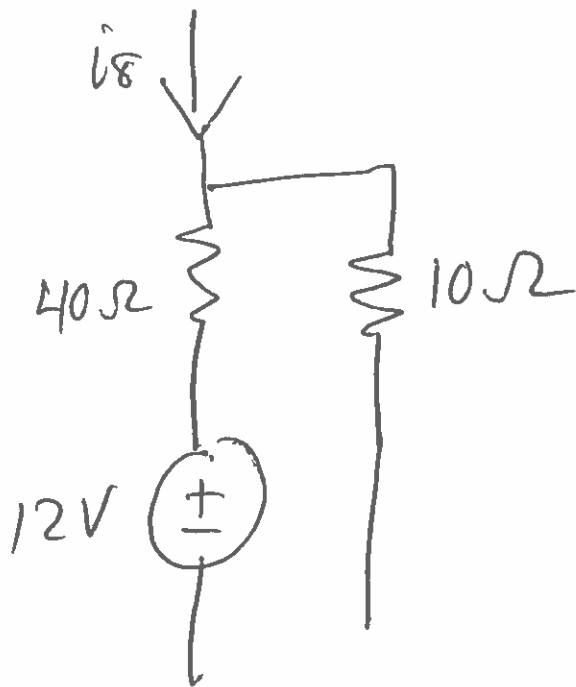

$$\hat{i}_{12V} = \left(\frac{\frac{1}{40}}{\frac{1}{40} + \frac{1}{10}} \right) \hat{i}_8 \\ = \frac{\frac{1}{40}}{\frac{5}{40}} \hat{i}_8 = \frac{1}{5} \hat{i}_8$$

$$\hat{i}_{12} = \frac{1}{5} (0.299A) = 0.0598A$$
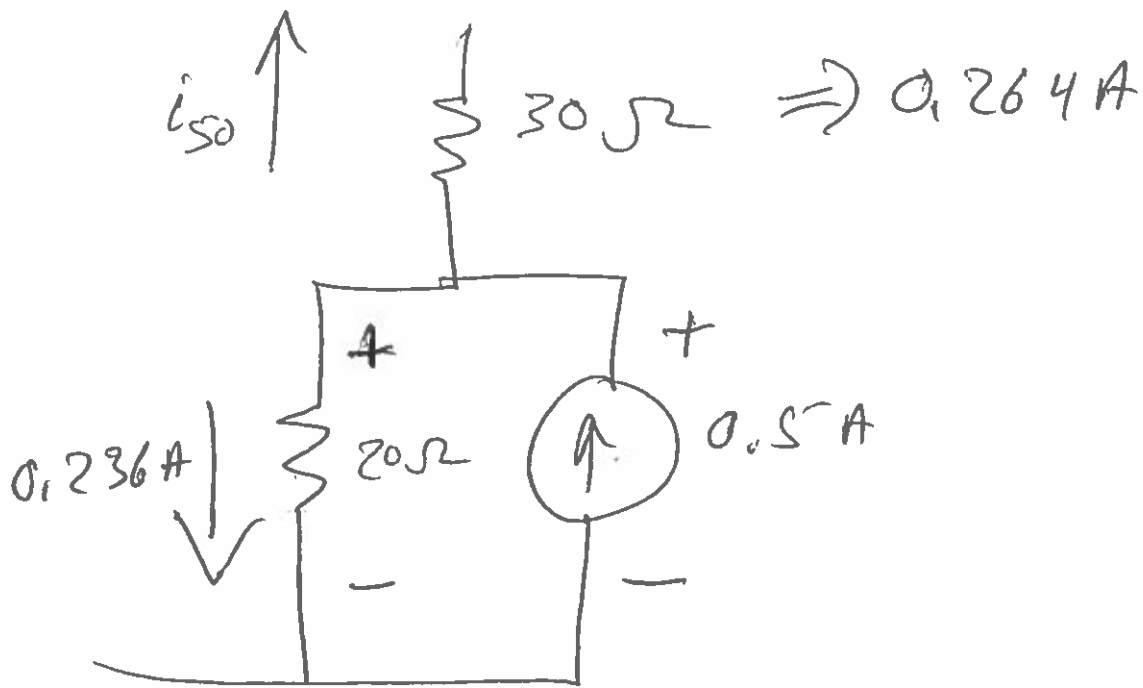
$$P_{12V} = -12V(0.06A) = \boxed{-0.72W}$$



$$i_{30} = 0,299\text{A} \rightarrow$$

$$i_{20} = 0,034\text{A} \uparrow$$

$$i_{\text{other } 20} = 0,236\text{A} \downarrow$$

$$0,299\text{A} - 0,034\text{A}$$

$$+ 0,236\text{A} = 0,501\text{A}$$

$$V = (0,236\text{A})(20\Omega) = 4,72\text{V}$$

$$P_{0,5\text{A}} = (0,5\text{A})(4,72\text{V}) = \boxed{2,36\text{W}}$$