

Super position


Super position is The idea that if you have MULTIPLE SOURCES Then you find is The sum of individual sources.

i_1 is created by V_1

i_2 is created by V_2

$$i_{TOT} = i_1 + i_2 = f(V_1 + V_2)$$

So imagine circuit R_2

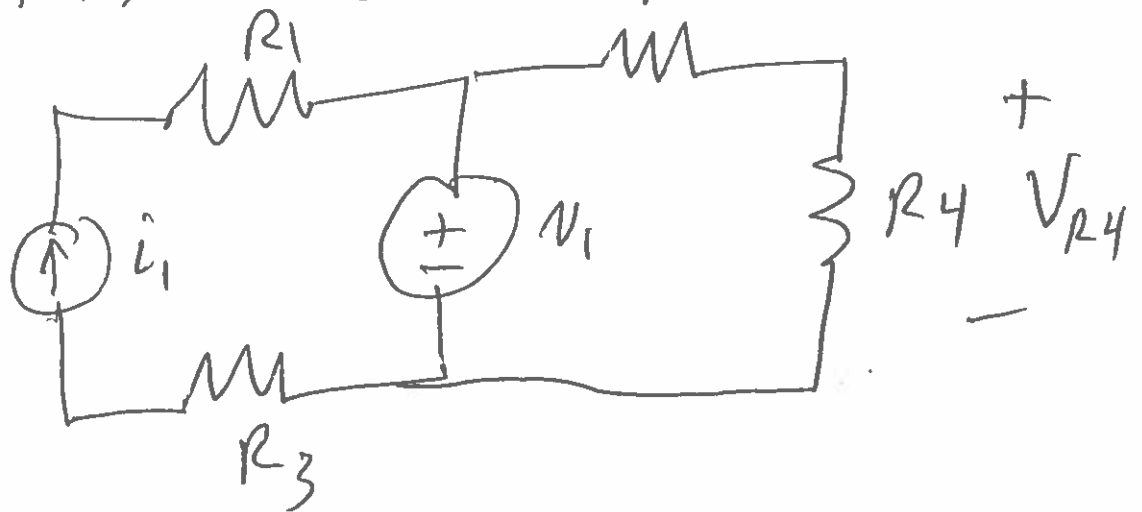

$$V_{R4} = f(i_1, V_1)$$

Find by Deactivating all sources but 1,

$$V_{R4} = f_1(i_1) + f_2(v_1)$$


To Deactivate a CURRENT source

replace current source with ~~short~~ open circuit.

To Deactivate a VOLTAGE source


replace voltage source with ~~open~~ short circuit.

So deactivate V_1

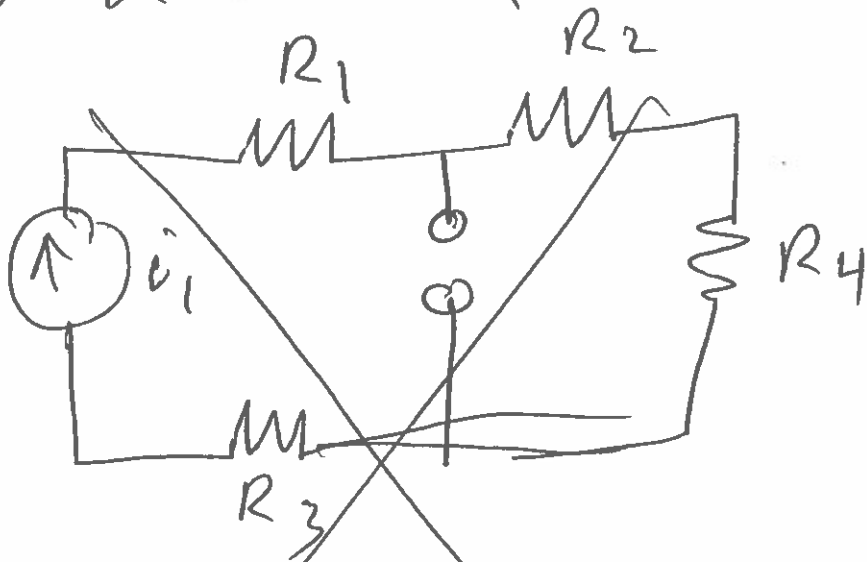


$$V_{R4} = i_1 R_4$$

Defective V_1

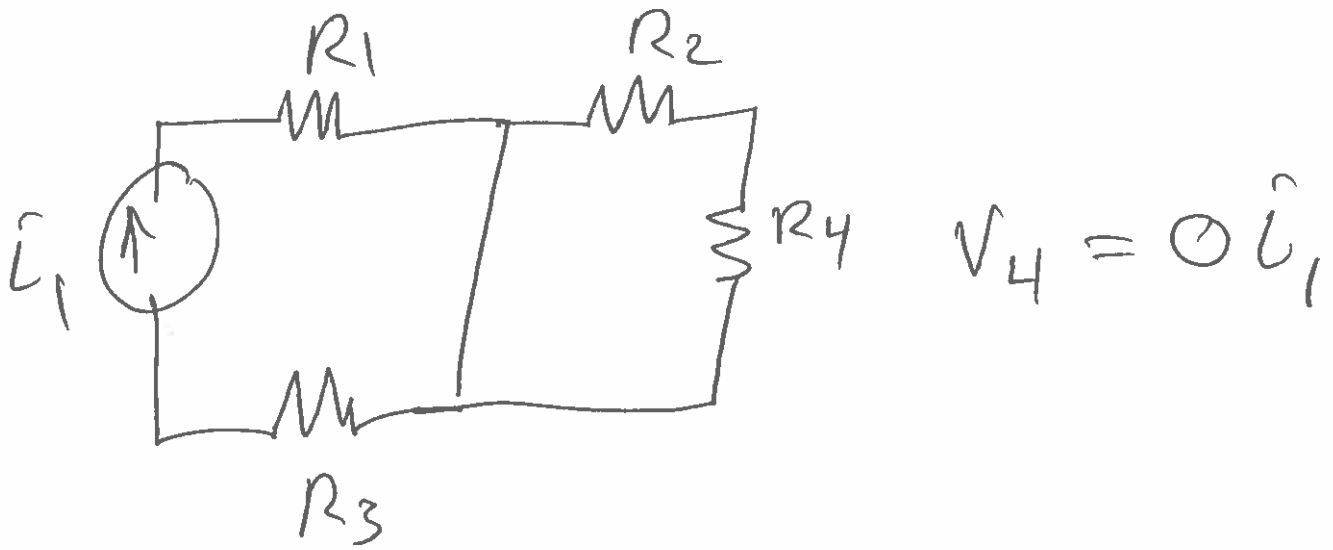


Defective V_1

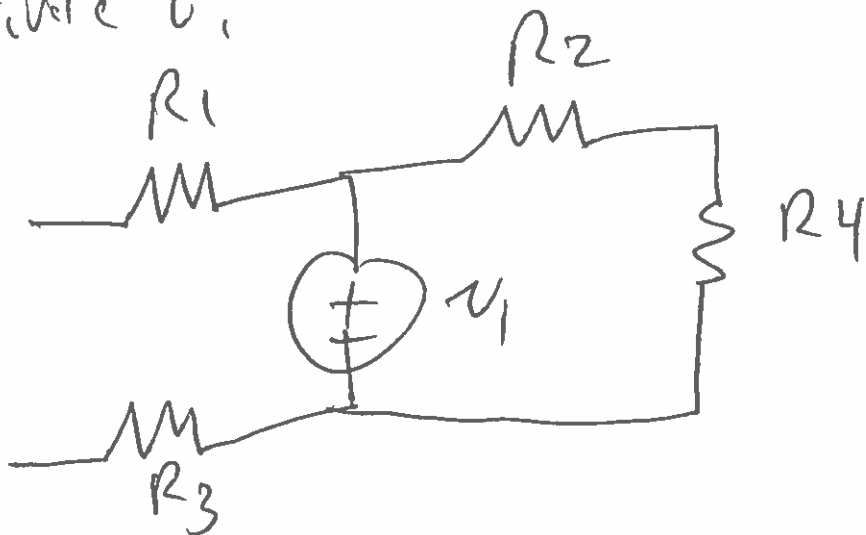

$$V_{R_4} = v_1 \frac{R_4}{R_2 + R_4}$$

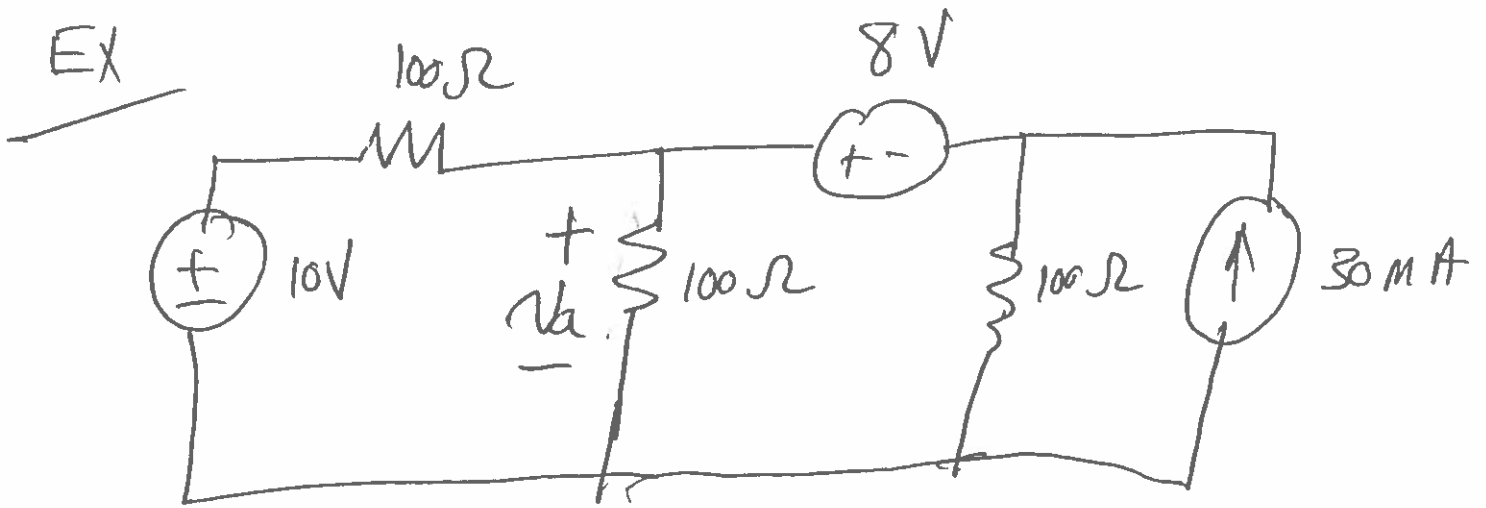
$$V_{\text{Total}} = 0 \hat{i}_1 + \left(\frac{R_4}{R_2 + R_4} \right) v_1$$



$$N_a = ?$$

$$N_a = N_{10V} + N_{8V} + N_{30mA}$$


N_{10V} Deactivate 8V 30mA

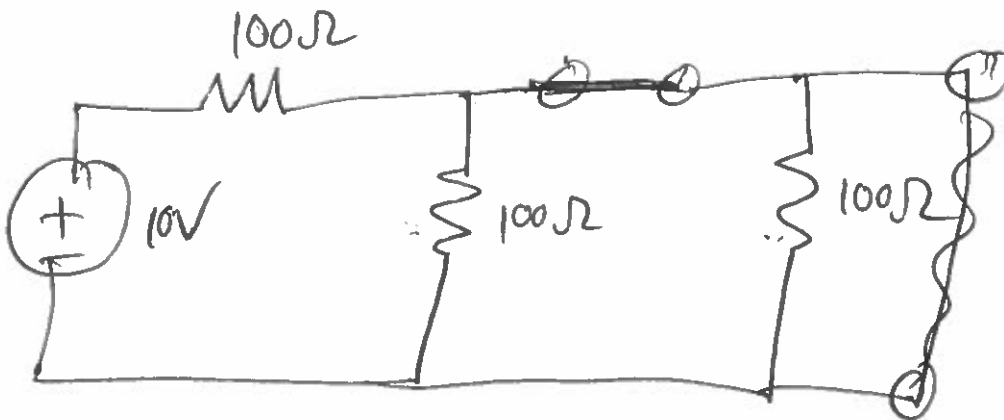

~~$$N_{10V} = \frac{10V}{2} = 5V$$~~




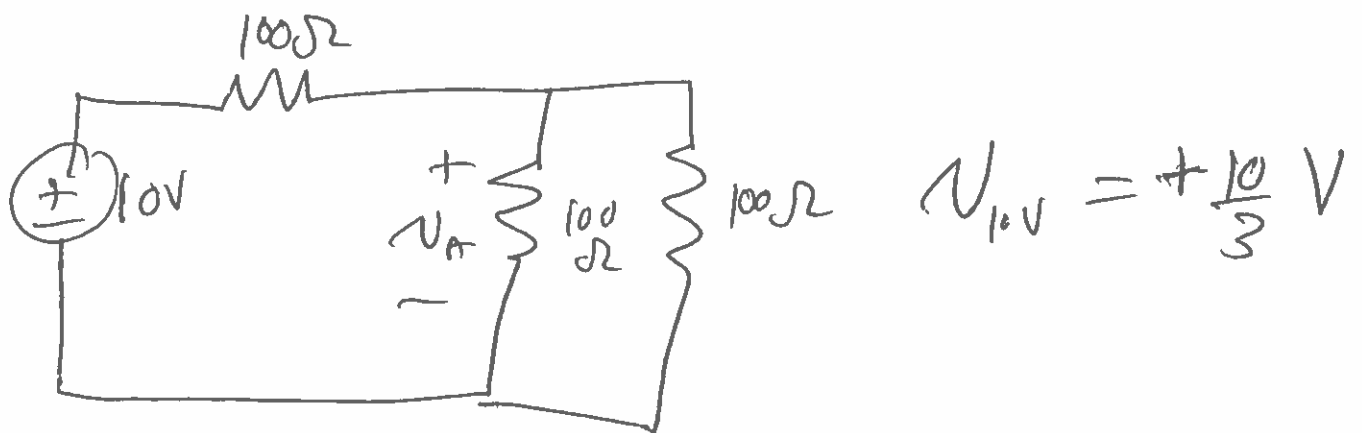
$$V_{50\Omega} = \frac{50\Omega}{150\Omega} (10V) = \frac{10}{3} V$$




$$V_{10V} = +\frac{10}{3} V$$

V_{8V} Deactivate 10V and 30mA

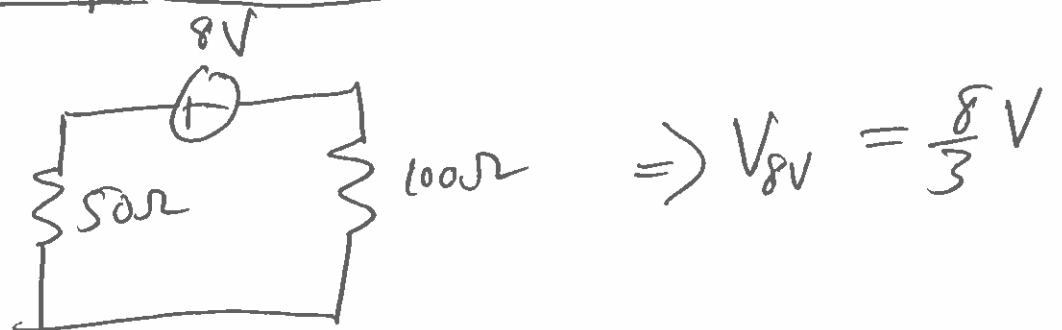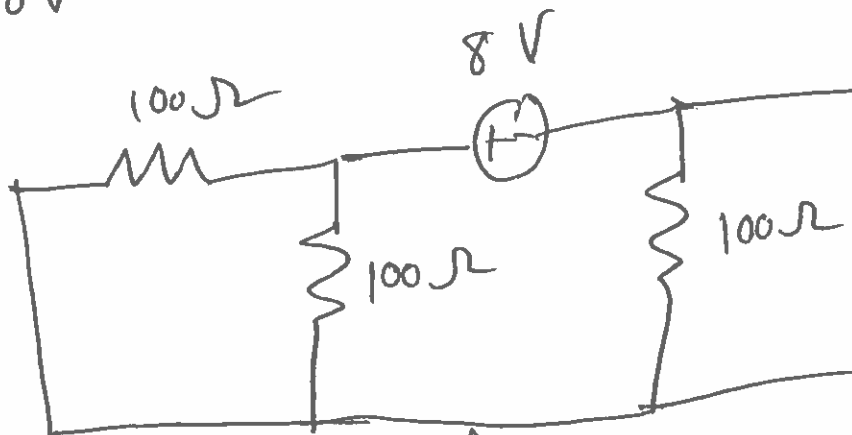

$$\Rightarrow V_{8V} = \frac{8}{3} V$$

30mA Deactivating 10V, 8V

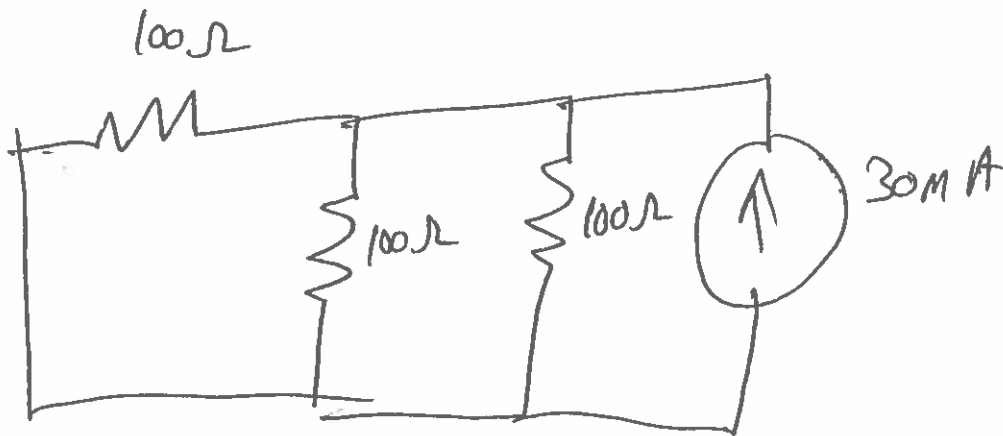


$$V_A = i \cdot 100\Omega = \frac{30\text{mA}}{3} (100\Omega) = 1000\text{mV}$$

$$V_{30\text{mA}} = +1\text{V}$$

$$V_A = +\frac{10}{3}\text{V} + \frac{8}{3}\text{V} + 1\text{V} = \frac{18}{3}\text{V} + 1\text{V}$$

$$V_A = 7\text{V}$$

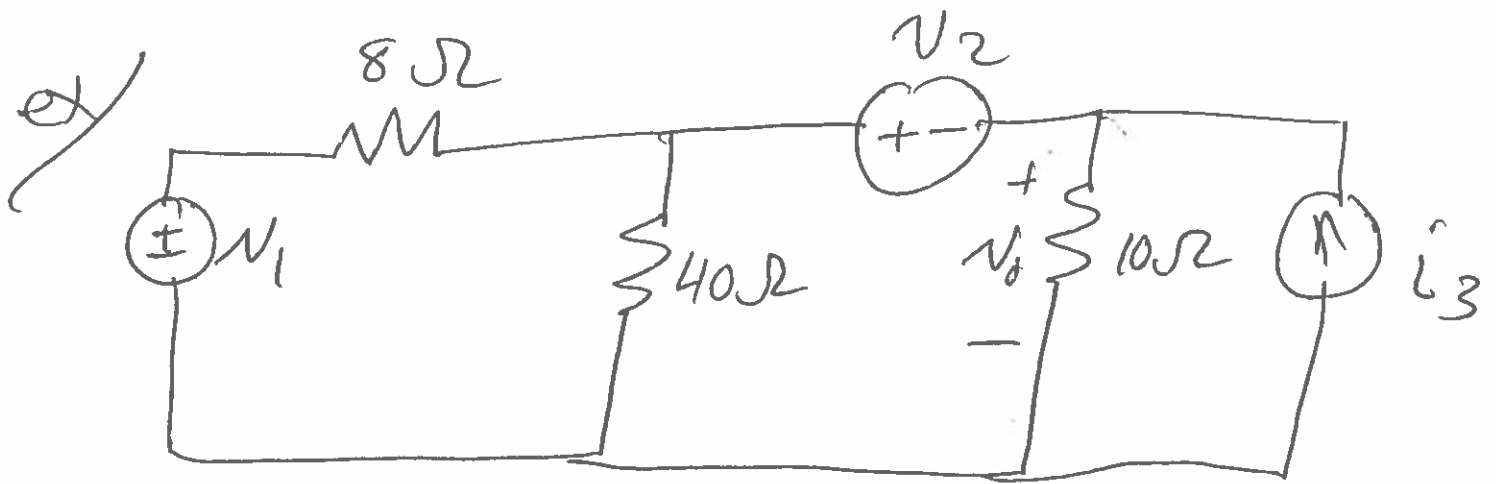
$$\text{or } V_A = +\frac{10}{3} (V_{10\text{V}}) + \frac{8}{3} (V_{8\text{V}}) + 1\text{V} (i_{30\text{mA}} \cdot R_{100})$$



find a, b, c such that

$$v_0 = a v_1 + b v_2 + c i_3$$

find c Deactivate v_1, v_2

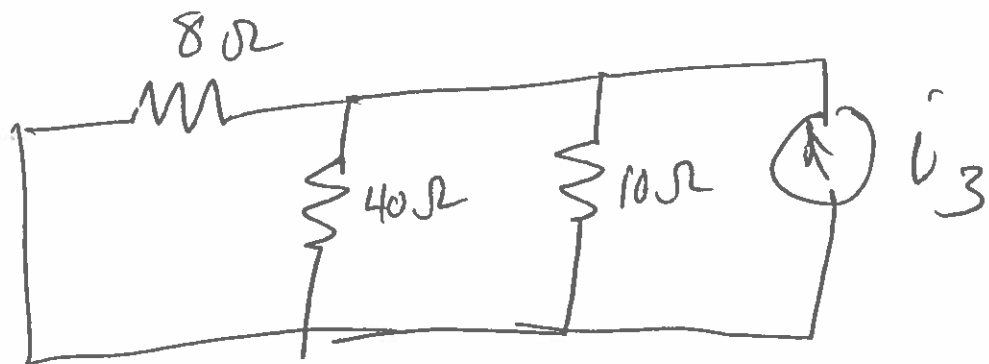

$$v_0 = (10\Omega) i_{10}$$

$$i_{10} = ? \quad i_{10} = \frac{\frac{1}{10\Omega} i_3}{\frac{1}{8\Omega} + \frac{1}{40\Omega} + \frac{1}{10\Omega}}$$

$$i_{10} = \frac{\frac{1}{10\Omega}}{\frac{5+1+4}{40\Omega}} \quad i_3 = \frac{40\Omega}{10\Omega} i_{10} = 0.4 i_3$$

$$N_0 = (10\Omega) i_{10} = 10\Omega (0.4 i_3) = \underline{(4\Omega) i_3}$$


$$C = 4\Omega$$

find θ Decentivere V_2, i_3



$$\frac{1}{40\Omega} + \frac{1}{10\Omega} = \frac{1+4}{40\Omega}$$
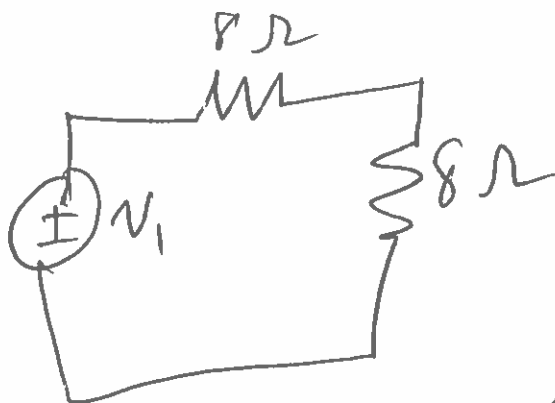
$$\frac{5}{40\Omega} \Rightarrow \frac{1}{8\Omega}$$




$$N_{10\Omega} = \frac{1}{2} V_1$$

$$N_0 = \frac{1}{2} V_1 \Rightarrow \boxed{a = \frac{1}{2}}$$

Find b

Resistors v_1, i_3

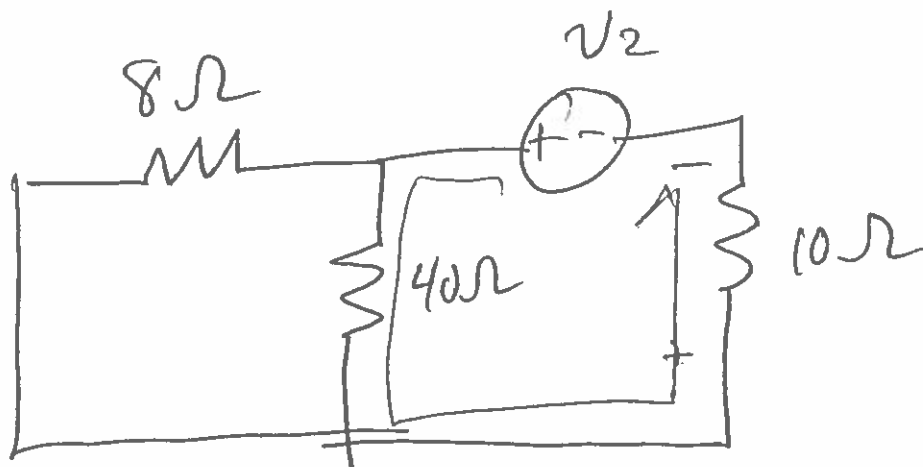

$$\frac{1}{8\Omega} + \frac{1}{40\Omega} = \frac{5+1}{40\Omega} = \frac{6}{40\Omega} = \frac{3}{20\Omega}$$

$$\frac{20}{3}\Omega \Rightarrow v_0 = \frac{10\Omega}{\frac{20}{3}\Omega + 10\Omega} v_2$$

$$\frac{10}{\frac{50}{3}} = \frac{30}{50} = \frac{3}{5}$$

$$v_0 = -\frac{3}{5} v_2$$

$$b = -\frac{3}{5}$$

$$v_0 = \frac{1}{2} v_1 - \frac{3}{5} v_2 + 4\Omega i_3$$