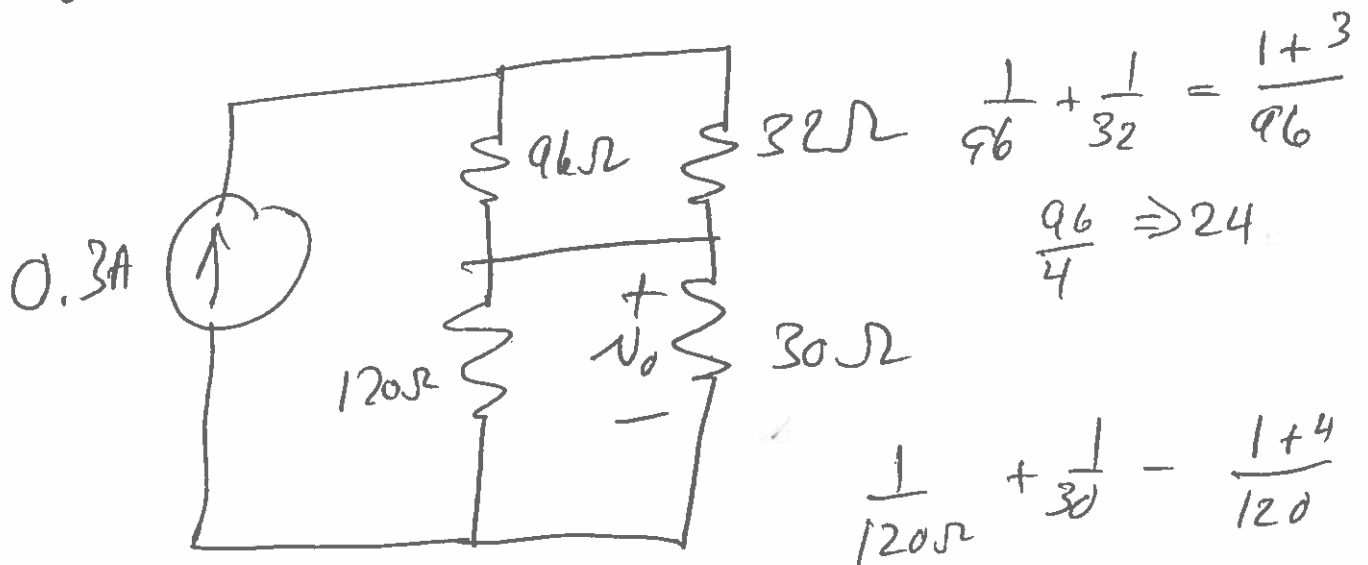


$$V_o = ?$$

N_{oi} Deactive the 20V




$$i_{30\Omega} = \frac{(0.3A) \frac{1}{30}}{\frac{120}{5} = 24} = \frac{24}{30} (0.3A)$$

$$V_{oi} = \frac{1}{24} \cdot \frac{24}{30} (0.3A) (30\Omega) = 24(0.3)V = 7.2V$$

$+7.2V$

Defective current supply

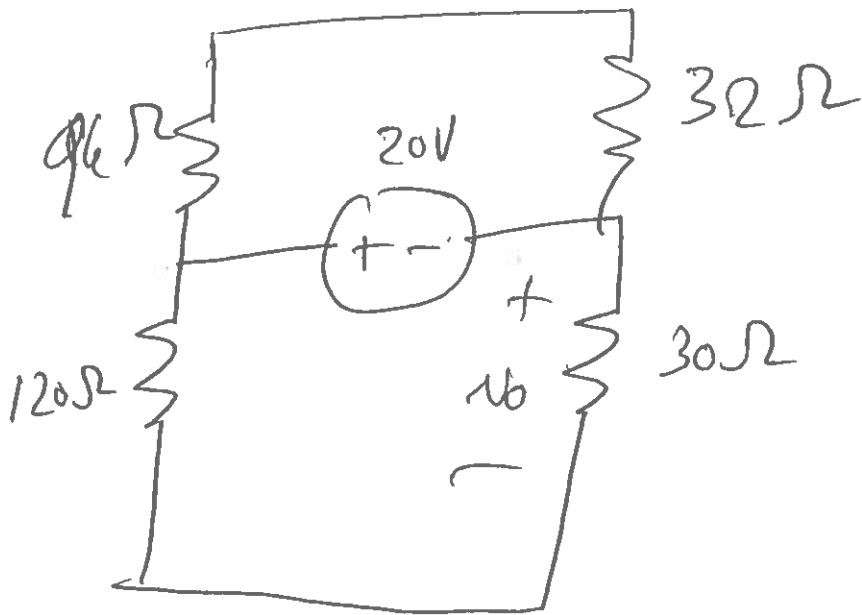


$$V_{30} = \frac{30\Omega}{150\Omega} (20V) = 4V$$

$$V_{30} = -4V$$

$$V_o = V_{30i} + V_{30V} = +7.2V + (-4V)$$

$$V_o = +3.2V$$

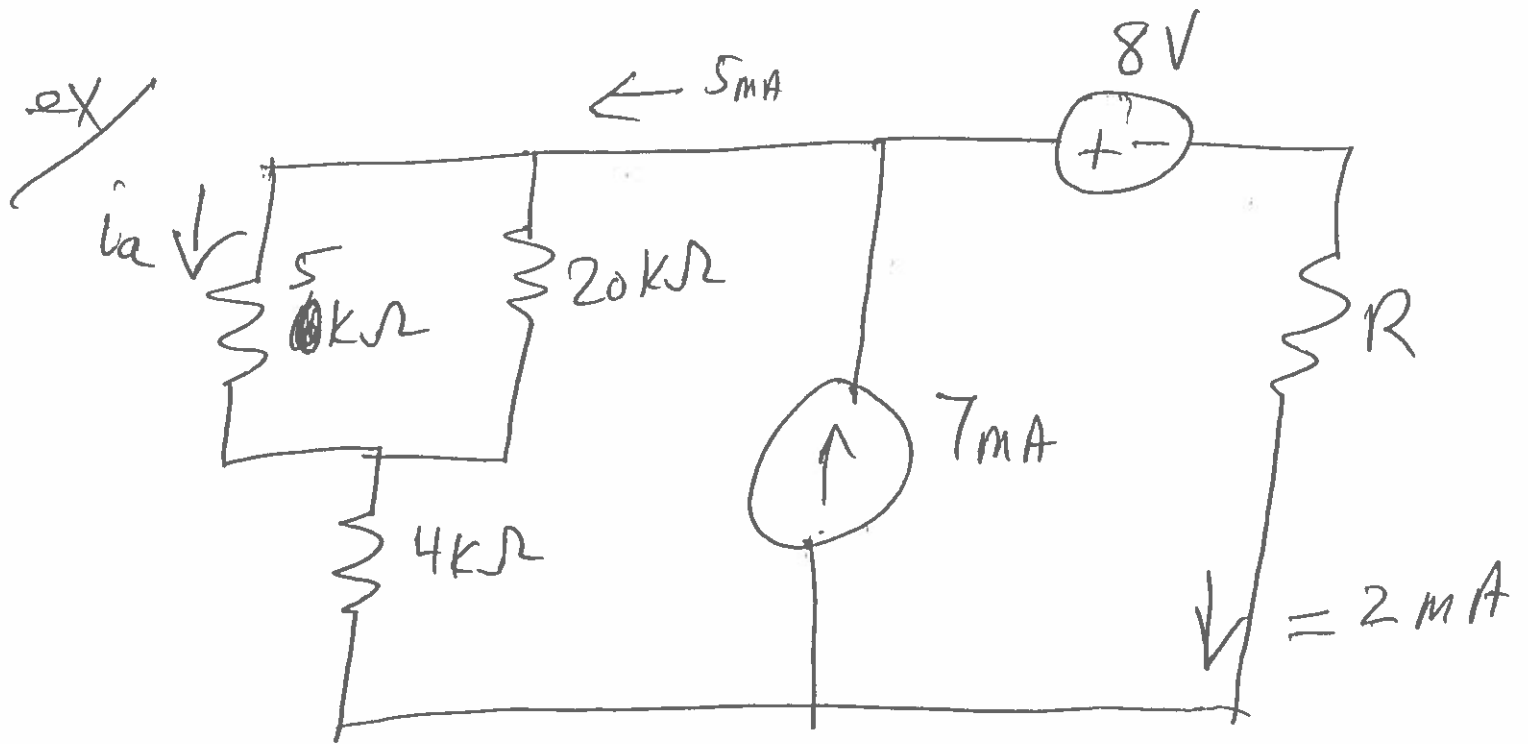


$$i_a = ? \quad R = ?$$

$$i_a = \frac{5\text{mA} \left(\frac{1}{5\text{k}\Omega}\right)}{\frac{1}{5\text{k}\Omega} + \frac{1}{20\text{k}\Omega}} = \frac{5\text{mA} \left(\frac{1}{5\text{k}\Omega}\right)}{\frac{4+1}{20\text{k}\Omega}}$$

$$i_a = 1\text{mA} \left(\frac{1}{1\text{k}\Omega}\right) \frac{20\text{k}\Omega}{5} = 4\text{mA} = i_a$$

$$5\text{k}\Omega \parallel 20\text{k}\Omega \Rightarrow 4\text{k}\Omega$$
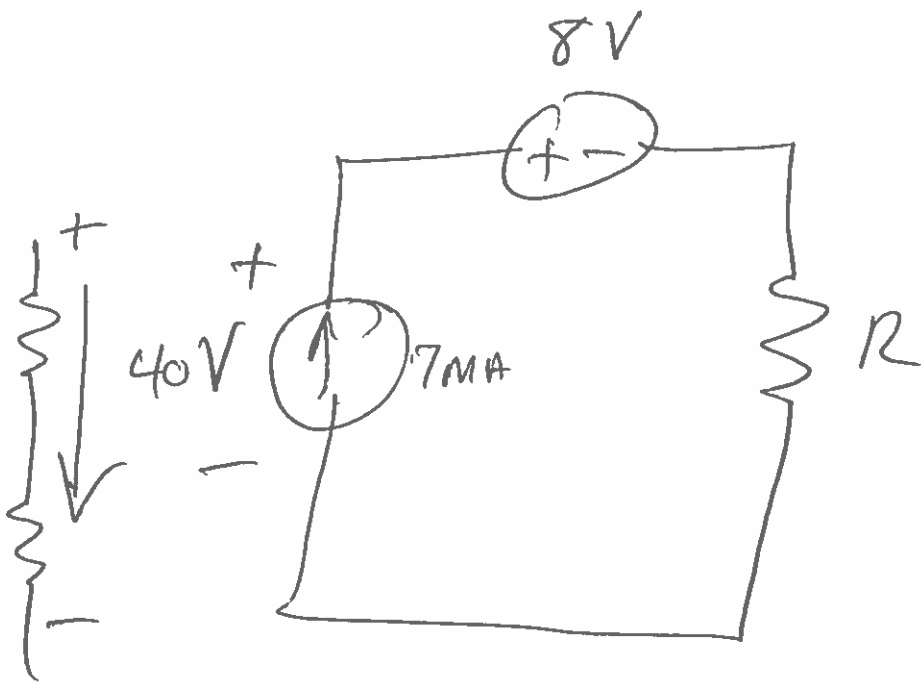
$$V_{7\text{mA}} = 5\text{mA} (8\text{k}\Omega) = 40\text{V}$$




$$40V - 8V = V_R = 32V$$

$$R = \frac{V_R}{I_R} = \frac{32V}{2mA} = 16k\Omega$$


$$R = 16k\Omega$$

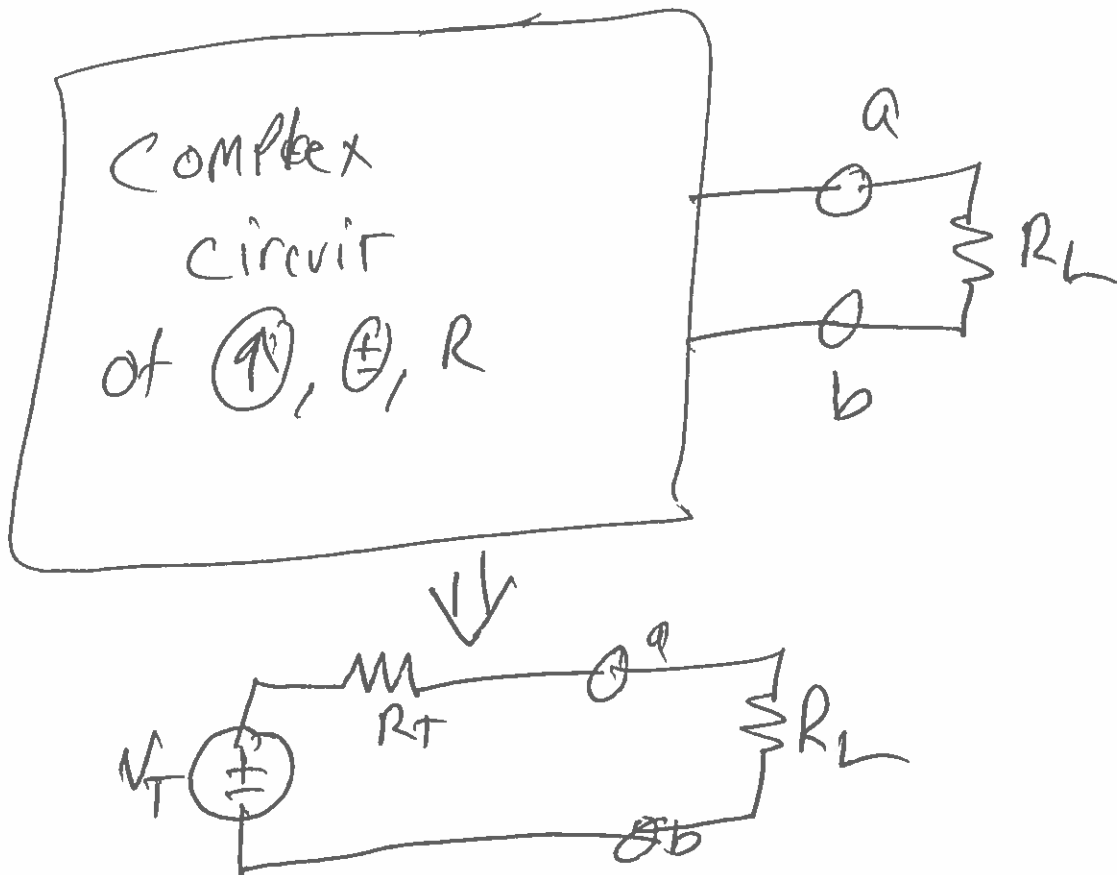Thevenin's Theorem requires for any circuit of resistive elements and energy sources with an identified terminal pair, the circuit can be replaced by a series combination of a voltage source, V_T , and a resistance R_T where V_T is the open circuit voltage V_{OC} the terminals and R_T is the ratio of the open circuit voltage to the short circuit current I_{SC} the terminals.




How To Find Thevenin equivalent

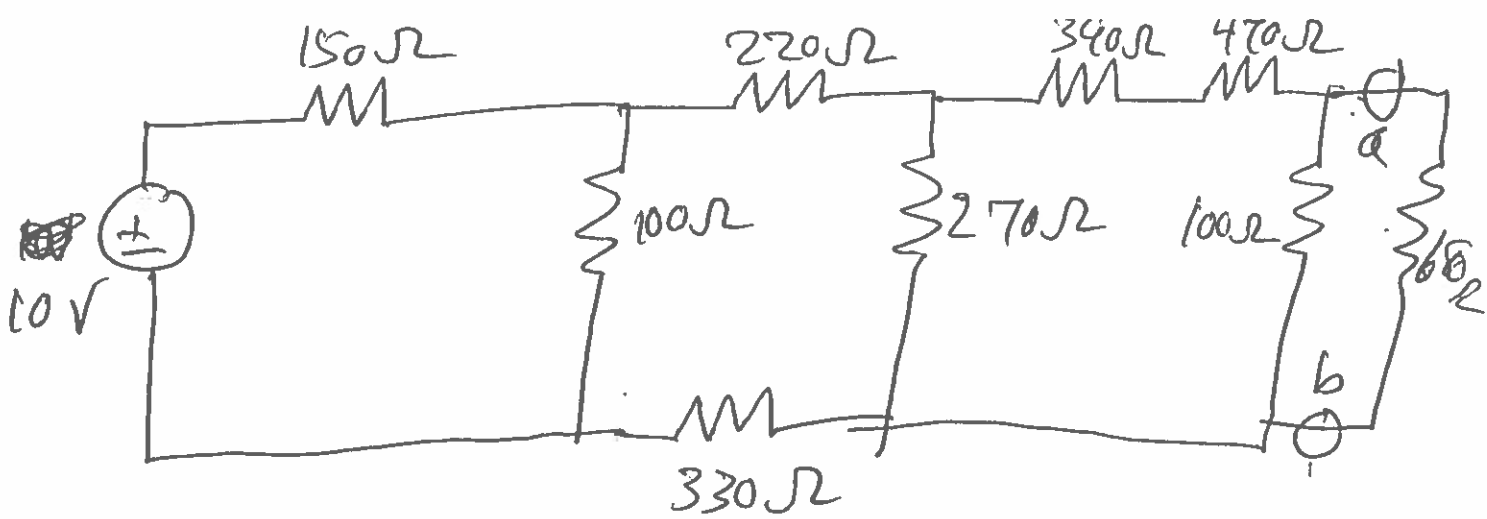
- 1) Deactivate power sources find R_T by circuit reduction
- 2) Deactivate voltage sources by replacing with short-circuits
- 3) Deactivate current sources by replacing with open-circuits
- 4) Find V_{OC} with sources active.




Find R_T

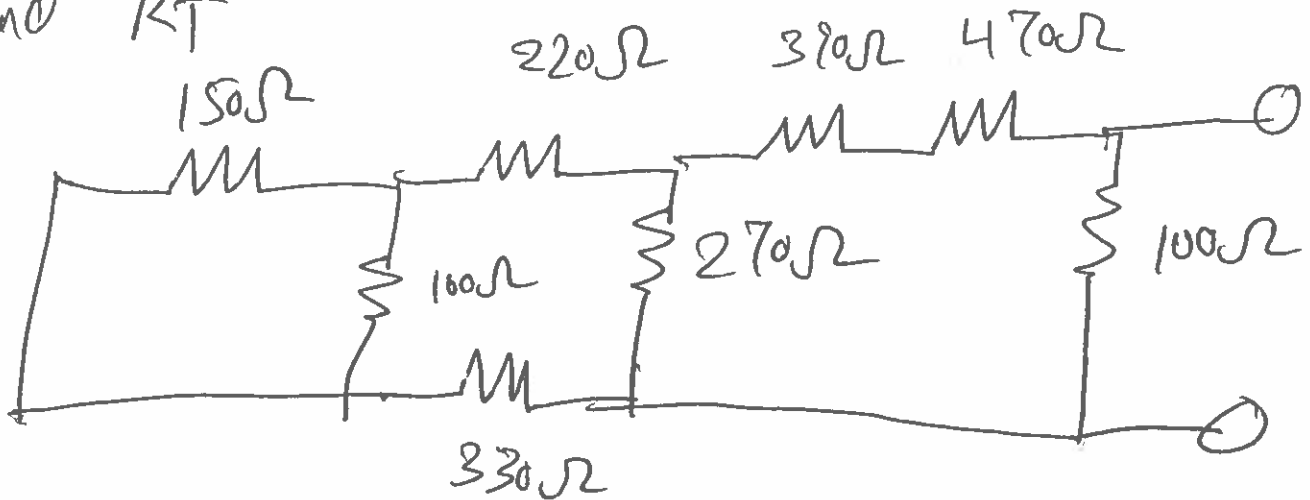
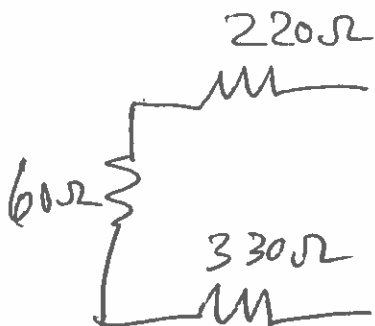
$$\frac{1}{150} + \frac{1}{100} = \frac{2+3}{300\Omega} = \frac{1}{60\Omega}$$




$$\Rightarrow 610\Omega$$

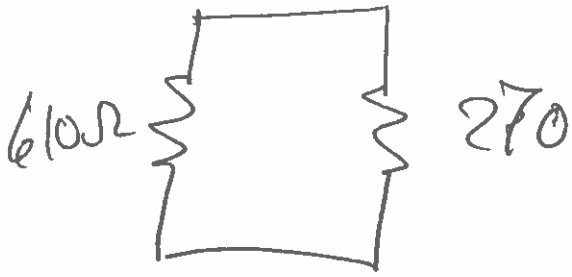


$$\frac{1}{610\Omega} + \frac{1}{270\Omega} \Rightarrow 187\Omega$$

$$0,0016 + 0,0037 = 0,0053$$

$$\frac{1}{0,0053} = 187,16\Omega$$

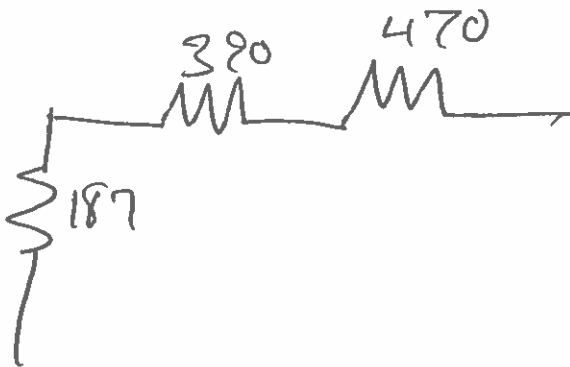


$$\Rightarrow 1047\Omega$$

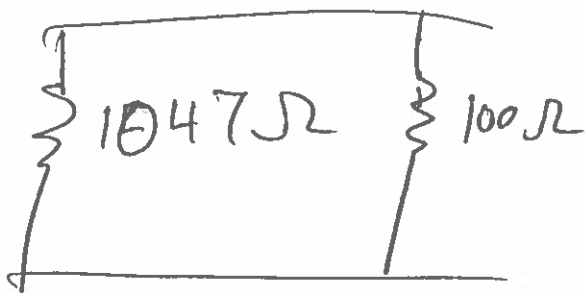

$$\frac{1}{1047\Omega} + \frac{1}{100\Omega}$$

$$\Rightarrow 91,3\Omega \quad R_T$$

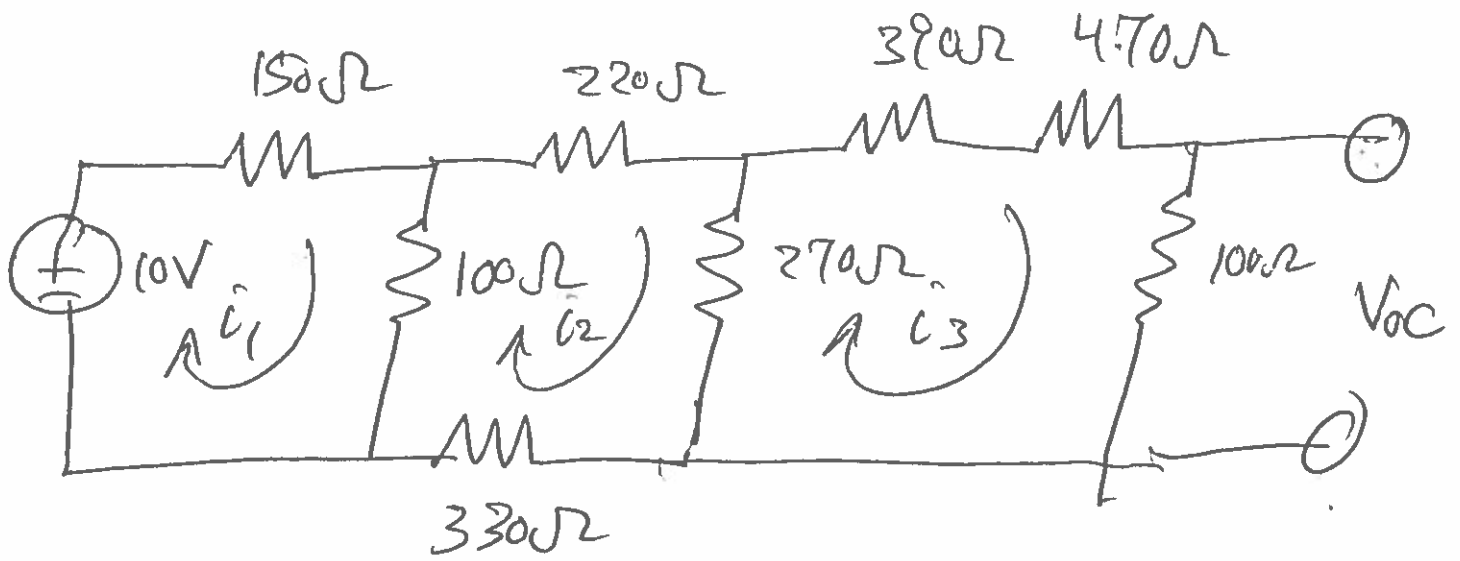

$$V_{OC} = 100\Omega \hat{i}_3$$

$$10V = \hat{i}_1 (150\Omega + 100\Omega) - \hat{i}_2 (100\Omega)$$

$$0 = -\hat{i}_1 (100\Omega) + \hat{i}_2 (100\Omega + 220\Omega + 270\Omega + 330\Omega) - \hat{i}_3 (270\Omega)$$

$$0 = -\hat{i}_2 (270\Omega) + \hat{i}_3 (270\Omega + 390\Omega + 470\Omega + 100\Omega)$$

USE MATLAB

$$\hat{i}_1 = 41.9495 \text{ mA}$$


$$\hat{i}_2 = 4.9737 \text{ mA}$$

$$\hat{i}_3 = 1.0698 \text{ mA}$$


$$V_{oc} = 100\Omega i_3 = 100\Omega (1.0698 \text{ mA})$$

$$V_{oc} = 0.1070 \text{ V}$$


Thevenin circuit is

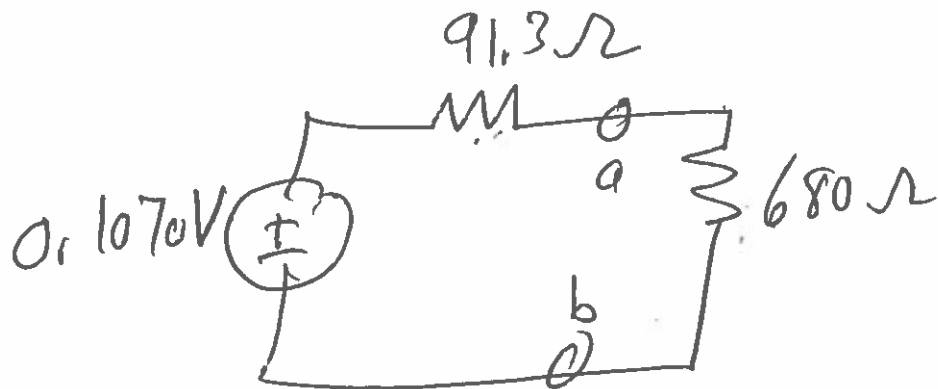

ex

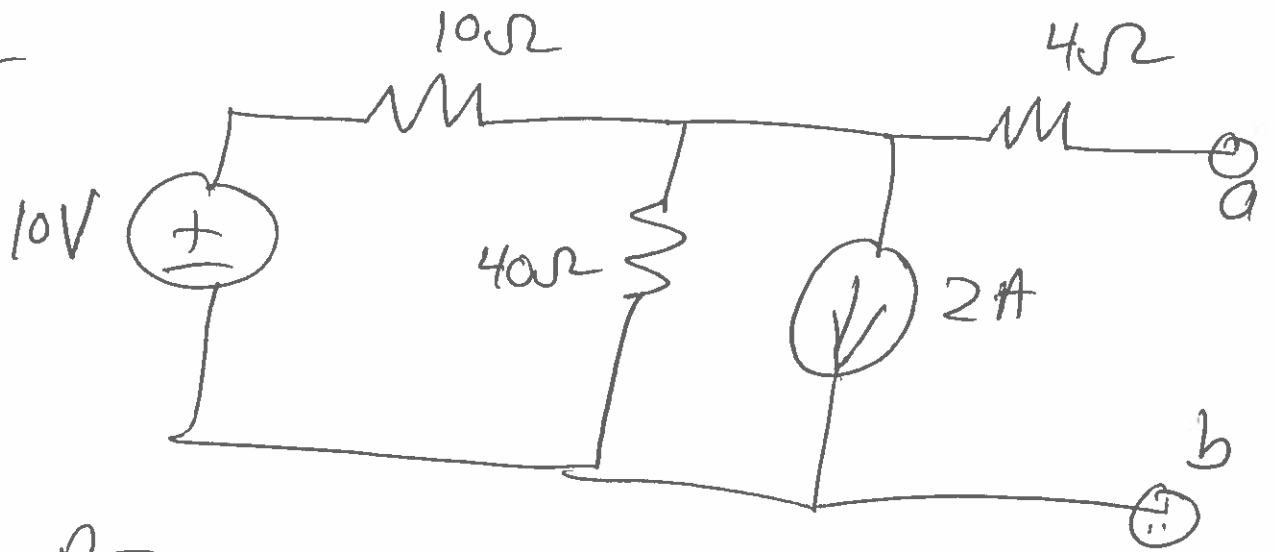

Find R_T

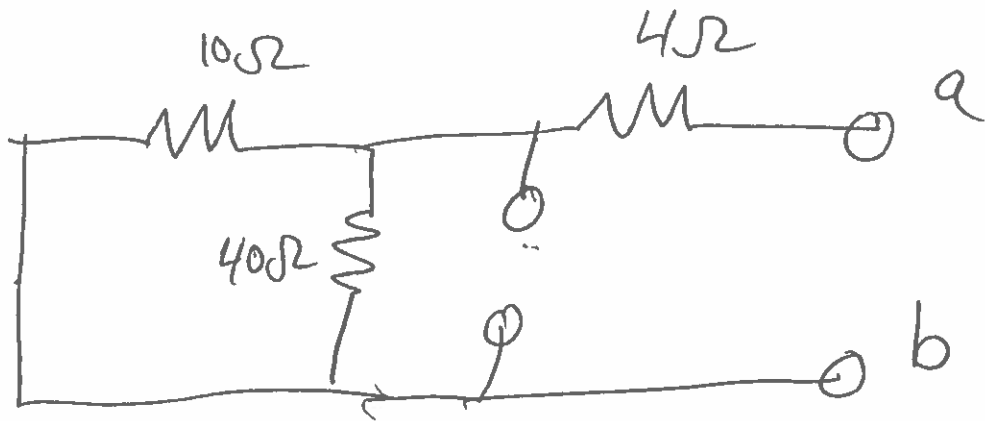

$$\frac{1}{10\Omega} + \frac{1}{40\Omega} = \frac{4+1}{40\Omega} = \frac{5}{40\Omega} = \frac{1}{8\Omega}$$

$$R_T = 8\Omega + 4\Omega = \boxed{12\Omega = R_T}$$