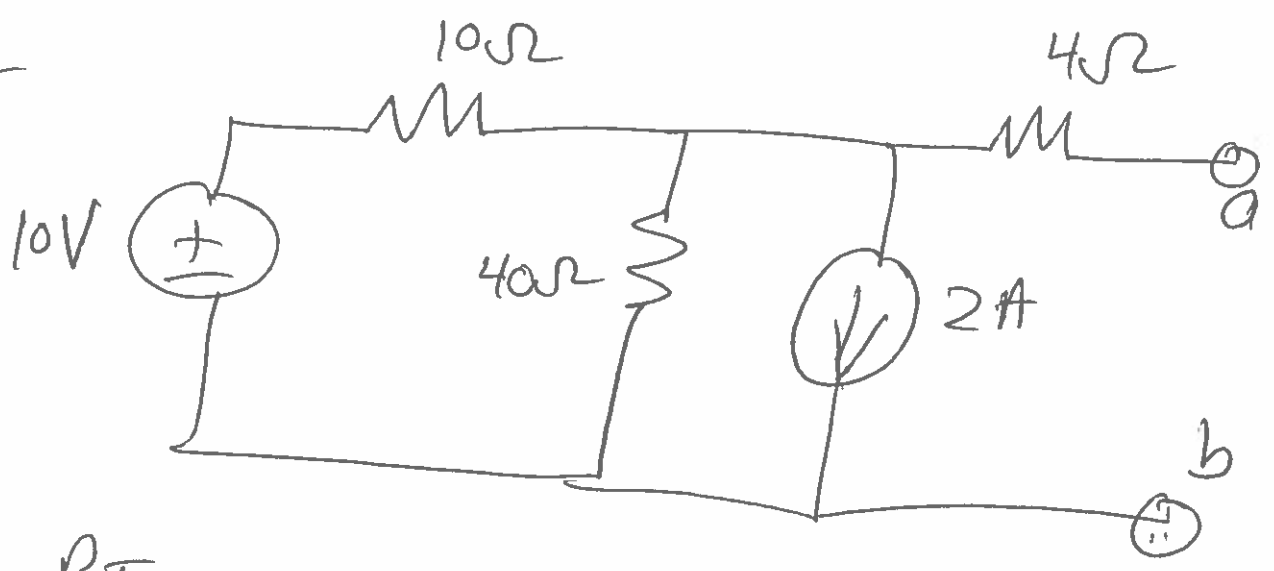


ex




Find R_T



$$\frac{1}{10\Omega} + \frac{1}{40\Omega} = \frac{4+1}{40\Omega} = \frac{5}{40\Omega} = \frac{1}{8\Omega}$$
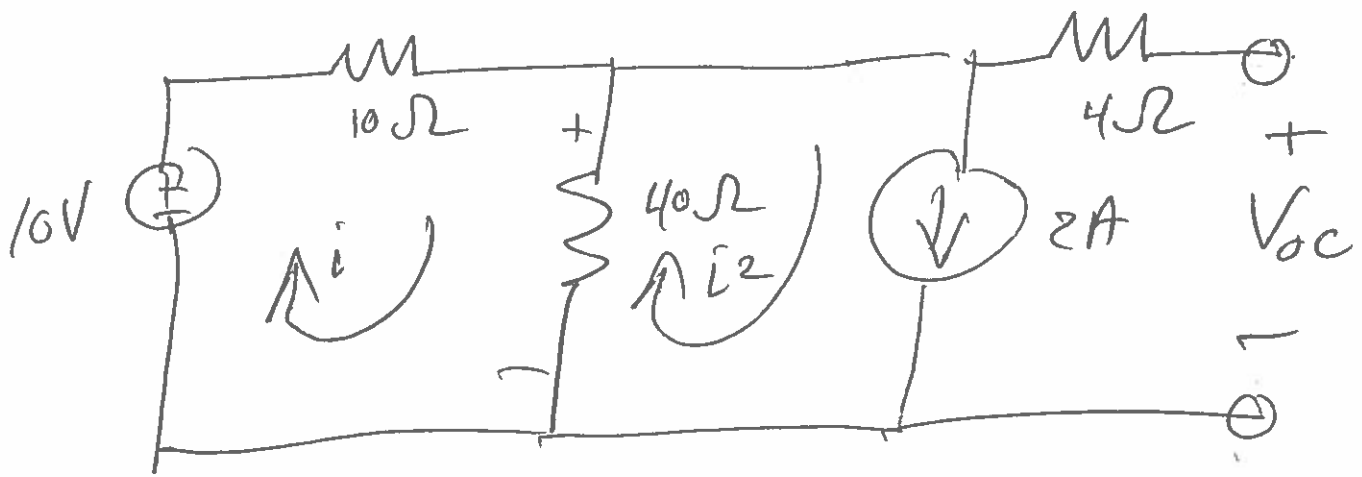
$$R_T = 8\Omega + 4\Omega = \boxed{12\Omega = R_T}$$



$$V_{oc} = V_{40\Omega} = (i_1 - i_2) 40\Omega$$

$$i_2 = 2A$$

$$10V = i_1 (10\Omega + 40\Omega) - i_2 (40\Omega)$$


$$10V = i_1 (50\Omega) - 80V$$

$$+90V = i_1 (50\Omega) \Rightarrow i_1 = \frac{90}{50} V$$


$$i_1 = 1.8A$$


$$V_{oc} = (1.8A - 2A) 40\Omega = -0.2A (40\Omega)$$

$$V_{oc} = -8.0V$$

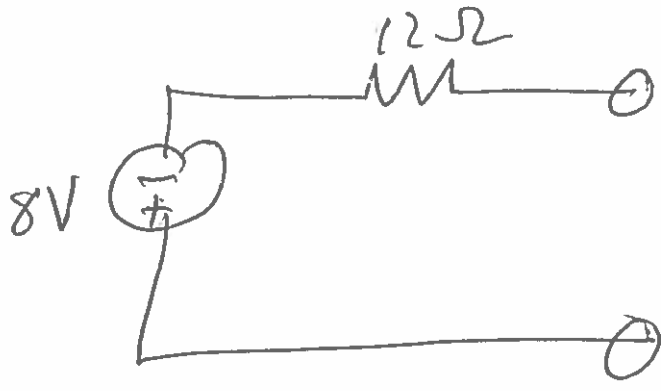


Thevenin
Equivalent
Circuit


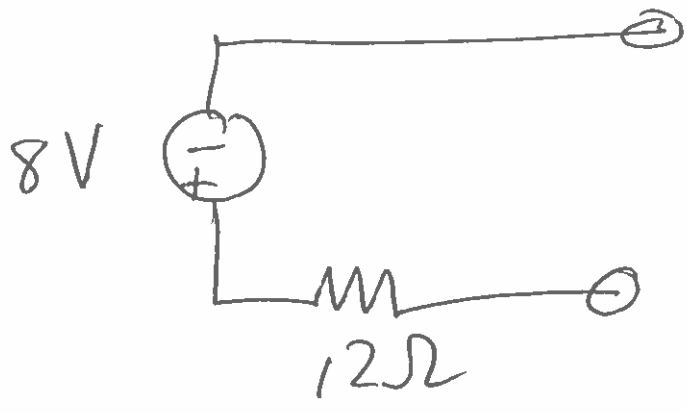


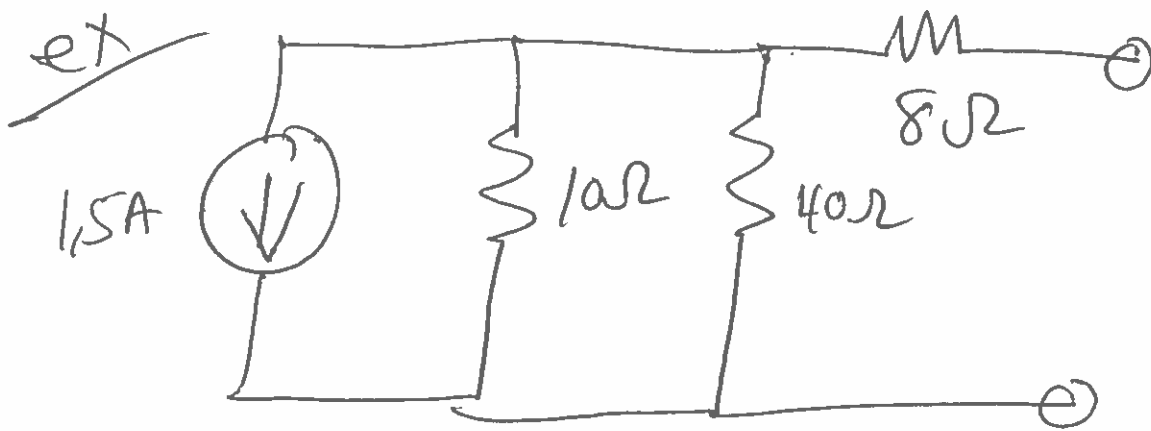


Thevenin EQ ?

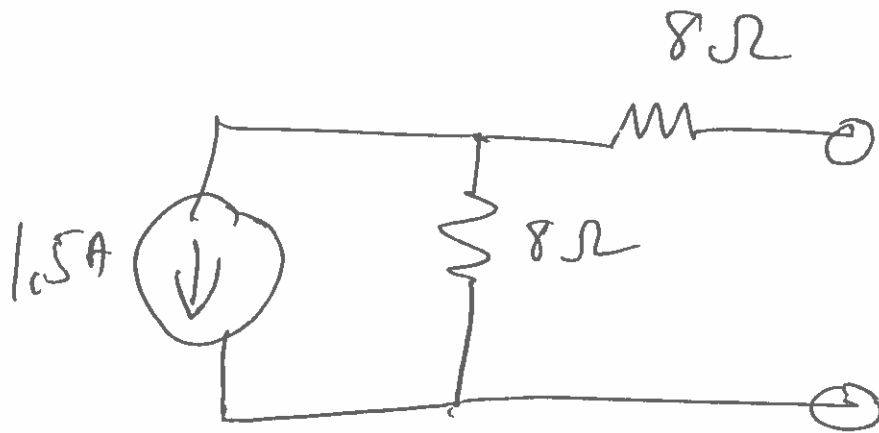

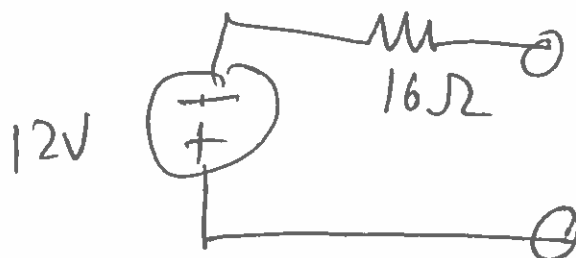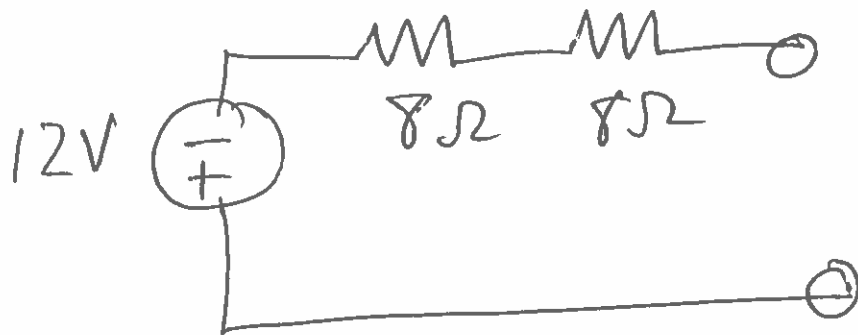
$$\frac{1}{10\Omega} + \frac{1}{40\Omega} = \frac{4+1}{40\Omega} = \frac{1}{8\Omega}$$




ex

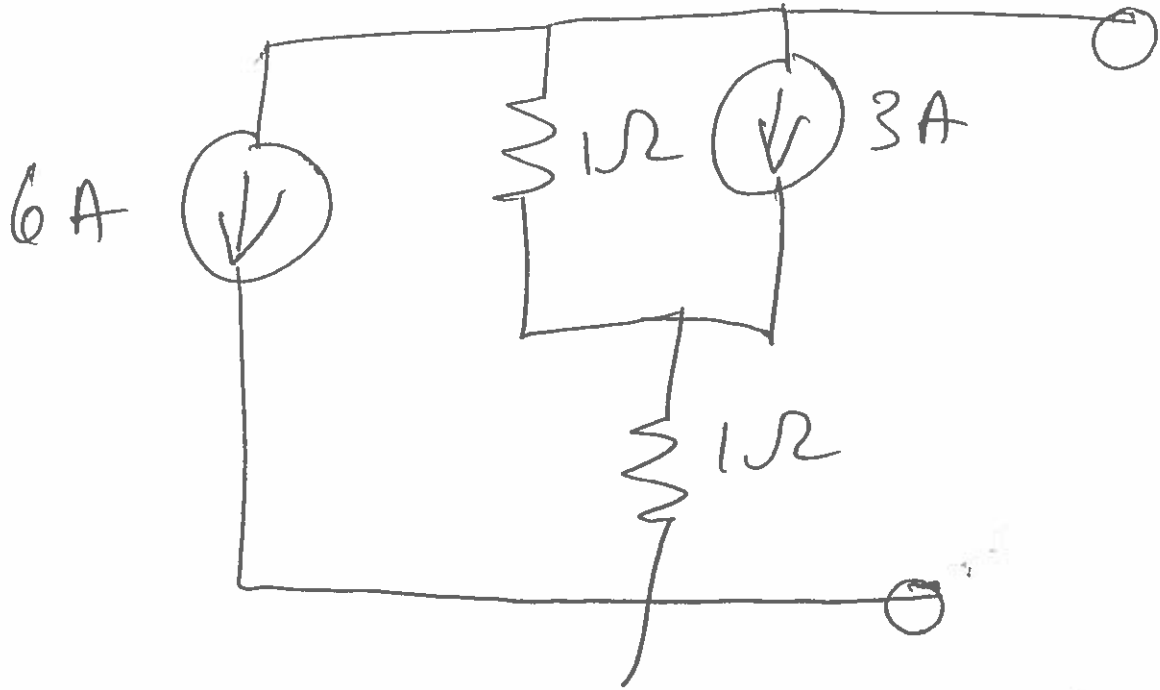

Deactivate sources

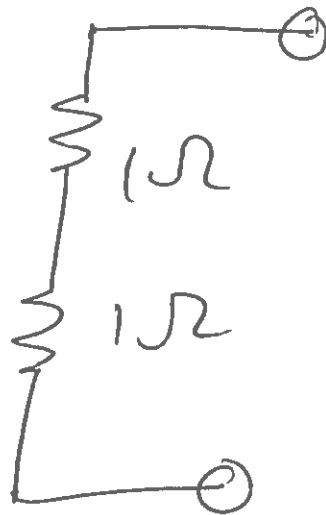


$$\Rightarrow R_T = 2\Omega$$

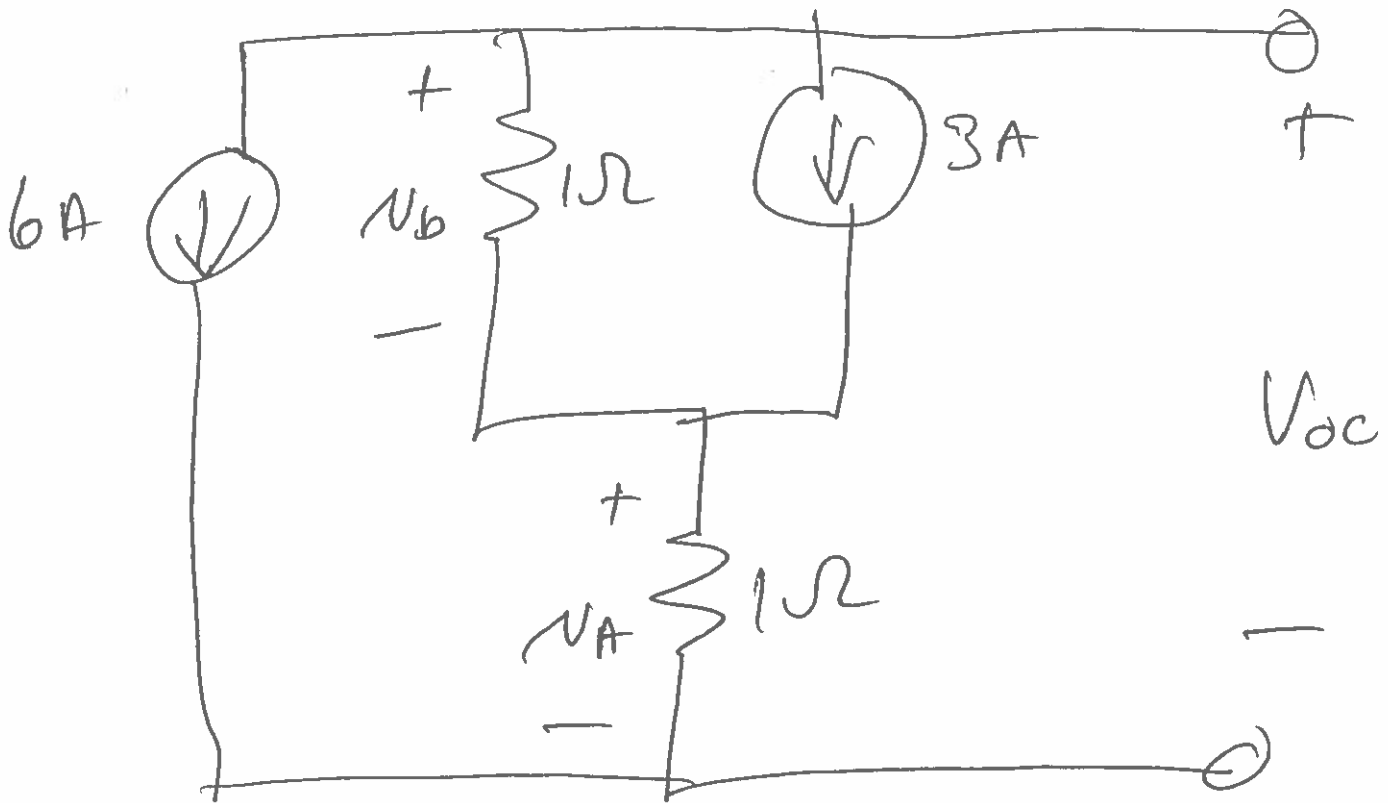

$$V_{oc} = V_b + V_a$$


$$V_a = -6A(1\Omega) = -6V$$

$$V_b = -9A(1\Omega) = -9V$$

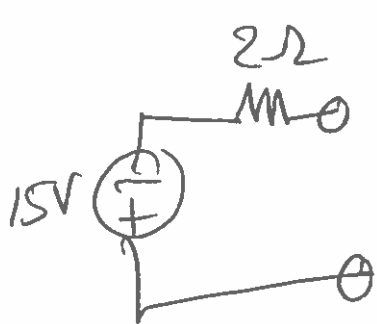


$$V_{oc} = -15V$$


⇐ Thevenin Equivalent!


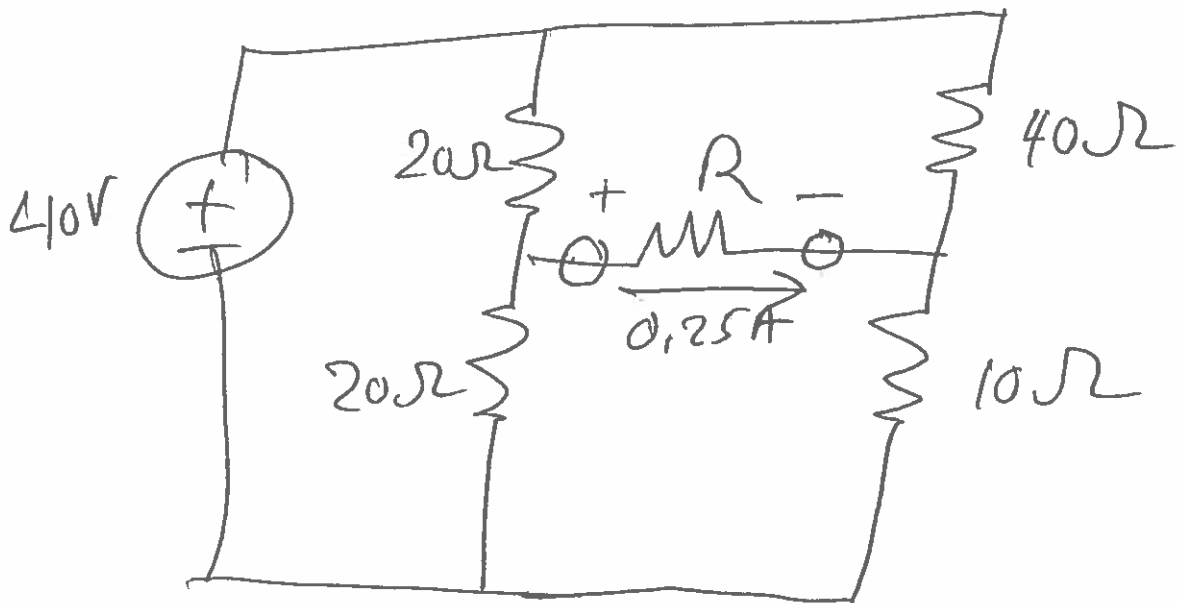


$R = ?$

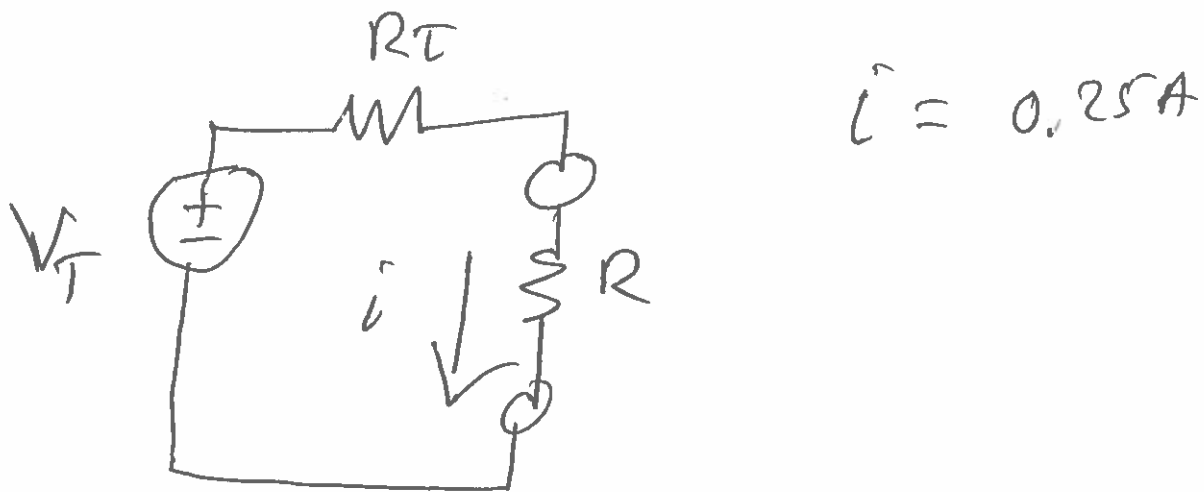


find R_T

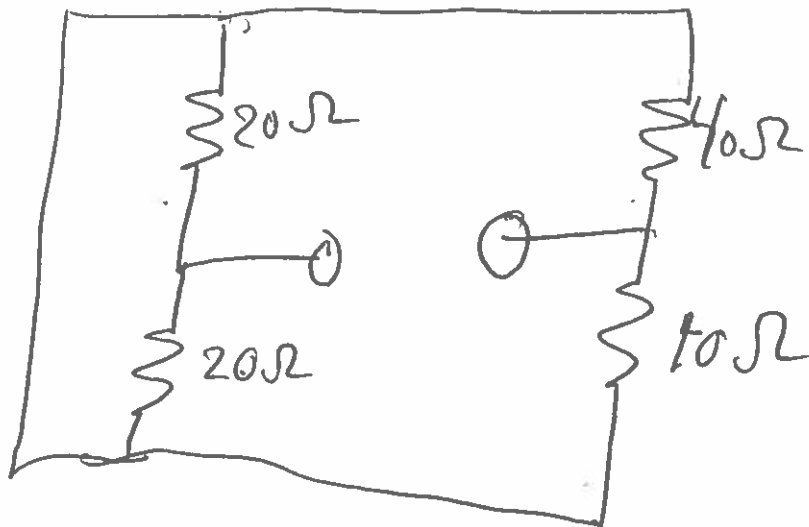

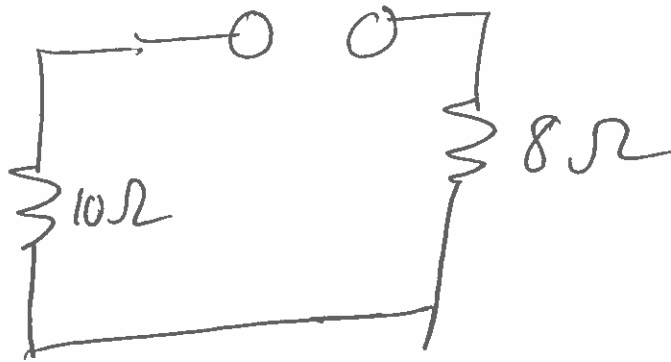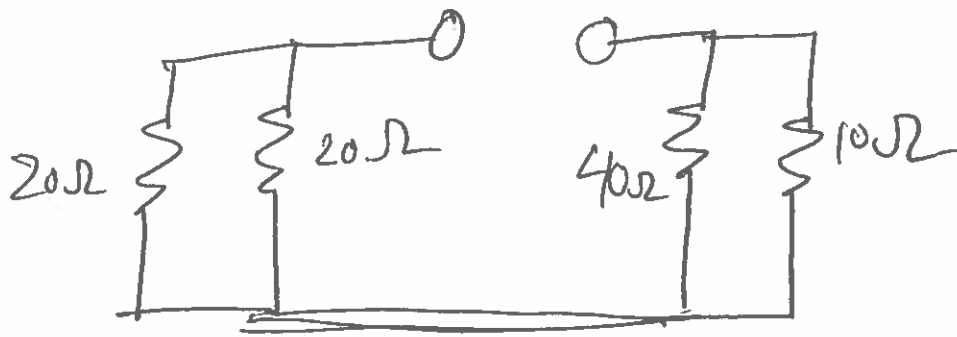


$$R_T = 18\Omega$$

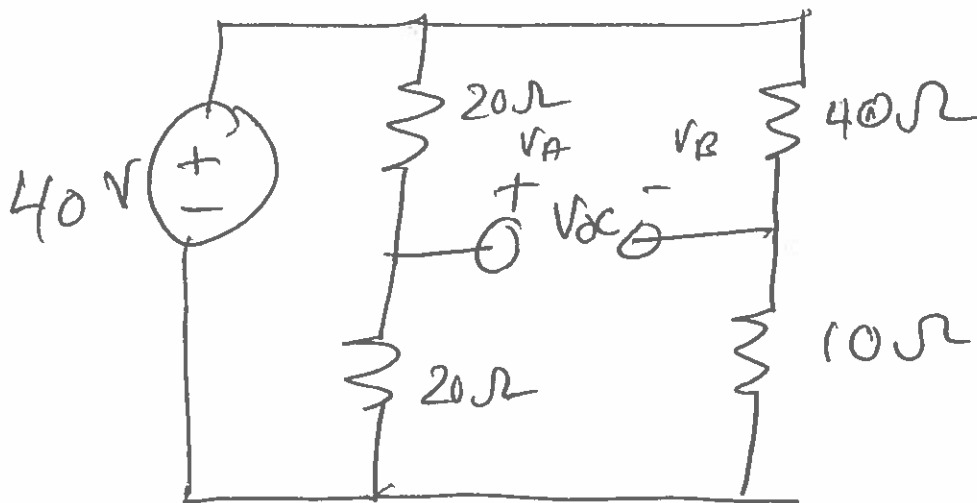

$$V_{OC} = V_A - V_B \quad V_A = 40V \left(\frac{20\Omega}{20\Omega + 20\Omega} \right) = 20V$$

$$V_B = 40V \left(\frac{10\Omega}{40\Omega + 10\Omega} \right) = 8V$$

$$V_{OC} = 20V - 8V = 12V$$


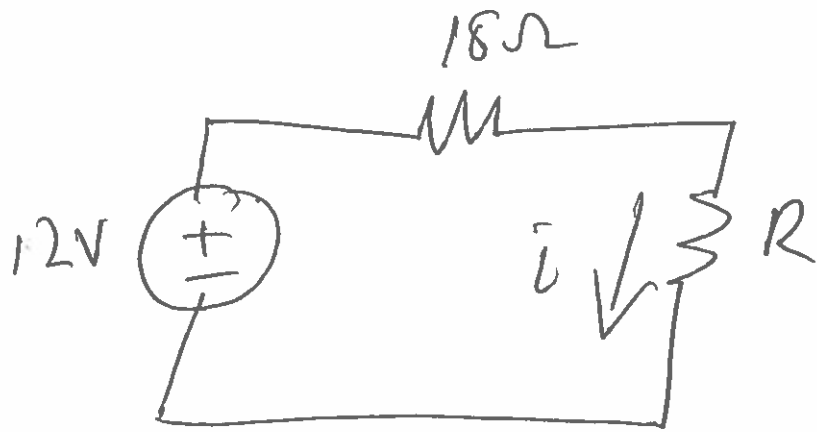


$$i = 0,25A = \frac{12V}{18\Omega + R}$$


$$18\Omega + R = \frac{12V}{0,25A} = 48\Omega$$

$$R = 48\Omega - 18\Omega = 30\Omega$$

Lab ex

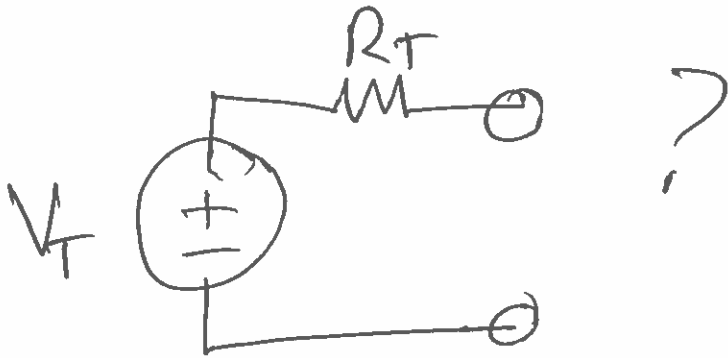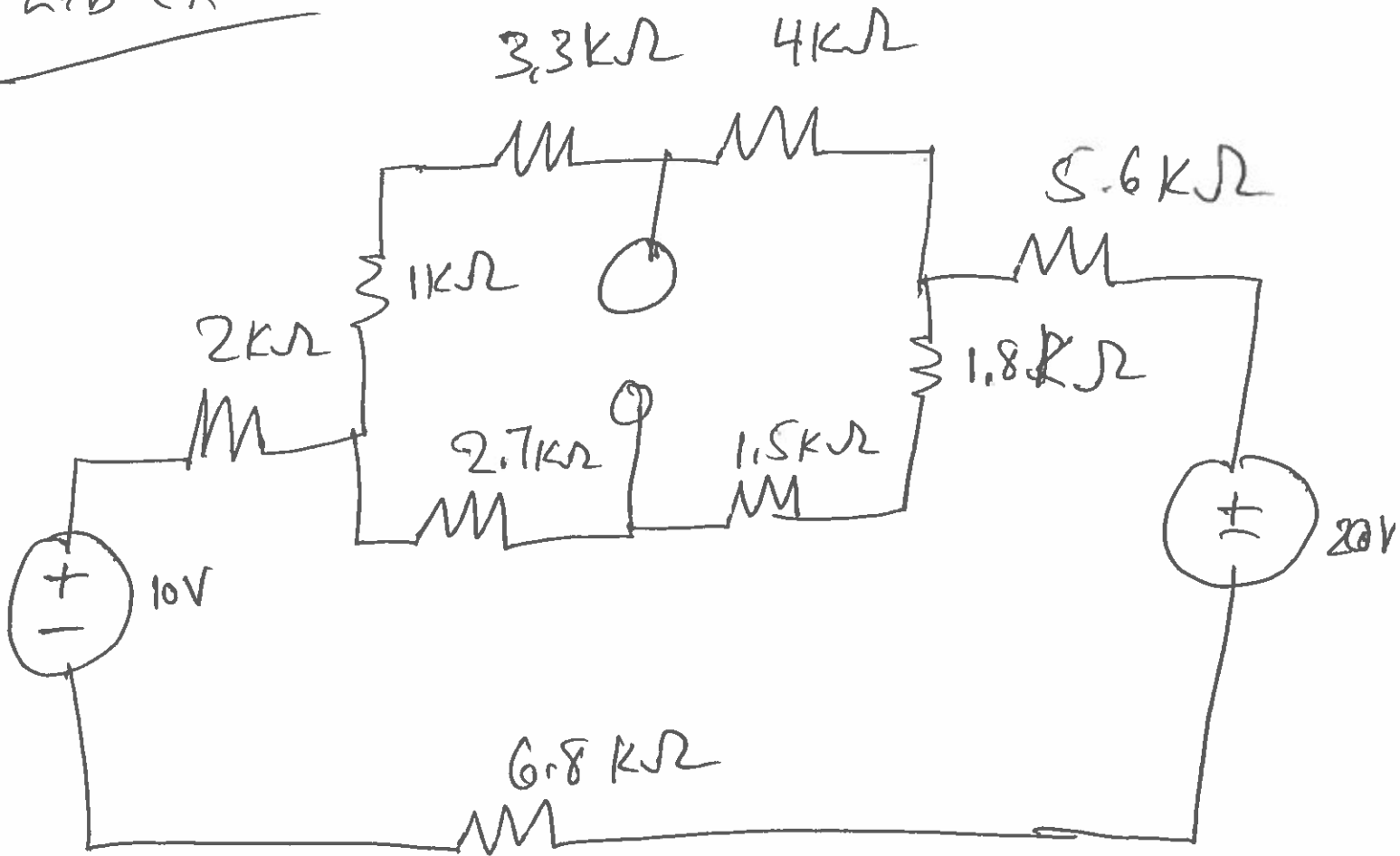


De activate power sources

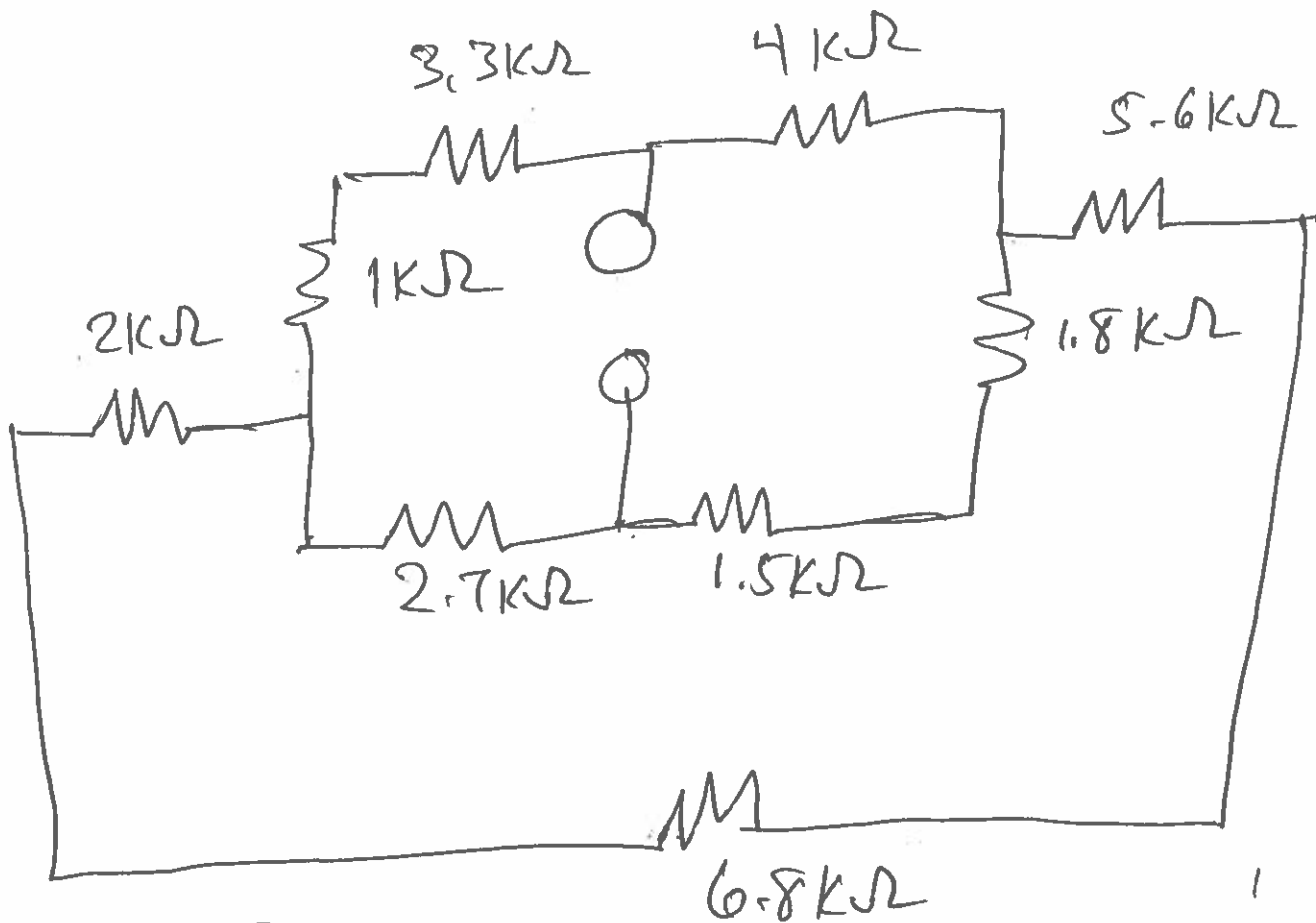

$R_T = ?$

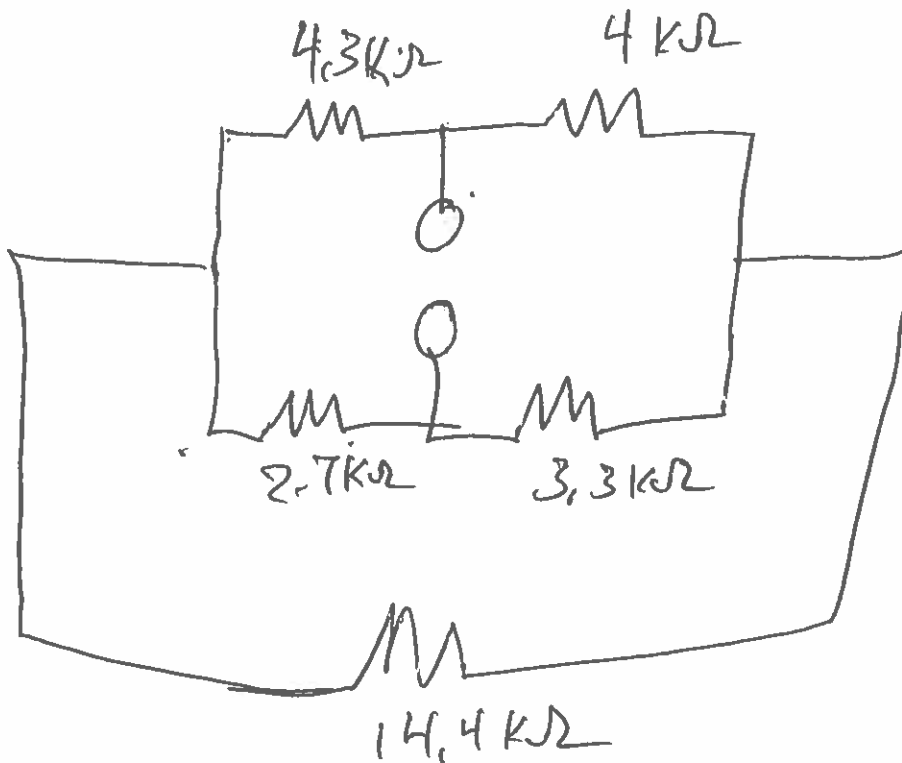
$$\begin{array}{r} 1 \\ 7.6 \\ \hline 6.8 \\ \hline 14.4 \end{array}$$



From ohm's law

$$R = \frac{V}{i}$$

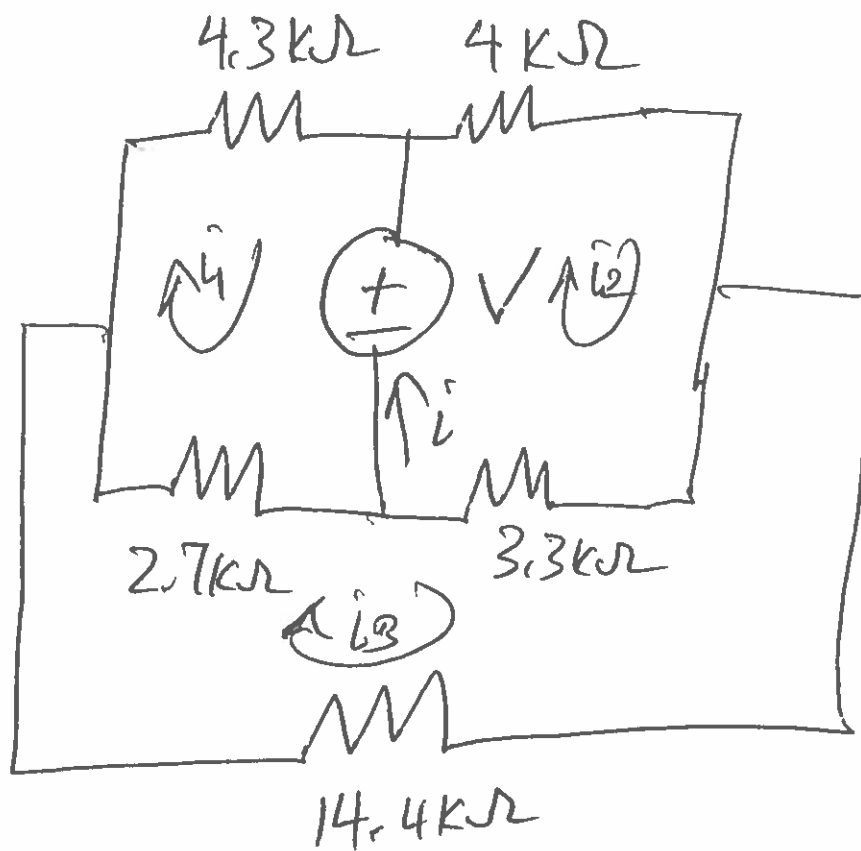So Place an arbitrary voltage source between terminals.



Find i $\Rightarrow R_T = \frac{V}{i}$ $i = i_2 - i_1$

Now write out Mesh equations

$$-V = i_1 (4.3k\Omega + 2.7k\Omega) - i_3 (2.7k\Omega)$$

$$+V = i_2 (4k\Omega + 3.3k\Omega) - i_3 (3.3k\Omega)$$

$$0 = i_3 (2.7k\Omega + 3.3k\Omega + 14.4k\Omega) - i_1 (2.7k\Omega) - i_2 (3.3k\Omega)$$