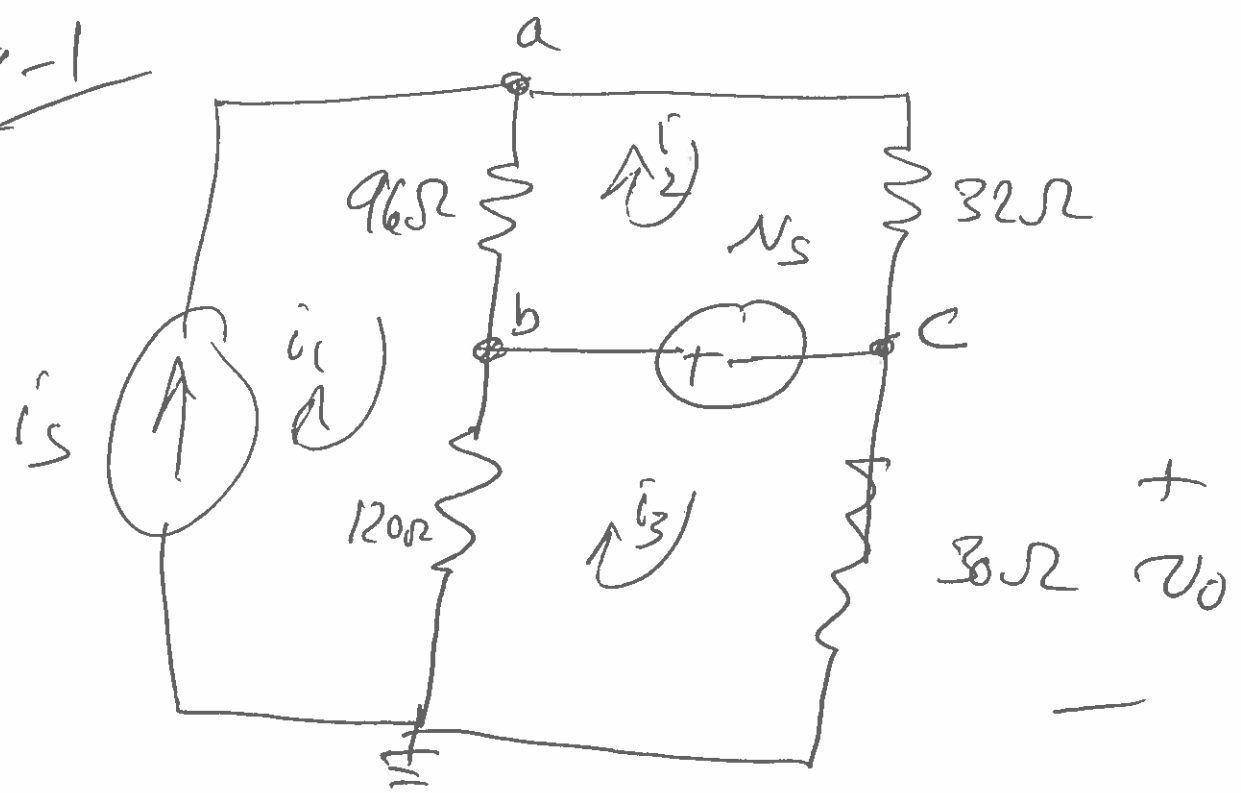


4.8-1



$$v_o = a i_s + b v_s$$

- Use Mesh
- Use voltage nodes

Mesh

$$\hat{i}_1 \Rightarrow \hat{i}_1 = i_s$$

$$\hat{i}_2 \Rightarrow v_s = \hat{i}_2 (96\Omega + 32\Omega) - \hat{i}_1 (96\Omega)$$

$$\hat{i}_3 \Rightarrow -v_s = \hat{i}_3 (30\Omega + 120\Omega) - \hat{i}_1 (120\Omega)$$

$$v_s = \hat{i}_2 (128\Omega) - \hat{i}_1 (96\Omega)$$

$$-v_s = \hat{i}_3 (150\Omega) - \hat{i}_1 (120\Omega)$$

$$V_o = i_3 (30\Omega)$$

from 3rd mesh equation



$$i_3 = \frac{i_s (120\Omega) - V_s}{150\Omega}$$

$$V_o = \left(\frac{i_s (120\Omega) - V_s}{150\Omega} \right) 30\Omega$$


Voltage nodes

$$V_o = V_c$$

Lab ex

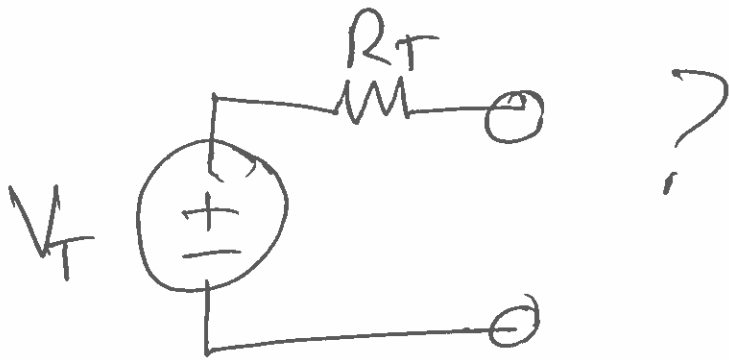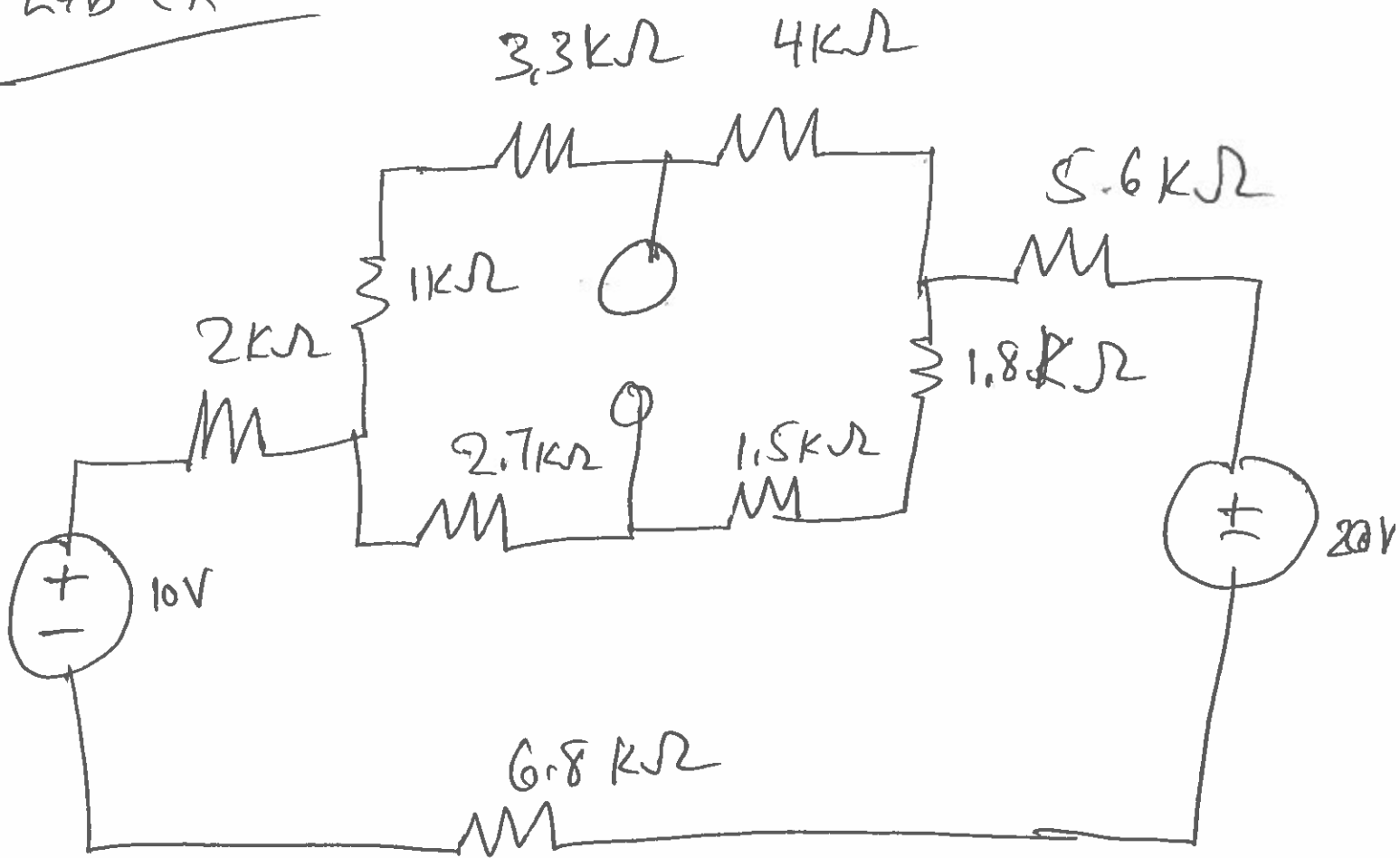


De activate power sources

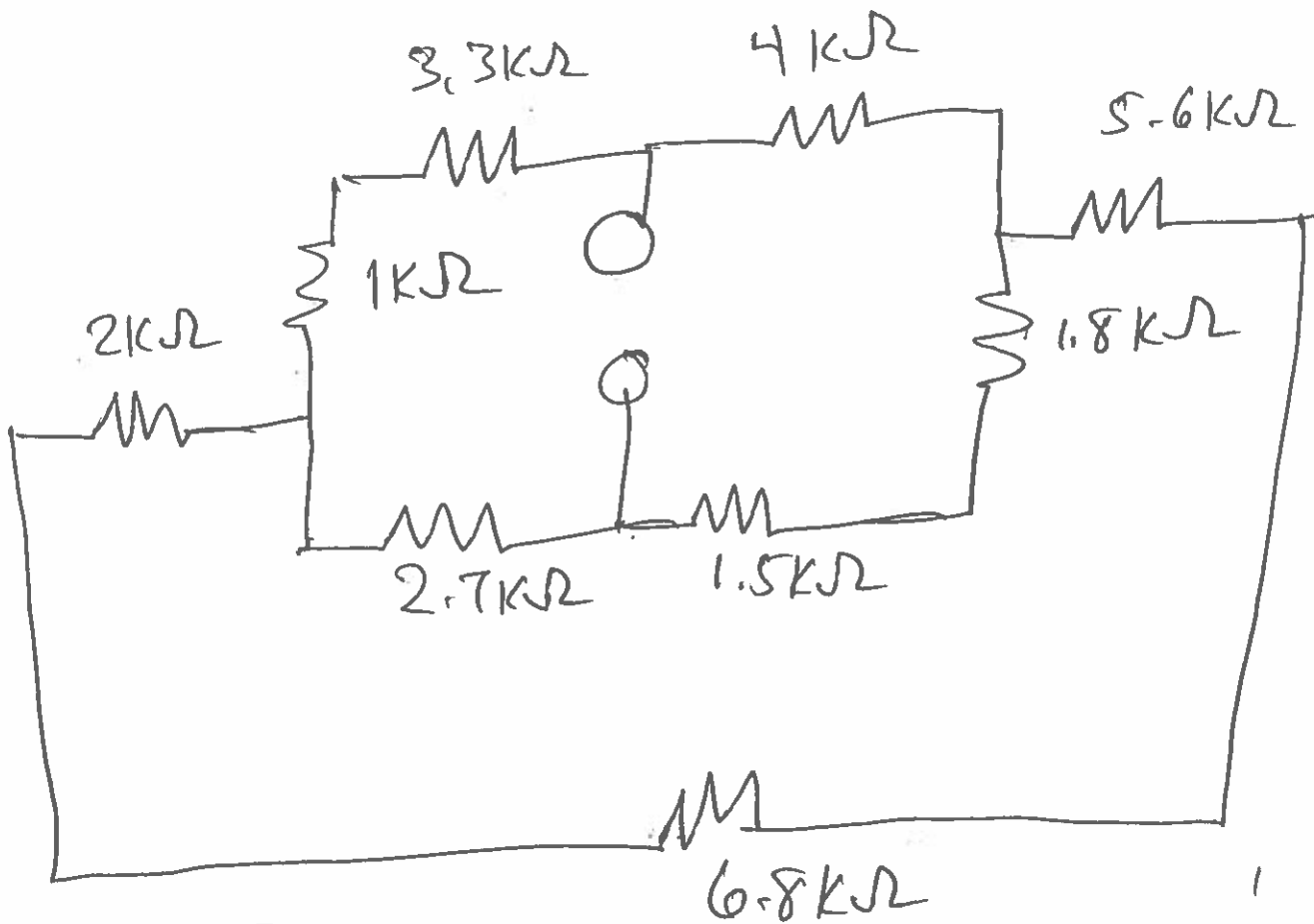

$R_T = ?$

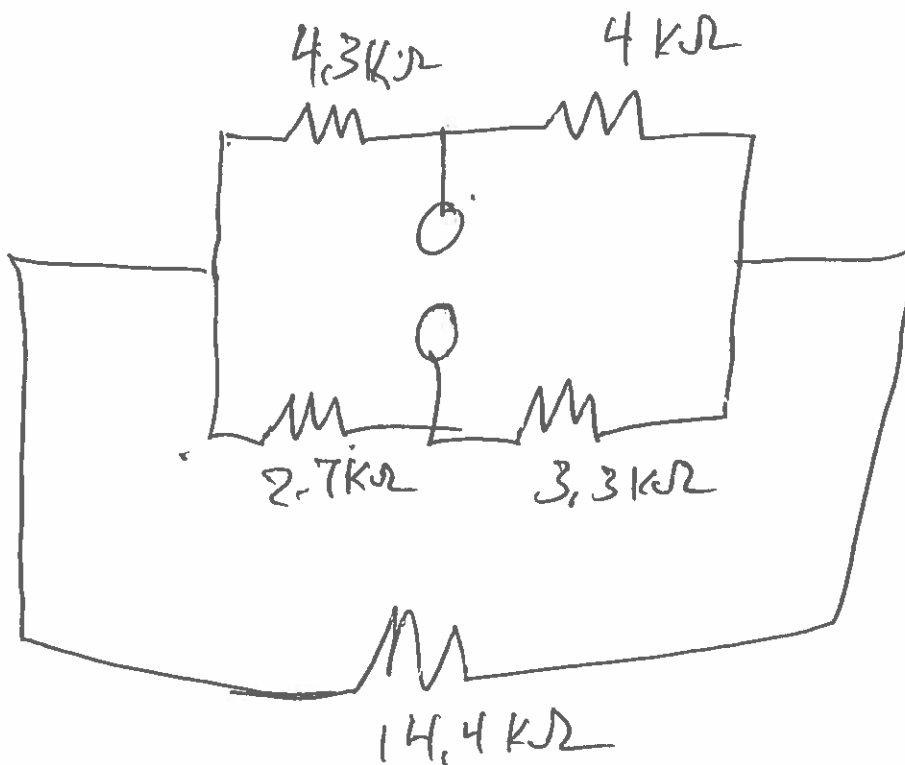
$$\frac{1}{\frac{1}{7.6} + \frac{1}{6.8}}$$



From ohm's law

$$R = \frac{V}{i}$$

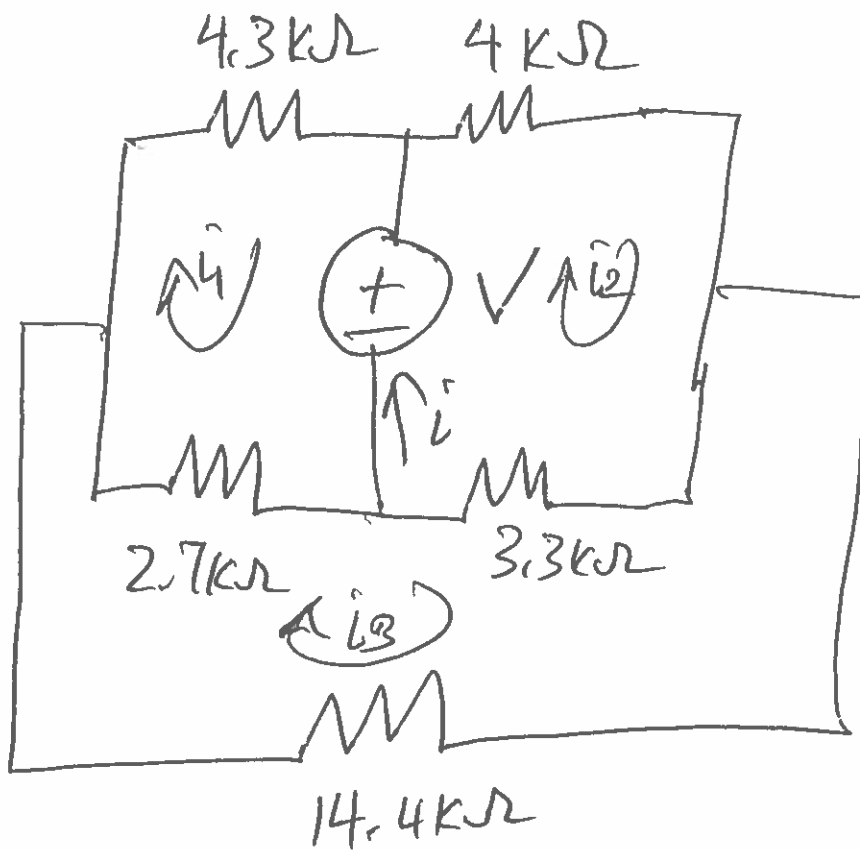So Place an arbitrary voltage source between terminals



Find \hat{i} $\Rightarrow R_T = \frac{V}{\hat{i}}$ $\hat{i} = \hat{i}_2 - \hat{i}_1$

Now write out Mesh equations

$$-V = \hat{i}_1 (4.3k\Omega + 2.7k\Omega) - \hat{i}_3 (2.7k\Omega)$$

$$+V = \hat{i}_2 (4k\Omega + 3.3k\Omega) - \hat{i}_3 (3.3k\Omega)$$

$$0 = \hat{i}_3 (2.7k\Omega + 3.3k\Omega + 14.4k\Omega) - \hat{i}_1 (2.7k\Omega) - \hat{i}_2 (3.3k\Omega)$$

Solve for 1st two equations

Understand
units for R
are $k\Omega$

$$\hat{i}_1 = \frac{\hat{i}_3 (2.7) - V}{4.3 + 2.7}$$

$$\hat{i}_1 = \frac{\hat{i}_3 (2.7) - V}{7.0}$$

$$\hat{i}_2 = \frac{\hat{i}_3 (3.3) + V}{4 + 3.3} = \frac{\hat{i}_3 (3.3) + V}{7.3} = \hat{i}_2$$

3rd eqn $0 = -\hat{i}_1 (2.7) - \hat{i}_2 (3.3) + \hat{i}_3 (20.4)$

$$0 = \left[\frac{\hat{i}_3 (2.7) - V}{7} \right] (2.7) - \left[\frac{\hat{i}_3 (3.3) + V}{7.3} \right] (3.3) + \hat{i}_3 (20.4)$$

$$0 = i_3 \left[\frac{(2.7)^2}{7} - \frac{(3.3)^2}{7.3} + 20.4 \right] + V \left[\frac{(2.7)}{7} - \frac{(3.3)}{7.3} \right]$$

$$0 = i_3 [17.87] + V [-0.066]$$

$$i_3 = \frac{V [0.066]}{[17.87]} = (3.69 \times 10^{-3}) V$$

$$i_3 = (3.69 \times 10^{-3}) V$$


$$i = i_2 - i_1 = \frac{i_3 (3.3) + V}{7.3} - \frac{i_3 (2.7) - V}{7.0}$$

$$i = i_3 \left[\frac{3.3}{7.3} - \frac{2.7}{7.0} \right] + V \left[\frac{1}{7.3} + \frac{1}{7.0} \right]$$

$$i = (3.69 \times 10^{-3}) V (0.066) + V (0.2798)$$

$$\bar{i} = V(0,280)$$
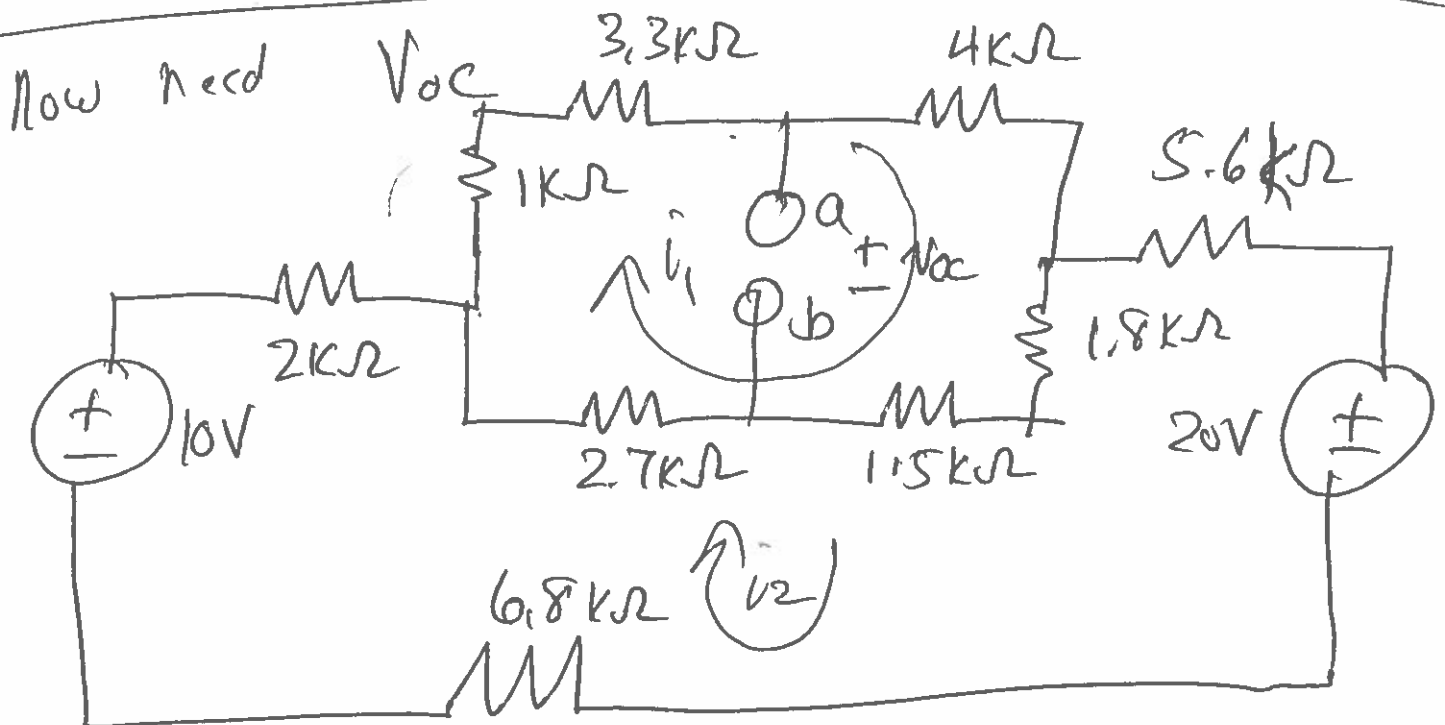
$$R_T = \frac{V}{\bar{i}} = \frac{V}{V(0,280)} = \boxed{3,57 \text{ k}\Omega}$$



find $\bar{i}_1, \bar{i}_2 \Rightarrow$ Do voltage walk from $b \rightarrow a$

Mesh equations

$$0 = \hat{i}_1 (1\text{k}\Omega + 33\text{k}\Omega + 4\text{k}\Omega + 1.5\text{k}\Omega + 2.7\text{k}\Omega) + 1.8\text{k}\Omega) - \hat{i}_2 (2.7\text{k}\Omega + 1.5\text{k}\Omega + 1.8\text{k}\Omega)$$

$$10\text{V} - 20\text{V} = \hat{i}_2 (6.8\text{k}\Omega + 2\text{k}\Omega + 2.7\text{k}\Omega + 1.5\text{k}\Omega + 1.8\text{k}\Omega + 5.6\text{k}\Omega) - \hat{i}_1 (2.7\text{k}\Omega + 1.5\text{k}\Omega + 1.8\text{k}\Omega)$$

$$0 = \hat{i}_1 (14.3\text{k}\Omega) - \hat{i}_2 (6.0\text{k}\Omega) \quad \times 6.0$$

$$-10\text{V} = -\hat{i}_1 (6.0\text{k}\Omega) + \hat{i}_2 (20.4\text{k}\Omega) \quad \times 14.3$$

$$-143\text{V} = \hat{i}_2 (255.7\text{k}\Omega) \Rightarrow \hat{i}_2 = \cancel{0.559} - 0.55925\text{mA}$$

$$\hat{i}_1 = \hat{i}_2 \left(\frac{6}{14.3} \right)$$

$$\hat{i}_1 = -0.23465\text{mA}$$

$$V_{ocL} = 2.7k\Omega (\hat{i}_2 - \hat{i}_1) - \hat{i}_1 (1k\Omega + 3.3k\Omega)$$

$$V_{ocL} = 2.7k\Omega (-0.55925mA - (-0.23465mA))$$

$$- (-0.23465mA) (4.3k\Omega)$$




$$V_{ocL} = 0.13258V$$

$$V_{ocR} = (1.5k\Omega + 1.8k\Omega) (\hat{i}_1 - \hat{i}_2) + \hat{i}_1 (4k\Omega)$$
$$= (3.3k\Omega) (-0.23465mA - (0.55925mA))$$


$$+ (-0.23465mA) (4k\Omega)$$

$$= 0.13258V \quad \checkmark$$

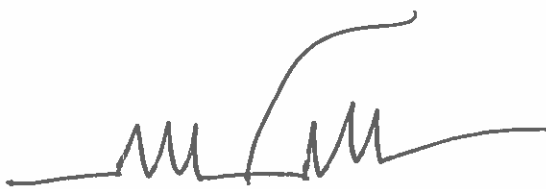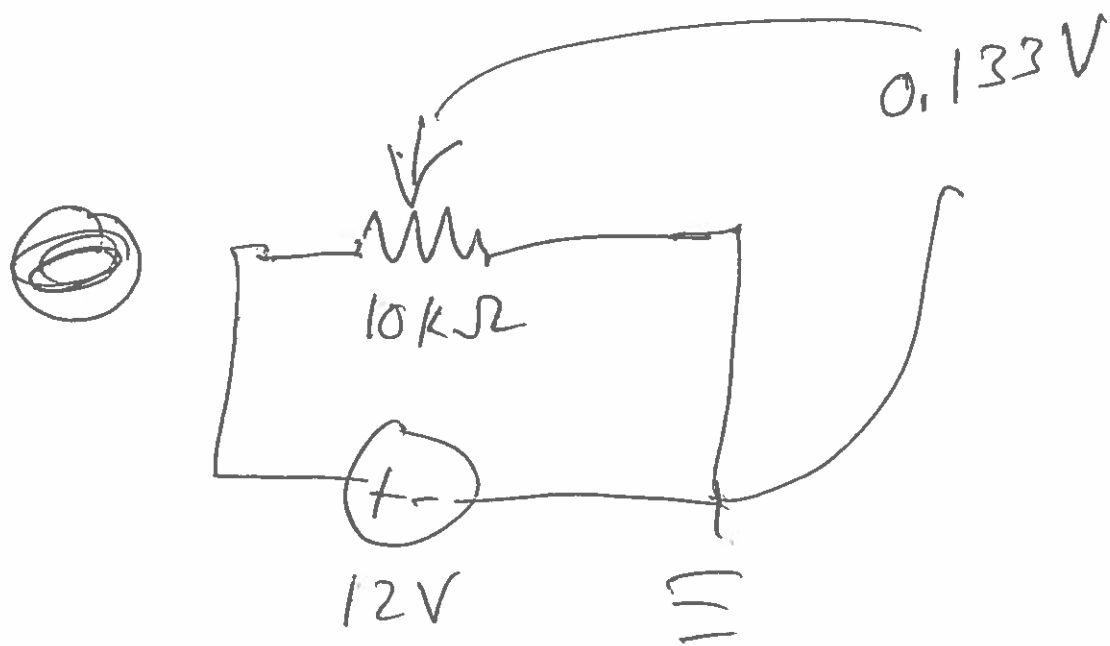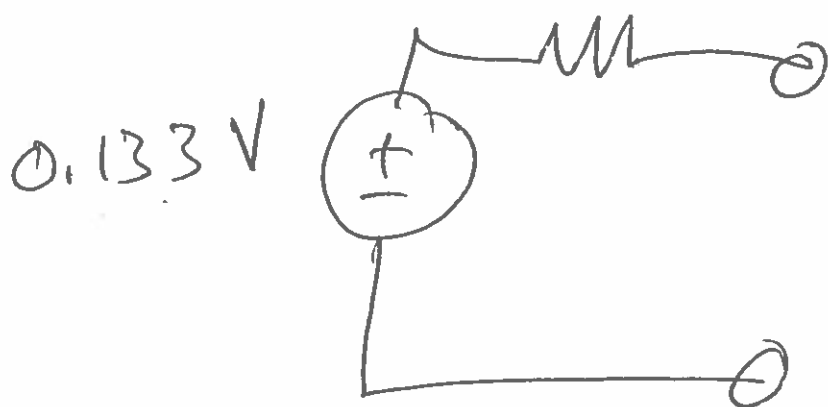
Thevenin circuit \Rightarrow
 $3.57\text{k}\Omega$




Norton Equivalent Circuit

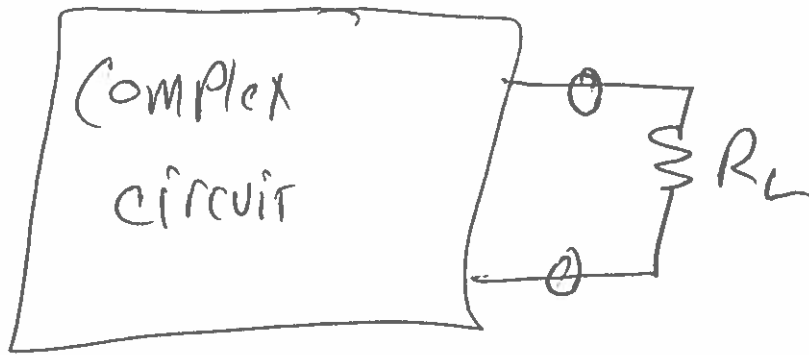

Replace it with

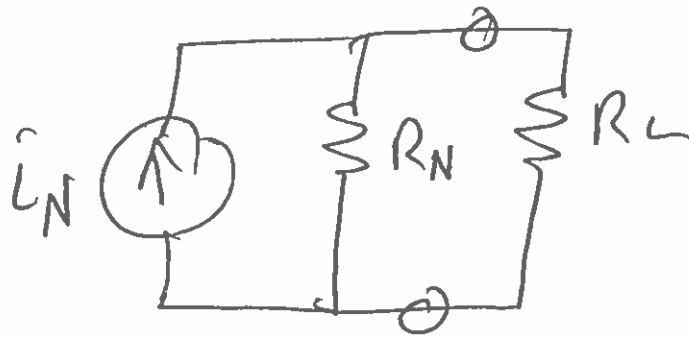

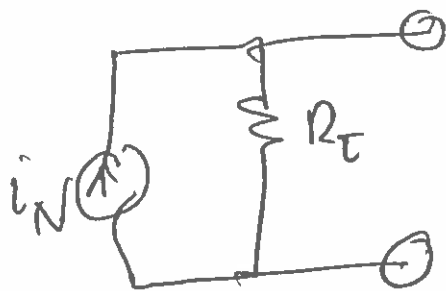
because of source Transformations $R_N = R_T$





Again Deactive power sources find

$$R_T = R_{\text{equivalent}}$$

i_N is $i_{\text{short circuit}}$

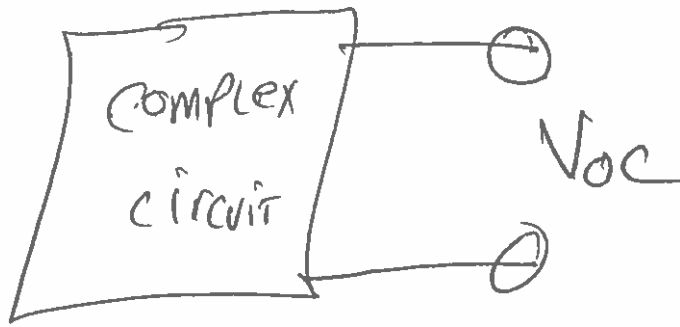


Thevenin

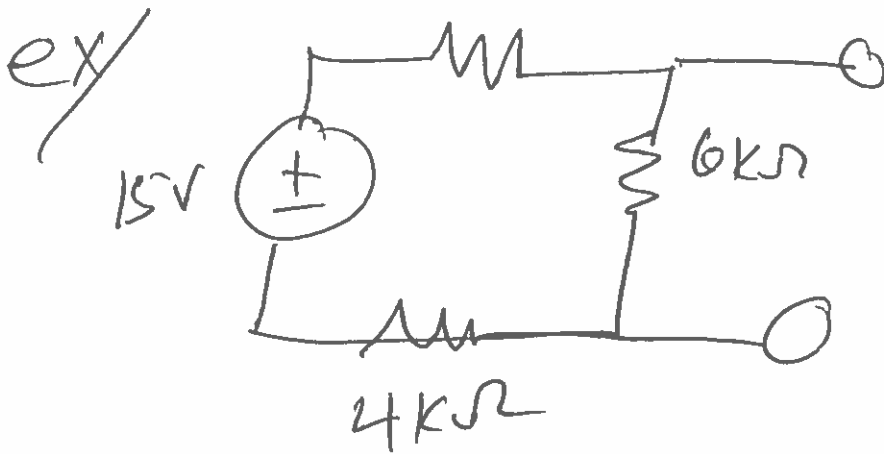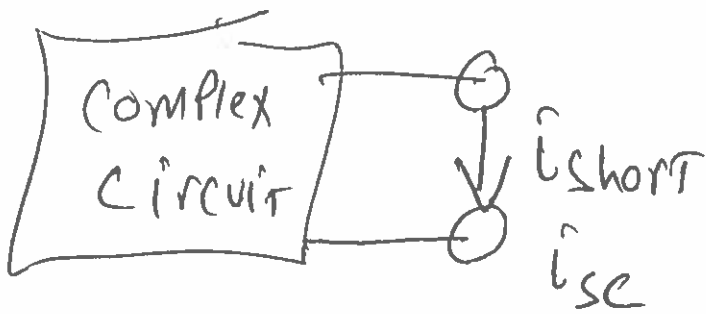

Find
Norton EQUIV.

Deactivate

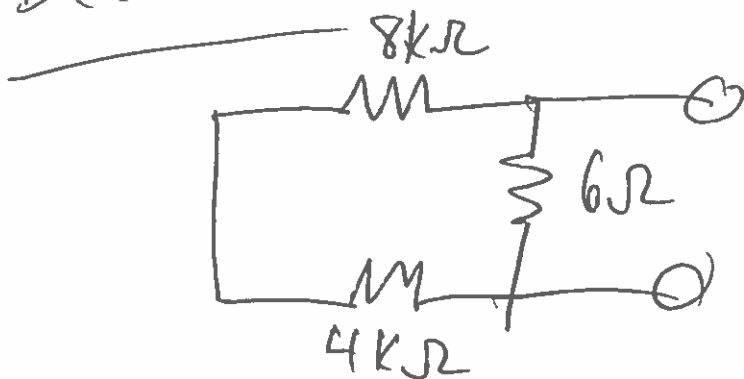


\Rightarrow




$$\frac{1}{12k\Omega} + \frac{1}{6k\Omega} = \frac{1+2}{12k\Omega} = \frac{3}{12k\Omega} = \frac{1}{4k\Omega}$$


$$R_T = 4k\Omega$$

8kΩ

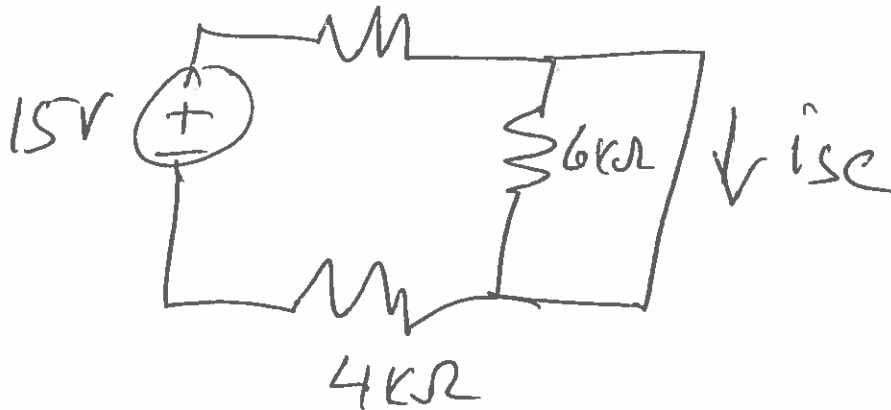

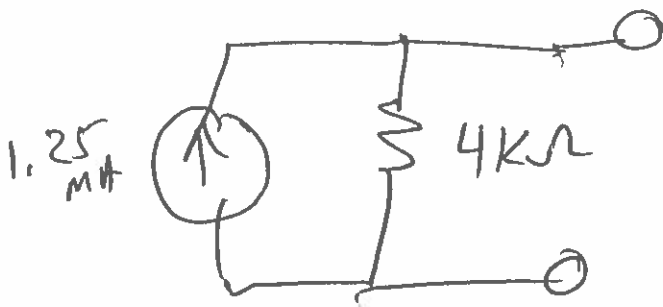
$$i_{sc} = \frac{15V}{12k\Omega} = 1,25mA$$



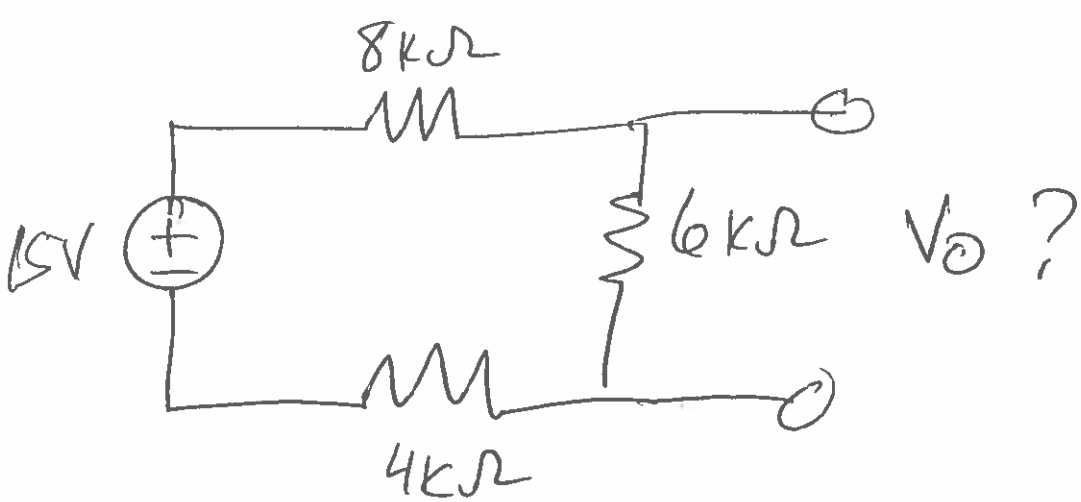


$$V_o = \frac{(15V) 6k\Omega}{8k\Omega + 4k\Omega + 6k\Omega} = 15V \left(\frac{6k\Omega}{18k\Omega} \right)$$

$$V_o = 5V$$

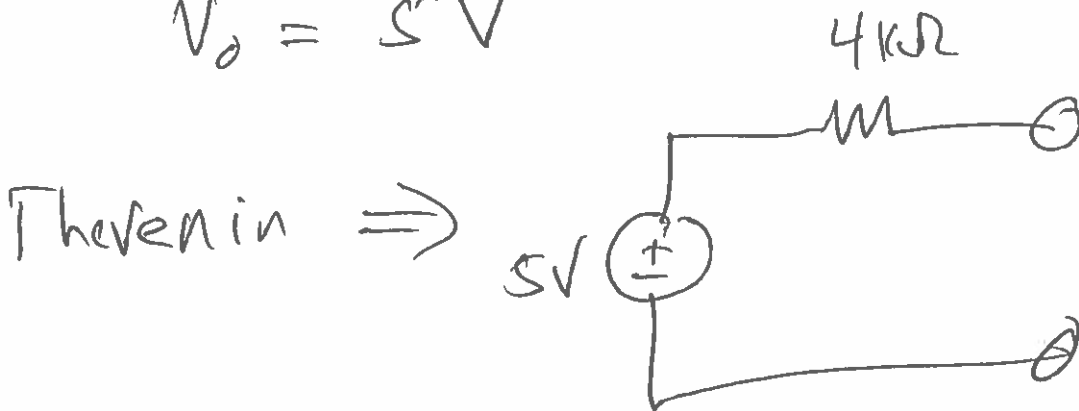

Source Transform

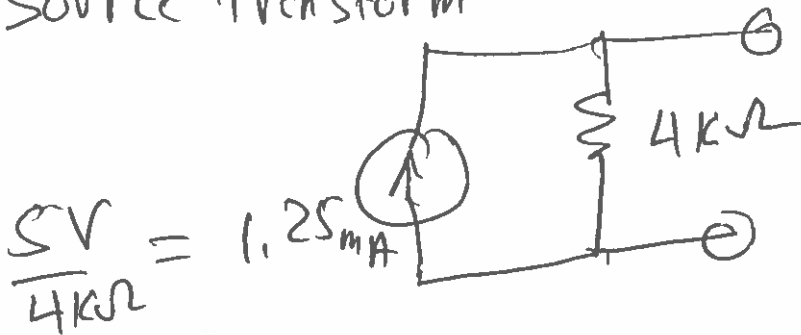

Recall Thevenin, Norton are dual circuits