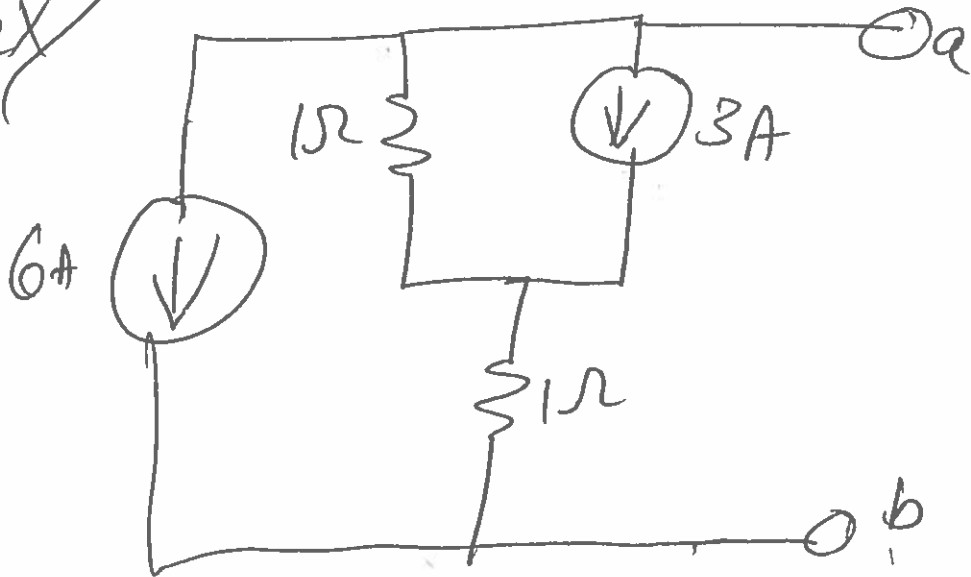



ex



Deactivating Power



$$\Rightarrow R_T = 2\Omega$$

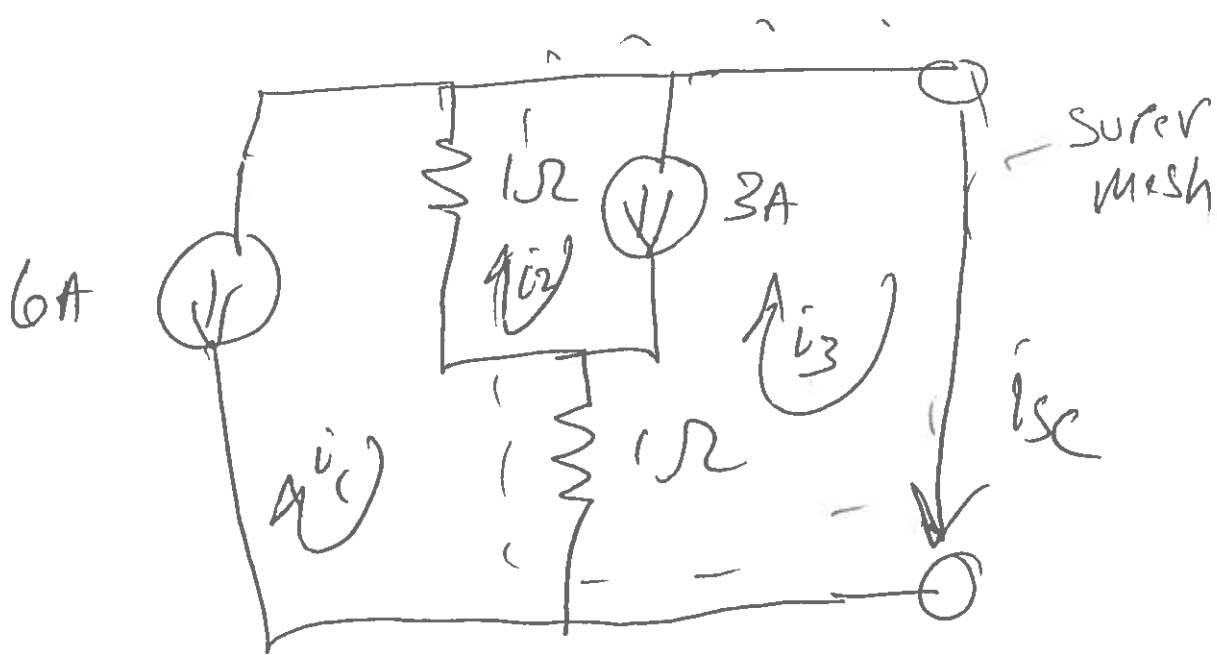

$$i_1 = -6A$$

$$i_2 - i_3 = 3A$$




$$i_2(1\Omega) + i_3(1\Omega) - i_1(1\Omega + 1\Omega) = 0$$



$$i_2 + i_3 = (6A(2\Omega)) = 12$$


$$i_2 + i_3 = 12A$$

$$-(i_2 - i_3 = 3A)$$
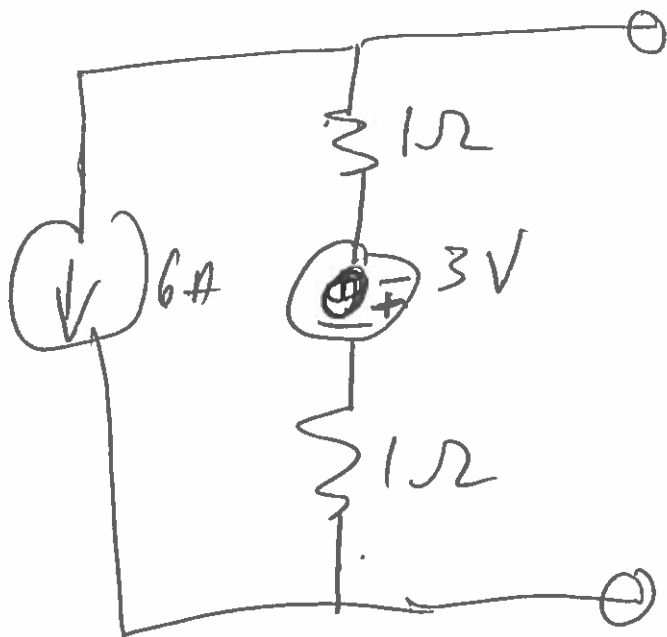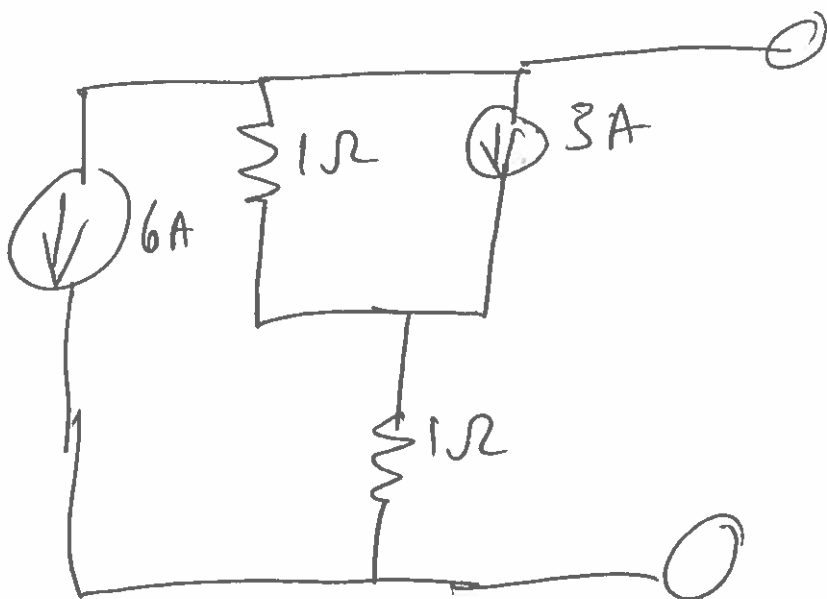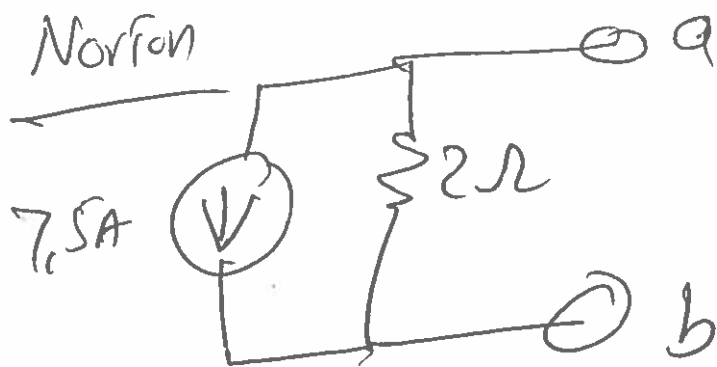
$$2i_3 = -15A \Rightarrow \underline{i_3 = -7.5A}$$





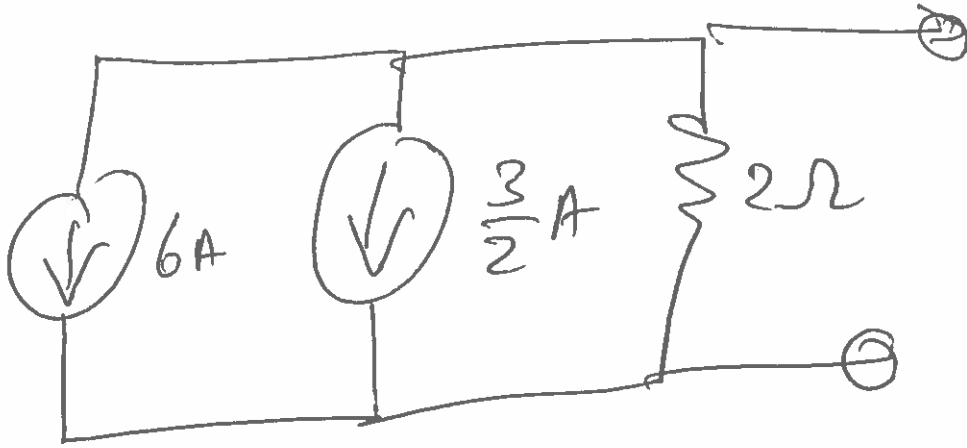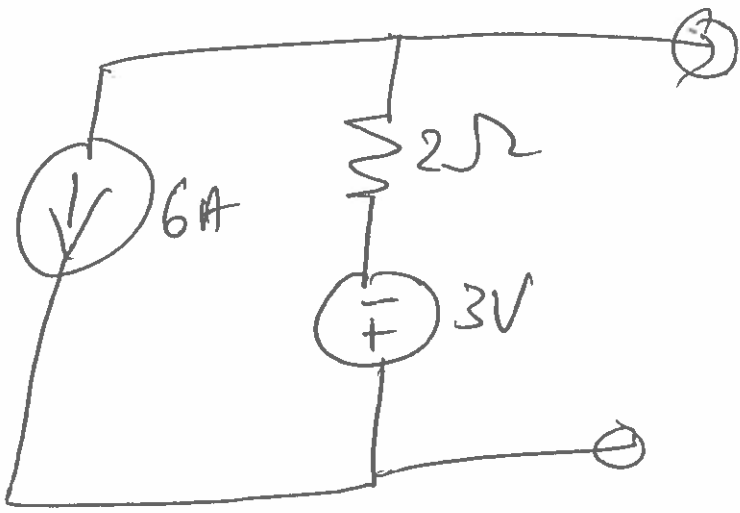

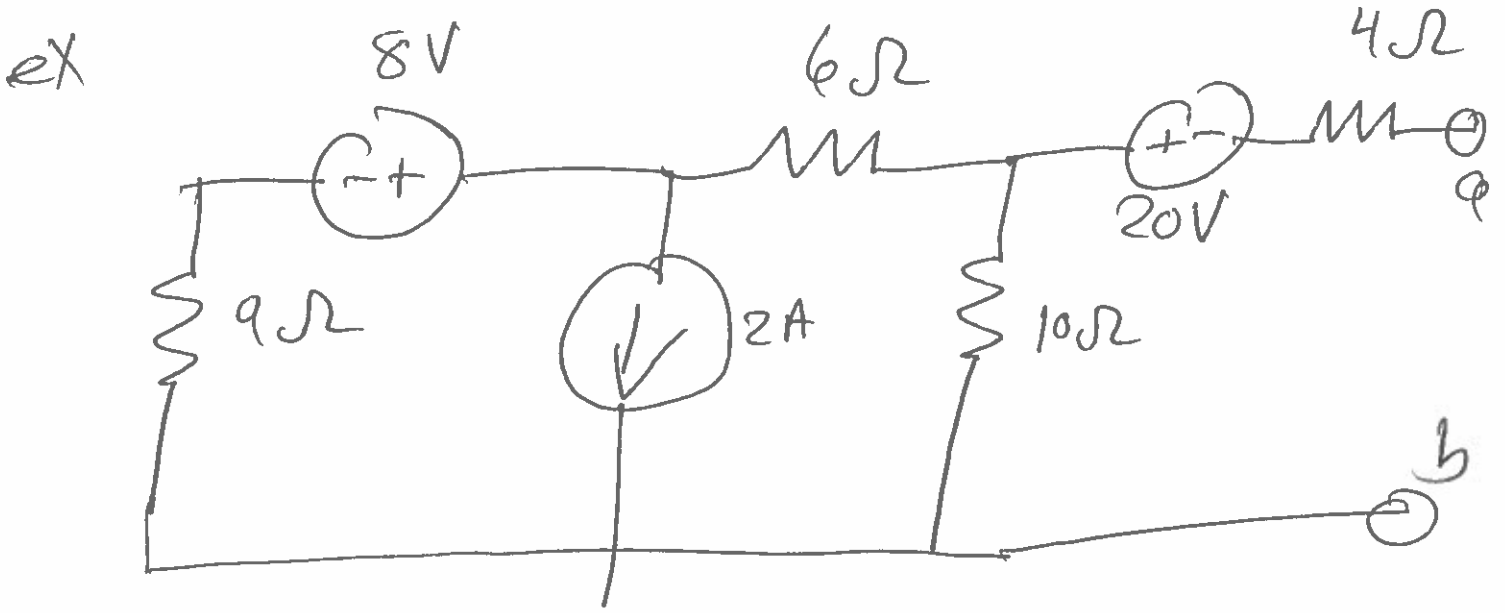



Find Norton - Equiv

DeActive Power

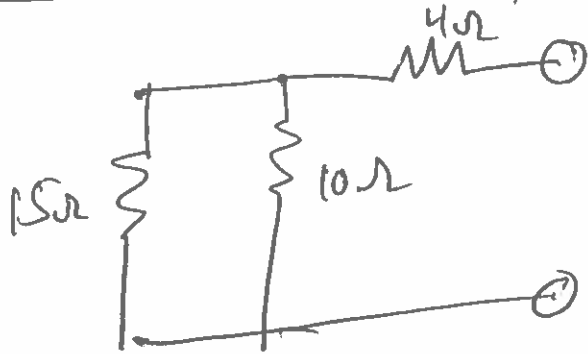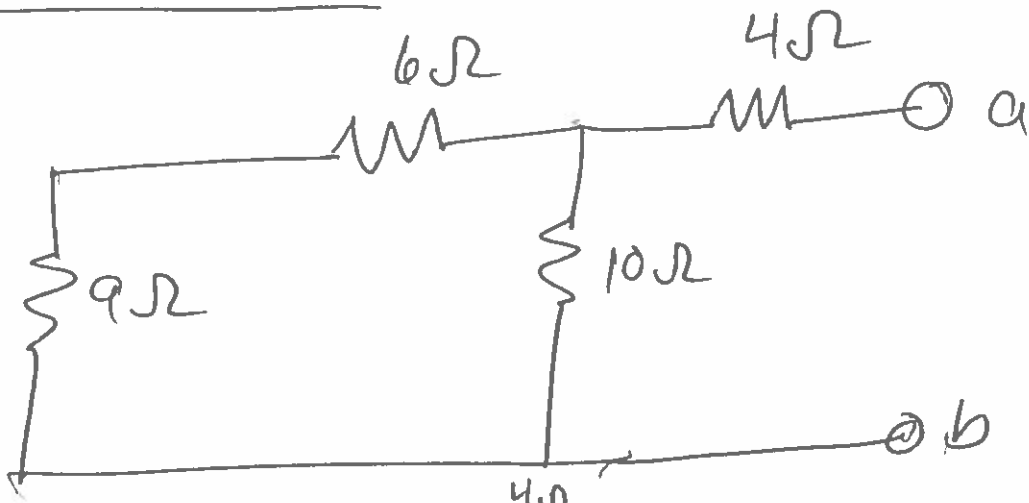
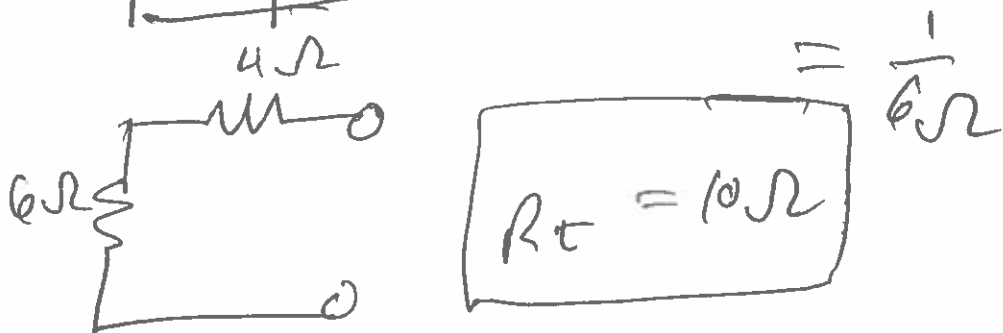
$$\frac{1}{15\Omega} + \frac{1}{10\Omega} = \frac{2+3}{30\Omega}$$



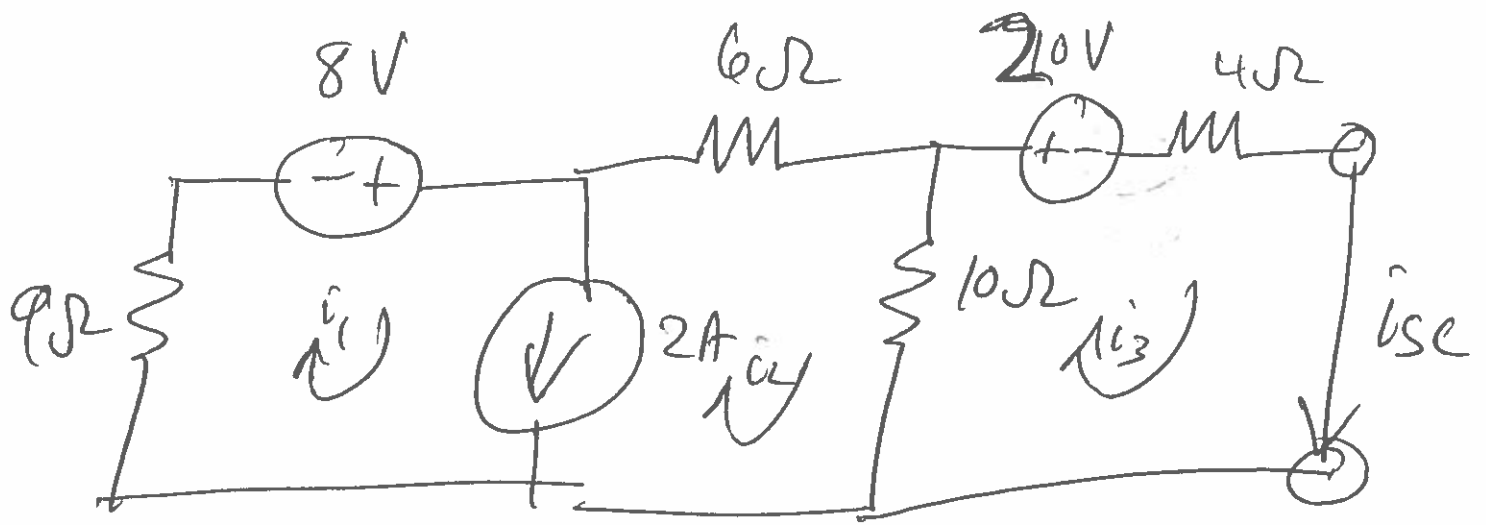

$$i_{sc} = i_3$$

Supermesh

$$i_1 - i_2 = 2A$$

$$8V = i_1(9\Omega) + i_2(6\Omega + 10\Omega) - i_3(10\Omega)$$


$$-20V = i_3(10\Omega + 4\Omega) - i_2(10\Omega)$$

MATLAB





$$i_1 = 0.64 A$$






$$i_2 = -1.36 A$$



$$i_3 = -2.4 A$$

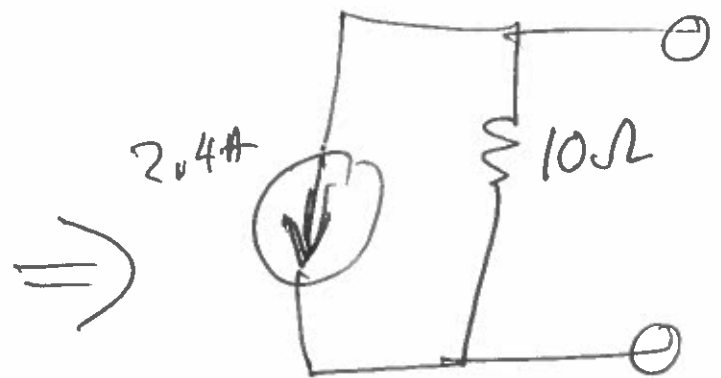


Source Transformations

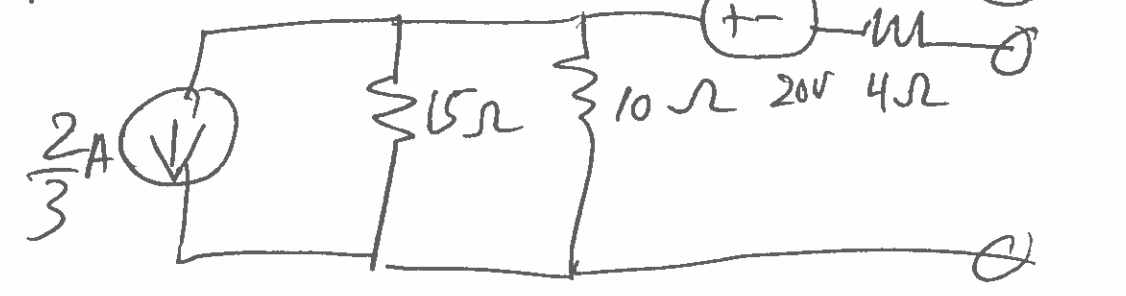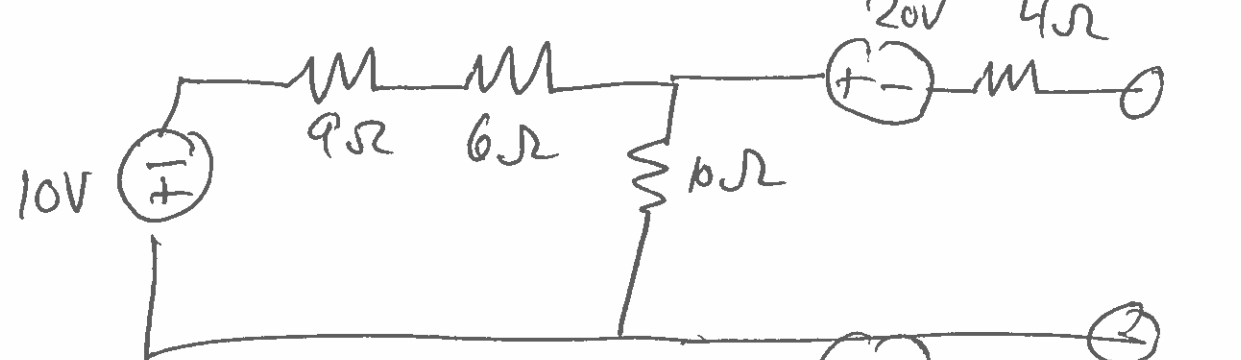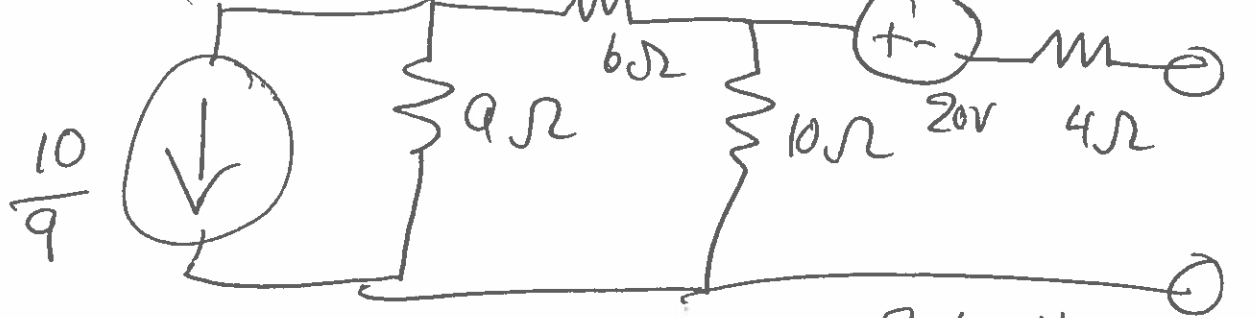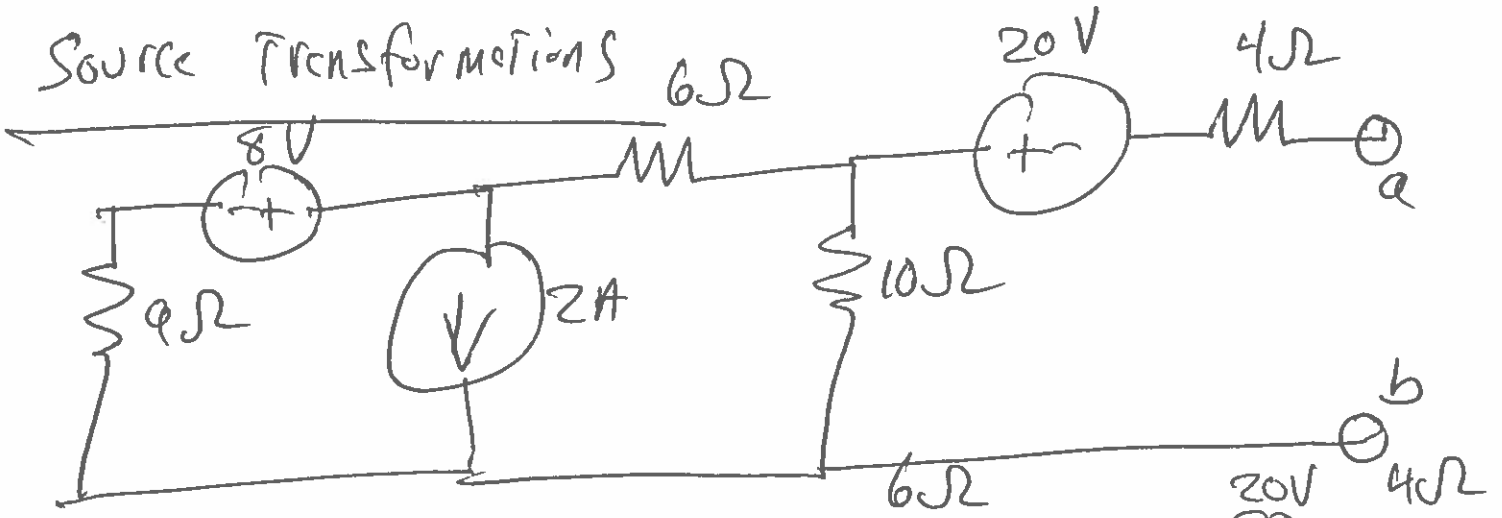

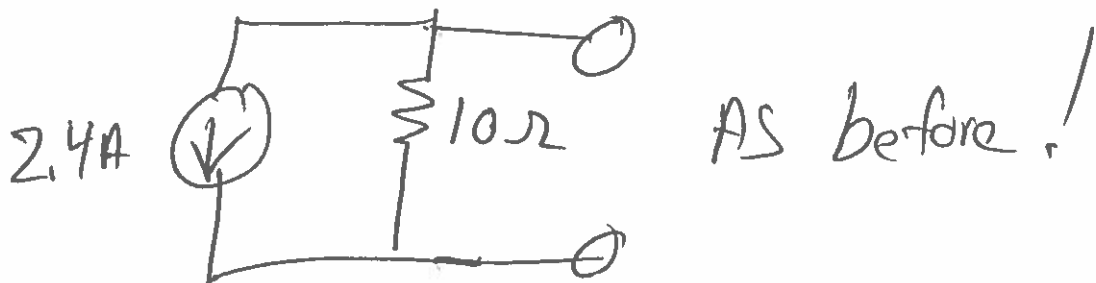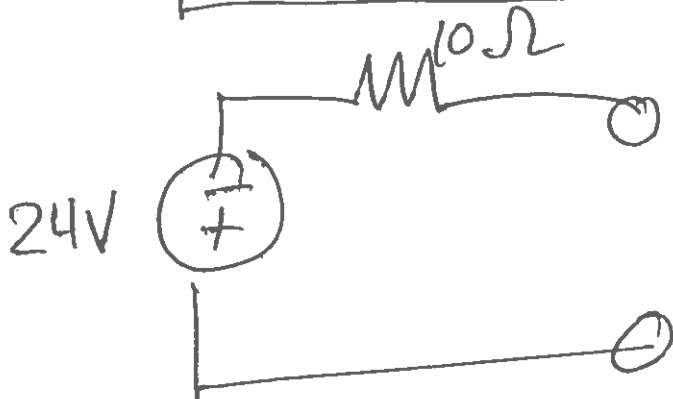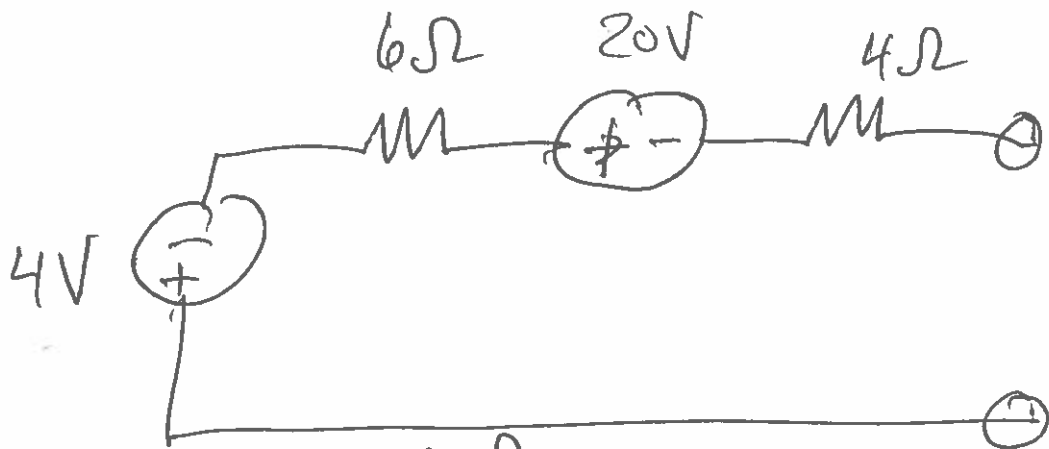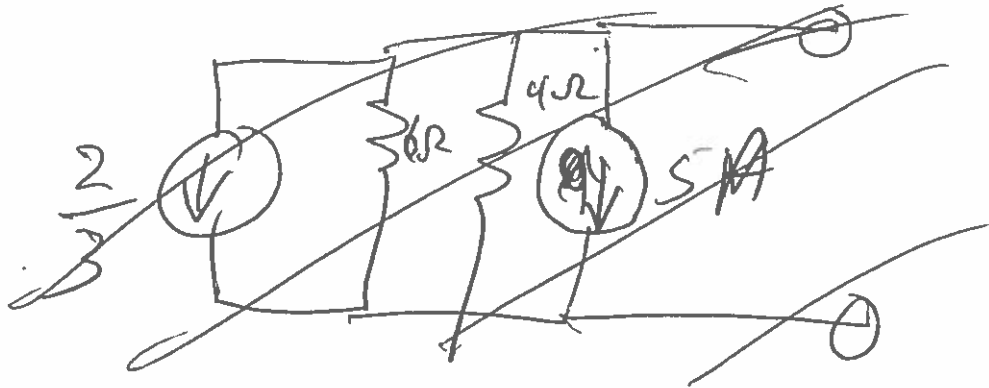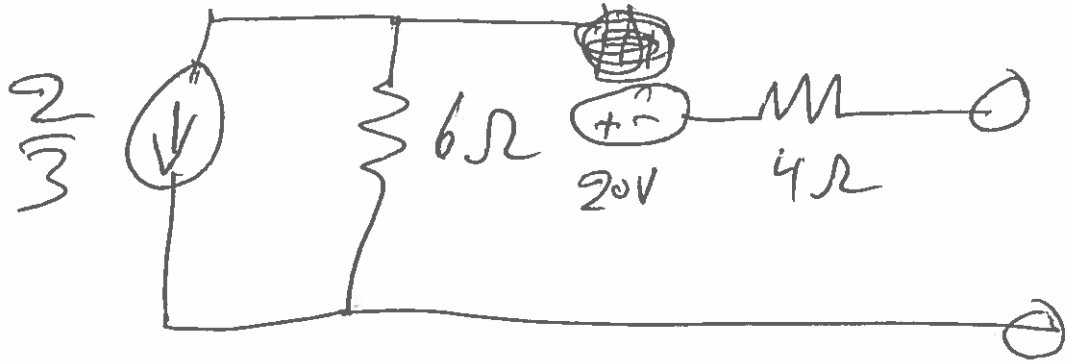

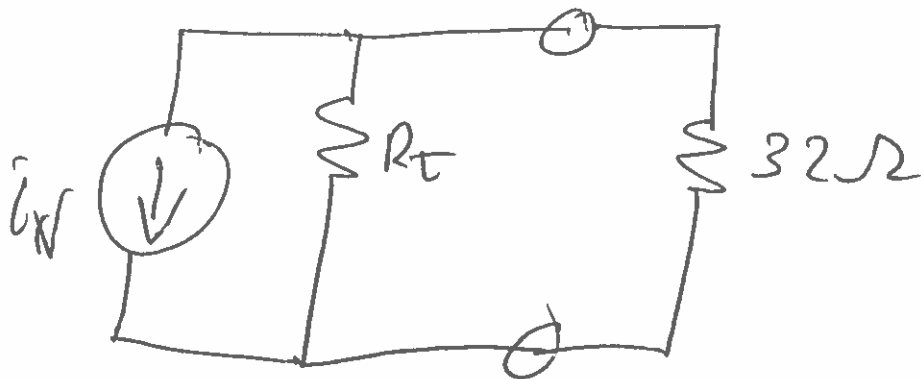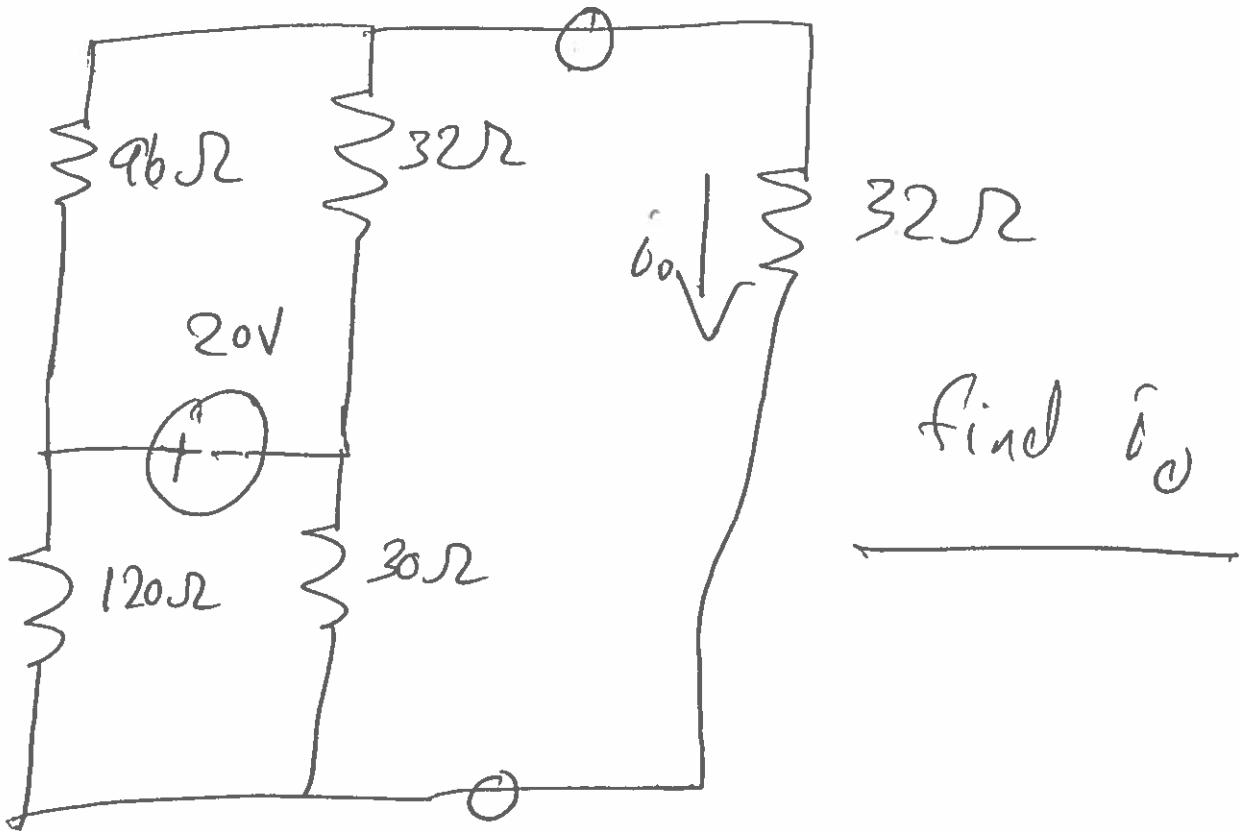

Deactive it

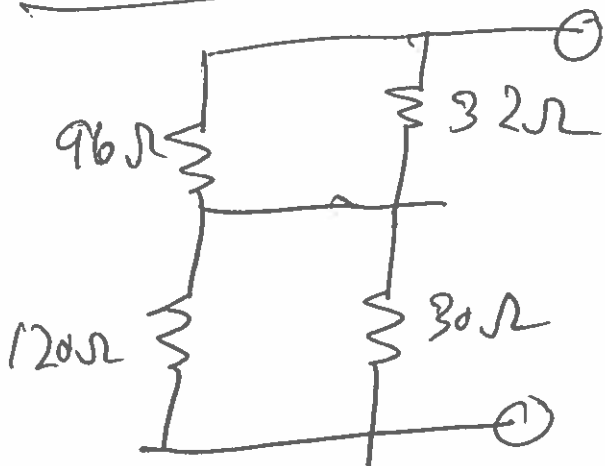


$$\frac{1}{\frac{1}{96} + \frac{3}{30}} = \frac{4}{96} = \frac{1}{24}$$

$$\Rightarrow \begin{array}{c} 24\Omega \\ 24\Omega \end{array}$$

$$\frac{1}{\frac{1}{120} + \frac{4}{30}} = \frac{5}{120} = \frac{1}{24}$$

$R_T = 48\Omega$

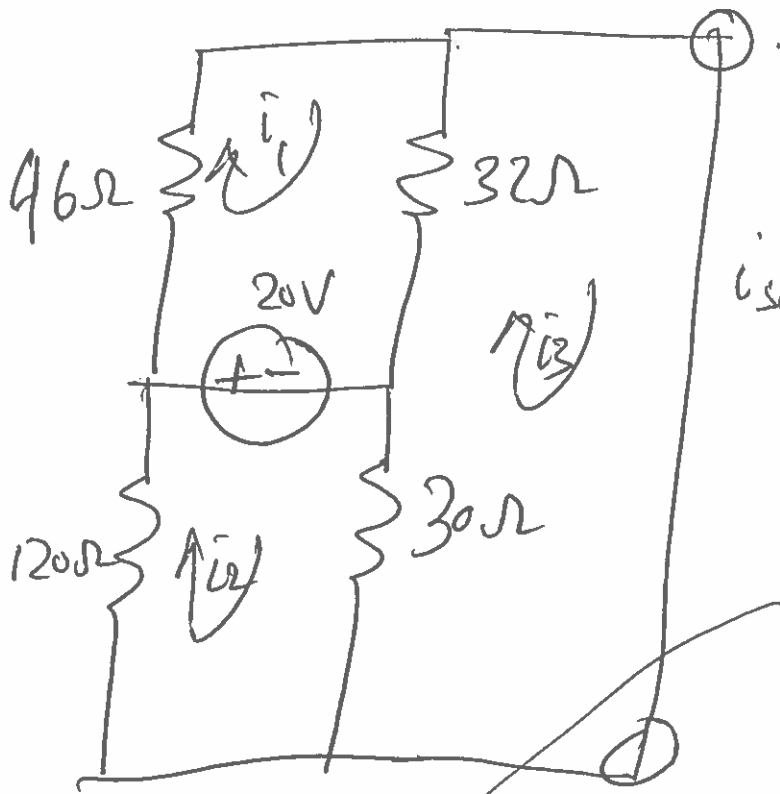

$$\text{isc } \hat{i}_N = \hat{i}_3$$

$$20V = \hat{i}_1 (96\Omega + 32\Omega) - \hat{i}_3 (32\Omega)$$

$$-20V = \hat{i}_2 (120\Omega + 30\Omega) - \hat{i}_3 (30\Omega)$$


$$0 = \hat{i}_3 (32\Omega + 30\Omega) - \hat{i}_1 (32\Omega) - \hat{i}_2 (30\Omega)$$

$$\Rightarrow \hat{i}_1 = \frac{20V + \hat{i}_3 (32\Omega)}{128\Omega}$$

$$\Rightarrow \hat{i}_2 = \frac{-20V + \hat{i}_3 (30\Omega)}{150\Omega}$$

$$0 = \hat{i}_3 (62\Omega) - (32\Omega) \left(\frac{20V + \hat{i}_3 (32\Omega)}{128\Omega} \right) - (30\Omega) \left(\frac{20V + \hat{i}_3 (30\Omega)}{150\Omega} \right)$$


$$\hat{i}_3 = 20.83 \text{ mA}$$

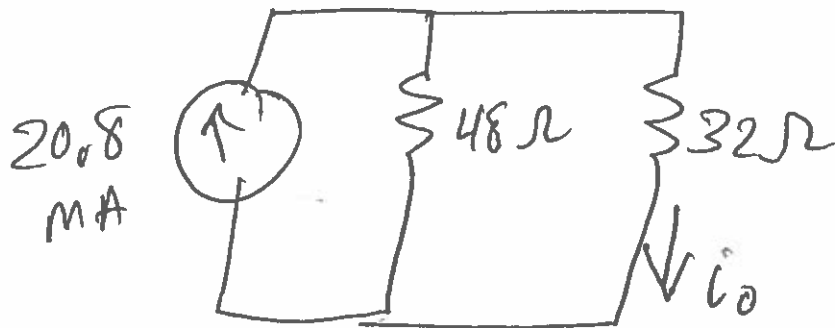

$$i_o = \frac{(20.8 \text{ mA}) \frac{1}{32\Omega}}{\frac{1}{32\Omega} + \frac{1}{48\Omega}} \Rightarrow \underline{12.5 \text{ mA}}$$

Any Complex Circuit

can be reduced to either

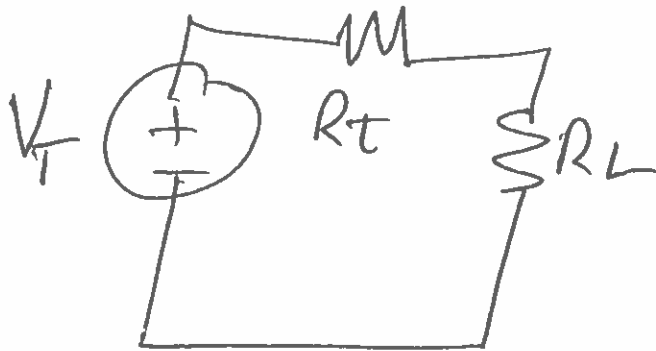

or



What value of R_L will draw maximum power from complex circuit?

$$P_L = \hat{i}_L^2 R_L$$

$$\hat{i}_L = \frac{V_E}{R_t + R_L}$$

$$P_L = \left(\frac{V_E}{R_t + R_L} \right)^2 R_L$$

$$P_L = \frac{V_E^2}{(R_t + R_L)^2} R_L$$

What R_L is Max?

$$\frac{\partial P_L}{\partial R_L} = \frac{V_E^2}{(R_t + R_L)^2} - \frac{2V_E^2 R_L}{(R_t + R_L)^3} = 0$$

$$\frac{V_E^2}{(R_t + R_L)^2} \left[1 - \frac{2R_L}{R_t + R_L} \right] = 0$$

$$1 - \frac{2R_L}{R_T + R_L} = 0$$

$$R_T + R_L - 2R_L = 0$$

$$R_T - R_L = 0$$

$$R_L = R_T$$

When Load resistance = Thevenin (Norton) Resistance

Maximum power is delivered to Load.