
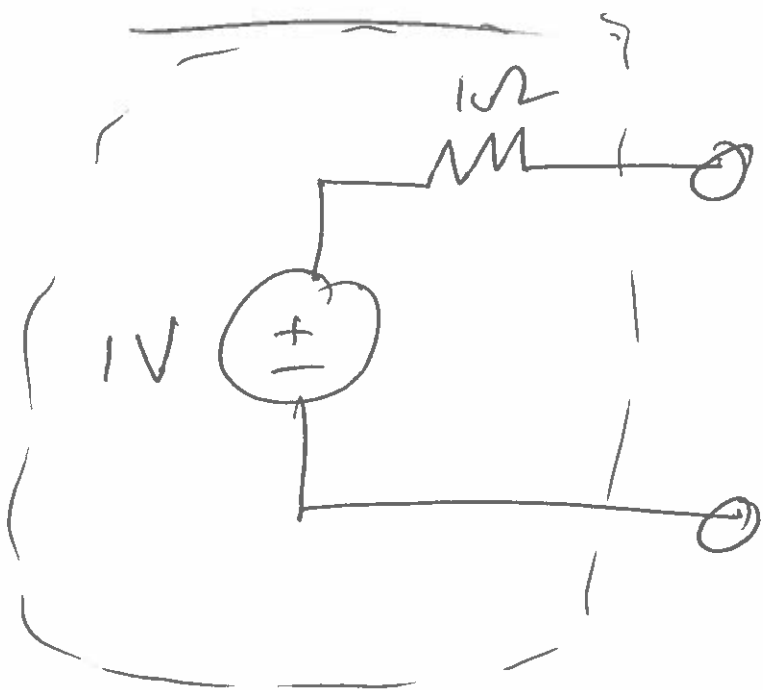



Box A

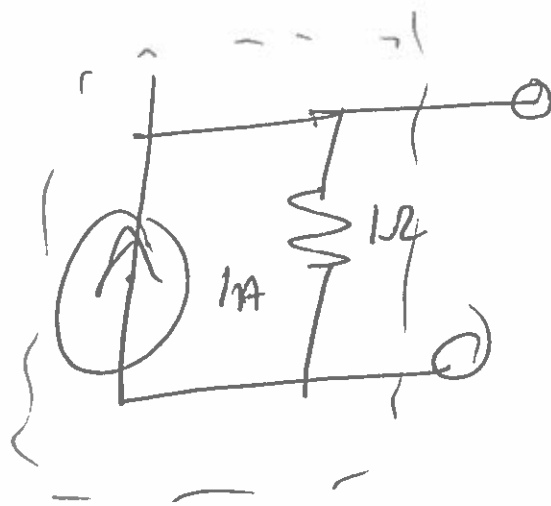


Box B



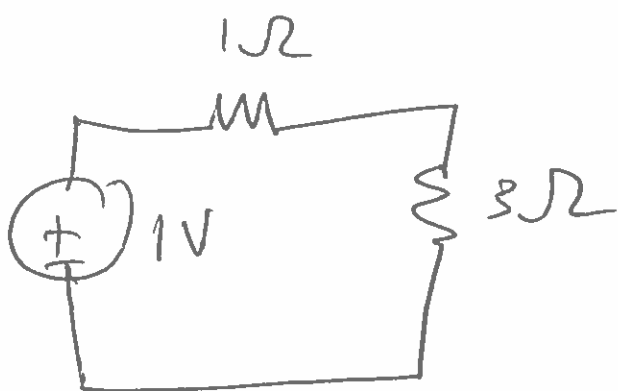How do you distinguish if you have a single wire?



$$V_{3\Omega} = 0.75V$$

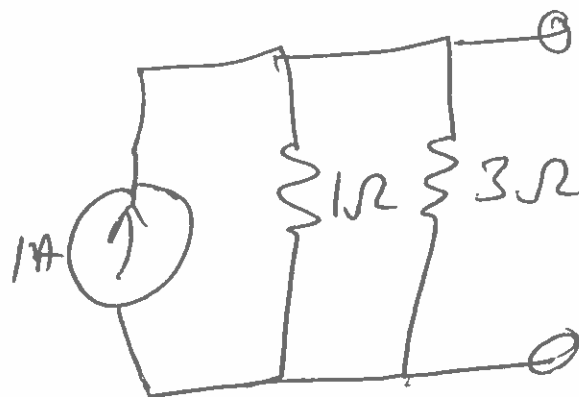


$$\begin{aligned} V_{3\Omega} &= i_{3\Omega} (3\Omega) \\ &= \left(\frac{1}{4}A\right) (3\Omega) \\ &= 0.75V \end{aligned}$$



ANSWER Short The Terminals

Box A Heats UP

Box B Cools down

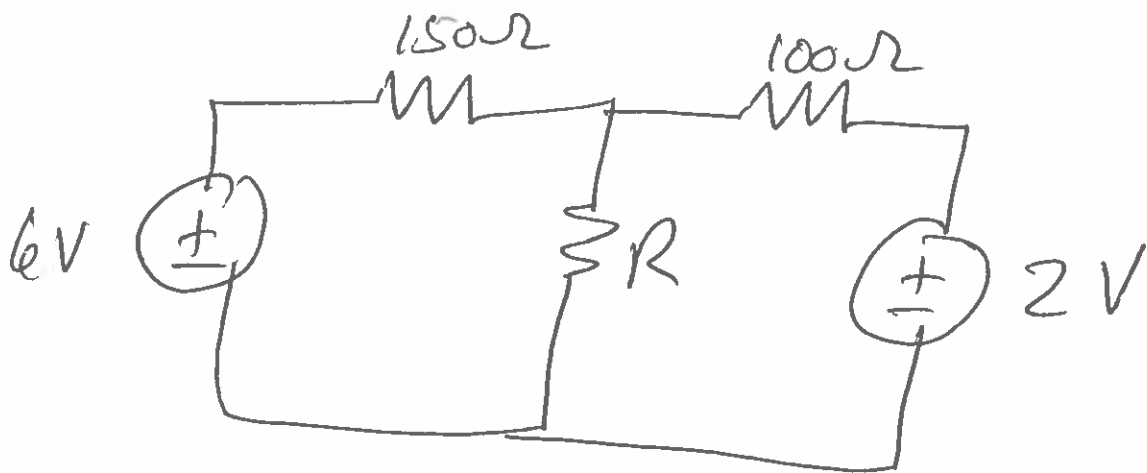

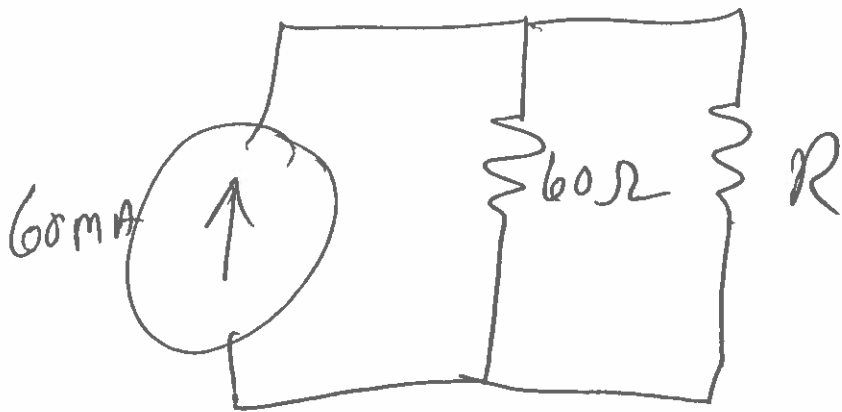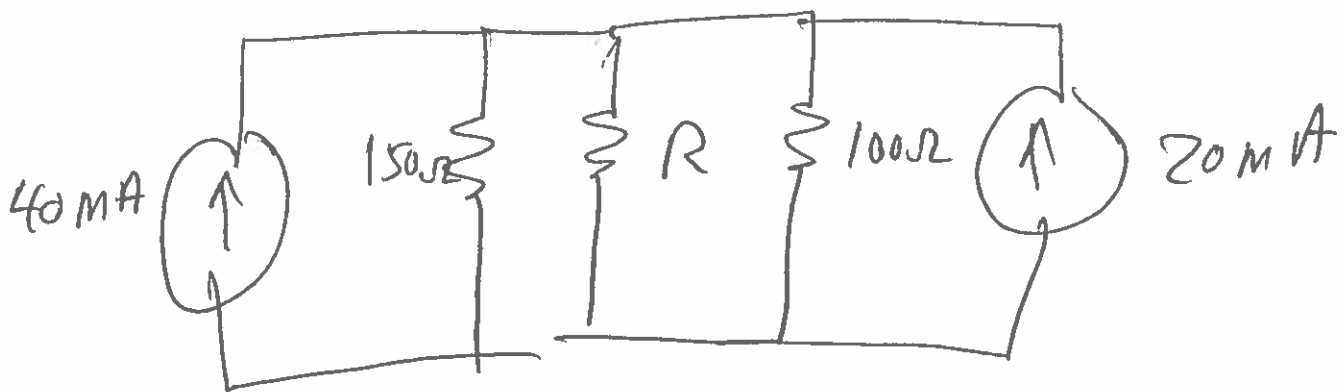What R Gives max power in R?
 What is that P_{max} ?



$$\frac{2 + 3}{300} = \frac{5}{300\Omega}$$

$$\Rightarrow R_{eff} = 60\Omega$$


$$R_{\text{Max Power}} = \boxed{60 \Omega}$$

$$P_{\text{max}} = i^2 R = (30 \text{ mA})^2 (60 \Omega)$$

$$(900 \times 10^{-6} \text{ A}) (60 \Omega)$$

$$= 54000 \cancel{\text{A}} 10^{-6} \text{ W}$$

$$= \boxed{54 \text{ mW}}$$

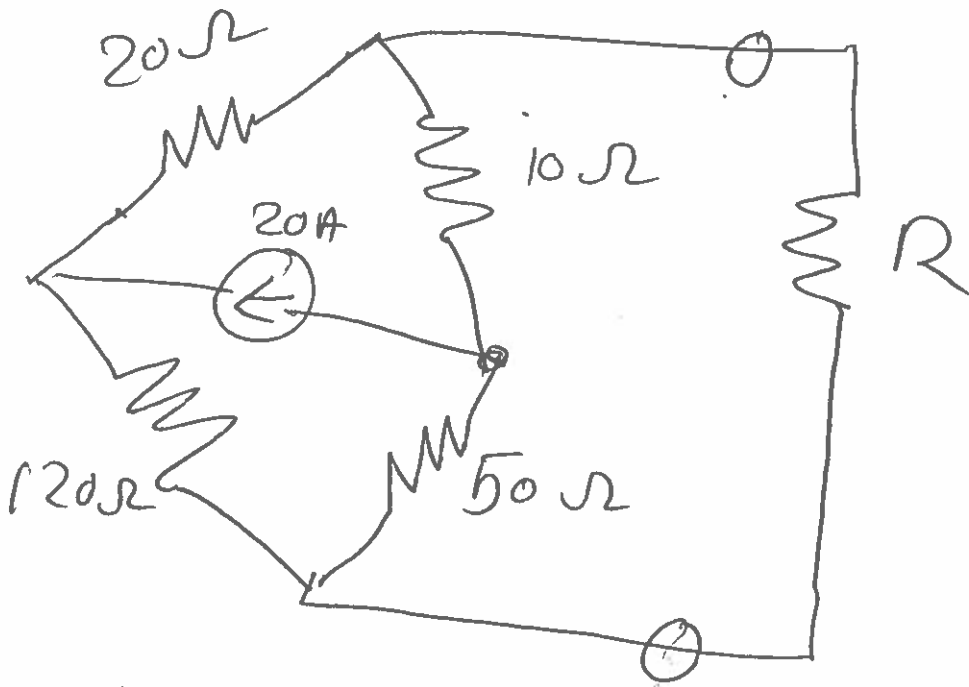



What R for max power?

What is max power?

First find Equivalent circuit

Deactive current source

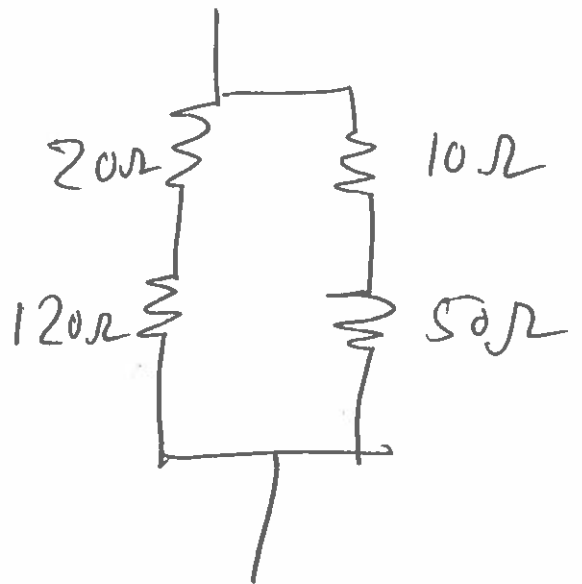

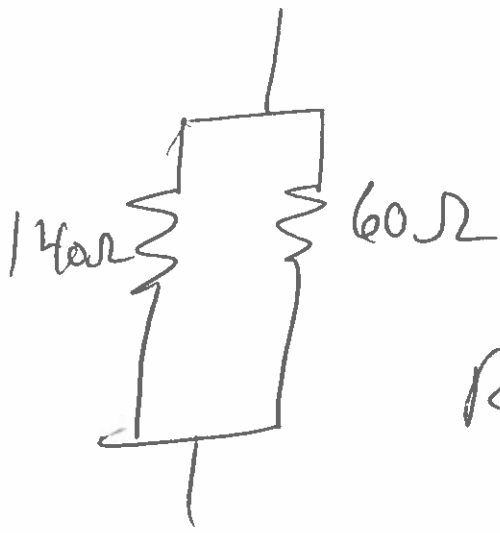


$$R_{\text{eff}} \Rightarrow \frac{1}{R_{\text{eff}}} = \frac{1}{140\Omega} + \frac{1}{60\Omega}$$

$$\text{or } R_{\text{eff}} = \frac{140\Omega(60\Omega)}{140\Omega + 60\Omega} = 42\Omega$$

$$R_{\text{load}} = 42\Omega$$

Find i_N

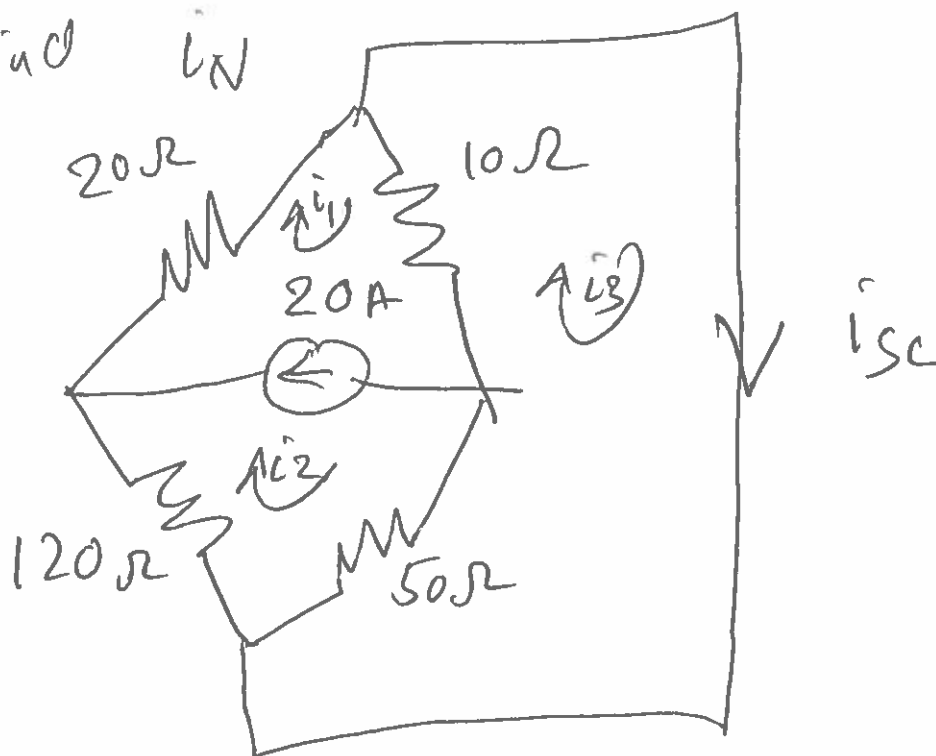

i_{sc}

$$\hat{i}_{sc} = i_3$$

$$\hat{i}_1 - \hat{i}_2 = 20 \text{ A}$$

$$0 = \hat{i}_1 (20 \Omega + 10 \Omega) + \hat{i}_2 (120 \Omega + 50 \Omega) - \hat{i}_3 (10 \Omega + 50 \Omega)$$

$$0 = \hat{i}_3 (10 \Omega + 50 \Omega) - \hat{i}_1 (10 \Omega) - \hat{i}_2 (50 \Omega)$$

Solve in MATLAB

$$\hat{i}_1 = 17.1429 \text{ A}$$

$$\hat{i}_2 = -2.8571 \text{ A}$$

$$\hat{i}_3 = 0.4762 \text{ A}$$

$$\hat{i}_5 = 0.4762 \text{ A}$$


Equivalent circuit is



$$R_{\max} = 42 \Omega$$

$$P_{\max} = \left(\frac{0.4762 \text{ A}}{2} \right)^2 (42 \Omega)$$


$$P_{\max} = 2.38 \text{ W}$$

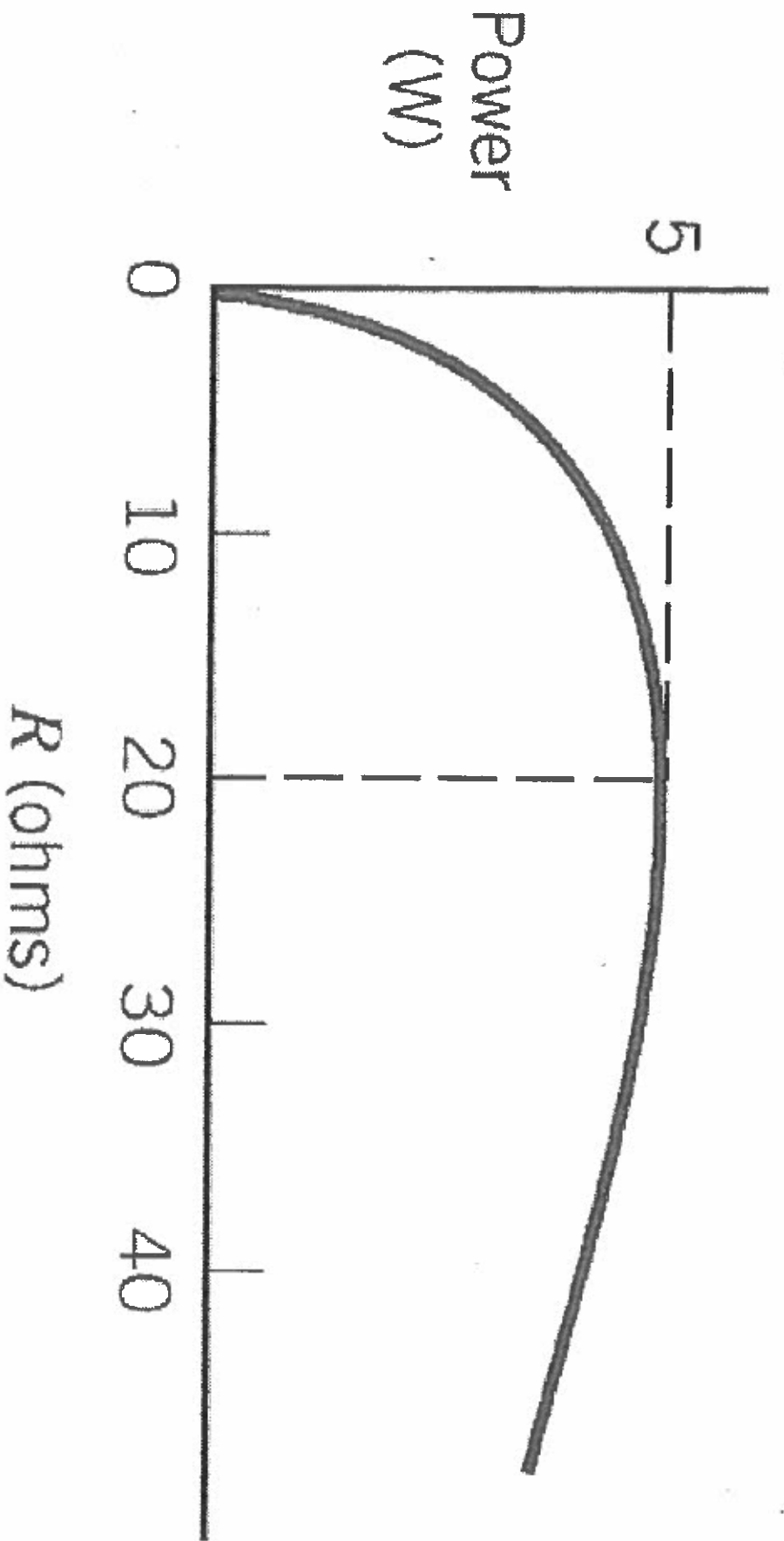

What is Thevenin Circuit?

$R_T = 20 \Omega$ That is where power is max.
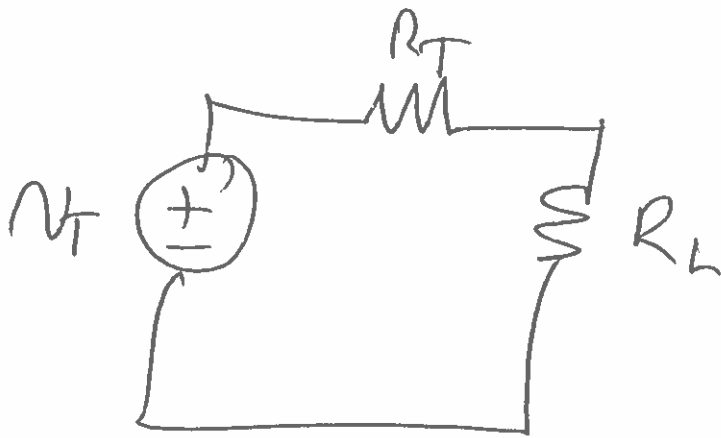
$$P_{\max} = 5W = i^2 R = \frac{V^2}{R}$$



$$i = \frac{V_T}{R_T + R_L}$$

$$i = \frac{V_T}{2R}$$

$$V_T = 20V$$
$$R_T = 20\Omega$$

$$P_{\max} = i^2 R = \left(\frac{V_T}{2R}\right)^2 R$$

$$P_{\max} = \frac{V_T^2}{4R} \quad V_T = \sqrt{P_m 4R}$$

$$V_T = \sqrt{(5W)(4)(20\Omega)} = \sqrt{400} \Rightarrow V_T = 20V$$