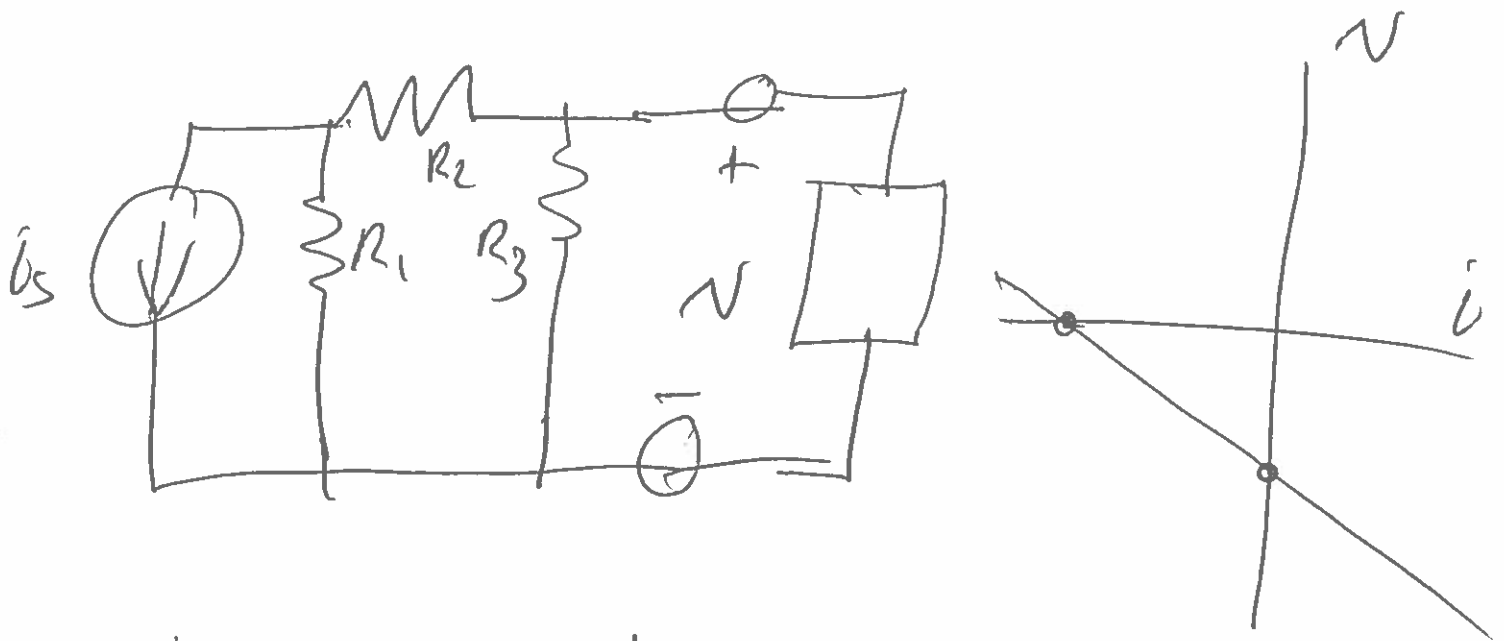


SOP-2



Choose  $R_1$ ,  $R_2$  and  $R_3$  That create Graph

HINTS: (1) Find  $V_{oc}$  and  $R_T$

(2) equation of line can be written

$$N = -R_T i + V_{oc}$$

(3) Set  $R_3 = 2 \times \text{slope}$

$$R_1 + R_2 = 2 \times \text{slope}$$

Use 2 Point form of line


$$(y - y_1) = \frac{(y_2 - y_1)}{(x_2 - x_1)} (x - x_1)$$



$$\frac{1}{R_T} = \frac{1}{R_1 + R_2} + \frac{1}{R_3} = \frac{R_3 + R_1 + R_2}{(R_1 + R_2) R_3}$$

$$R_T = \frac{(R_1 + R_2) R_3}{R_1 + R_2 + R_3} = 500 \Omega$$

Find  $V_{oc}$

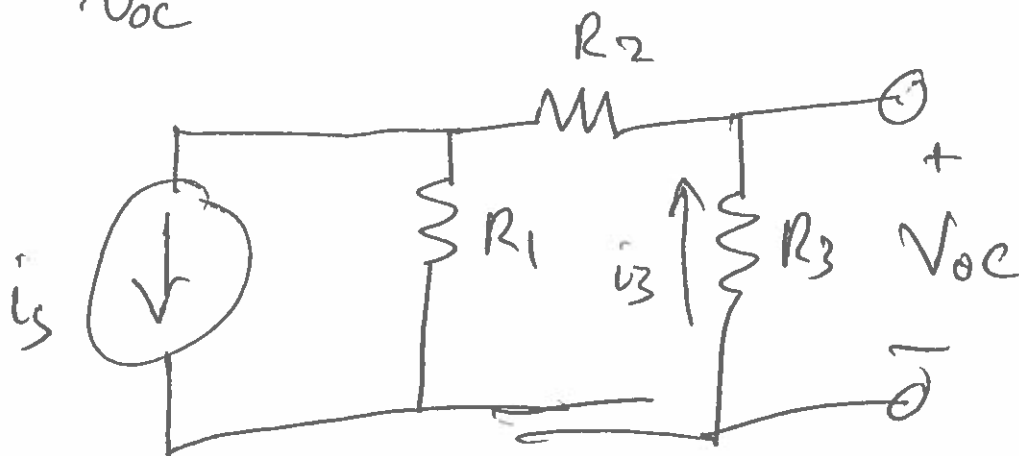

$$V_{oc} = -i_3 R_3$$

$$i_3 = i_s \left( \frac{\frac{1}{R_2 + R_3}}{\frac{1}{R_2 + R_3} + \frac{1}{R_1}} \right) = i_s \left( \frac{R_1}{R_1 + R_2 + R_3} \right)$$

$$V_{oc} = -i_s \left( \frac{R_1}{R_1 + R_2 + R_3} \right) R_3$$

$$-i_3 \frac{R_1 R_3}{R_1 + R_2 + R_3} = -3V$$

2nd 
$$\frac{(R_1 + R_2) R_3}{R_1 + R_2 + R_3} = 500 \Omega$$

3rd Hint  $\Rightarrow R_3 = 2(500 \Omega) = 1000 \Omega$

and  $R_1 + R_2 = 2(500 \Omega) = 1000 \Omega$

Choose  $R_3 = 1000 \Omega$   $R_1 = R_2 = 500 \Omega$

Check

$$R_t = \frac{(500 \Omega + 500 \Omega) (1000 \Omega)}{(500 \Omega + 500 \Omega + 1000 \Omega)} = \frac{(1000 \Omega)^2}{2000 \Omega}$$

$$= \frac{1000 \Omega}{2} = 500 \Omega \checkmark$$

$$V_{oc} = -3V$$

$$\hat{V}_{oc} = -3V = -\hat{I}_S \frac{R_1 R_3}{R_1 + R_2 + R_3}$$

$$\hat{I}_S = \frac{3V (R_1 + R_2 + R_3)}{R_1 R_3} = 3V \left( \frac{500\Omega + 500\Omega + 1000\Omega}{(500\Omega)(1000\Omega)} \right)$$

$$= 3V \frac{(2000\Omega)}{500\Omega (1000\Omega)} = \frac{2}{500\Omega} (3V) = \frac{6V}{500\Omega}$$

$$\hat{I}_S = 0.012A \Rightarrow 12 \text{ mA}$$

One solution  $\hat{I}_S = 12 \text{ mA}$

$$R_1 = 500\Omega$$

$$R_2 = 500\Omega$$


$$R_3 = 1000\Omega$$

Another  $\hat{I}_S = 12 \text{ mA}$

$$R_1 = 1000\Omega \quad R_2 = 1000\Omega \quad R_3 = 667\Omega$$

# Operational Amplifiers


Replaced Transistors in modern circuits

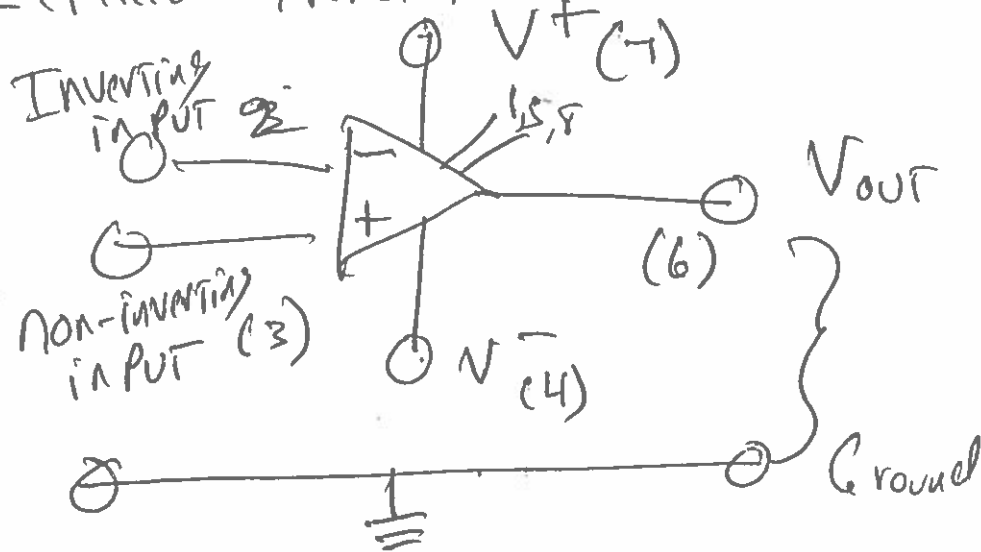

$V^+$  - Positive Power to OP-AMP


$V^-$  - Negative Power to OP-AMP

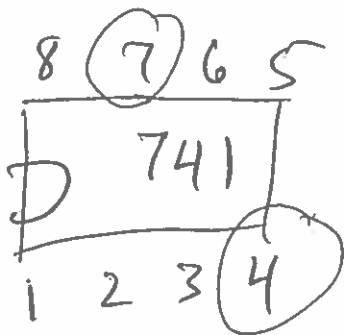Traditional  $V^+, V^-$  is symmetric  $\pm 12V$



$\pm 15V$   
 $\pm 10V$

more traditionally circuits show

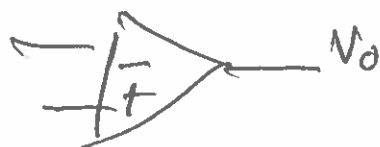


# Ideal VS Non-ideal OP-AMP Behavior

4 Rules of OP-AMPS push ideal OP-AMP Behavior

## 4 Rules

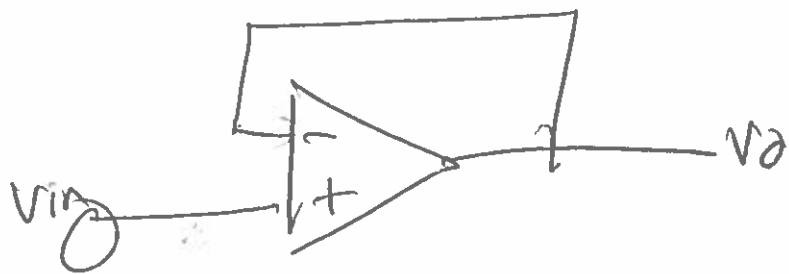- 1) Circuit of OP-AMP with closed negative feedback loop will adjust output of OP-AMP to make  $V_{-} = V_{+}$  (non-inverting) input  
inverting input
- 2)  $V_{-}$  and  $V_{+}$  draw no current  
input impedance to  $V_{-}, V_{+}$  is  $\infty$ .  
Impedance is the total opposition to flow of current in a P.C.  $Z = R$   $Z$  is impedance
3. The ~~gain~~ output impedance is zero.  
(The output does provide or absorb current)
4. The Gain or Voltage Amplification can be  $\infty$ ,



Voltage follower  
(Buffer)

