
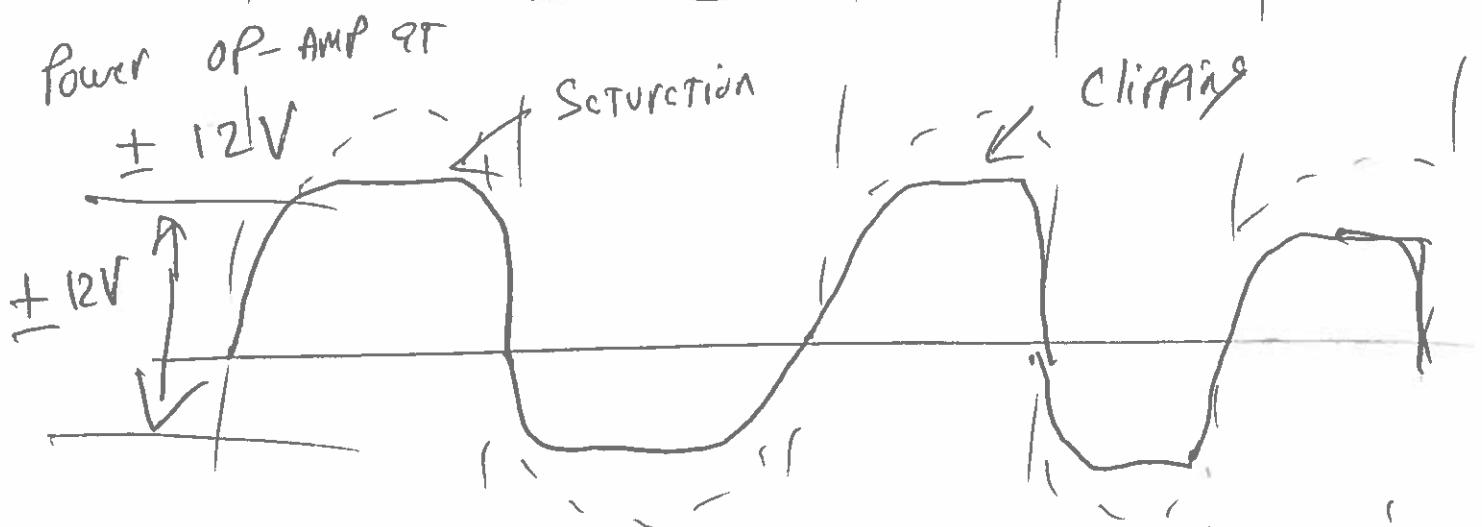
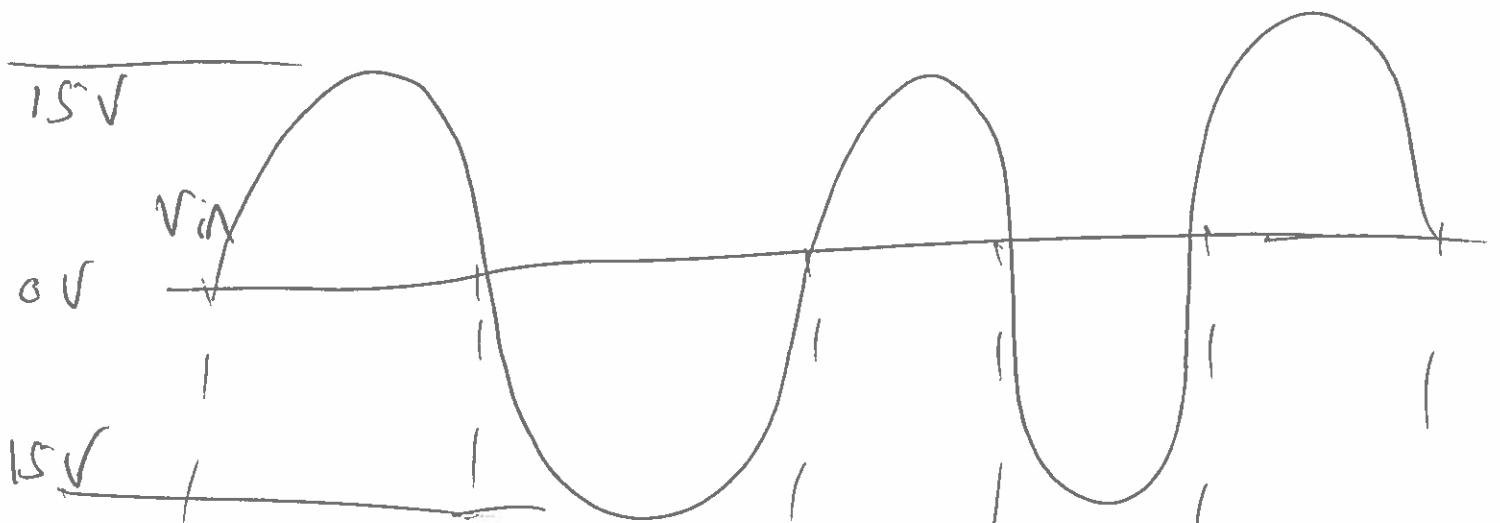


Voltage follower
(Buffer)

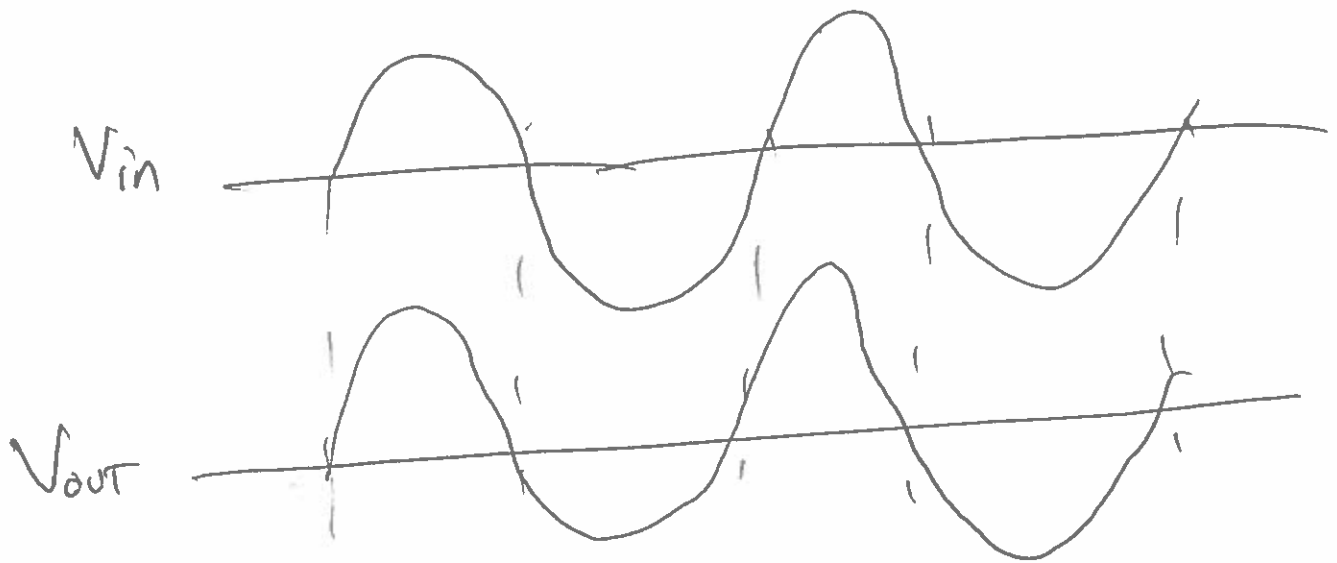

AMPLIFICATION also known Gain of circuit

$$G = \frac{V_{out}}{V_{in}}$$

For a VOLTAGE follower $G = +1$


Why use a VOLTAGE follower or Buffer

A wire gives some RESULT.

Protection! keep sensitive instruments

from getting too much CURRENT


or VOLTAGE.

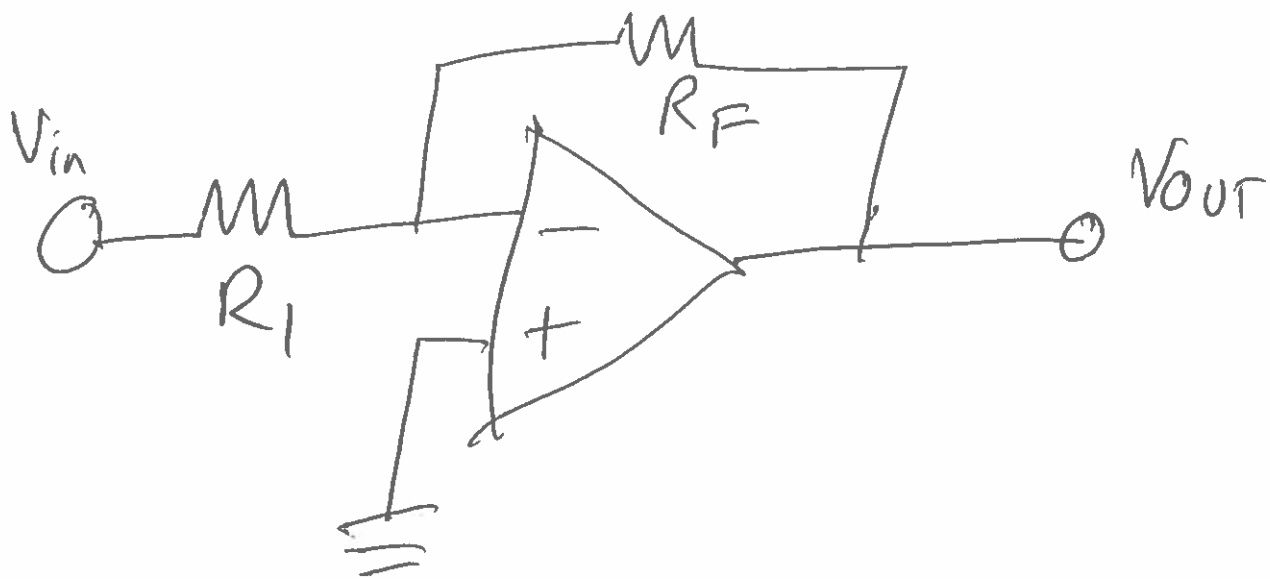

$$V_{out} = ?$$

2nd rule of OP-AMPS

INPUTS DRAW NO CURRENT

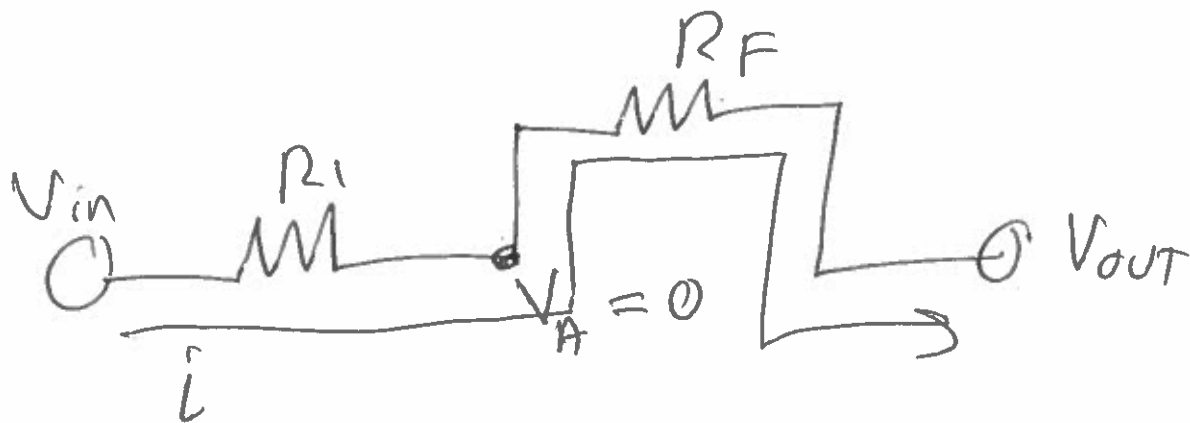

1ST rule of OP-AMPS


V_o MUST adjust to make

$$I = \frac{V_{in} - 0}{R_1} = \frac{0 - V_{out}}{R_F}$$

$$V_- = V_+$$

$$V_{out} = -\frac{R_F}{R_1} V_{in}$$


Inverting - Amplifier

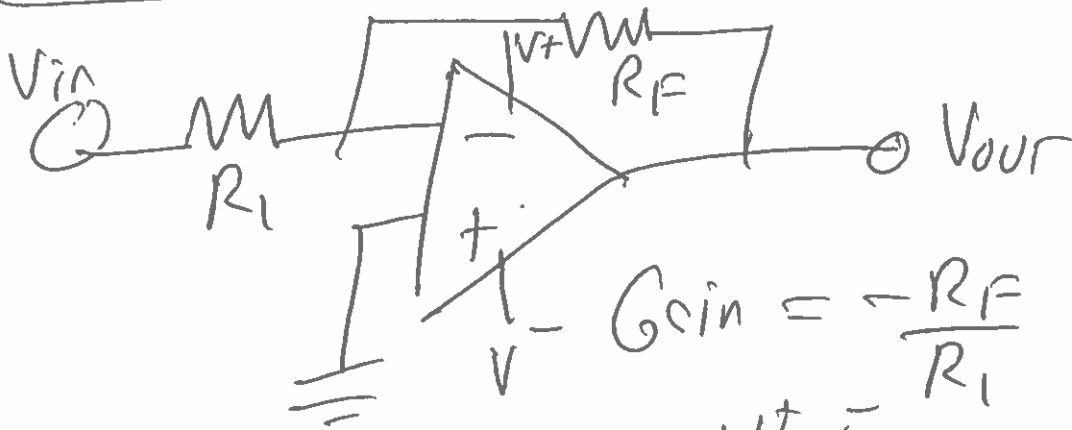


$$\text{Gain} = -\frac{R_F}{R_i}$$

V^+, V^- pins 7, 4 \Rightarrow Power of P-AMP

Let $R_F = 10 R_i$

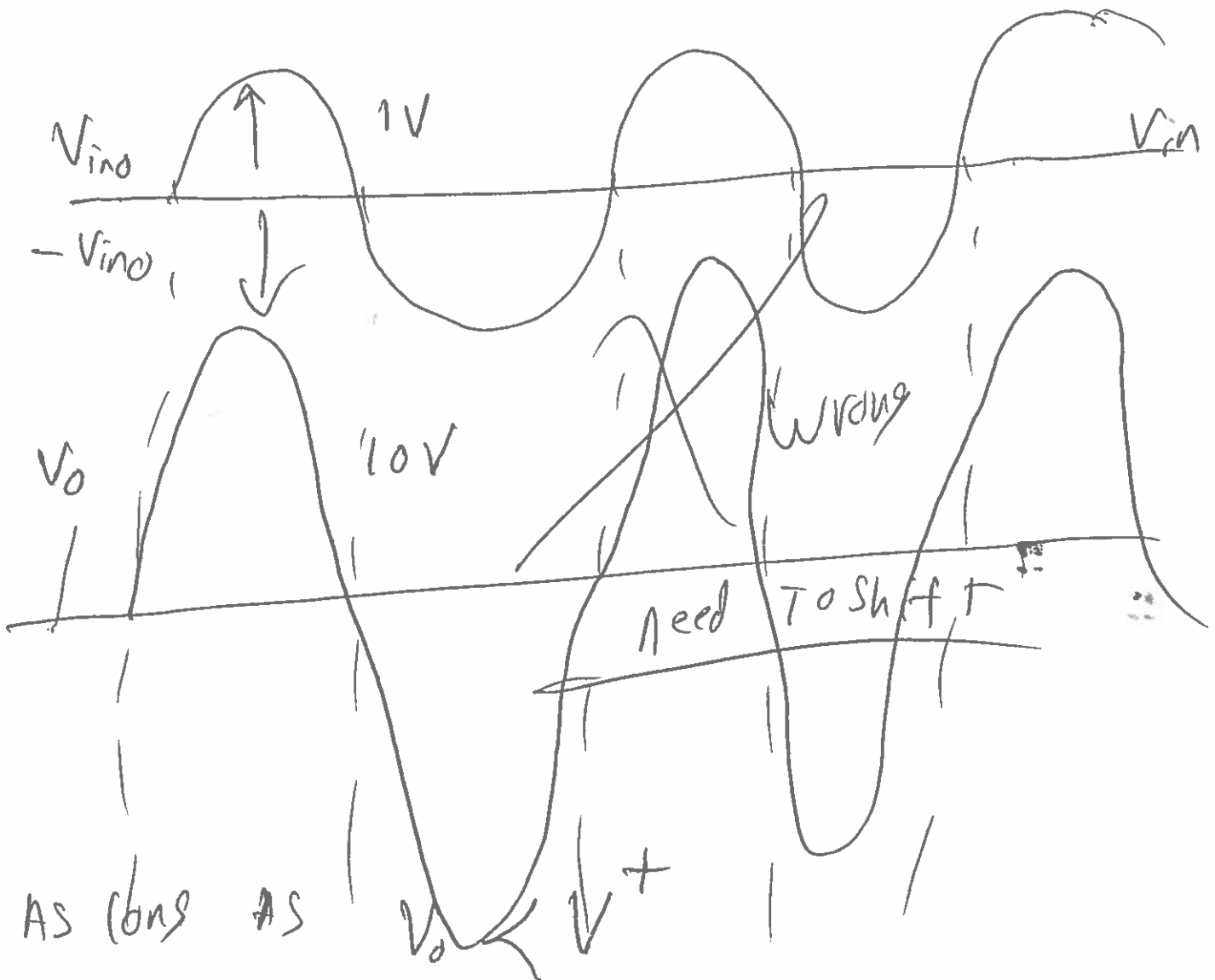

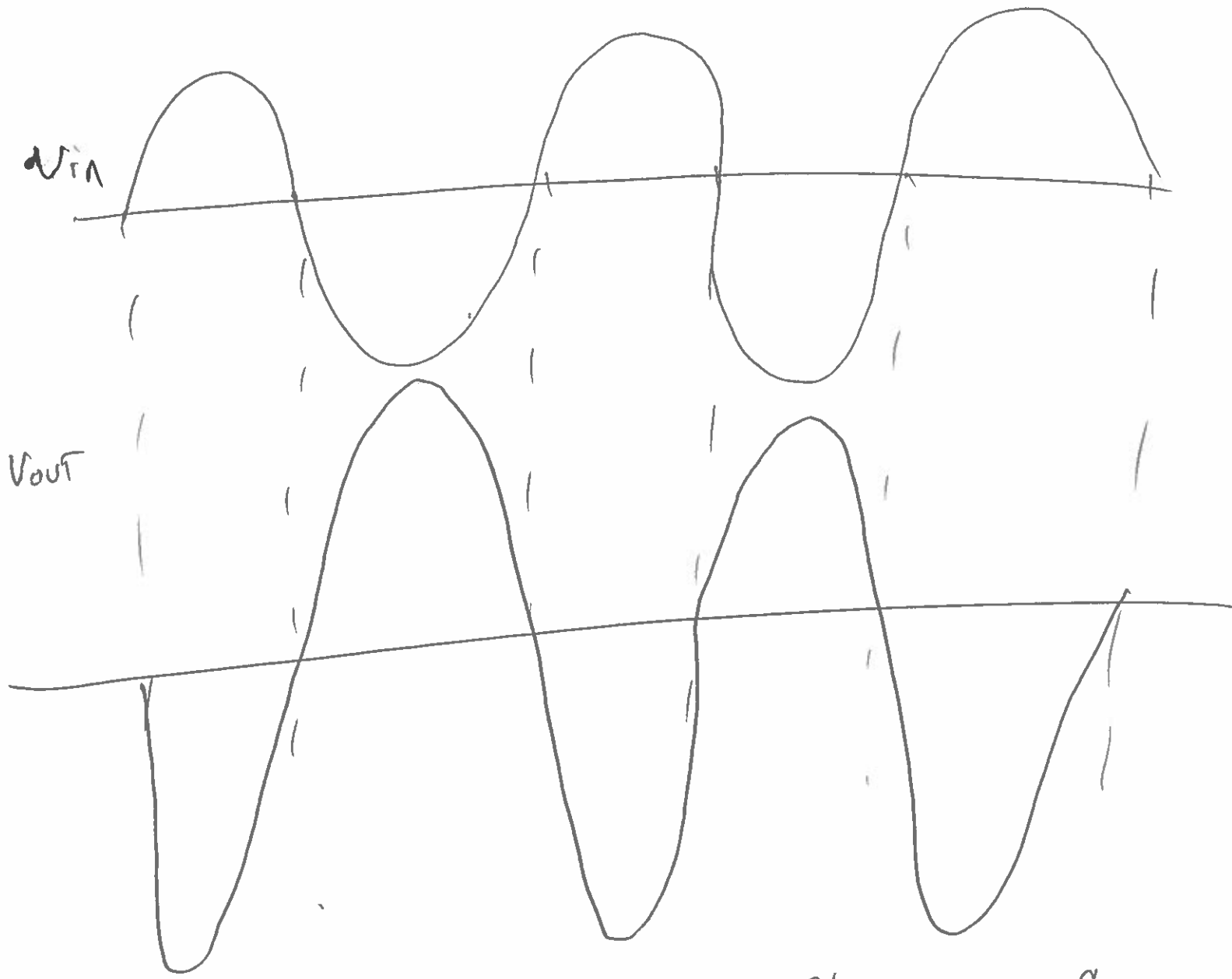

inverting amplifier Phase = 180°


Positive vs Negative Feed back

Positive feed back

$$V_o = K V_{in}$$

Negative feed back

$$V_o = K (V_{in} - V_{ref})$$

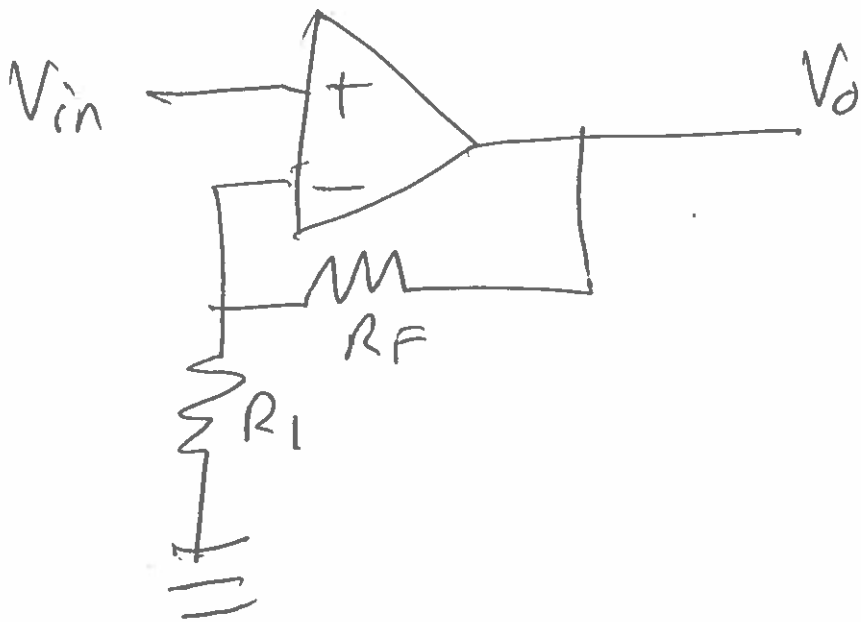

$$I = \frac{V_{in} - V_o}{R_F} = \frac{0 - V_{in}}{R_1}$$

$$V_{in} - V_{out} = + \frac{R_F}{R_1} V_{in}$$

$$V_{OUT} = V_{in} + \frac{R_F}{R_1} V_{in}$$


$$V_{OUT} = \left(1 + \frac{R_F}{R_1}\right) V_{in}$$

$$\text{Gain} = + \left(1 + \frac{R_F}{R_1}\right)$$

Non-Inverting Amplifier

Minimum Gain = 1 if $R_F = 0$ (Short circuit)


Remember

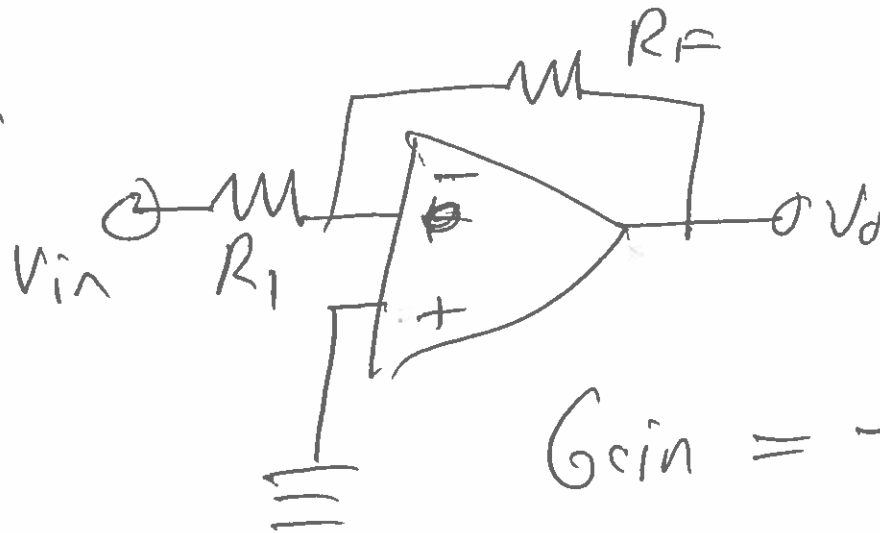

$$\text{Gain} = - \frac{R_F}{R_1}$$

if $R_1 > R_F$ Gain smaller

Alternative Non-inverting Amplifier

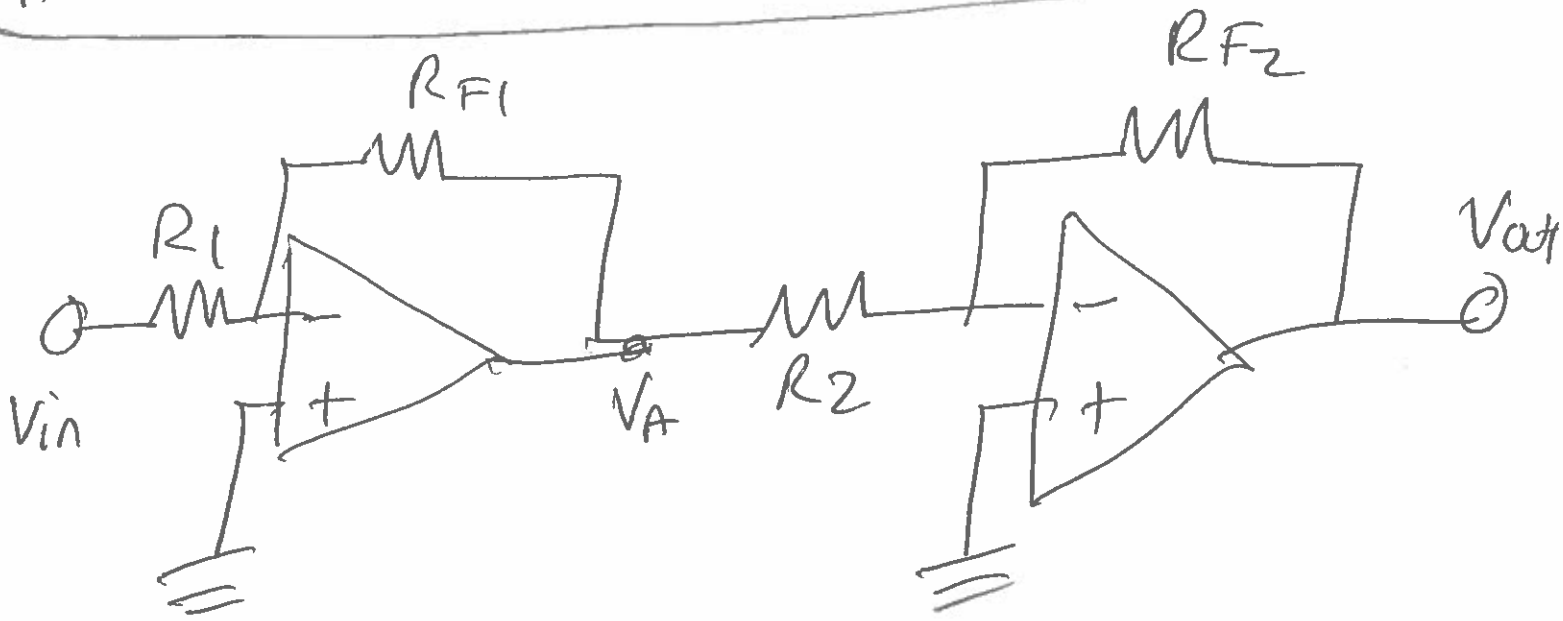

$$V_{\cancel{out}}^A = -\frac{R_{F1}}{R_1} (V_{in})$$

$$V_{out} = -\frac{R_{F2}}{R_2} V_A$$

$$V_{out} = \left(\frac{R_{F2} R_{F1}}{R_2 R_1} \right) V_{in}$$

Use $R_{F2} = R_2$