
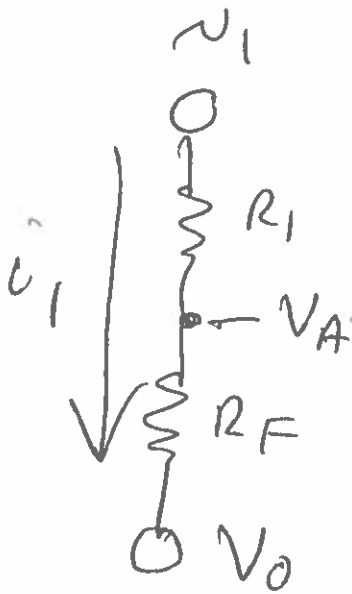


$$V_o = ?$$

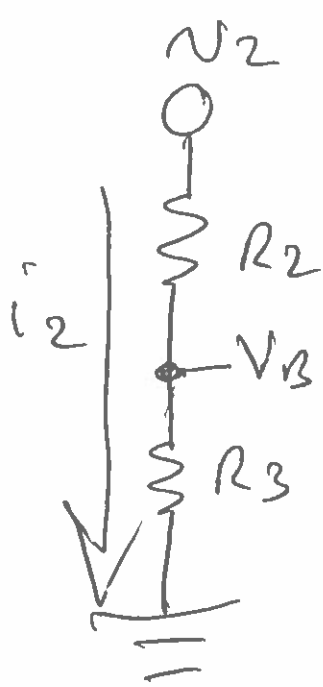

$$V_A = V_B$$

$$i_1 = \frac{V_1 - V_A}{R_1} = \frac{V_A - V_o}{R_F}$$

$$i_2 = \frac{V_2 - V_B}{R_2} = \frac{V_B - 0}{R_3}$$

$$V_B = \frac{R_3}{R_2} V_2 - \frac{R_3}{R_2} V_B$$

$$V_B \left(1 + \frac{R_3}{R_2}\right) = \frac{R_3}{R_2} V_2$$

$$V_B \left(\frac{R_2 + R_3}{R_2}\right) = \frac{R_3}{R_2} V_2$$

$$V_B = \left(\frac{R_3}{R_2 + R_3}\right) V_2$$

$$V_A - V_0 = \frac{R_F}{R_1} V_1 - \frac{R_F}{R_1} V_A$$

$$V_A + \frac{R_F}{R_1} V_A = V_0 + \frac{R_F}{R_1} V_1$$

$$V_A \left(\frac{R_1 + R_F}{R_1}\right) = V_0 + \frac{R_F}{R_1} V_1$$


$$V_A = \left(\frac{R_1}{R_1 + R_F}\right) \left(V_0 + \frac{R_F}{R_1} V_1\right)$$

Use $V_A = V_B$

$$\left(\frac{R_1}{R_1 + R_F}\right) \left(V_0 + \frac{R_F}{R_1} V_1\right) = \left(\frac{R_3}{R_2 + R_3}\right) V_2$$


$$V_0 = \left(\frac{R_1 + R_F}{R_1}\right) \left(\frac{R_3}{R_2 + R_3}\right) V_2 - \frac{R_F}{R_1} V_1$$
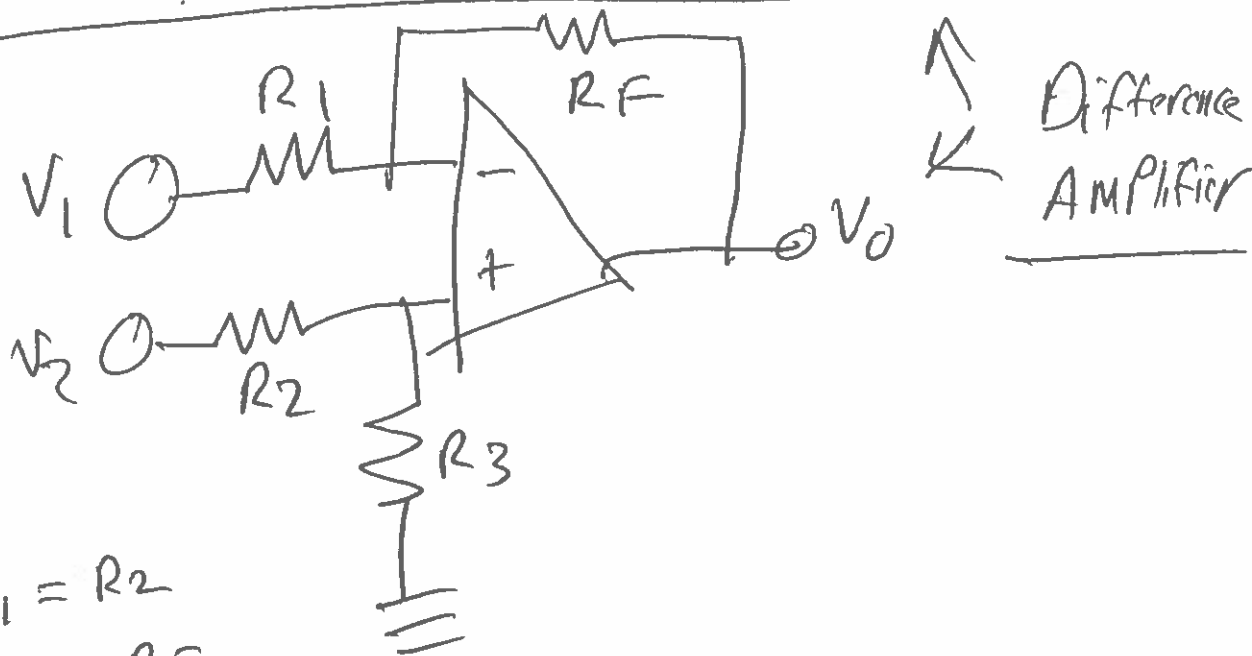
$$V_0 = \frac{R_3}{R_1} \left(\frac{R_1 + R_F}{R_2 + R_3}\right) V_2 - \frac{R_F}{R_1} V_1$$



if $R_1 = R_2$
and $R_3 = R_F$
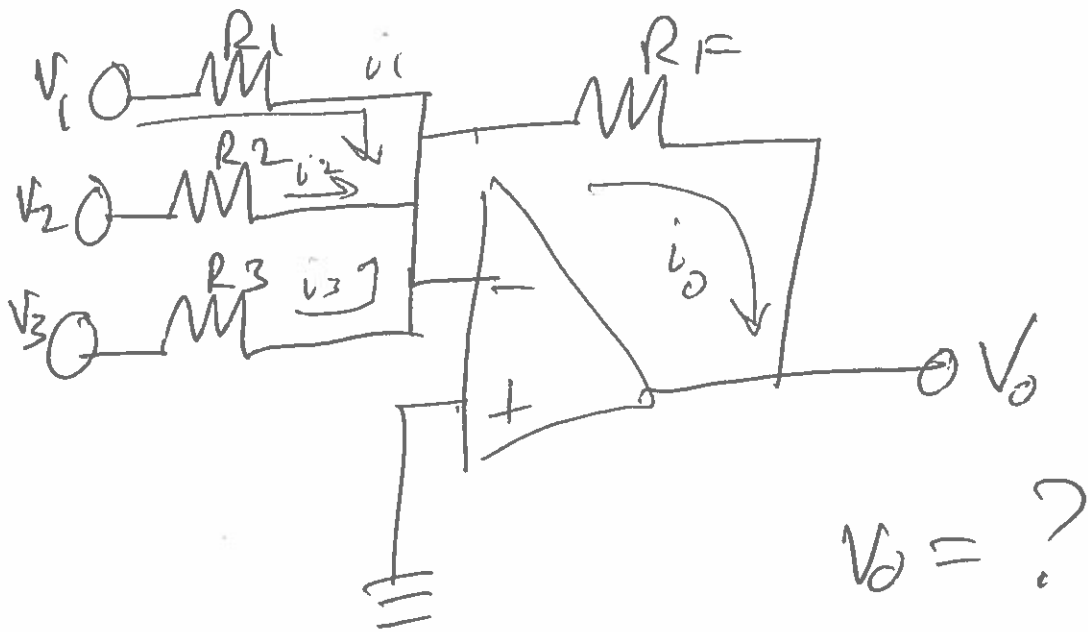
$$V_0 \rightarrow \frac{R_F}{R_1} (V_2 - V_1)$$



$$\bar{i}_1 = \frac{V_1}{R_1} \quad \bar{i}_2 = \frac{V_2}{R_2} \quad \bar{i}_3 = \frac{V_3}{R_3}$$

$$\bar{i}_0 = \bar{i}_1 + \bar{i}_2 + \bar{i}_3 = \frac{0 - V_0}{R_F}$$

$$\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} = -\frac{V_0}{R_F}$$

$$V_0 = -R_F \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right)$$

Summing Amplifier

$$z = -5x + 2y + 4w$$

$$z = -5x + 2y + 4w$$

$$z = -5x - (-2y - 4w) \quad \text{— save later}$$


$$\rightarrow \underline{z = 2y + 4w - 5x} \quad \text{— close to a summing AMP}$$

$$z = - \left(-2 \left(y + 2w - \frac{5}{2}x \right) \right)$$

$$= - \left(-R_F \left(\frac{V_y}{R_1} + \frac{V_w}{R_2} - \frac{V_x}{R_3} \right) \right)$$

$$R_1 = 1 \quad R_2 \sim \frac{1}{2} \quad R_3 \sim \frac{2}{5}$$



$$R_F \sim 2$$

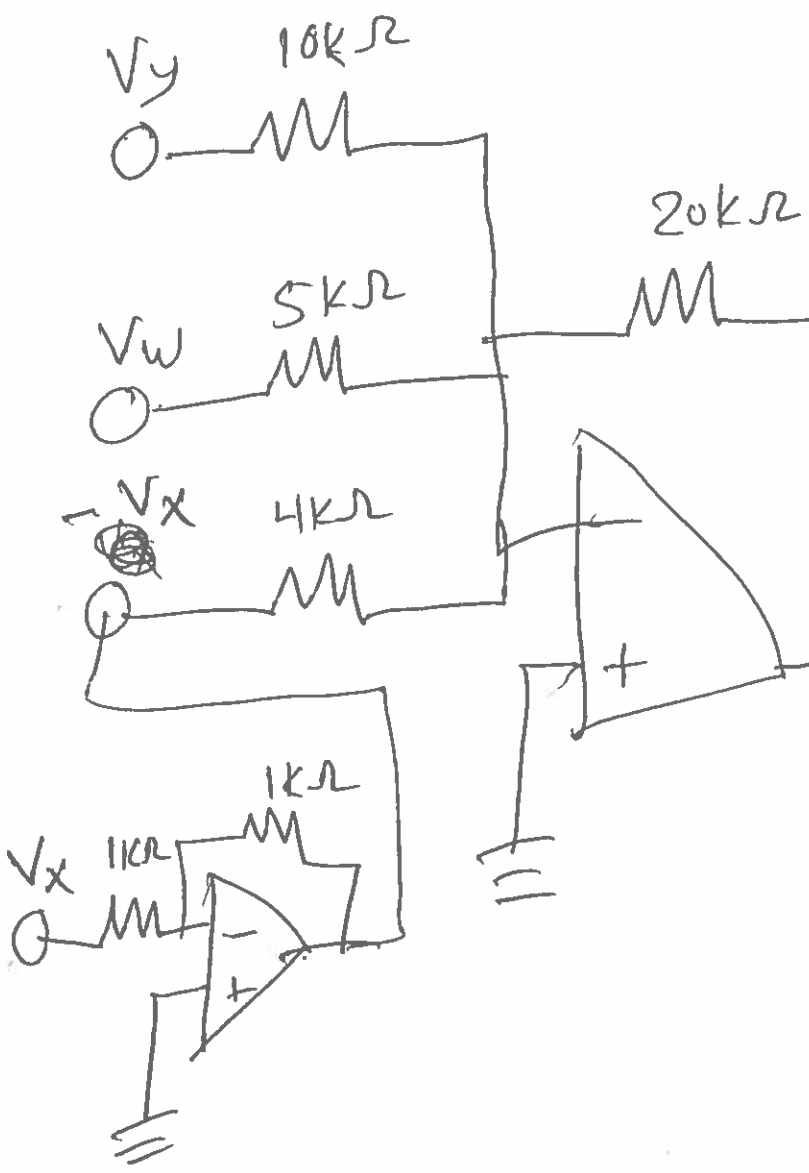


$$- 20k\Omega \left(\frac{V_y}{10k\Omega} + \frac{V_w}{5k\Omega} + \frac{-V_x}{4k\Omega} \right)$$

$$= -2V_y - 4V_w + 5V_x$$

$$V_2 = 2V_y + 4V_w - 5V_x$$

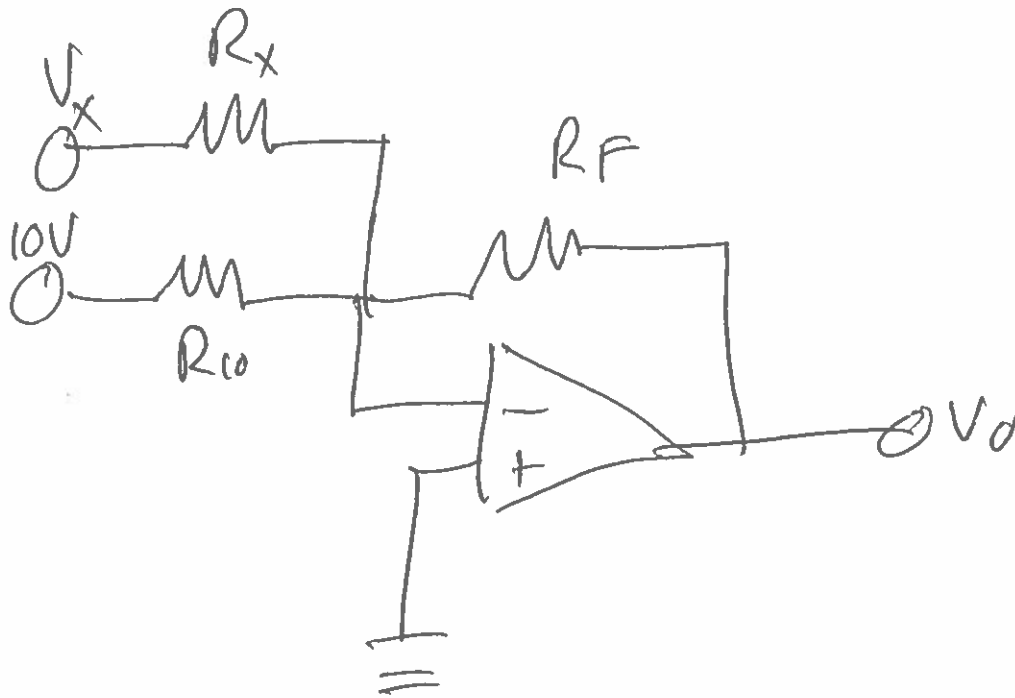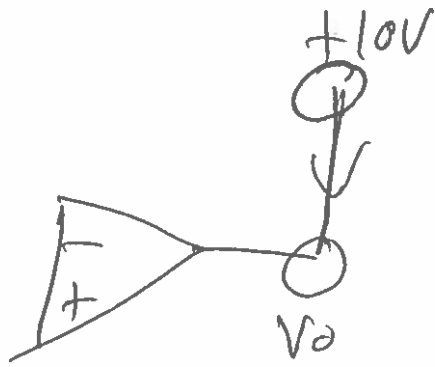
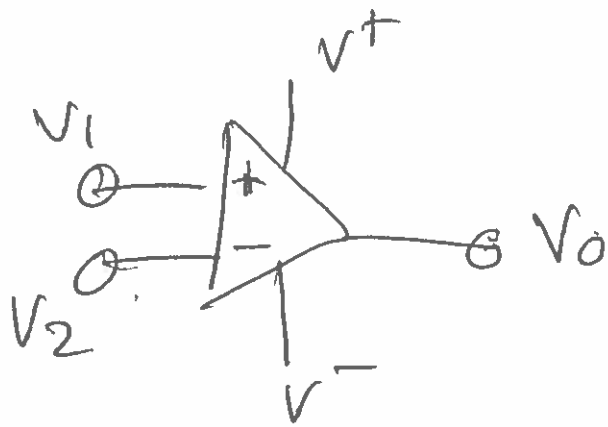
$$V_o = -R_F \left(\frac{V_x}{R_x} + \frac{10V}{R_{10}} \right)$$



$$V_o = ?$$

$$\text{if } V_1 > V_2$$

$$10V > 8V$$

$$\text{if } V_1 < V_2$$

$$8V < 10V$$

$$V_o = +12V \quad \text{at } V^+$$

$$V_o = -12V \quad \text{at } V^-$$