

Advantages of Instrumentation AMP

$$1) G_D = 1 + \frac{R_1}{R_2}$$

$$G_{cm} = 1 \quad \text{if } \frac{R_1}{R_2} \gg 1$$

$$G_D \gg G_{cm}$$

\Rightarrow CMRR will be Good

CMRR is independent of internal resistances which normal difference amplifier is not.

Using modified voltage follower before


difference AMP in the instrumentation

AMP creates large impedances for

input voltages keeping ideal OP

AMP behavior.

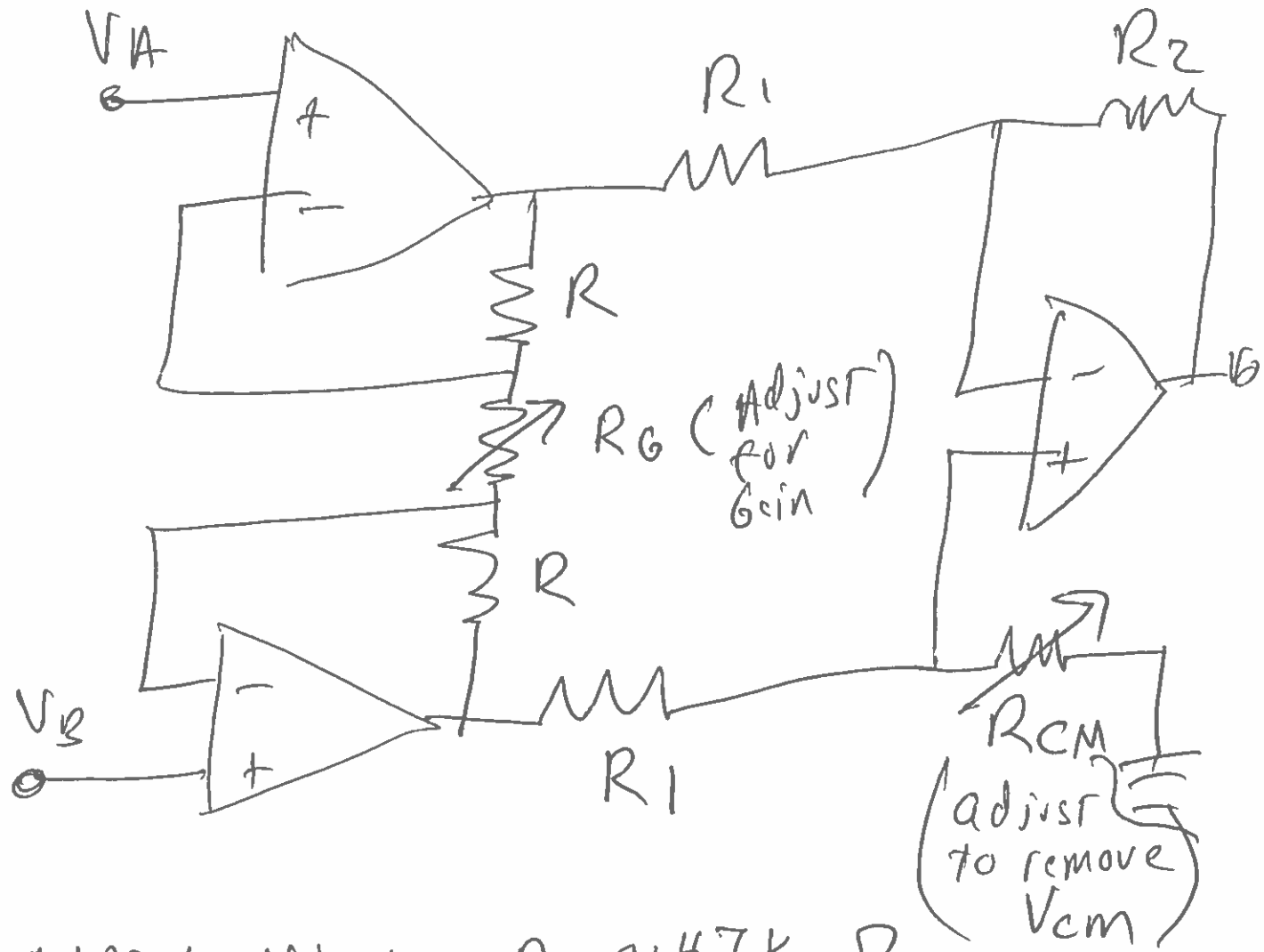Finally Resistor matching not so critical!



Typical values

$$R \sim 47K \Omega$$

$$R_G \sim 10K \Omega \text{ variable}$$


$$R_1 \sim 470 \Omega$$

$$R_2 \sim 4.7K \Omega$$

$$R_{cm} \sim 10K \Omega \text{ variable}$$

Short $V_A - V_B$

Adjust R_{cm} to
Get $V_d = 0$.

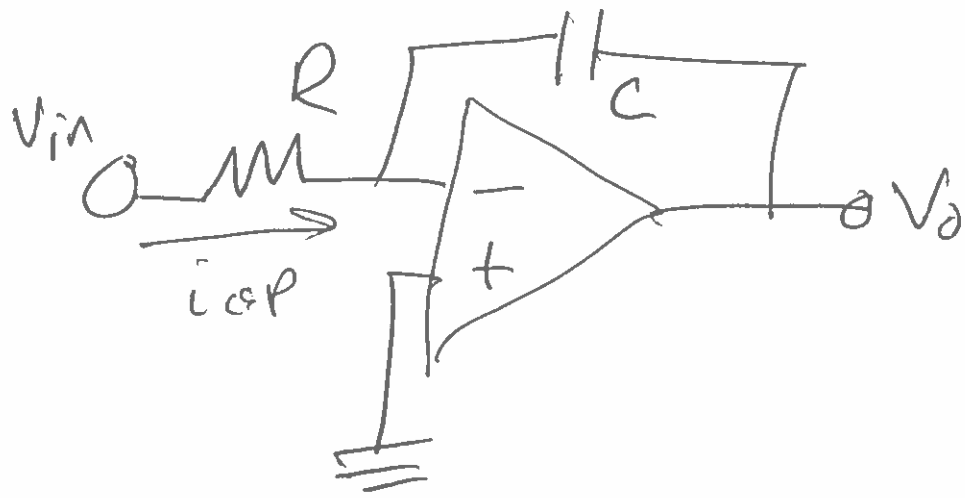


$$i_{csp} = \frac{dq}{dt} = \frac{d(cV)}{dt}$$

~~$$i_{csp} = c \frac{dV_{out}}{dt}$$~~


$$i_{csp} = c \frac{d(-V_{out})}{dt} = \frac{V_{in} - 0}{R}$$

$$\frac{d}{dt} V_{out} = -\frac{1}{RC} V_{in}$$
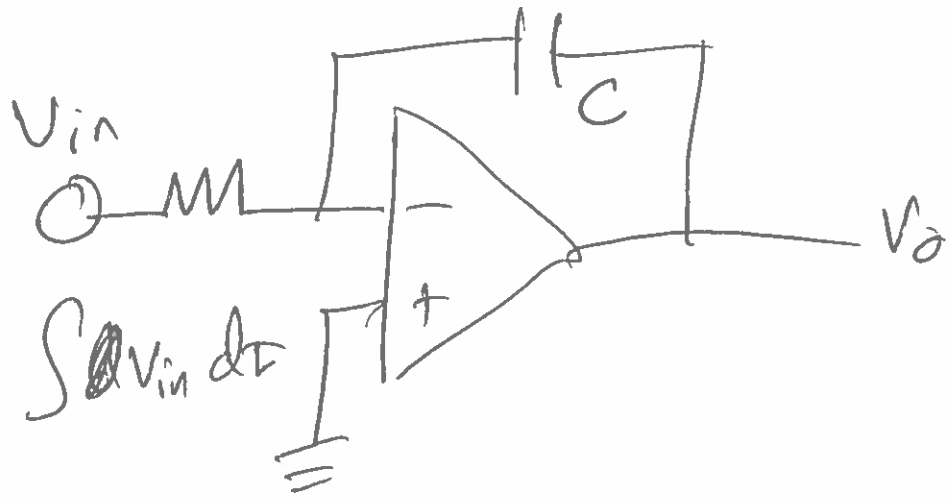
$$V_{out} = -\frac{1}{RC} \int V_{in} dt \Rightarrow \text{INTEGRATOR}$$


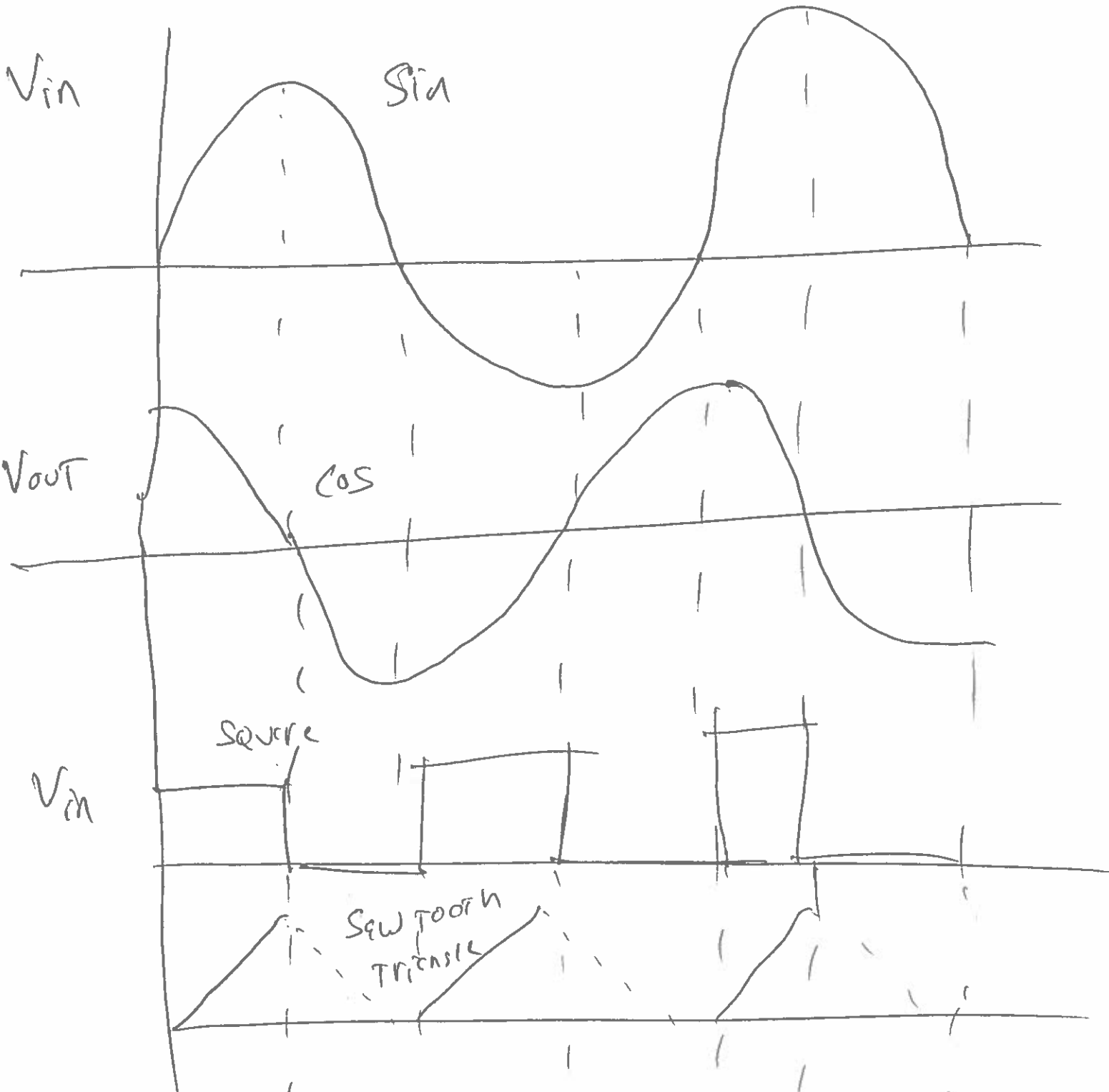
$$V_{out} = -\frac{1}{RC} \int V_{in} dt$$



A capacitor accepts charge until the voltage across capacitor equals voltage trying to put charge onto capacitor.


If voltage outside capacitor goes below voltage across capacitor, capacitor gives up the charge.


Low frequency will lead to periods of bitness. (uncharging)

~~STRESS~~
~~STRESS~~

⇒ This circuit passes high frequency signals ⇒ High Pass Filter.

$$\omega = \frac{1}{\sqrt{LC}}$$

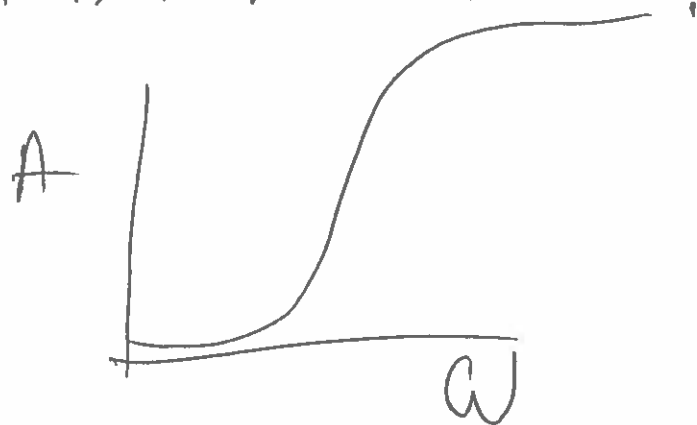

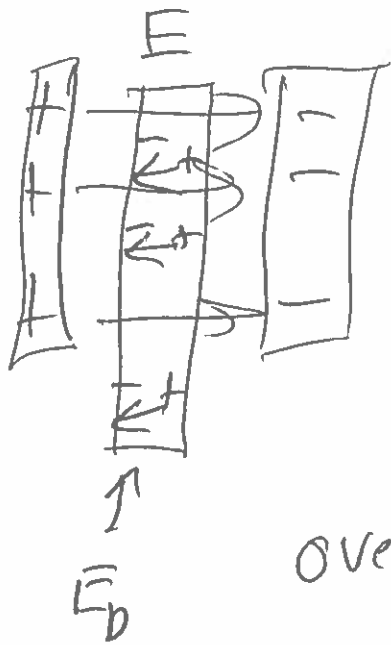

over all $E \downarrow$ $E \propto \frac{V}{d}$

for A.C. $X_c = \frac{i}{\omega C}$ = capacitive reactance


which is opposition to current flow

$$i = \frac{V}{X_c} = \omega C V$$

as $\omega \rightarrow 0$ $i \rightarrow 0$

if $\omega \rightarrow \infty$ $i \rightarrow \infty$

$$Q = C V$$

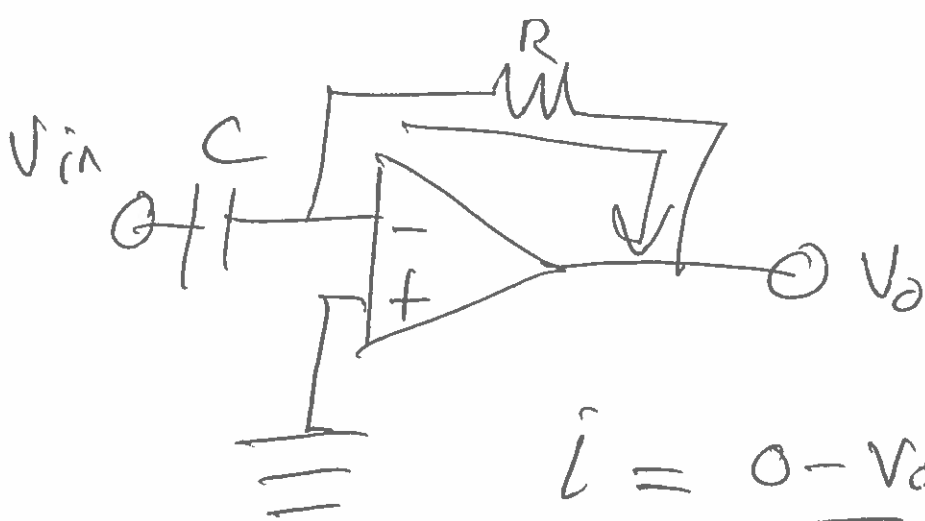

$$\dot{i} = \frac{0 - V_o}{R} = -\frac{V_o}{R}$$

$$\dot{i} = \frac{dq}{dt} = C \frac{dV_{in}}{dt} = -\frac{V_o}{R}$$

$$V_o = -RC \frac{dV_{in}}{dt} \quad \text{Differentiator}$$

and Low Pass filter

