

Time Schedule for Remaining work

Friday APR 9 Ch 6 Homework

Friday APR 23 Ch 7 Homework

Thurs APR 8 Thevenin Lab

Thurs APR 15 OP-AMPS I Lab


Thurs APR 22 OP-AMPS II Lab

Tues APR 20 Final Exam Handed out

~~Fri~~ Wed APR 28 Final Exam Due

APR 23 - All Homework/Labs
must be turned in.

Node Analysis with OP-AMPS

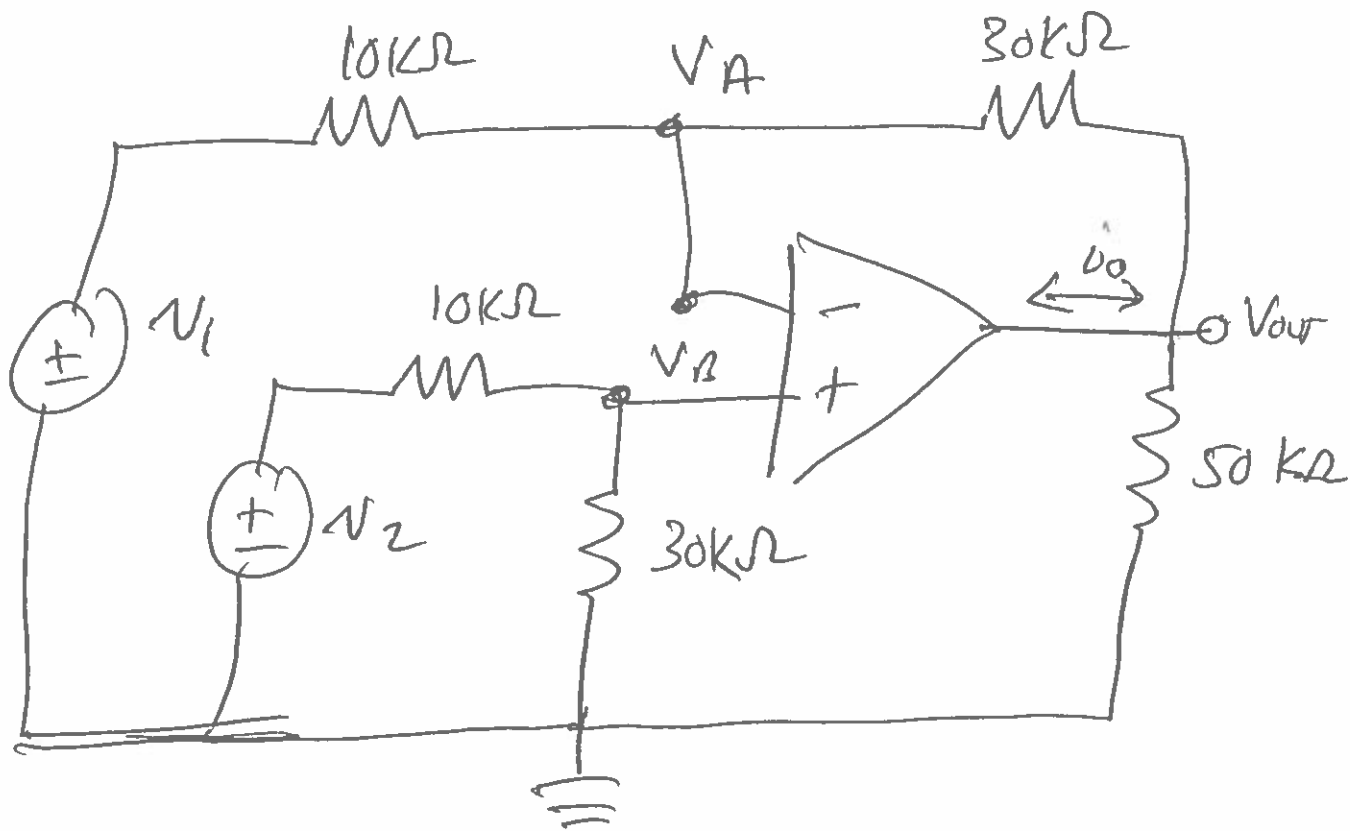

OP-AMP is either a current source or sink to V_{out} . So you can not write V_{out} as a primary node equation.

LATER US $V_A = V_B$

V_A node equation

$$0 = V_A \left(\frac{1}{10k\Omega} + \frac{1}{30k\Omega} \right) - V_{out} \left(\frac{1}{30k\Omega} \right) - V_1 \left(\frac{1}{10k\Omega} \right)$$

V_B Node

$$0 = V_B \left(\frac{1}{10k\Omega} + \frac{1}{30k\Omega} \right) - V_2 \left(\frac{1}{10k\Omega} \right)$$

$$V_A = V_B$$

$$V_B \left(\frac{4}{30k\Omega} \right) = V_2 \left(\frac{1}{10k\Omega} \right)$$

$$V_B = \frac{3}{4} V_2$$

$$V_A \left(\frac{4}{30k\Omega} \right) = V_{out} \left(\frac{1}{30k\Omega} \right) + V_1 \left(\frac{1}{10k\Omega} \right)$$

$$V_A = \frac{1}{4} V_{out} + \frac{3}{4} V_1$$

$$V_A = V_B \quad \frac{3}{4} V_2 = \frac{1}{4} V_{out} + \frac{3}{4} V_1$$

$$V_{out} = 3 (V_2 - V_1)$$

$$V_{out} = 3(V_2 - V_1)$$

$$i_0 = ?$$

$$i_0 = i_{50} + i_{30}$$


$$i_{50} = \frac{V_{out}}{50k\Omega} = \frac{3(V_2 - V_1)}{50k\Omega}$$

$$i_{30} = \frac{V_{out} - V_A}{30k\Omega} \quad V_A = \frac{1}{4}(V_{out} + 3V_1)$$

$$i_{30} = \frac{3(V_2 - V_1) - \frac{1}{4}(3(V_2 - V_1) + 3V_1)}{30k\Omega}$$

$$= \frac{3V_2 - 3V_1 - \frac{3}{4}V_2}{30k\Omega} = \frac{\frac{5}{4}V_2 - 3V_1}{30k\Omega}$$
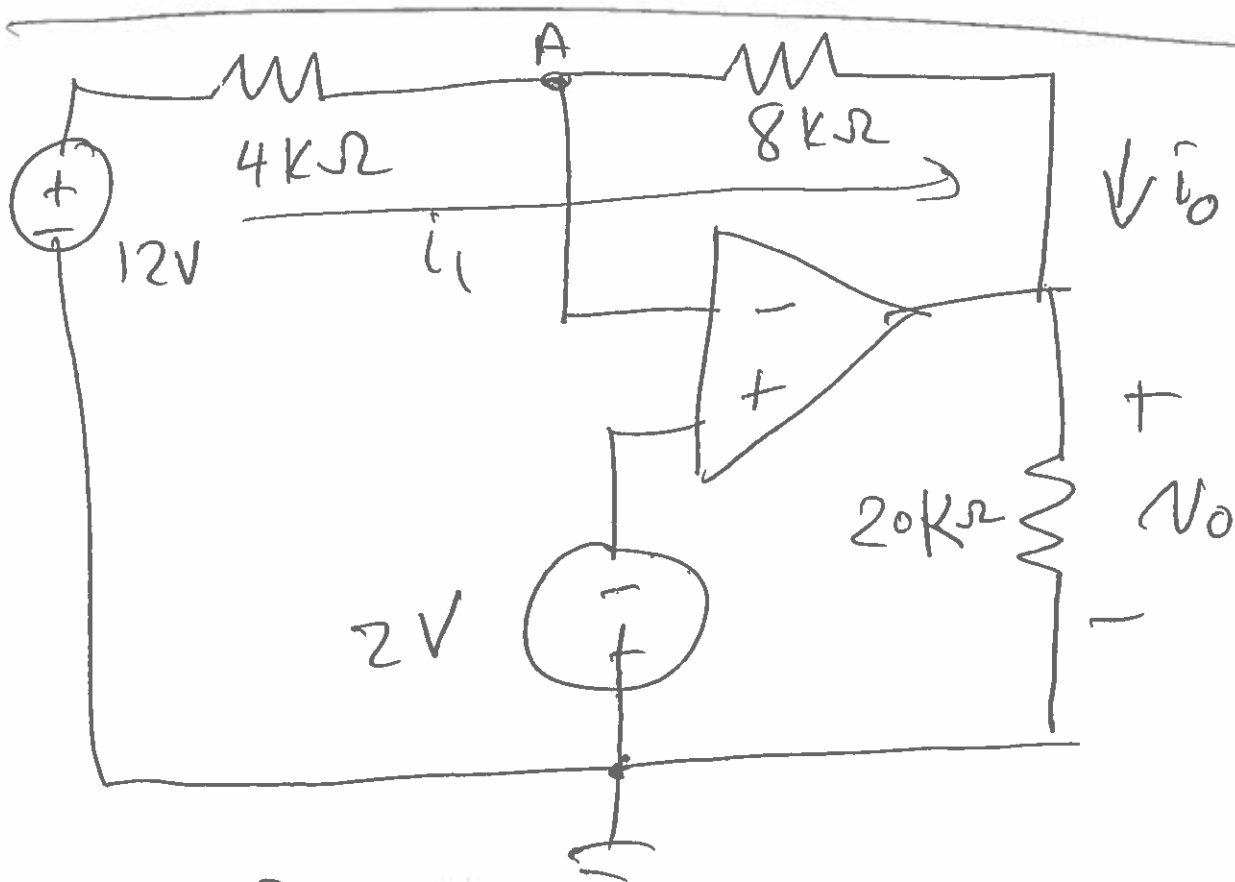
$$\hat{i}_0 = \frac{3}{50k\Omega} (V_2 - V_1) + \frac{(\frac{5}{4}V_2 - 3V_1)}{30k\Omega}$$



$$\hat{i}_0 = ? \quad V_o = ? \quad V_A = -2V$$

$$\hat{i}_1 = \frac{12V - (-2V)}{4k\Omega} = \frac{14V}{4k\Omega} = \frac{14}{4} \text{ mA}$$

$$\hat{i}_1 = \frac{-2V - V_o}{8k\Omega} = \frac{14}{4} \text{ mA}$$

$$28 \overset{V}{\cancel{\mu A}} = -2V - V_o$$

$$V_o = -30V$$


$$i_o = i_1 = 3.5 \text{ mA}$$

i in or out of OP-AMP

$$i_{\text{ground}} = \frac{-30V}{20k\Omega} = -1.5 \text{ mA}$$

i in or out of OP-AMP

$$i = 5.0 \text{ mA in.}$$

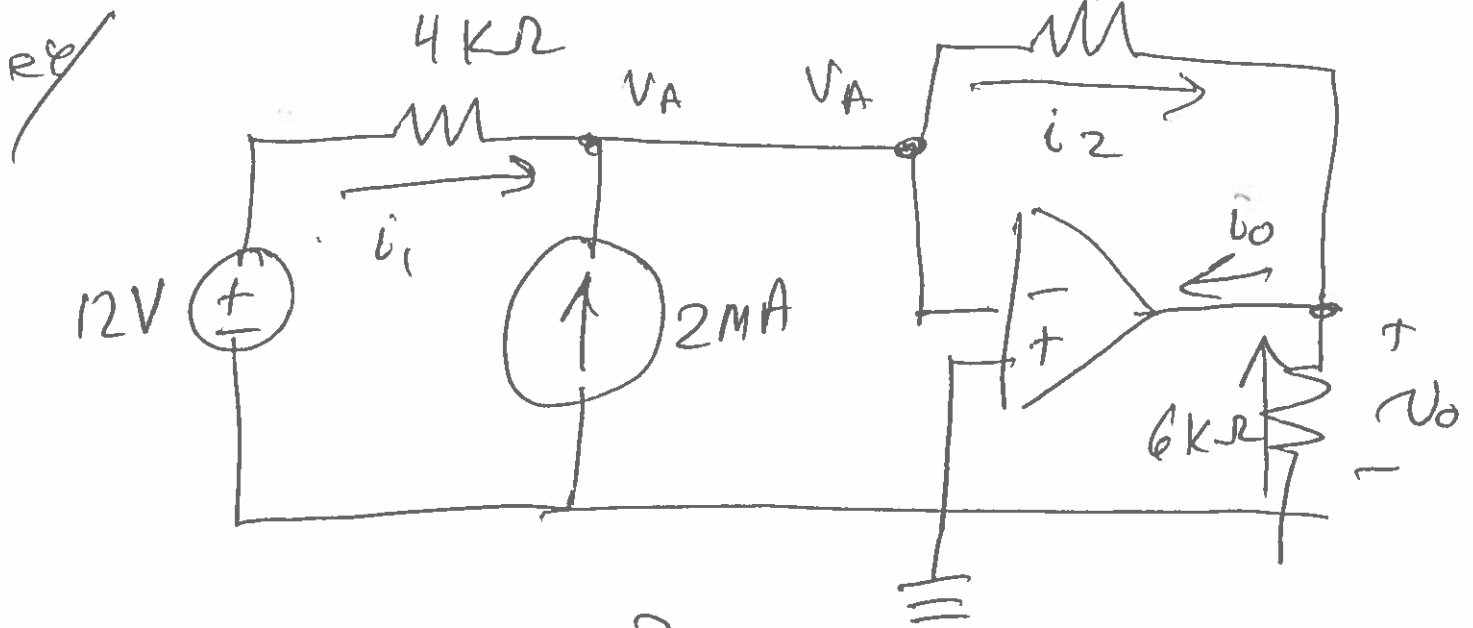

$$i_o, V_o = ?$$

$$V_A = 0$$

$$i_1 = \frac{12V}{4k\Omega} = 3mA$$

$$i_2 = i_1 + 2mA$$

$$= 3mA + 2mA = 5mA$$

$$V_o = -(5mA)(3k\Omega) = -15V$$

$$i_{6k\Omega} = \frac{15V}{6k\Omega} = 2.5mA$$

$$i_o = 5mA + 2.5mA = 7.5mA$$

