
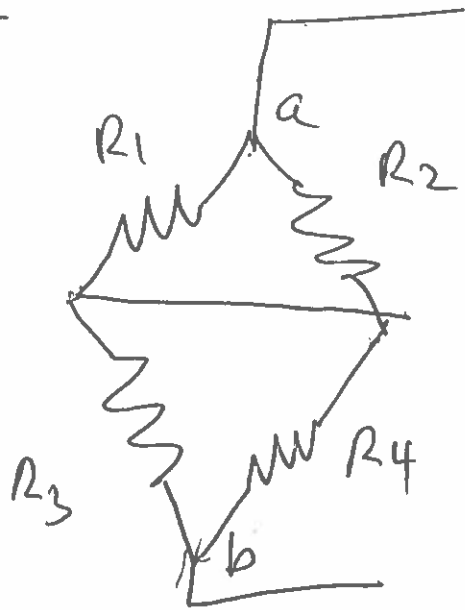


$V_o = ?$

R_T

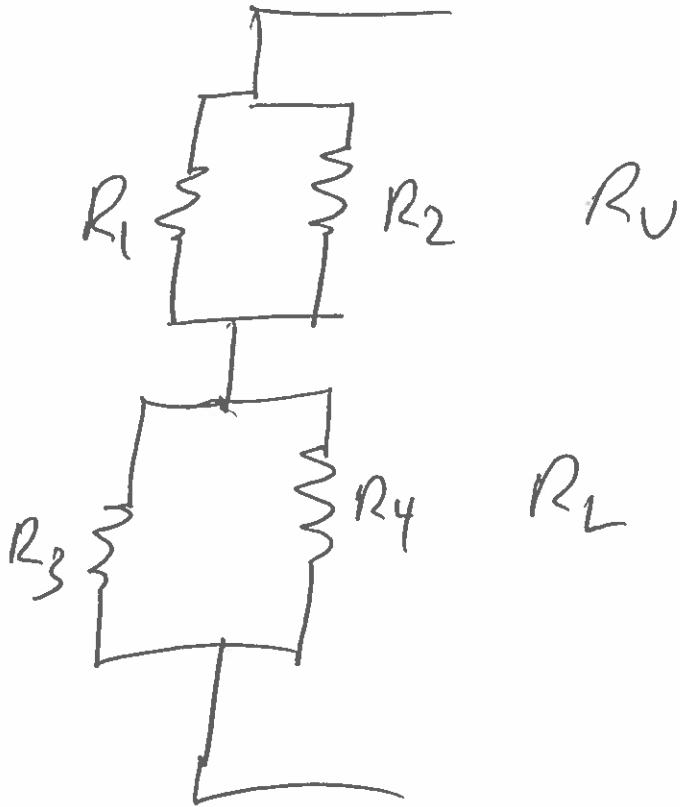

~~$R_U = R$~~




$$R_U = \frac{R_1 R_2}{R_1 + R_2}$$

$$R_L = \frac{R_3 R_4}{R_3 + R_4}$$

$$R_T = \frac{R_1 R_2}{R_1 + R_2} + \frac{R_3 R_4}{R_3 + R_4}$$

$$V_a - V_b = V_T$$

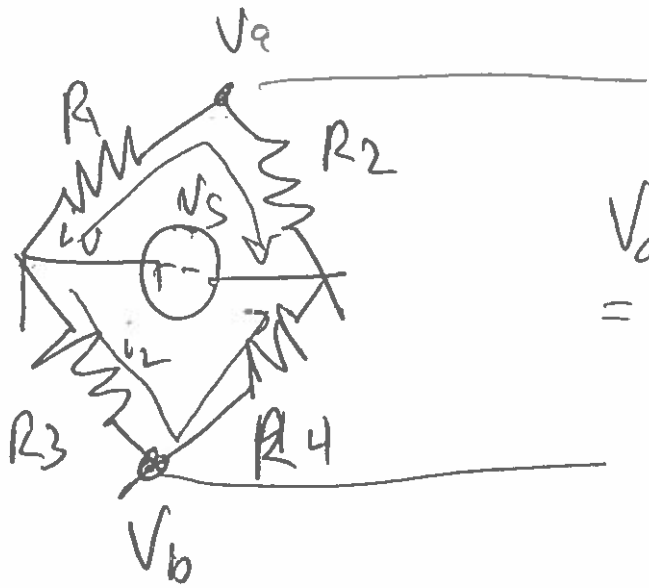

$$V_{oc} = v_t$$

$$i_L = \frac{V_s}{R_1 + R_2}$$

$$i_L = \frac{V_s}{R_3 + R_4}$$

$$V_a = i_L R_2 = \frac{V_s R_2}{R_1 + R_2}$$


$$V_b = i_L R_4 = \frac{V_s R_4}{R_3 + R_4}$$

$$V_E = V_s \left(\frac{R_2}{R_1 + R_2} - \frac{R_4}{R_3 + R_4} \right)$$

by rules of OP-AMPS No current
 can be in branch touching V_-

$$\text{So } V_a = V_c$$


Do a voltage node equation for V_a

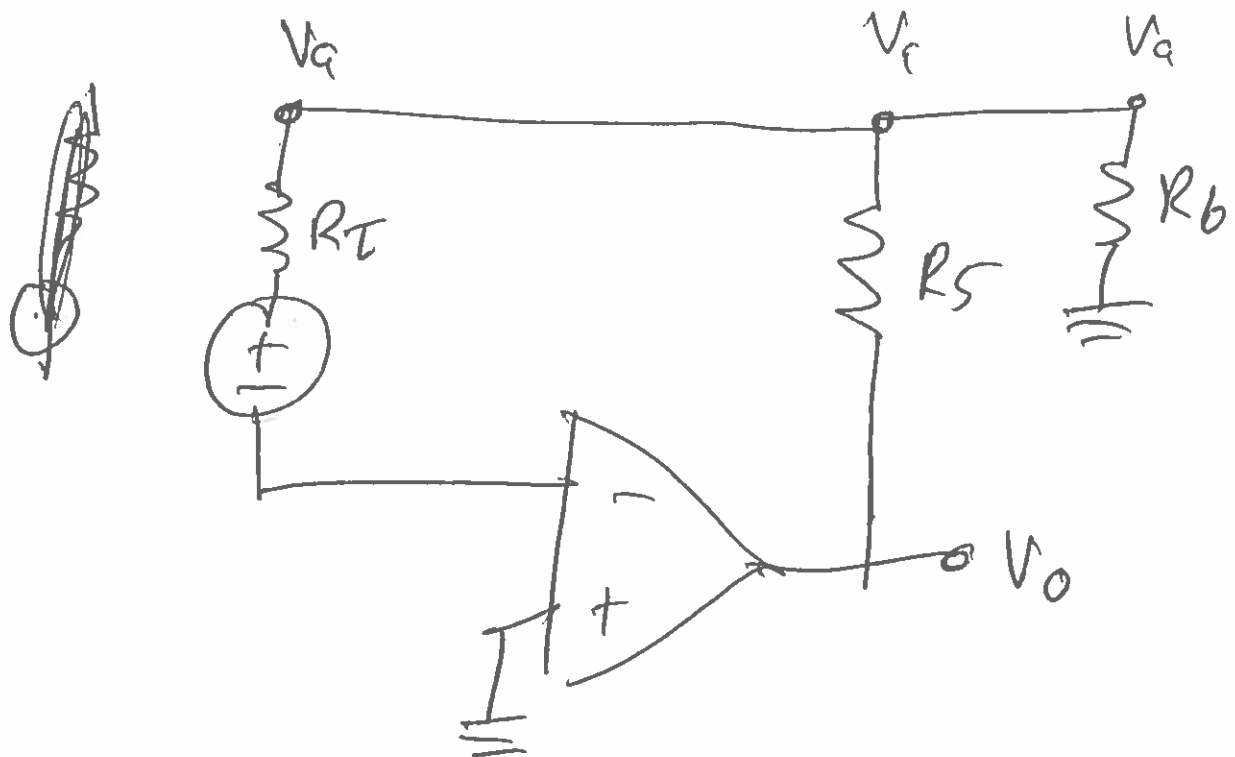

$$0 = V_a \left(\cancel{\frac{1}{R_T}} + \frac{1}{R_5} + \frac{1}{R_b} \right) - V_o \left(\frac{1}{R_5} \right)$$


$$V_o = V_a \left(1 + \frac{R_5}{R_b} \right) = V_s \left(\frac{R_2}{R_1 + R_2} + \frac{R_4}{R_3 + R_4} \right) \left(1 + \frac{R_5}{R_b} \right)$$
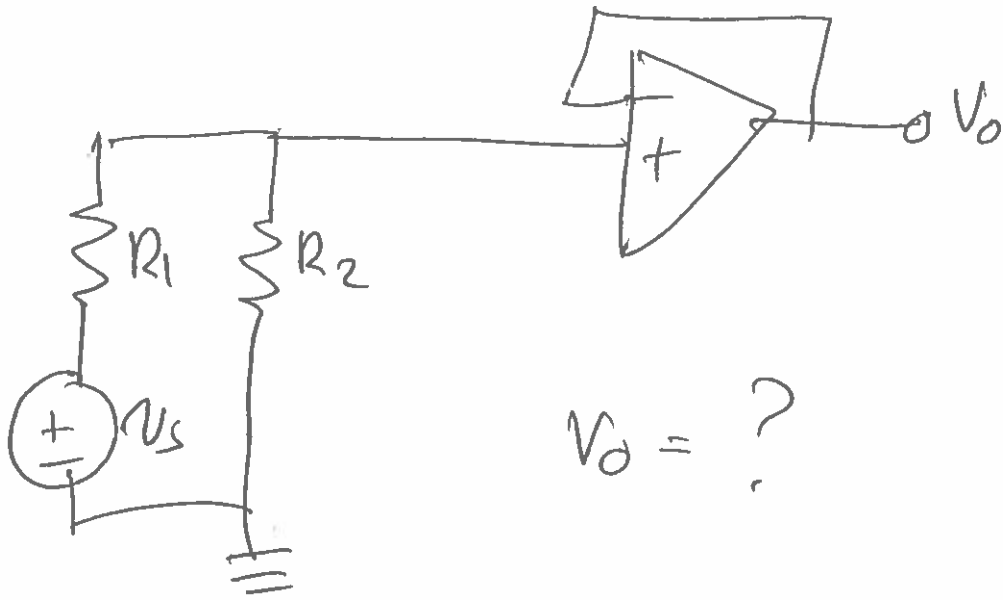
$$\boxed{V_o = V_s \left(\frac{R_2}{R_1 + R_2} + \frac{R_4}{R_3 + R_4} \right) \left(1 + \frac{R_5}{R_b} \right)}$$



$$V_o = ?$$

$$V_o = V_S \frac{R_2}{R_1 + R_2}$$

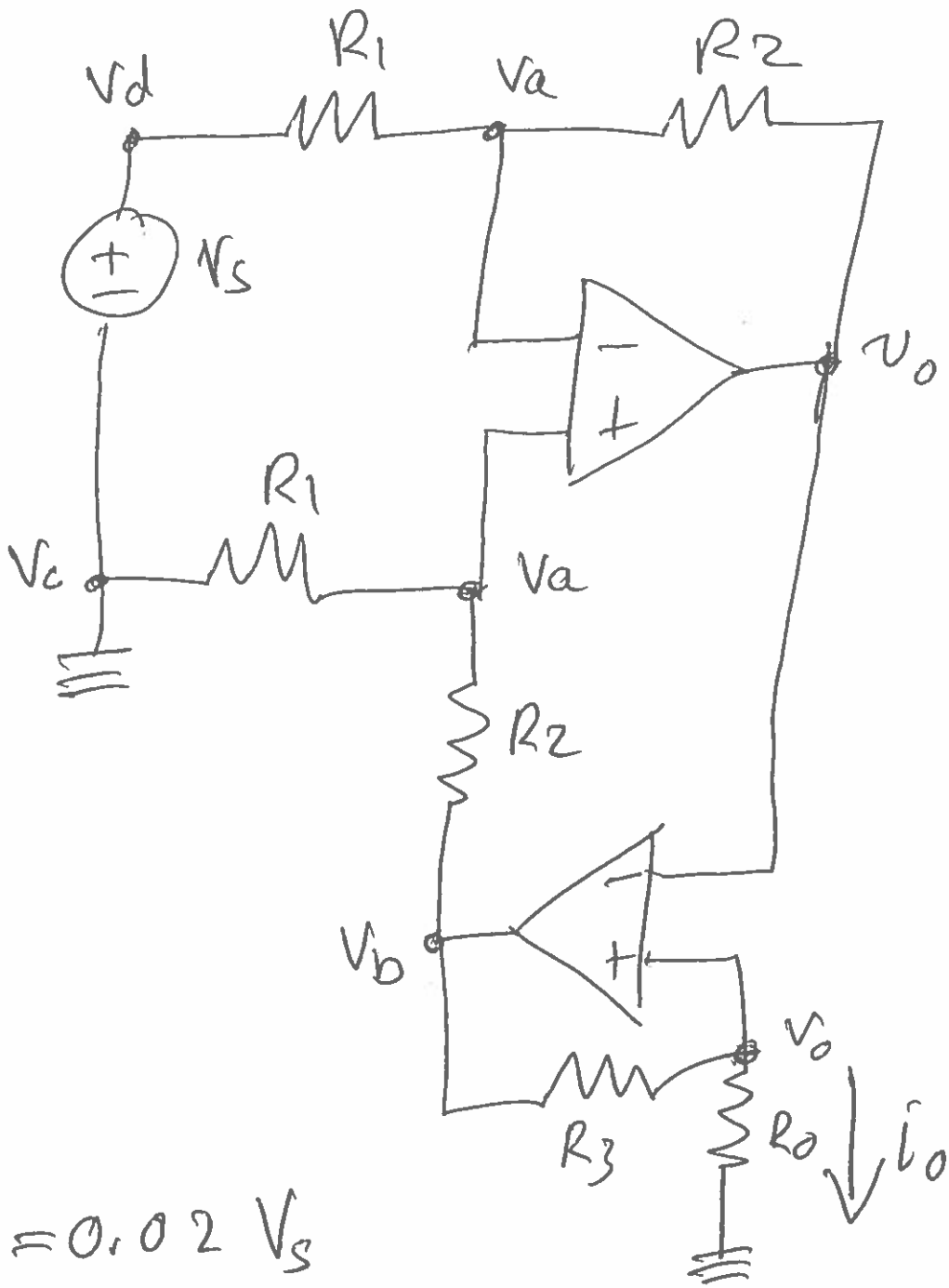

$$i_o = 0.02 V_s$$

Find R_0 , R_1 , R_2 , and R_3

$$i_o = \frac{V_o}{R_0}$$

$$v_c = 0 \Rightarrow v_d = V_s$$

TOP V_a Node equation

$$0 = V_a \left(\frac{1}{R_1} + \frac{1}{R_2} \right) - V_s \left(\frac{1}{R_1} \right) - V_o \left(\frac{1}{R_2} \right)$$

Bottom V_a Node equation

$$0 = V_a \left(\frac{1}{R_1} + \frac{1}{R_2} \right) - V_b \left(\frac{1}{R_2} \right)$$

Lower V_o Node

$$0 = V_o \left(\frac{1}{R_o} + \frac{1}{R_3} \right) - V_b \left(\frac{1}{R_3} \right)$$

$$V_b = V_o \left(1 + \frac{R_3}{R_o} \right)$$

Two V_a Node equations can be combined to

give

$$V_b \left(\frac{1}{R_2} \right) = V_s \left(\frac{1}{R_1} \right) + V_o \left(\frac{1}{R_2} \right)$$

$$V_o \left(1 + \frac{R_3}{R_o}\right) \left(\frac{1}{R_2}\right) = V_s \left(\frac{1}{R_1}\right) + V_o \left(\frac{1}{R_2}\right)$$

$$V_o \left(\frac{1}{R_2}\right) + V_o \left(\frac{R_3}{R_o R_2}\right) - V_o \left(\frac{1}{R_2}\right) = V_s \left(\frac{1}{R_1}\right)$$

$$V_o = V_s \frac{R_o R_2}{R_1 R_3}$$

$$\hat{i}_o = \frac{V_o}{R_o} = V_s \frac{R_2}{R_1 R_3}$$

$$\hat{i}_o = V_s \left(\frac{R_2}{R_1 R_3}\right)$$

$$\Rightarrow \frac{R_2}{R_1 R_3} = 0.02$$

R_0 can be any value Let's make it

$$R_0 = 1 \text{ k}\Omega$$

if $R_1 = R_2 = 1 \text{ k}\Omega$


$$\frac{1}{R_3} = 0.02$$

$$R_3 = \frac{1}{0.02} = 50 \text{ k}\Omega$$

One solution is

$$R_0 = R_1 = R_2 = 1 \text{ k}\Omega$$

$$R_3 = 50 \text{ k}\Omega$$

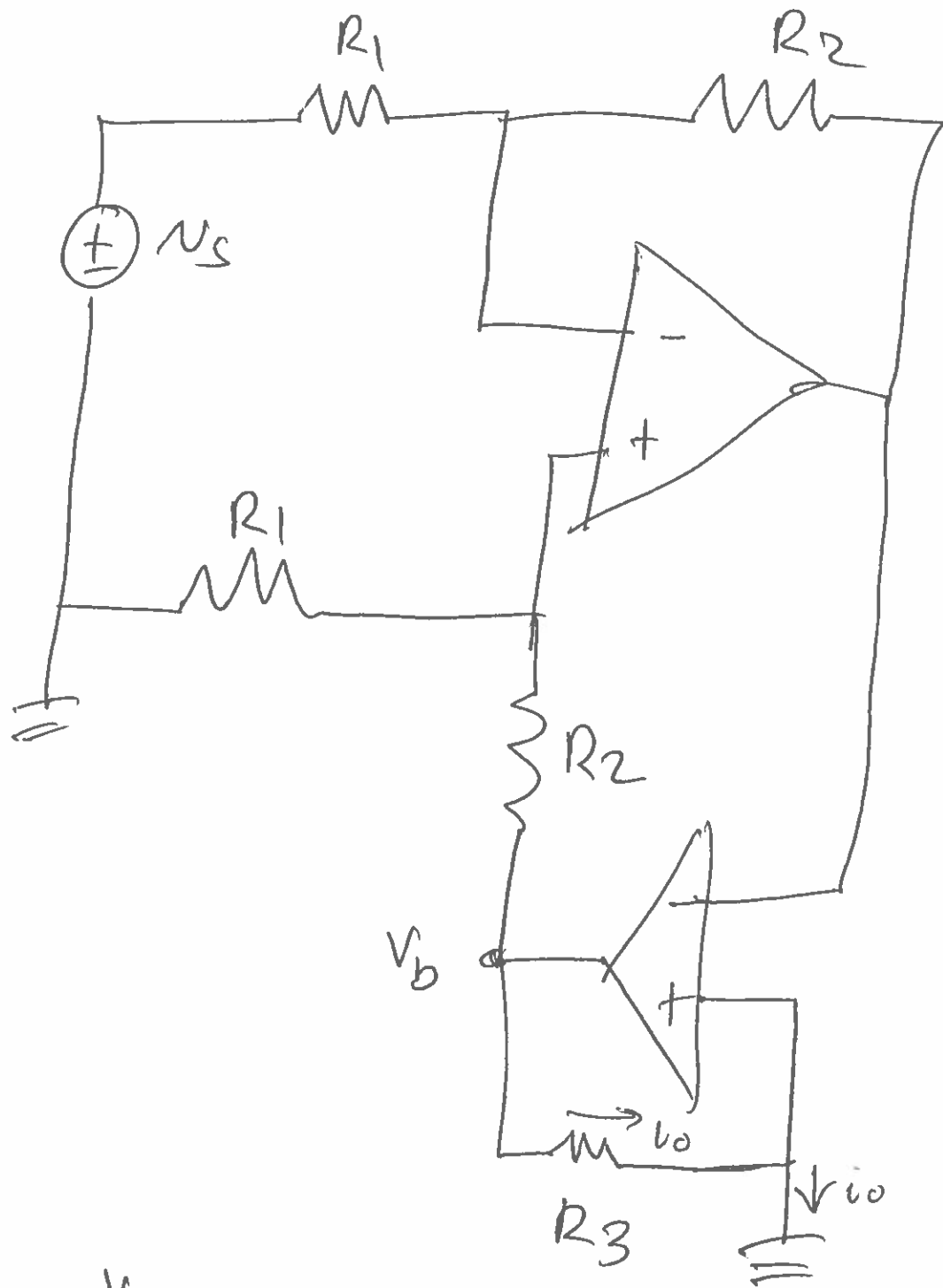

$$i_o = \frac{V_b}{R_3}$$

$$V_b = V_s \frac{R_2}{R_1} + V_o \quad V_o = V_s \frac{R_0 R_2}{R_1 R_3}$$

$$V_b = V_s \frac{R_2}{R_1} \quad i_o = V_s \frac{R_2}{R_1 R_3} \quad \checkmark = 0$$