

Energy Storage Elements - capacitors, inductors

Capacitors Two conductors separated by a dielectric store charge which provides storing energy in an electric field.

Primary purpose of a capacitor is to maintain

the local voltage.

If voltage locally ~~increases~~ ^{increases} capacitor takes more charge onto conductors if


voltage locally decreases capacitor releases charge from conductors.

$$Q = CV$$

How to find C ?


Consider Parallel Plate Capacitor separated by

Q Vacuum.

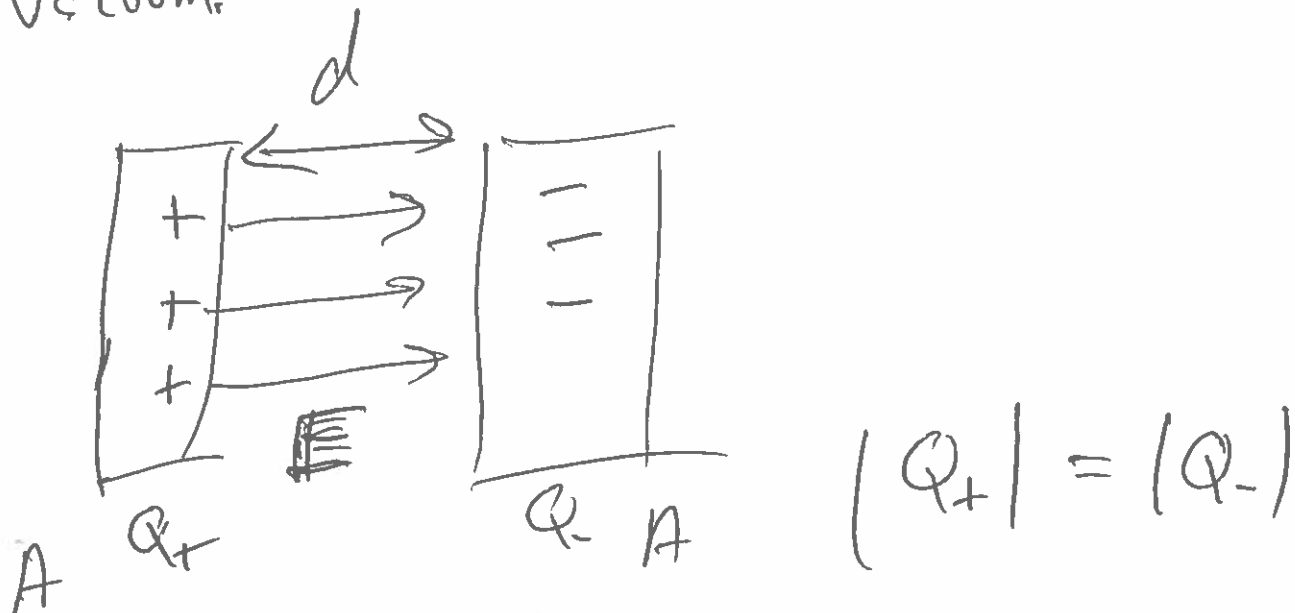

$E = ?$ Use Gauss's Law

Gaussian Surface

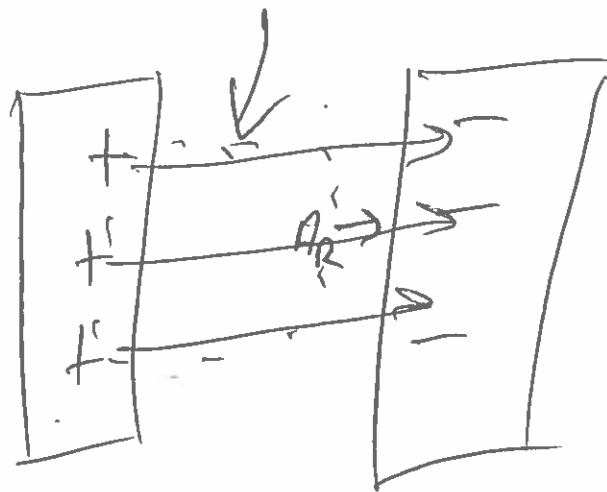

$$\Phi_{\text{surface}} = E A_R = \frac{Q_{\text{enc}}}{\epsilon_0}$$

make A_R size of Plate


$Q_{\text{enc}} = Q$ on Plate

If A not Plate Area


$$Q_{enc} = \sigma A_R$$

$$\underline{E} A_R = \frac{\sigma A_R}{\epsilon_0}$$

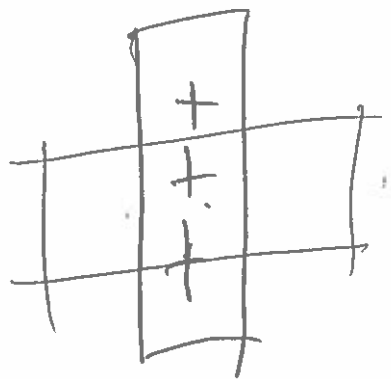$E = \frac{\sigma}{\epsilon_0}$ which is field
inside capacitor


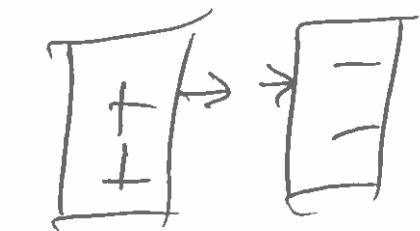
$$E_{cond} = \frac{\sigma}{2\epsilon_0}$$




$$\frac{\sigma_+}{2\epsilon_0} + \frac{\sigma_-}{2\epsilon_0} = \frac{\sigma}{\epsilon_0}$$

$$E = \frac{Q}{A\epsilon_0}$$

$$V =$$

$$-\frac{dV}{dx} = E$$

$$V_B - V_A = -\int_A^B E dx$$

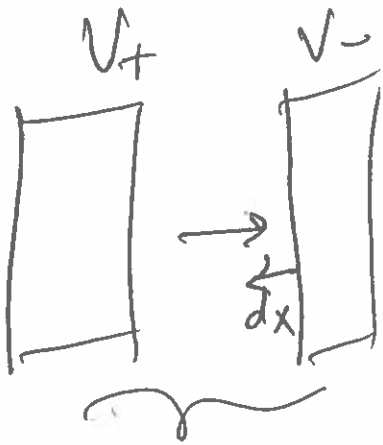

$$\Delta V = V_+ - V_- = -\int_{-}^{+} \vec{E} \cdot d\vec{x} = -\int E dx$$

$$V_{cp} = \Delta V = E \int_0^d dx = Ed$$

units of Electric field $N/C = \frac{Nm}{Cm} = \frac{J}{Cm}$

$$= \frac{J/C}{m} = \frac{V}{m}$$

$$Ed = V$$


~~$$V = \frac{Ed}{d}$$~~
$$E = \frac{V}{d}$$

$$E_{cap} = \frac{Q}{A\epsilon_0} = \frac{V}{d}$$

$$Q = \frac{A\epsilon_0 V}{d} \quad Q = CV$$

$$\Rightarrow C = \frac{A\epsilon_0}{d} \quad \underline{\text{Parallel Plate}}$$

Cylindrical Capacitor

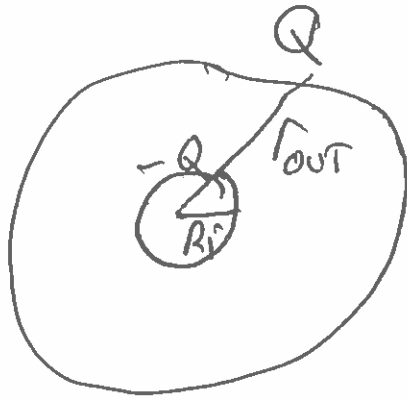



Capacitance depends on Geometry
and materials of capacitor

NOT ON VOLTAGE or charge.

$$C_{\text{diel}} = \epsilon_r C_0$$

ϵ_r - dielectric constant.


dielectric

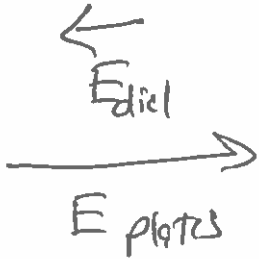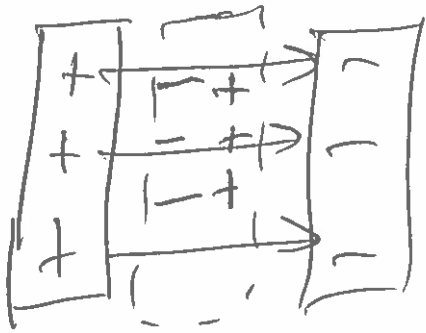



E_{cap} is reduced

$$Q = CV$$

$$i = \frac{dq}{dt} = C \frac{dv}{dt}$$

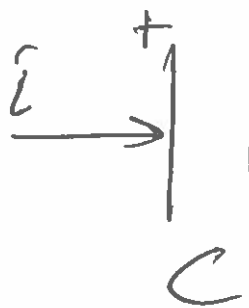


+ i

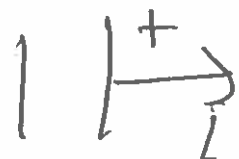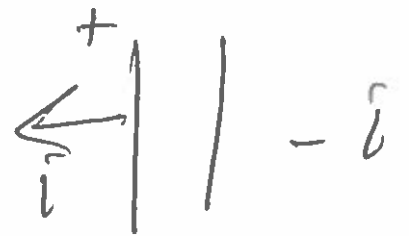


If V is constant



$$i = 0$$

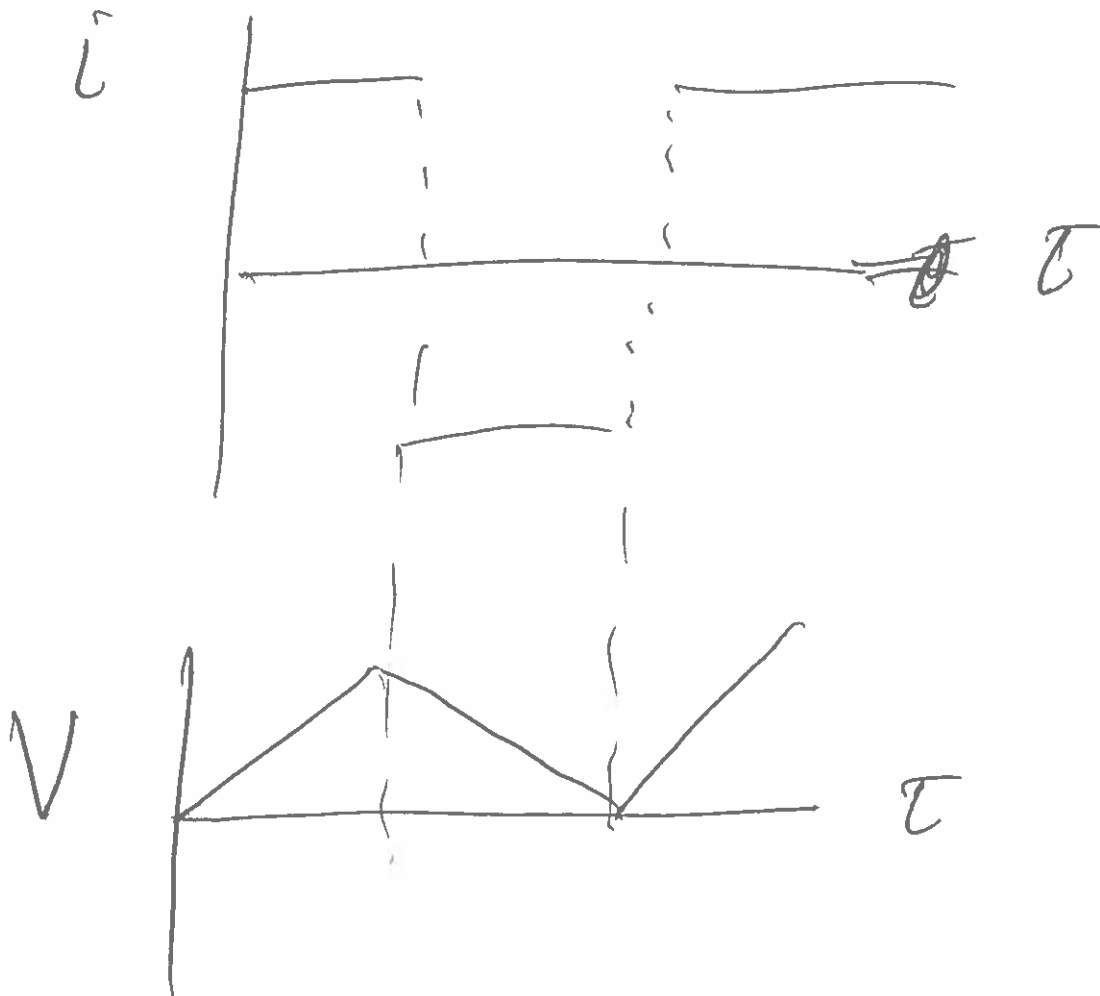Voltage must be continuous on a capacitor, while current can be discontinuous, voltage cannot be.



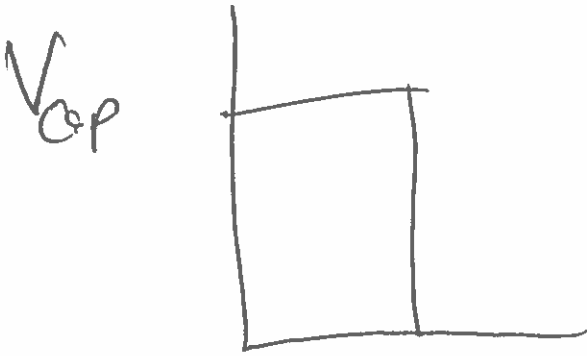

can never
look so.

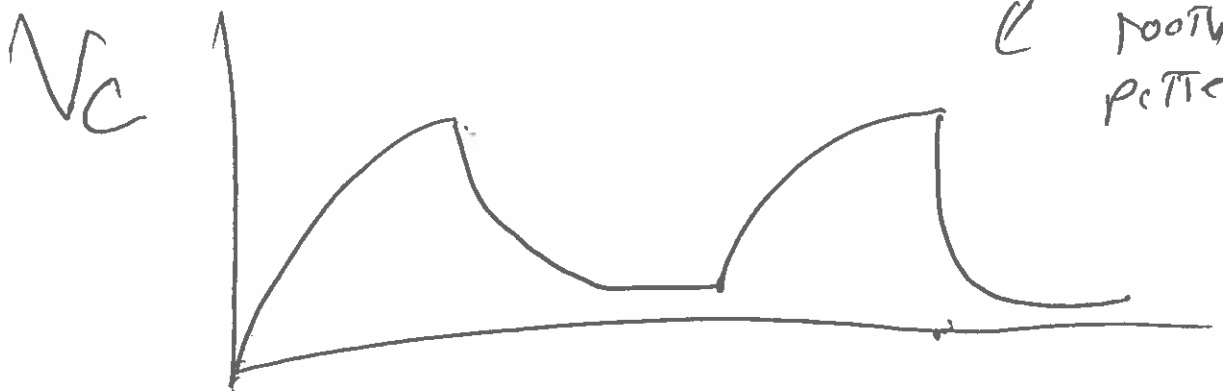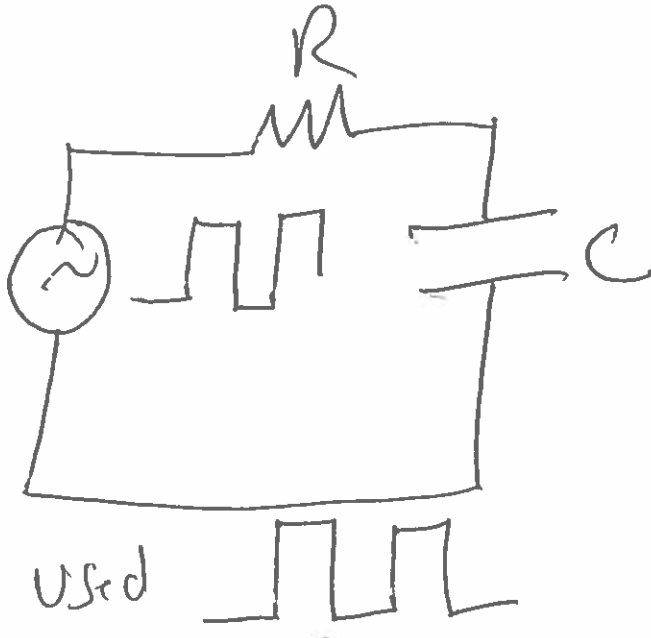


$$V_{cp}(t^-) = V_{cp}(t^+)$$

$t^-, t^+ \quad 0^-, 0^+ \quad 1^-, 1^+$

infinitesimal
differences

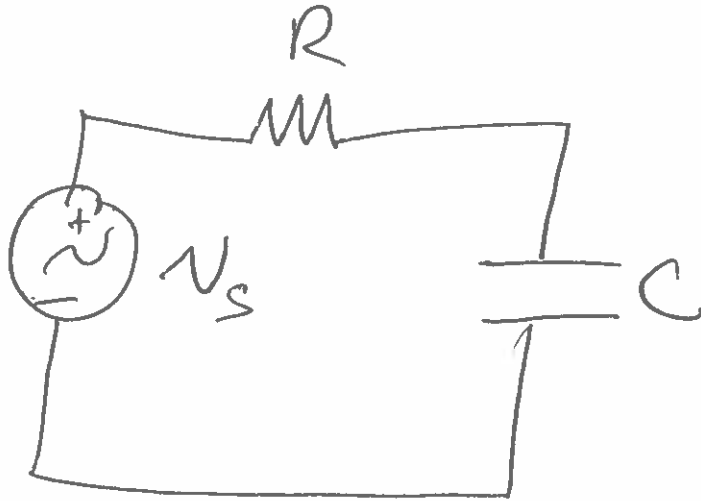VOLTAGE ACROSS A CAPACITOR CANNOT
CHANGE INSTANTANEOUSLY



$$V_s = A \sin(\omega t)$$

$$V_c = ? B \sin(\omega t)$$

$$i = C \frac{dV_c}{dt} = C \frac{d}{dt} (B \sin(\omega t))$$

$$i = CB\omega \cos(\omega t)$$

$$\sin(90^\circ - \theta) = \cos(\theta)$$

Phase difference between sin and cos

cos is ahead of sin by 90° or $\frac{\pi}{2}$

Current creates voltage on capacitor

So current is ahead in phase of

voltage on a capacitor.


Capacitor $i = C \frac{dV}{dt}$ i ahead of V

Resistor $i = \frac{1}{R} V$ i in phase with V

Inductor $V_i = L \frac{di}{dt}$ i behind of V


E \perp i The i \perp E men

E is emf \Rightarrow voltage

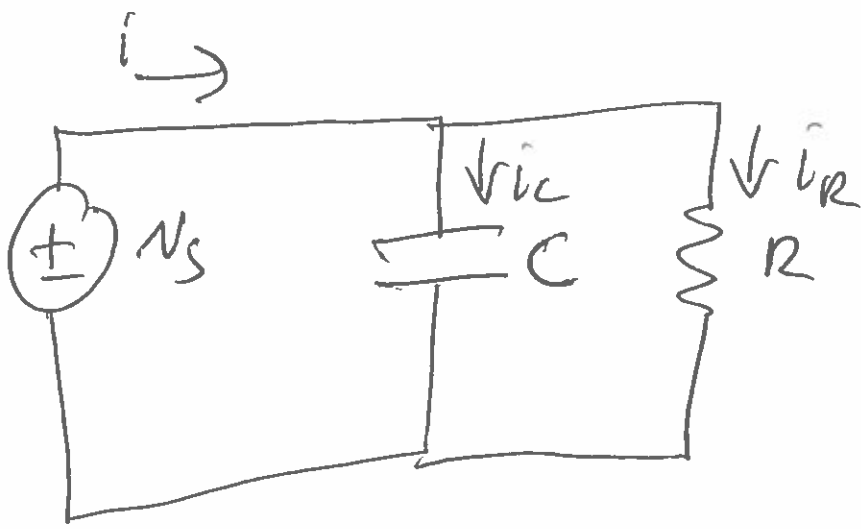

$$C = 1 \text{ F} \quad R = 1 \Omega \quad 0 \leq t \leq 2$$
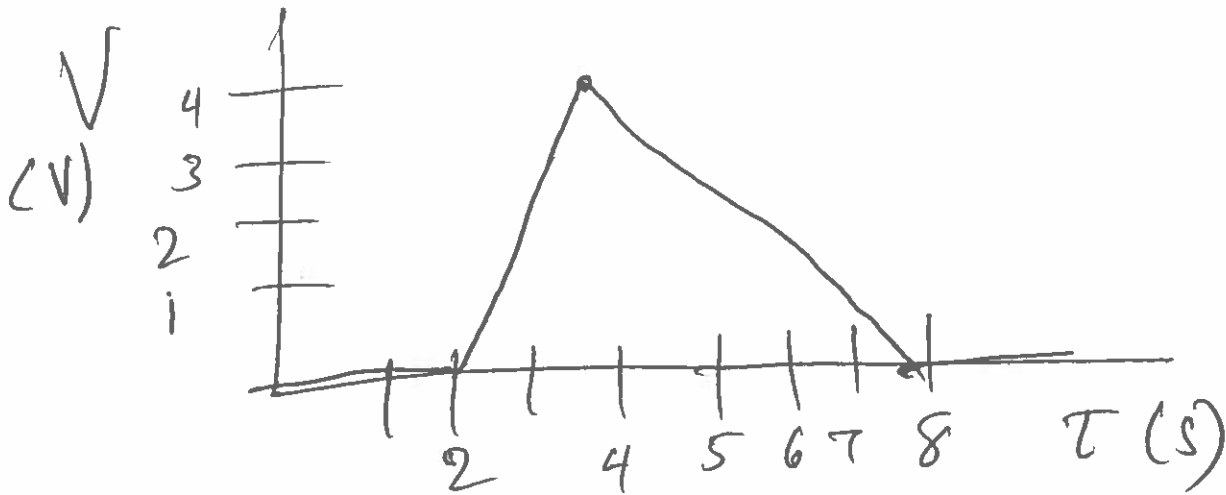
$$i = ? \quad \text{if} \quad V_s = \begin{cases} 2t - 4 & 2 \leq t \leq 4 \text{ s} \\ 8 - t & 4 \leq t \leq 8 \text{ s} \\ 0 & t \geq 8 \text{ s} \end{cases}$$



$$\hat{I} = \hat{I}_C + \hat{I}_R$$

$$\hat{I}_R = \frac{V_s}{R} = \begin{cases} 0 & 0 \leq t \leq 2 \text{ s} \\ 2t - 4 & 2 \leq t \leq 4 \text{ s} \\ 8 - t & 4 \leq t \leq 8 \text{ s} \\ 0 & t \geq 8 \text{ s} \end{cases}$$

$$i_c = C \frac{dv}{dt}$$