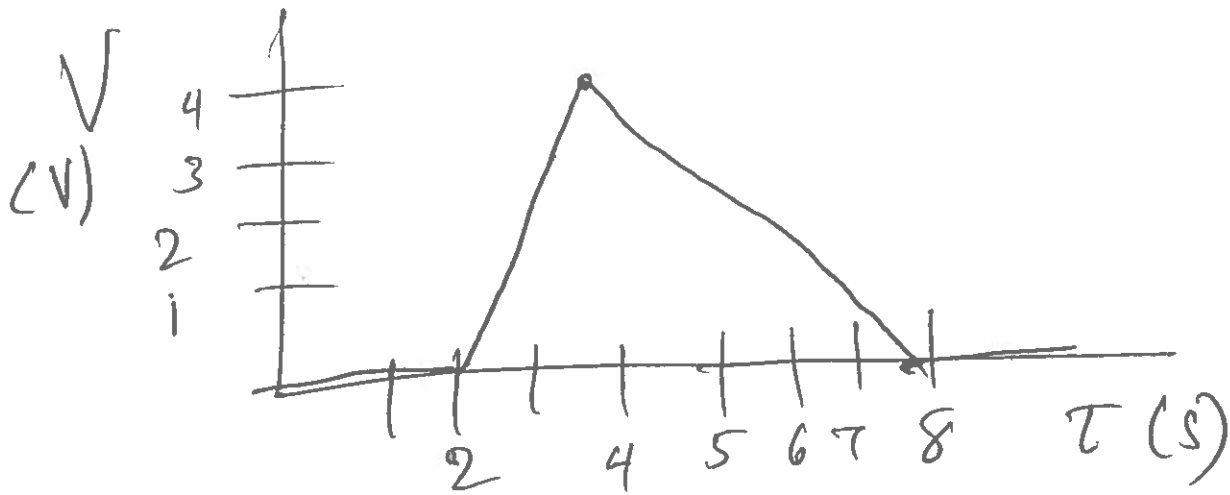


$$C = 1 \text{ F} \quad R = 1 \Omega \quad 0 \leq t \leq 2$$

$$i = ? \quad \text{if} \quad V_s = \begin{cases} 2t - 4 & 2 \leq t \leq 4 \text{ s} \\ 8 - t & 4 \leq t \leq 8 \text{ s} \\ 0 & t \geq 8 \text{ s} \end{cases}$$



$$i = i_c + i_R$$

$$i_R = \frac{V_s}{R} = \begin{cases} 0 & 0 \leq t \leq 2 \text{ s} \\ 2t - 4 & 2 \leq t \leq 4 \text{ s} \\ 8 - t & 4 \leq t \leq 8 \text{ s} \\ 0 & t \geq 8 \text{ s} \end{cases}$$

$$i_c = C \frac{dV}{dt} \quad \cdot C = 1F$$

$$i_c = \begin{cases} 0 & = \frac{d0}{dt} = 0 \\ 2 & = \frac{d}{dt} (2t - 4) = 2 \\ -1 & = \frac{d}{dt} (8 - t) = -1 \\ 0 & \end{cases}$$

$$i = i_c + i_r = \begin{cases} 0 & 0 \leq t \leq 2s \\ 2t - 2 & 2 \leq t \leq 4s \\ 7 - t & 4s \leq t \leq 8s \\ 0 & t \geq 8s \end{cases}$$

---

eg/  $\frac{1}{C} \int i_c dt = v_c(t)$        $v_c(t) = 12 \cos(2t + 30^\circ)$   
 $C = 0.125 \text{ F}$

$i_c = ?$

$i_c = C \frac{dv}{dt} = (0.125 \text{ F}) \frac{dv}{dt}$

$\frac{dv}{dt} = \frac{d}{dt} (12 \cos(2t + 30^\circ))$

$= -12 \sin(2t + 30^\circ) (2)$

$= -24 \sin(2t + 30^\circ) = -24 \cos(2t + 120^\circ)$

~~$\sin(A+B) = \sin(A)\cos(B) + \cos(A)\sin(B)$~~

~~$\sin(120) = \cos(60)$~~

$$\frac{dV}{dt} = -24 \sin(2t + 30^\circ)$$

~~$$\sin(2t + 30 + 90)$$~~

$$i = (.125 F)(24) \cos(2t + 120^\circ)$$


$$\cos(2t + 120^\circ) = -\sin(2t + 30^\circ)$$

$$i = 3 \cos(2t + 120^\circ)$$

$$V = 12 \cos(2t + 30^\circ)$$

$i$  is  $90^\circ$  ahead of  $V$

ee/

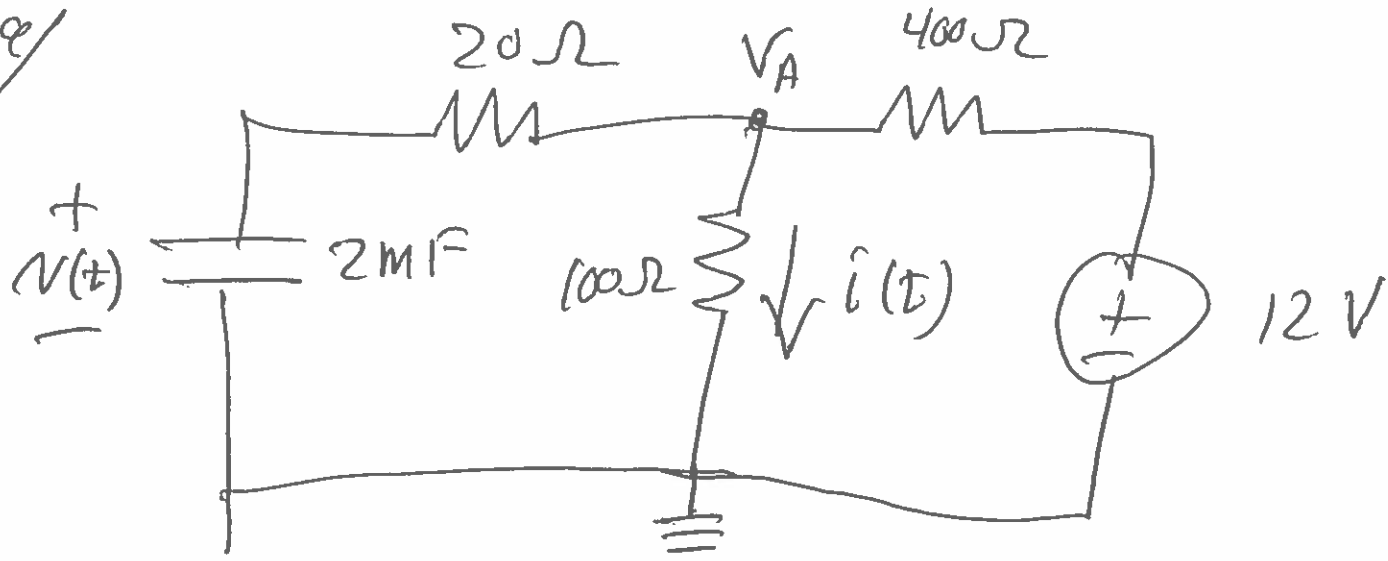

$$V(t) = 2.4 + 5.6 e^{-5t} \text{ V}$$

for  $t \geq 0$

$$i(t) = ?$$

$$i(t) = \frac{V_A}{100 \Omega}$$

$$0 = V_a \left( \frac{1}{100 \Omega} + \frac{1}{20 \Omega} + \frac{1}{400 \Omega} \right) - 12 \text{ V} \left( \frac{1}{400 \Omega} \right) - V(t) \left( \frac{1}{20 \Omega} \right)$$

$$0 = V_a \left( \frac{4 + 20 + 1}{400 \Omega} \right) - \frac{12 \text{ V}}{400 \Omega} - \frac{V(t) 20}{400 \Omega}$$

$$0 = 25V_A - 12V - 20V(t)$$

$$V_A = \frac{12V + 20(2.4 + 5.6e^{-5t})}{25}$$

$$V_A = \frac{60V + 112e^{-5t}}{25}$$

$$\hat{i}(t) = \frac{60V + 112Ve^{-5t}}{2500\Omega}$$


$$\hat{i}(t) = 24 + 44.8e^{-5t} \text{ mA}$$

# Energy Storage in a Capacitor

---

$$W_C = ?$$

empty capacitor

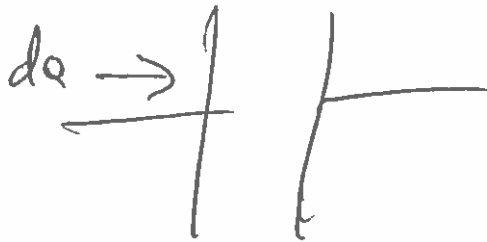


Work to put  
first  $dq$  on  
plates?

$$W_{\text{first } dq} = 0$$

once on plates  $dq \Rightarrow dV$

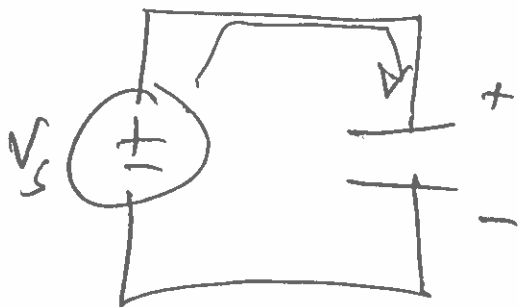next  $dq$  must overcome  $dV$  to be  
on plates



$$W = \int \vec{F} \cdot d\vec{s}$$

$$dF = dqE$$

$$\text{Energy} = \int \text{Power } dt$$

$$= \int i v dt$$

$$= \int \frac{dq}{dt} v dt$$

$$= \int v dq$$

$$= \int \frac{q}{c} dq = \frac{1}{c} \int q dq$$

$$W = \frac{1}{c} \frac{1}{2} q^2 = \frac{q^2}{2c}$$

Using  $q = cV$

$$W = \frac{1}{2} c V^2 = \frac{1}{2} q V = \frac{1}{2c} q^2$$

---

ENERGY stored in capacitor

$$W = \frac{1}{2} C V^2$$

$$V = E d$$

↑ electric field  
↑ plate sep.

$$W = \frac{1}{2} C (E^2 d^2)$$

$$C_{\text{parallel plate}} = \frac{\epsilon_0 A}{d}$$

$$W = \frac{1}{2} \frac{\epsilon_0 A}{d} E^2 d^2 = \frac{1}{2} \epsilon_0 \underbrace{(A d)}_{\text{volume}} E^2$$

$$\frac{W}{\text{Vol}} = U_E = \frac{1}{2} \epsilon_0 E^2$$

$$U_B = \frac{1}{2 \mu_0} B^2$$

Light Intensity  ~~$\propto E^2$~~

If light is incoherent  ~~$I_{\text{tot}} = I_1$~~

$$E_{\text{tot}}^2 = E_1^2 + E_2^2$$

If light is coherent

$$E_{\text{Tot}}^2 = (E_1 + E_2)^2$$

$$= E_1^2 + E_2^2 + \underbrace{2E_1 E_2 \cos \phi}$$


is source  
of interference

Fringes


Coherent light ~~is~~ <sup>is</sup> in phase both

spatially and temporally

Spatial Phase

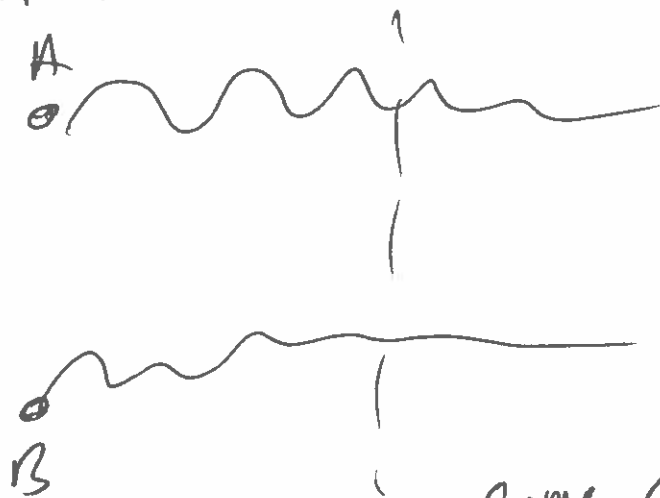

Travel same distance  
They are in phase

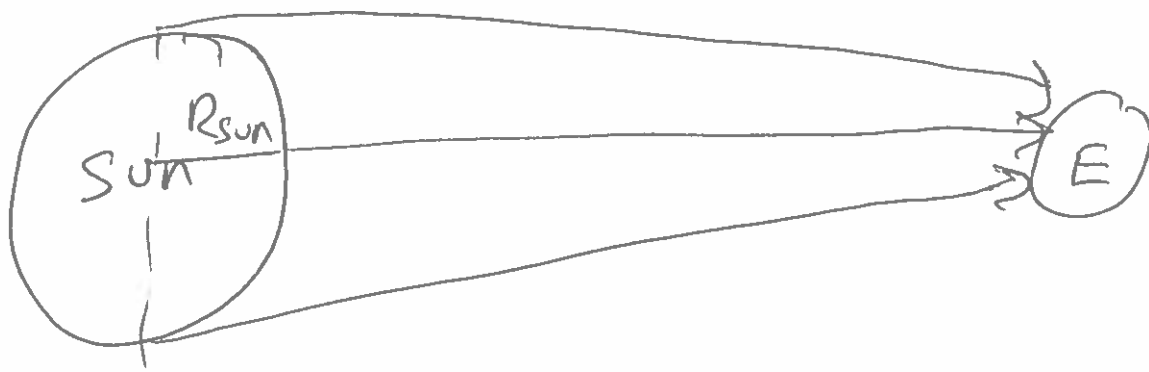

$$R_{\text{sun}} \sim 10^8 \text{ m}$$

Light from edge of sun hitting  
 Earth same time as light from center  
 traveled  $\sim 10^8 \text{ m}$  more

So it is 1-3 seconds older than  
 light from center  $\Rightarrow$  not in phase  
 because of time difference.

Young  
 Double slit

