

Find current, Power and energy
for a capacitor $(C=5mF)$ with a voltage
profile shown (on next page) Book ex ~~7-3-2~~
7-3-2

Use 3 data points

$$(0,0), (2,100), (3,50)$$


$$(y - y_1) = \frac{(y_2 - y_1)}{(x_2 - x_1)} (x - x_1)$$

$$y - 0 = \frac{(100 - 0)}{(2 - 0)} (x - 0)$$

$$\Rightarrow y = 50x$$

$$(y - 100) = \frac{(50 - 100)}{3 - 2} (x - 2)$$

$$y = -50x + 200$$

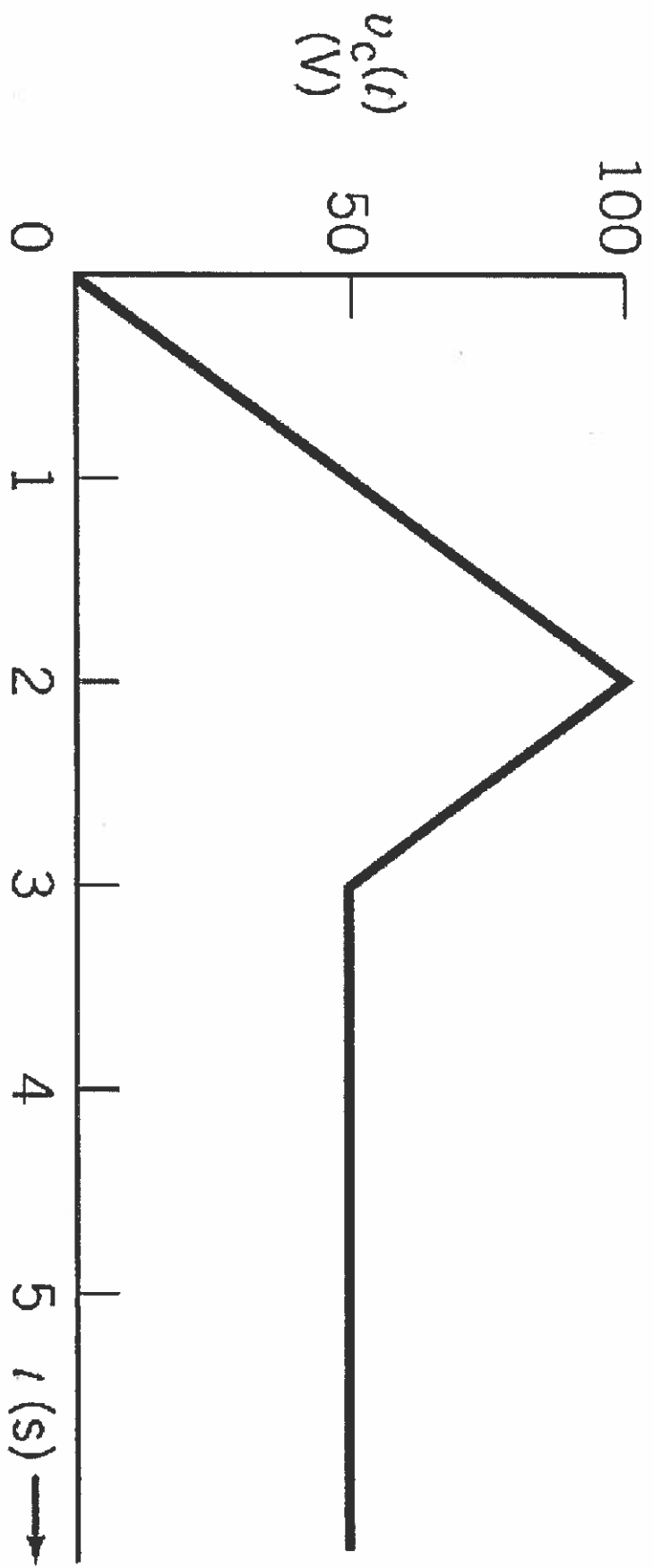

07-03-03

$$V_c(t) = \begin{cases} 50 \text{ V} & 0 \leq t \leq 2 \text{ s} \\ -50 \text{ V} + 200 \text{ V} & 2 \text{ s} \leq t \leq 3 \text{ s} \\ 50 \text{ V} & t \geq 3 \text{ s} \end{cases}$$

$$i_c = C \frac{dV_c}{dt} = 5 \text{ mF} \begin{cases} \frac{d}{dt}(50t) & 0 \leq t \leq 2 \\ \frac{d}{dt}(-50t + 200) & 2 \leq t \leq 3 \\ 0 & t \geq 3 \end{cases}$$

$$i_c = \begin{cases} 5 \times 10^{-3} (50) & \text{mA} = 0,25 \text{ A} & 0 \leq t \leq 2 \\ 5 \times 10^{-3} (-50) & \text{mA} = -0,25 \text{ A} & 2 \leq t \leq 3 \\ 5 \times 10^{-3} (0) & = 0 \text{ A} & t \geq 3 \text{ s} \end{cases}$$

$$\text{Power} = iV$$

$$P = \begin{cases} 0,25A (50t) & 0 \leq t \leq 2s \\ -0,25A (-50t + 200) & 2s \leq t \leq 3s \\ 0 & (50) \end{cases} = \begin{cases} 12,5t \text{ W} & 0 \leq t \leq 2s \\ 12,5t - 50 \text{ W} & 2s \leq t \leq 3s \\ 0 & \text{W } t \geq 3s \end{cases}$$

$$W \Rightarrow W(t) - W(a) = \int_a^t P(t) dt$$

$0 \leq t \leq 2s$

$$W(t) - W(0s) = \int_0^t 12,5t dt = 6,25t^2 - 0$$

$$W(t) = 6,25t^2 \text{ (J)} \quad 0 \leq t \leq 2s$$

$$W(0) = 0 \quad \checkmark$$

$$W(2) = 6,25(2)^2 = 25 \text{ J}$$

$$2 \leq t \leq 3 \text{ s}$$

$$W(t) - W(2) = \int_2^t (2.5t - 50) dt$$

$$W(t) - 25 \text{ J} = 6.25 t^2 \Big|_2^t - 50t \Big|_2^t$$

$$W(t) = 25 \text{ J} + 6.25 t^2 - \underbrace{25 \text{ J}}_{6.25(2)^2} - 50t + \underbrace{50}_{100}$$

$$W(t) = 6.25 t^2 - 50t + 100 \text{ J}$$

$$W(3) = 6.25(3)^2 - 50(3) + 100 \text{ J}$$


$$\begin{array}{r} \cancel{48.75} \quad \quad \quad - 50 \text{ J} \\ \hline \cancel{25} \quad 56.25 \text{ J} \end{array}$$

$$\underline{W(3) = 6.25 \text{ J}}$$


$$W(t) - W(3) = \int_3^t 0 \, d\tau = 0$$

$$W(t) = W(3) = 6.25 \text{ J} \quad \text{for } t \geq 3 \text{ s}$$

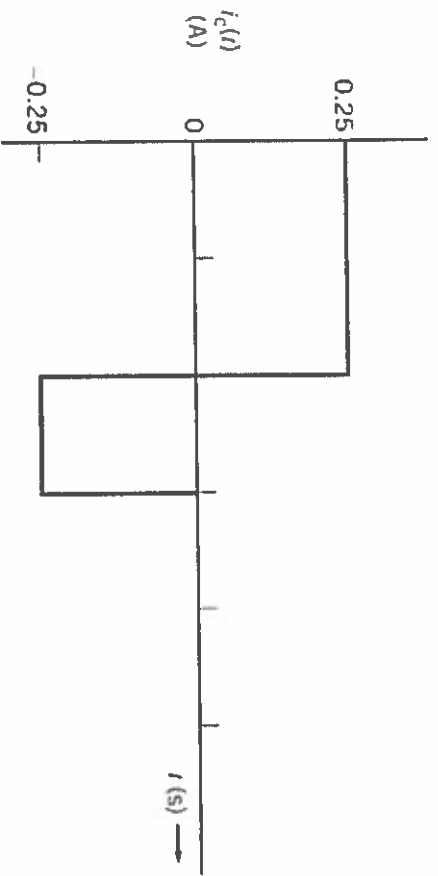
$$W(t) = \begin{cases} 6.25 t^2 \text{ J} & 0 \leq t \leq 2 \text{ s} \\ 6.25 t^2 - 50t + 100 \text{ J} & 2 \text{ s} \leq t \leq 3 \text{ s} \\ 6.25 \text{ J} & t \geq 3 \text{ s} \end{cases}$$



(a)

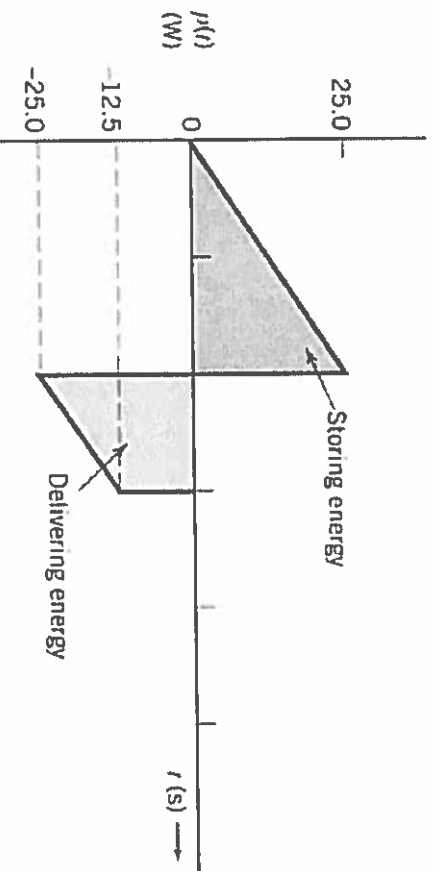

(b)

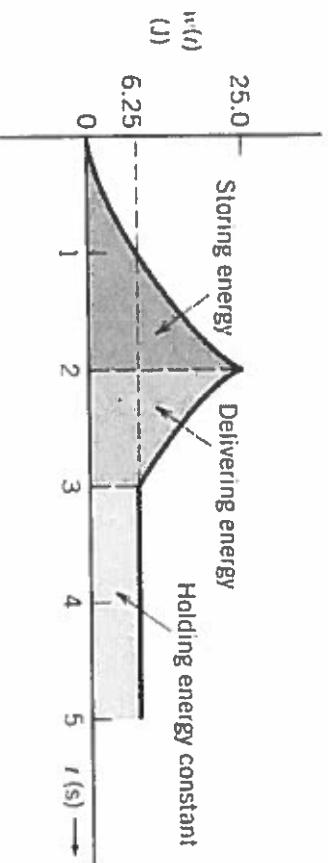

(c)

```
%Program to solve a lecture example
%version 2009-04-02 DW Donovan
clear all;

C=0.005;

t1=[0:0.01:2]';
t2=[2:0.01:3]';
t3=[3:0.01:6]';
t=[t1;t2;t3];

v1=50*t1;
v2=-50*t2+200;
v3=50*t3./t3;
v=[v1;v2;v3];

i1=C*(50)*t1./t1;
i2=C*(-50)*t2./t2;
i3=C*(0)*t3./t3;
ii=[i1;i2;i3];

p1=12.5*t1;
p2=12.5*t2-50;
p3=0*t3./t3;
p=[p1;p2;p3];

wc1=0.5*C*v1.^2;
wc2=0.5*C*v2.^2;
wc3=0.5*C*v3.^2;
wc=[wc1;wc2;wc3];

wi1=6.25*t1.^2;
wi2=6.25*t2.^2-50*t2+100;
wi3=6.25*t3./t3;
wi=[wi1;wi2;wi3];

figure
plot (t,v,'k')
ttv='Lecture Example Plotting Voltage across a 5 mF capacitor';
tn='D.W. Donovan -- ';
tttv=[ttv '\newline' tn date];
title(tttv)
xlabel('Time, t, (s)')
ylabel('Voltage, Vc, (V)')
axis([-1 7 -10 110])

figure
plot(t,ii,'k')
tti='Lecture Example Plotting Current through a 5 mF capacitor';
tn='D.W. Donovan -- ';
ttti=[tti '\newline' tn date];
title(ttti)
```


```
xlabel('Time, t, (s)')
ylabel('Current, ic, (A)')
axis([-1 7 -0.3 0.3])
```

```
figure
plot(t,p,'k')
ttp='Lecture Example Plotting Power to a 5 mF capacitor';
tn='D.W. Donovan -- ';
tttp=[ttp '\newline' tn date];
title(tttp)
xlabel('Time, t, (s)')
ylabel('Power, P, (W)')
axis([-1 7 -30 30])
```


```
figure
plot(t,wc,'k')
ttwc='Lecture Example Plotting Energy in a 5 mF capacitor using (1/2)CV^{2}';
tn='D.W. Donovan -- ';
ttwc=[ttwc '\newline' tn date];
title(tttwc)
xlabel('Time, t, (s)')
ylabel('Energy, W, (J)')
axis([-1 7 -5 30])
```

```
figure
plot(t,wi,'k')
ttwi='Lecture Example Plotting Energy in a 5 mF capacitor using integral of Power';
tn='D.W. Donovan -- ';
ttwi=[ttwi '\newline' tn date];
title(tttwi)
xlabel('Time, t, (s)')
ylabel('Energy, W, (J)')
axis([-1 7 -5 30])
```

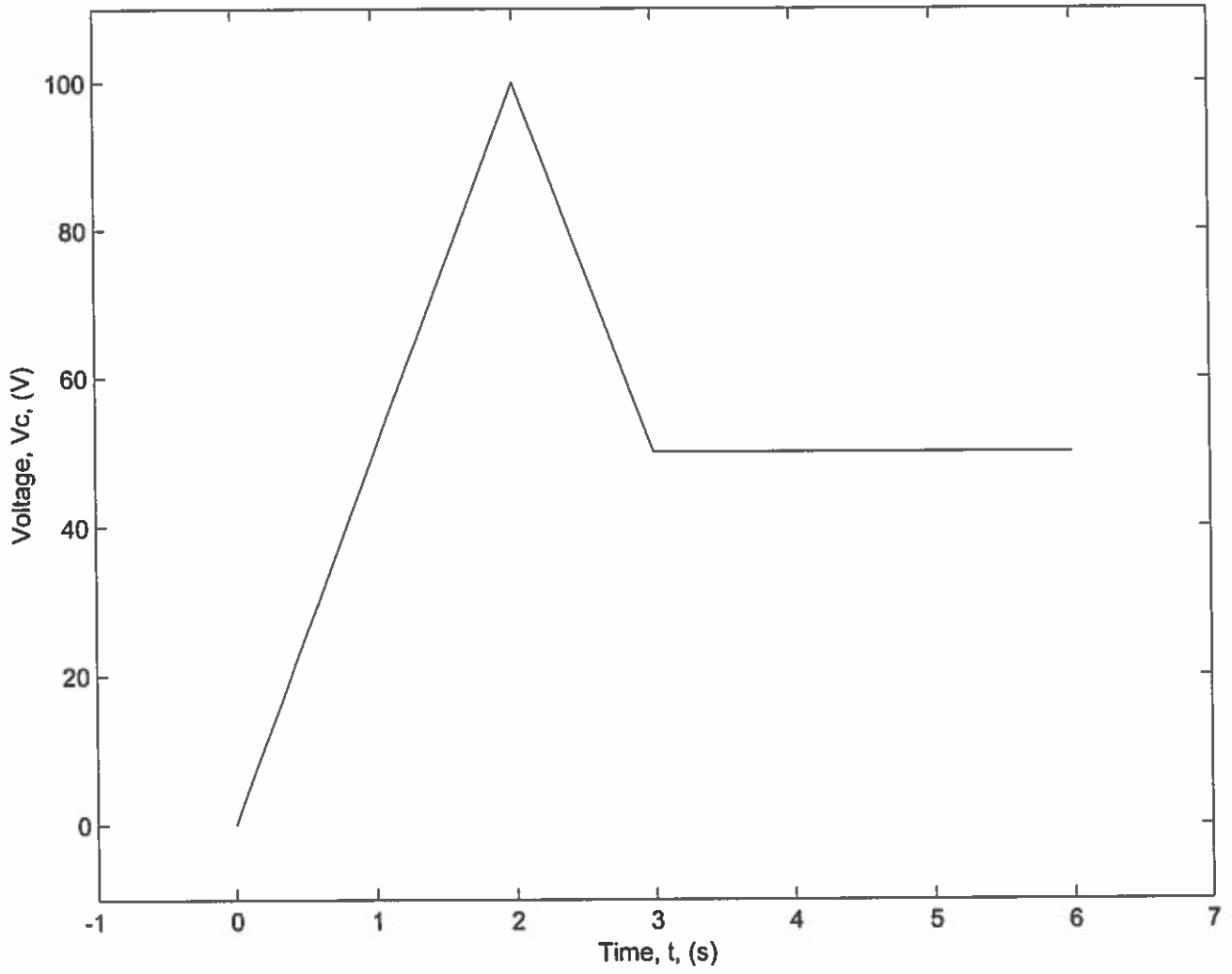
Lecture Example Plotting Voltage across a 5 mF capacitor
D.W. Donovan -- 02-Apr-2009



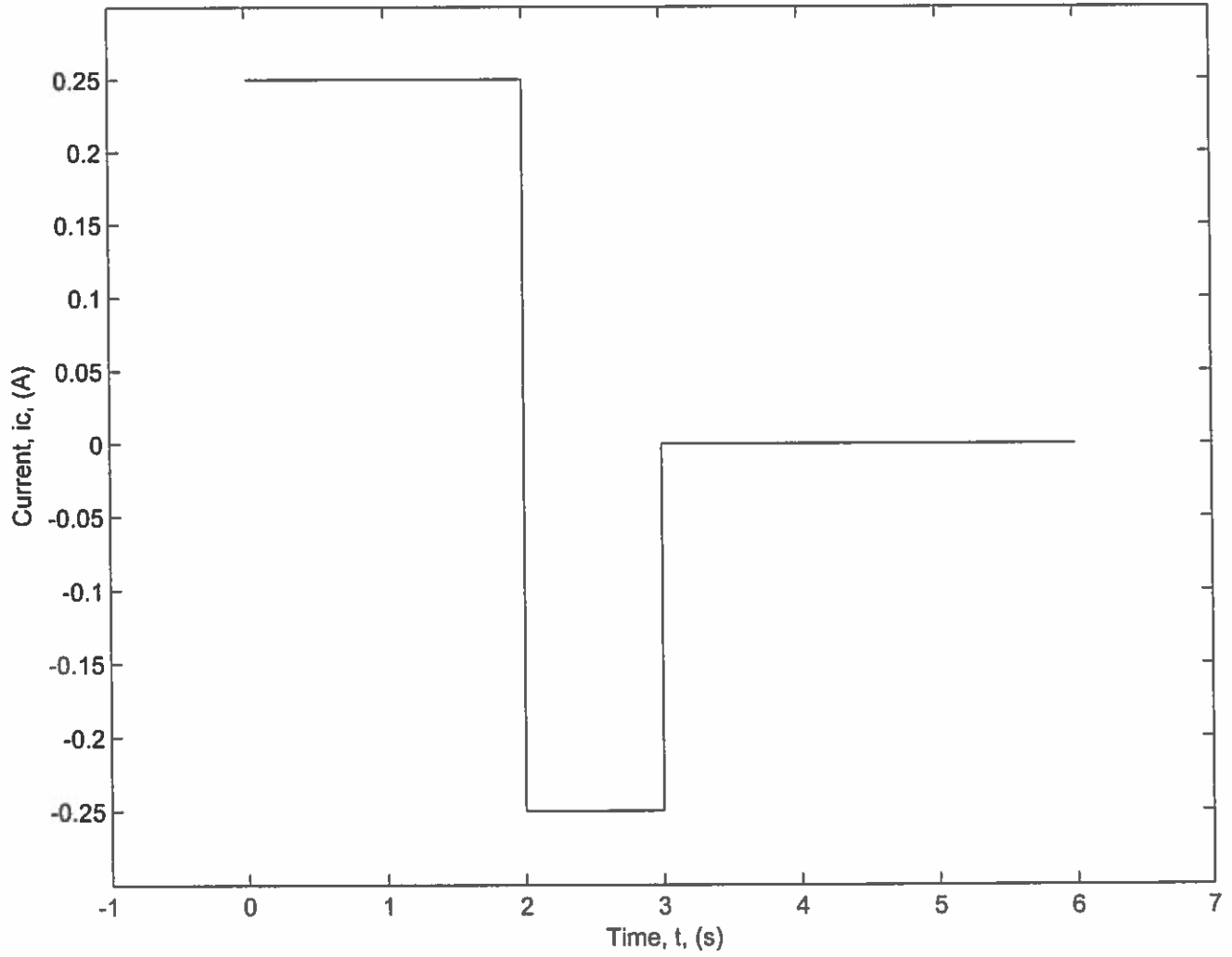
Lecture Example Plotting Current through a 5 mF capacitor
D.W. Donovan -- 02-Apr-2009



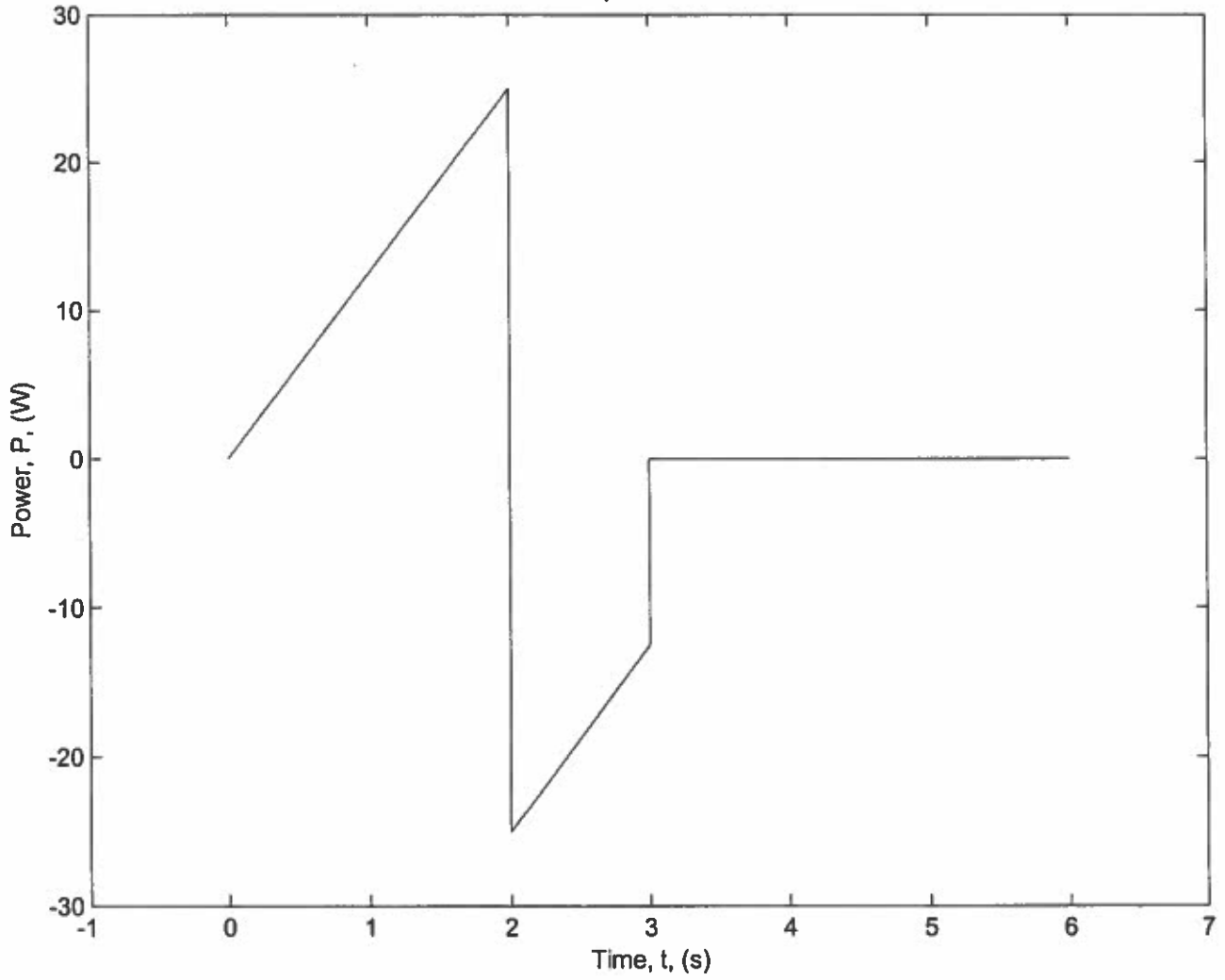
Lecture Example Plotting Power to a 5 mF capacitor
D.W. Donovan -- 02-Apr-2009



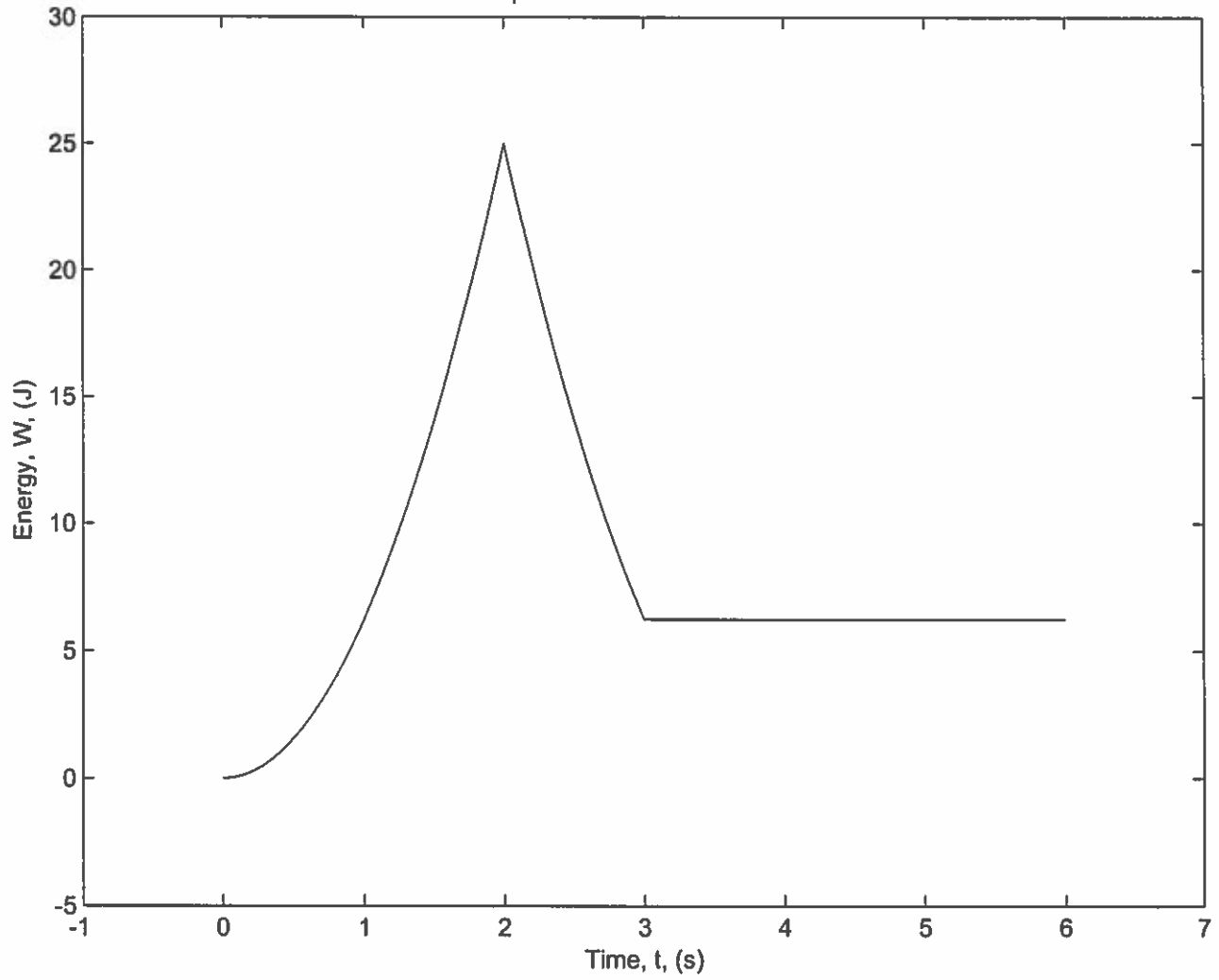Lecture Example Plotting Energy in a 5 mF capacitor using $(1/2)CV^2$
D.W. Donovan -- 02-Apr-2009



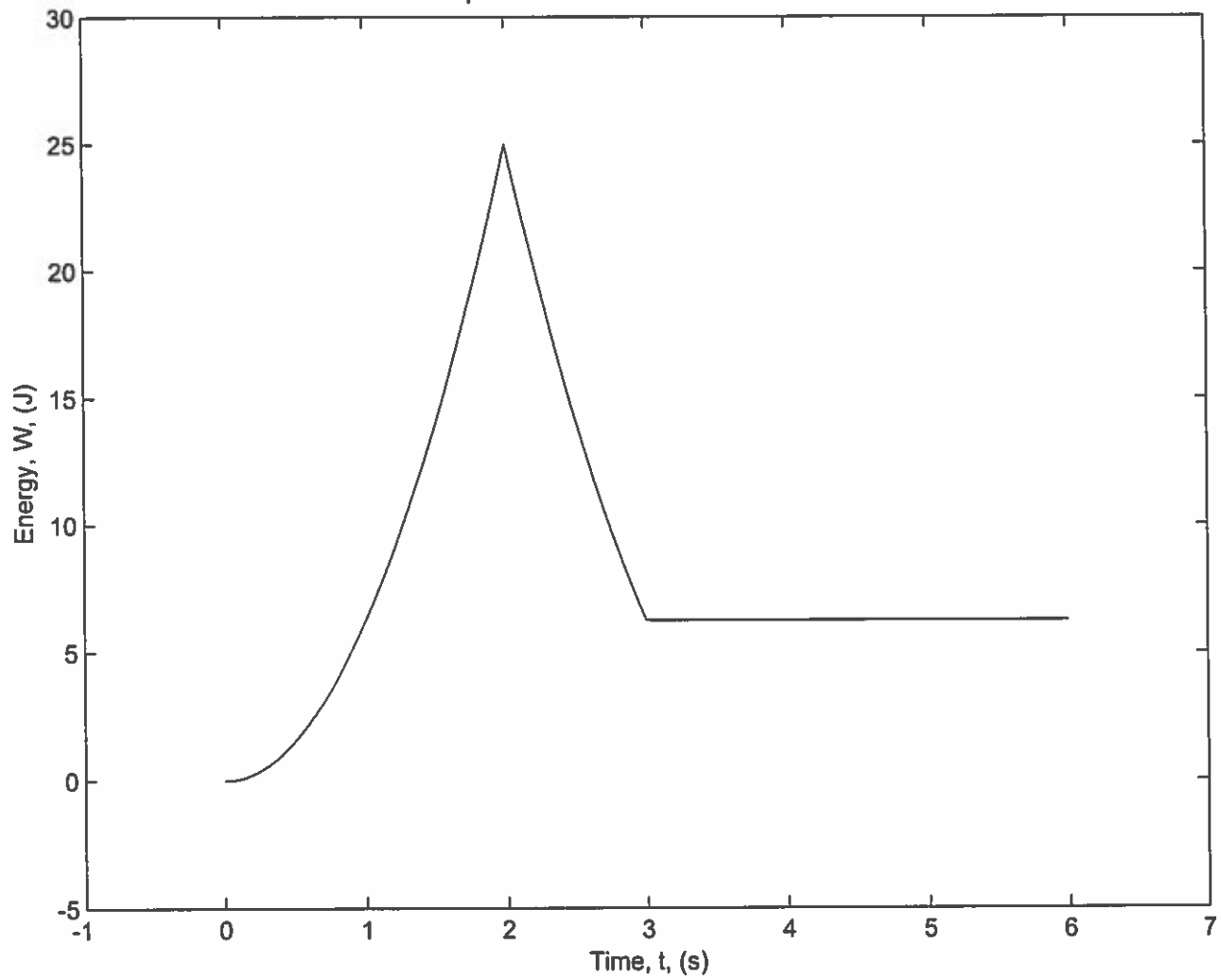
Lecture Example Plotting Energy in a 5 mF capacitor using integral of Power
D.W. Donovan -- 02-Apr-2009



$$i \Rightarrow Q = \int i dt$$

$$V = \frac{Q}{C} = \frac{1}{C} \int i dt$$

Capacitors in series / parallel

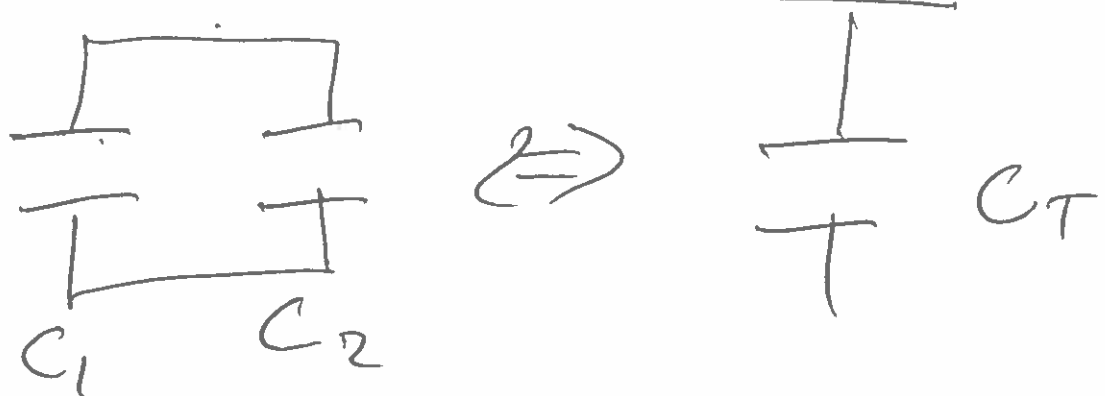


$$V_1 = V_2 = V_{\text{eff}}$$

Voltages
must equilibrate

$$\frac{Q_1}{C_1} = \frac{Q_2}{C_2} = \frac{Q_{\text{eff}}}{C_{\text{eff}}}$$

$$Q_1 + Q_2 = C_1 V + C_2 V \Rightarrow (C_1 + C_2) V$$
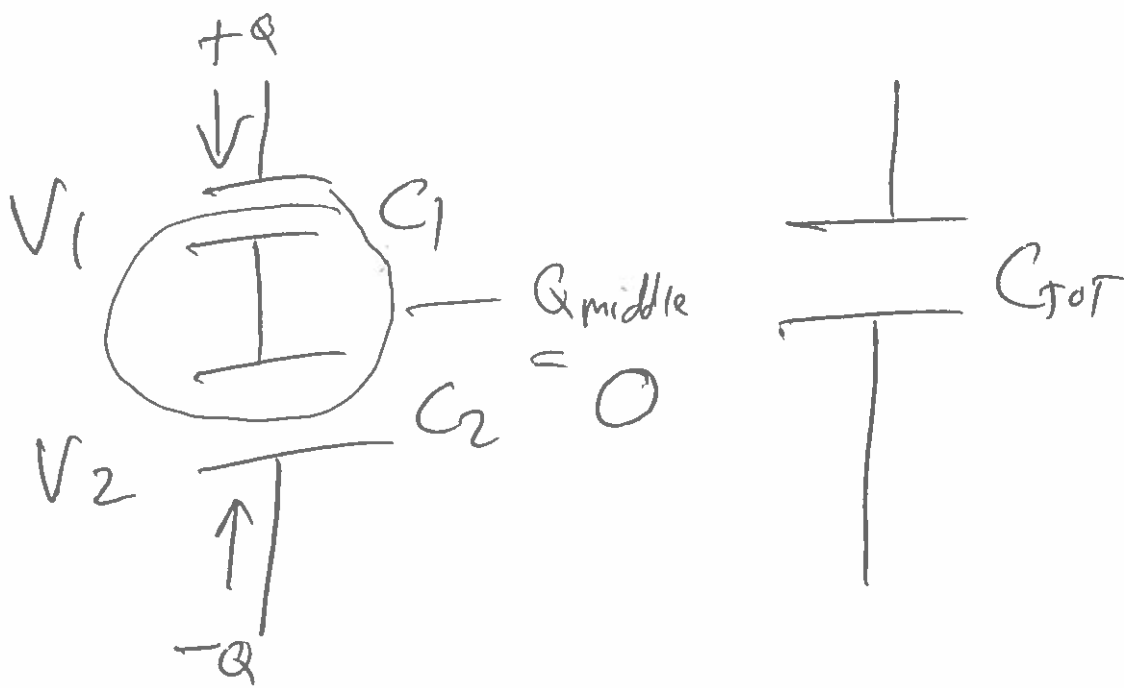
$$C_{\text{TOT}} = C_1 + C_2 + \dots + C_n \quad \text{Parallel}$$



$$V_{\text{TOT}} = V_1 + V_2 = \frac{Q}{C_1} + \frac{Q}{C_2} = \frac{Q}{C_{\text{TOT}}}$$

$$\frac{1}{C_{\text{TOT}}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_n}$$

~~Parallel~~
Series


Inductors are typically coils

that induce currents due to Faraday's Law

Faraday's Law $\mathcal{E} = -N \frac{d\Phi_B}{dt}$



EMF \mathcal{E} is similar but different

from voltage

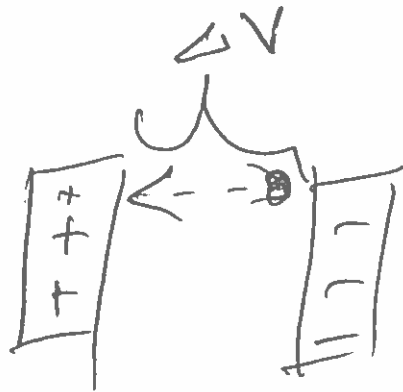

$\Delta V > 0$ implies going from - plate
to positive plate

\vec{E} goes from + \rightarrow -

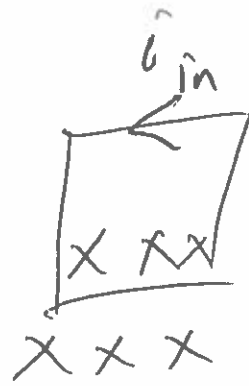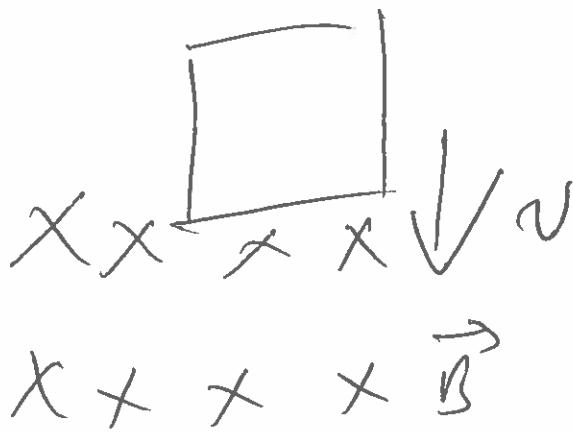

Which
way
is i_{ind} .

Magnetic flux $\Phi_B = \int \vec{B} \cdot d\vec{A}$
is increasing

So induced Field wants to
oppose increase in Φ_B so

$B_{induced}$ points out of paper (1)

Now i_{ind} to create B_{ind}

MUST go counter clockwise