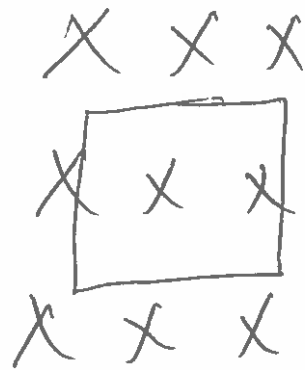


Which way
is i_{ind} .

magnetic flux $\Phi_B = \int \vec{B} \cdot d\vec{A}$
is increasing

So induced Field wants to
oppose increase in Φ_B so
 $B_{induced}$ points out of paper (1)


Now i_{ind} to create B_{ind}
MUST go counter clockwise



What is the direction of current induced at this point?

There is no change in Φ_B

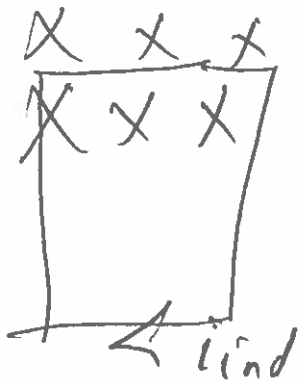So No induced E field or emf
and therefore No current induced.




What is direction of induced current now?

Φ_B is decreasing induced B must add to existing $B \Rightarrow i_{ind}$ clockwise


What is difference between induced \vec{E} and static E fields?

induced \vec{E} are NOT conservative!

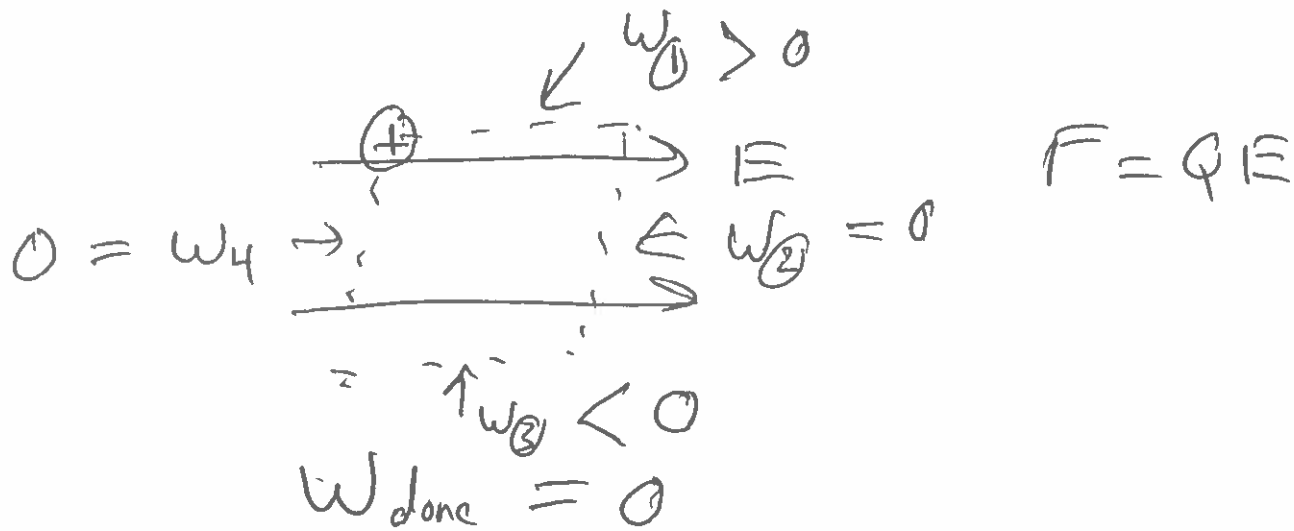

i_{ind}
 \vec{E}_{in}

Self-inductance

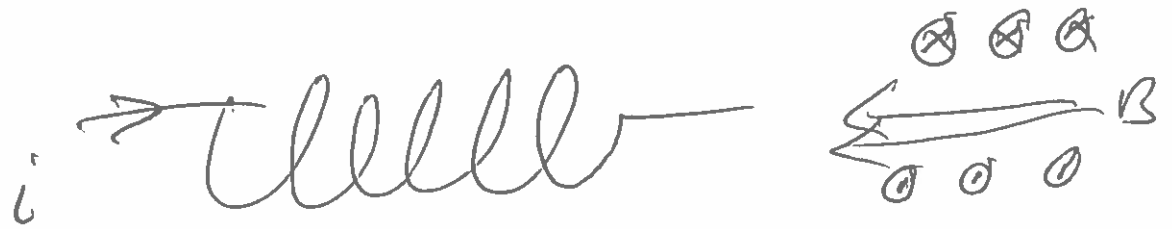

When i first starts $\Delta \Phi_B$

\dot{I}_{induced} opposes \dot{I}_{wire}

So \dot{I}_{induced} tries to prevent \dot{I}_{wire} from changing

After long time what is $\Delta \Phi_B = 0$

So $\dot{I}_{\text{ind}} = 0$

Coil acts like short circuit

if i_{wire} drops $\Delta \Phi_B$ does change

it gets weaker so i_{ind} goes

in same direction as i_{wire}

Inductors try to maintain constant

current in a circuit

Similar to capacitors trying to maintain

constant voltage.

$$V_L = L \frac{di}{dt}$$

L is self-inductance (inductance)

it has units of Henrys (H)

Faraday Tells us

$$\mathcal{E} = -N \frac{d\Phi_B}{dt}$$

$$\mathcal{V} = \mathcal{E} = -N \frac{d}{dt} (\vec{B} \cdot \vec{A})$$

for a solenoid $B = \mu_0 n i = \mu_0 \frac{N}{L^*} i$

drop - sign \Rightarrow polarity

L^* - Length of Solenoid

$$\mathcal{V} = N \frac{d}{dt} \left(\frac{\mu_0 N i}{L^*} \right) = \frac{\mu_0 N^2}{L^*} \frac{di}{dt}$$

$$C = \frac{1}{\sqrt{\mu_0 \epsilon_0}}$$

$$\mathcal{V} = \left(\frac{\mu_0 N^2}{L^*} \right) \frac{di}{dt}$$

$$\mu_0 = 4\pi \times 10^{-7} \frac{T \cdot m}{A}$$

- Permeability of free space (vacuum)

$$\hat{i}_{C_{\text{cap}}} = C \frac{dV}{dt}$$

V must be
CONTINUOUS

$$V_L = L \frac{di}{dt}$$

i must be
CONTINUOUS

$$V_{C_{\text{cap}}}(t^+) = V_{C_{\text{cap}}}(t^-)$$

$$\hat{i}_L(t^+) = \hat{i}_L(t^-)$$

for inductor if i is constant

inductor acts like short-circuit

for a capacitor if V is constant

capacitor acts like an open circuit

for A.C.

X_C - capacitive reactance

$$= \frac{-i^{\sqrt{-1}}}{\omega C}$$

measured in Ω ohms

X_L - inductive reactance

$$= i^{\sqrt{-1}} \omega L$$

also measured in Ω

if $\omega \rightarrow 0$ D.C.

$X_C \rightarrow \infty$ (open circuit)

$X_L \rightarrow 0$ (short circuit)


in a capacitor voltage lags behind current.

in an inductor voltage leads current.


ELI the ICE man

What is phase relationship between
voltage and current in a resistor?

They are in phase

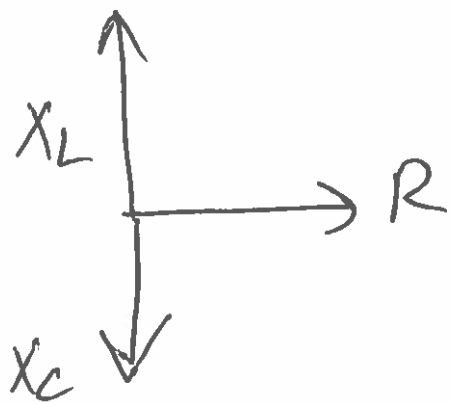

Phasor Diagram

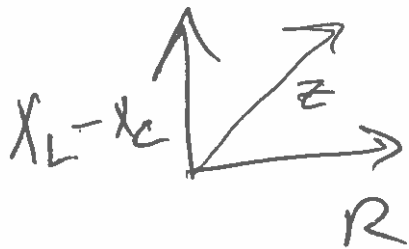

$$Z = \sqrt{(X_L - X_C)^2 + R^2}$$

Z is impedance

Z or impedance is the total opposition
to the flow of current in an A.C.
circuit.

Phasors are Pseudo vectors,

A vector is an object that transforms as a vector under coordinate rotation.

$$Z = \sqrt{(x_L - x_C)^2 + R^2}$$

min $Z \Rightarrow$ if $x_L - x_C = 0$

$$x_L = \omega L$$

$$x_C = \frac{1}{\omega C}$$

$$\omega L = \frac{1}{\omega C}$$

$$\omega^2 = \frac{1}{LC}$$

$$x_L - x_C = \omega L - \frac{1}{\omega C}$$

$$\omega_0 = \sqrt{\frac{1}{LC}}$$

Resonance frequency is $\min Z$


$$\omega_0 = \sqrt{\frac{1}{LC}}$$

$$V = L \frac{di}{dt}$$

$$di = \frac{V}{L} dt$$

$$i_{ind} = \frac{1}{L} \int_{t_0}^t v dt + i(t_0)$$
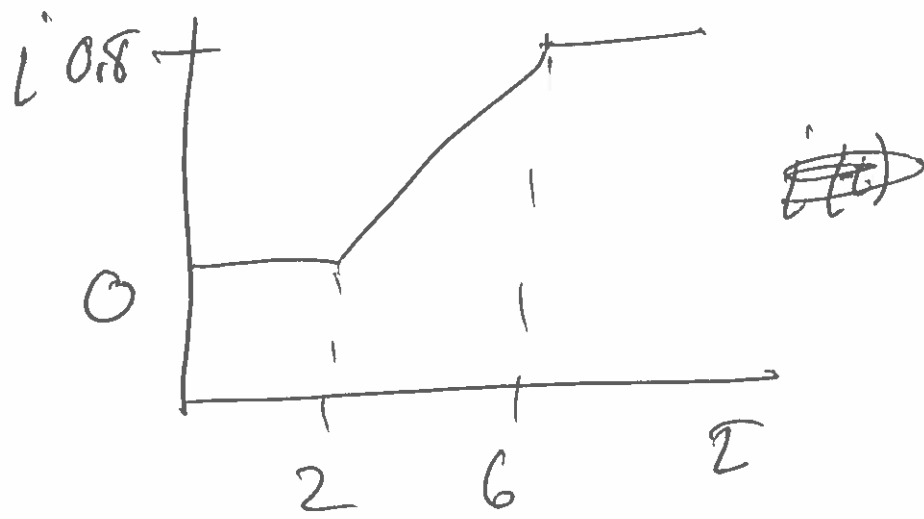
$$V_{cap} = \frac{1}{C} \int_{t_0}^t i dt + v(t_0)$$



$$i(t) = \begin{cases} 0 & 0 \leq t < 2 \text{ s} \\ 0.2t - 0.4 & 2 \text{ s} \leq t < 6 \text{ s} \\ 0.8 & t \geq 6 \text{ s} \end{cases}$$

$$L = 0.5 \text{ H}$$

$$v_L(t) = ?$$

$$\frac{di}{dt} = \begin{cases} 0 & 0 \leq t \leq 2s \\ 0.2t & 2s \leq t \leq 6s \\ 0 & t \geq 6s \end{cases}$$

$$v = L \frac{di}{dt} = \begin{cases} 0 & \cancel{0 \leq t \leq 2s} \quad 0 \leq t \leq 2s \\ 0.1 & 2s \leq t \leq 6s \\ 0 & t \geq 6s \end{cases}$$

What if instead

$$v_L = \begin{cases} 0 & 0 \leq t \leq 2s \\ 0.2t - 0.4 & 2s \leq t \leq 6s \\ 0.8 & t \geq 6s \end{cases}$$

$$i(t) = \frac{1}{L} \int v dt + i(t_0)$$