

$$\frac{di}{dt} = \begin{cases} 0 & 0 \leq t \leq 2s \\ 0.2t & 2s \leq t \leq 6s \\ 0 & t \geq 6s \end{cases}$$

$$v = L \frac{di}{dt} = \begin{cases} 0 & \cancel{0 \leq t \leq 2s} \quad 0 \leq t \leq 2s \\ 0.1 & 2s \leq t \leq 6s \\ 0 & t \geq 6s \end{cases}$$

What if instead

$$v_L = \begin{cases} 0 & 0 \leq t \leq 2s \\ 0.12t - 0.4 & 2s \leq t \leq 6s \\ 0.8 & t \geq 6s \end{cases}$$

$$L = 0.5H$$

$$i(0^-) = 0$$

$$i(t) = \frac{1}{L} \int v dt + i(t_0)$$

$$0 \leq t \leq 2s$$

$$v(t) = 0 \Rightarrow i(t) = 0$$

$$i(2s) = 0$$

$$\dot{i}(6s) = 3,2 \text{ A}$$

$$t \geq 6$$

$$i(t) = \int_6^t 0,8 dt + \underbrace{i(6)}_{3,2 \text{ A}}$$

$$i(t) = \frac{(\frac{1}{15})}{2} (0,8t)^2 + 3,2 \text{ A}$$

$$i(t) = 1,6(t-6) + 3,2 \text{ A}$$

$$= 1,6t - 9,6 + 3,2$$

$$= 1,6t - 6,4$$

$$i(6) = 1,6(6) - 6,4 = 9,6 - 6,4 = 3,2 \checkmark$$

$$2s \leq t \leq 6s$$

$$i(t) = \frac{1}{L} \int_2^t (0,2\tau - 0,4) d\tau + i(2s)$$

$$i(t) = \frac{1}{15H} \left[0,1t^2 - 0,4t \right]_2^t + 0$$
$$= 2 \left[0,1t^2 - 0,4t - (0,1(2)^2 - 0,4(2)) \right]$$

$$= 2 (0,1t^2 - 0,4t - \underbrace{(-0,4)}_{-1,4})$$


$$i(t) = 0,2t^2 - 0,8t + 0,8$$

$$i(2) = 0,2(2^2) - 0,8(2) + 0,8$$
$$0,8 - 0,8(2) + 0,8 = 0 \checkmark$$

$$i(6) = 0,2(6^2) - 0,8(6) + 0,8$$
$$7,2 - \del{4,8} + 0,8 \Rightarrow 3,2$$

$$\dot{L}(t) = \begin{cases} 0 & \underline{0 \leq t \leq 2} \\ 0.2t^2 - 0.8t + 0.8 & \\ 1.6t - 6.4 & \end{cases}$$
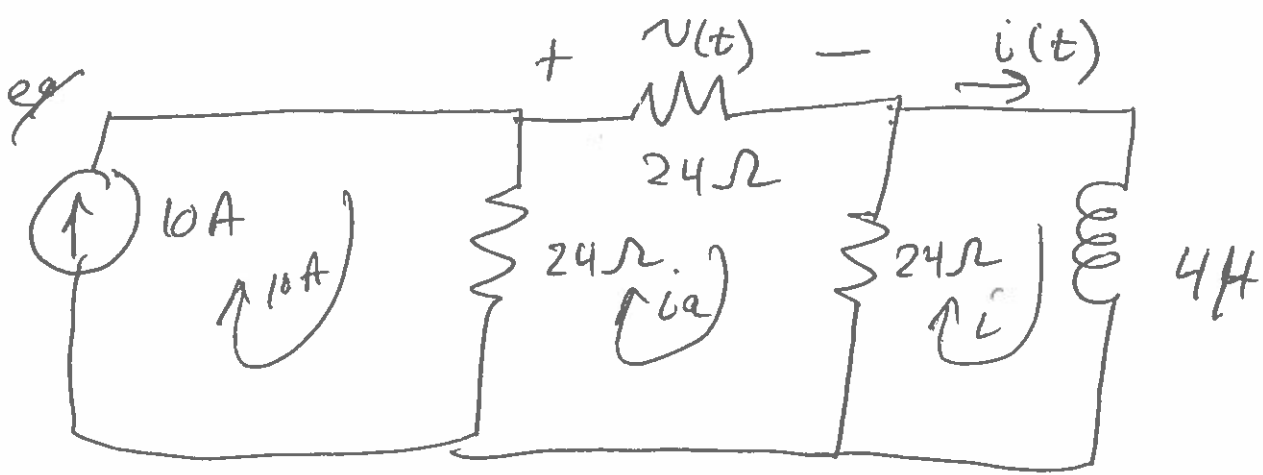
$$A \quad \begin{cases} 0 \leq t \leq 2 \\ 2 \leq t \leq 6 \\ t \geq 6 \end{cases}$$



$$i(t) = 5 - e^{-4t} \text{ A for } t \geq 0$$

$$v(t) = ?$$

$$v(t) = i_q (24\Omega)$$

$$0 = i_q (24\Omega + 24\Omega + 24\Omega)$$

$$- 10\text{A}(24\Omega) - i(t)(24\Omega)$$

$$i_q (3) = +10\text{A} + (5 - e^{-4t}) = 15\text{A} - e^{-4t} \text{ A}$$

$$i_q = 15\text{A} - \frac{1}{3}e^{-4t} \text{ A} = 5\text{A} - \frac{1}{3}e^{-4t} \text{ A}$$

$$v(t) = 24\Omega \left(5 - \frac{1}{3}e^{-4t} \right) \text{ A} = \underline{120 - 8e^{-4t}} \text{ V}$$


$$P = v i = \frac{d}{dt} L i i$$

$$W = \int P dt = L \int i di$$

$$W_L = \frac{1}{2} L i^2$$

$$W_C = \frac{1}{2} C V^2$$


inductors in Series / Parallel

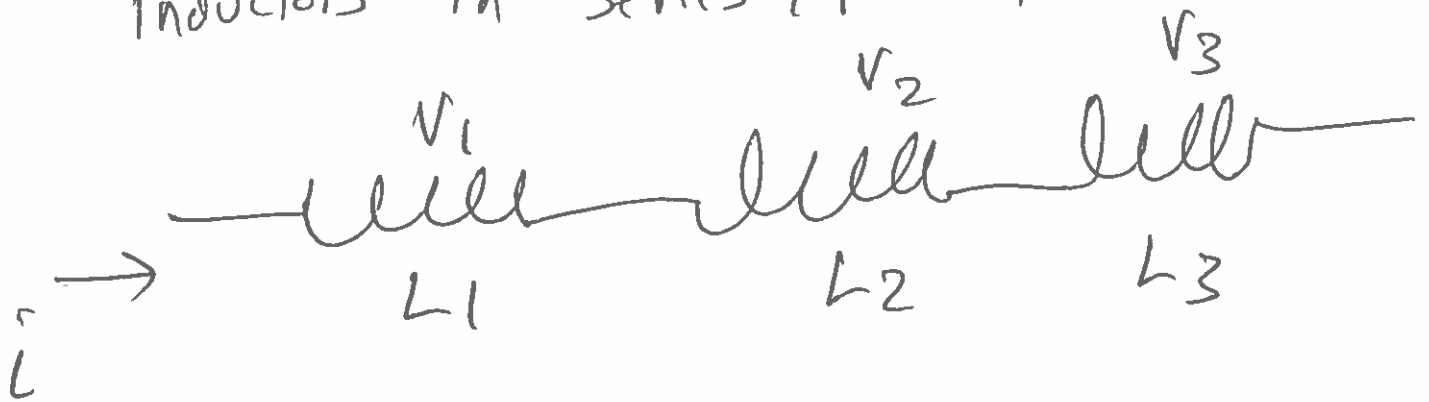

$$V_{\text{total}} = V_1 + V_2 + V_3$$

$$L_{\text{TOT}} \frac{di}{dt} = L_1 \frac{di}{dt} + L_2 \frac{di}{dt} + L_3 \frac{di}{dt}$$
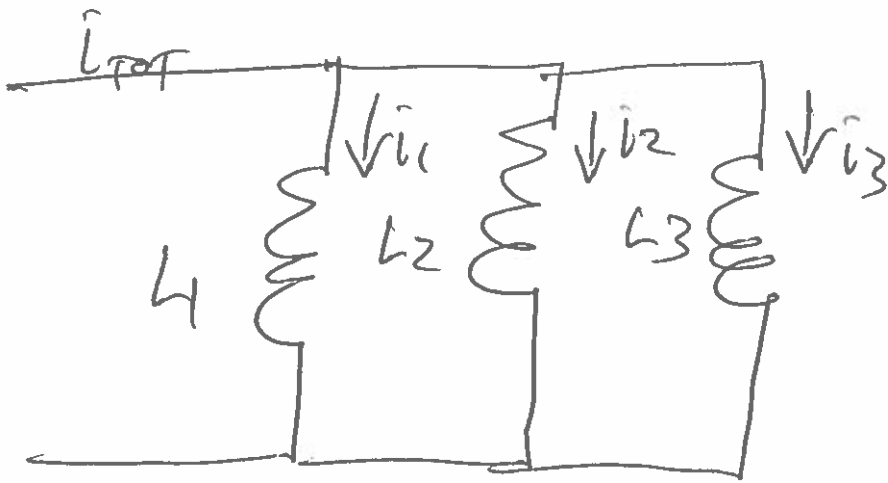
$$L_{\text{TOT series}} = L_1 + L_2 + L_3$$



$$i_{tot} = i_1 + i_2 + i_3$$

$$\frac{1}{L_{tot}} \int v_{tot} d\tau = \frac{1}{L_1} \int v_1 d\tau + \frac{1}{L_2} \int v_2 d\tau + \frac{1}{L_3} \int v_3 d\tau$$

but $v_{tot} = v_1 = v_2 = v_3$

$$\Rightarrow \frac{1}{L_{tot \text{ parallel}}} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3}$$

CONTINUITY CONDITIONS

Remember $v_C(t_0^-) = v_C(t_0^+)$


$$i_L(t_0^-) = i_L(t_0^+)$$

VOLTAGE cannot be discontinuous across a capacitor
CURRENT cannot be discontinuous through an inductor

AT Steady State (D.C. conditions)

Inductors act like short circuits
Capacitors act like open circuits

e) Inductor only

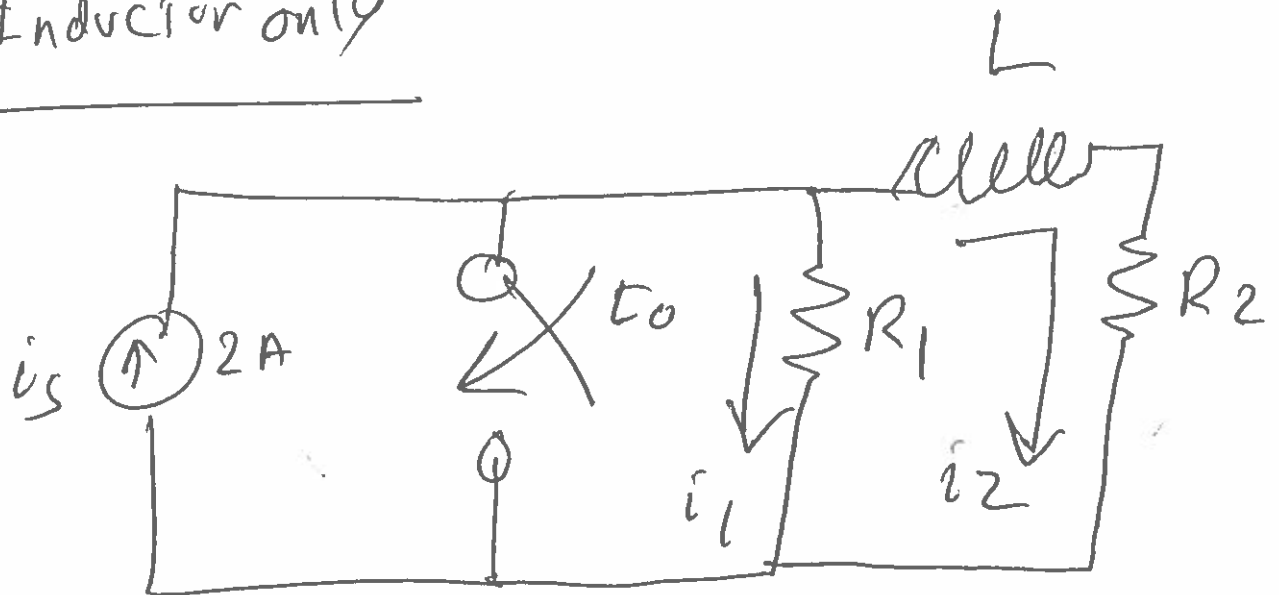

if $R_1 = R_2$ $i_1(t \leq t_0) = ?$

$i_2(t \leq t_0) = ?$

$$i_1(t < t_0) = 1 \text{ A} = i_1(t_0^-)$$

$$i_2(t < t_0) = 1 \text{ A} = i_2(t_0^-)$$

After t_0

$$i_1(t_0^+) = 0$$

$$i_2(t_0^+) = 1 \text{ A}$$

$$\tau_L = \frac{L}{R}$$

$$\hat{i}_L(t) = \hat{i}_0 e^{-t/\tau_L}$$

$$\tau_C = RC$$

$$e^{-1} = 0.37$$

$$e^{-t/\tau_C} \leftarrow \begin{array}{l} \text{time} \\ \text{constant} \end{array}$$

$$e^{-5} = \cancel{0.0067} \\ 0.0067$$

5 Time constants is time to either fully charge or fully discharge