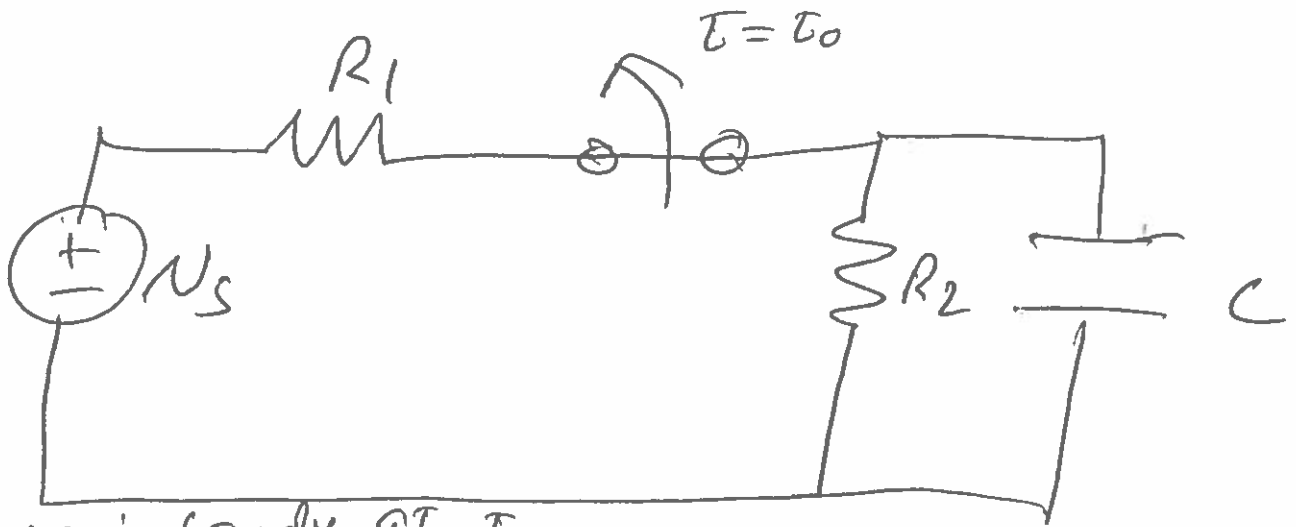


eg




Assume circuit steady at t_0

$$i_{R_2}(t_0^-) = \frac{V_S}{R_1 + R_2}$$

$$V_C(t_0^-) = i R_2 \\ = \frac{V_S R_2}{R_1 + R_2}$$

$$i_{R_2}(t_0^+) = \frac{V_S}{R_1 + R_2} = \frac{V_C}{R_2} - \frac{V_S R_2 / (R_1 + R_2)}{R_2}$$

$$i_{R_2}(t > t_0^+) \rightarrow 0$$

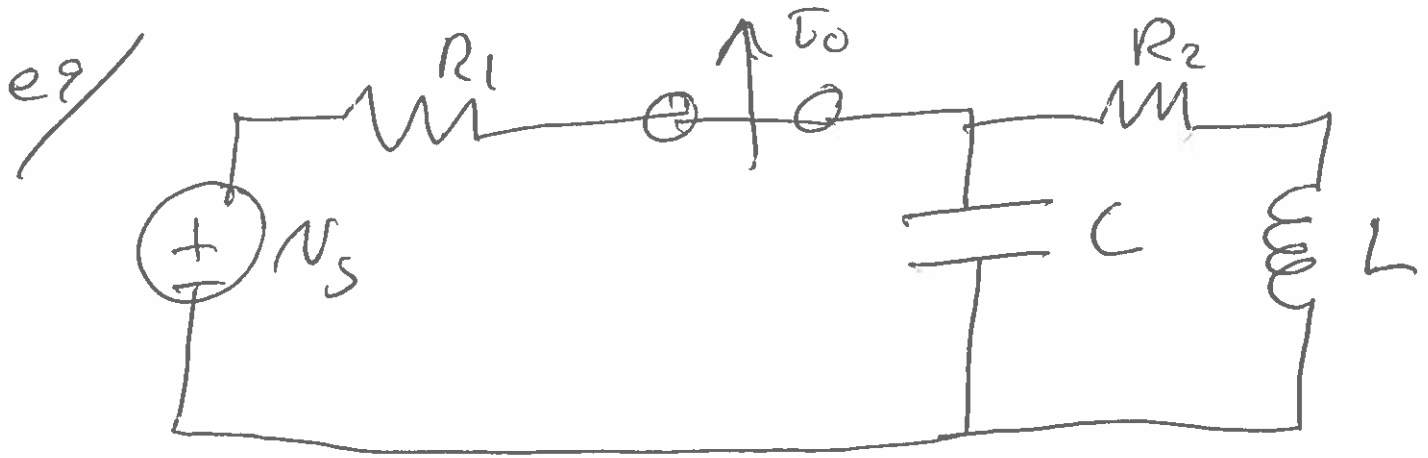


find $v_C(t_0^+)$, $i_L(t_0^+)$

$$V_S = 10 \text{ V} \quad R_1 = 2 \Omega \quad R_2 = 3 \Omega$$


$$C = 0.5 \text{ F} \quad L = 1 \text{ H}$$

Steady-state before switch opens

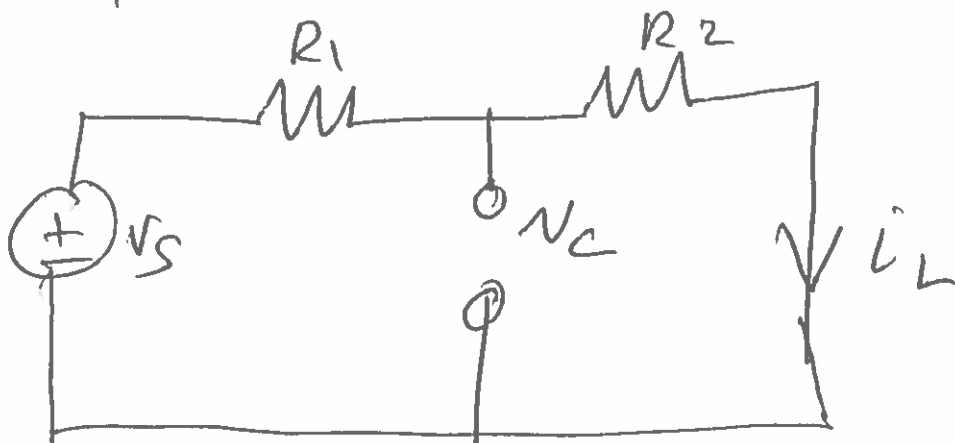

$$i_L = \frac{10 \text{ V}}{2 \Omega + 3 \Omega} = \frac{10 \text{ V}}{5 \Omega} = 2 \text{ A}$$

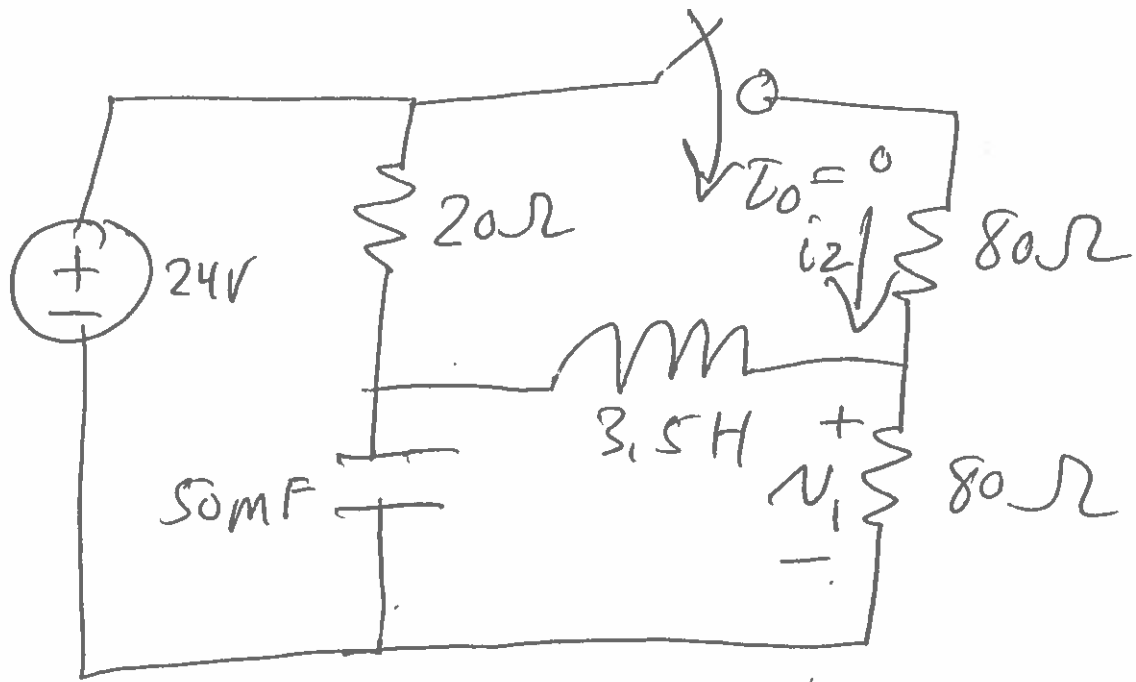
$$v_C = i_L R_2 = (2 \text{ A})(3 \Omega) = 6 \text{ V}$$



$$i_2(0_s^-) = ? \quad i_2(0_s^+) = ?$$

$$v_1(0_s^-) = ? \quad v_1(0_s^+) = ?$$

Steady state prior to $t = 0$

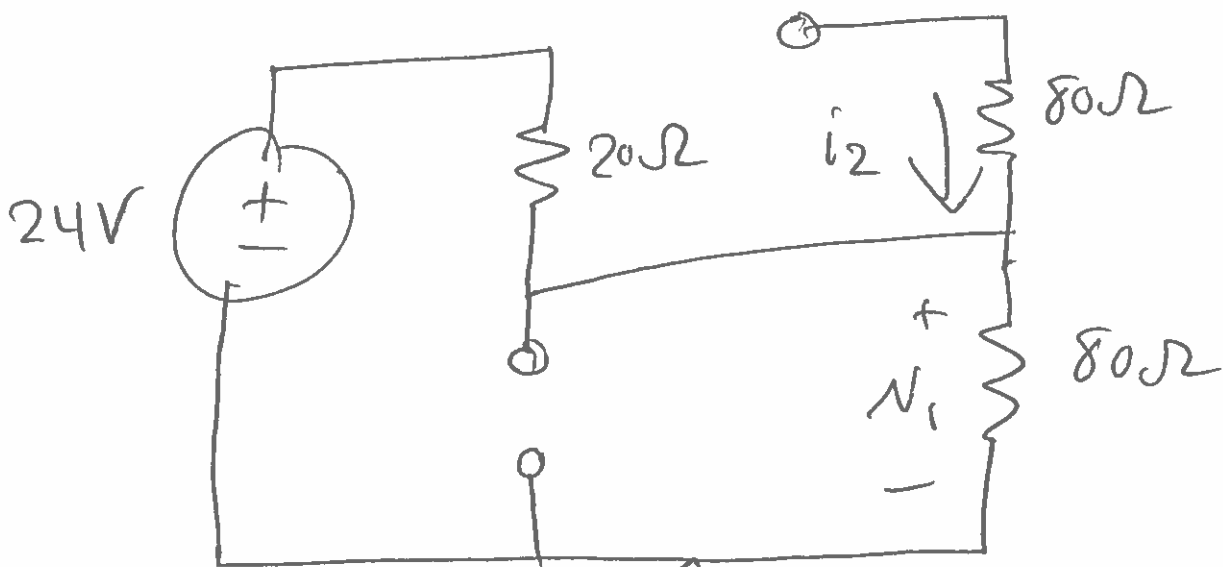


$$i_2(0_s^-) = 0$$

$$V_1(0^-) = 24V \left(\frac{80\Omega}{80\Omega + 20\Omega} \right) = 19.2V$$

$$V_1(0^-) = 19.2V$$

~~Steady~~ Circuit AS Switch Thrown

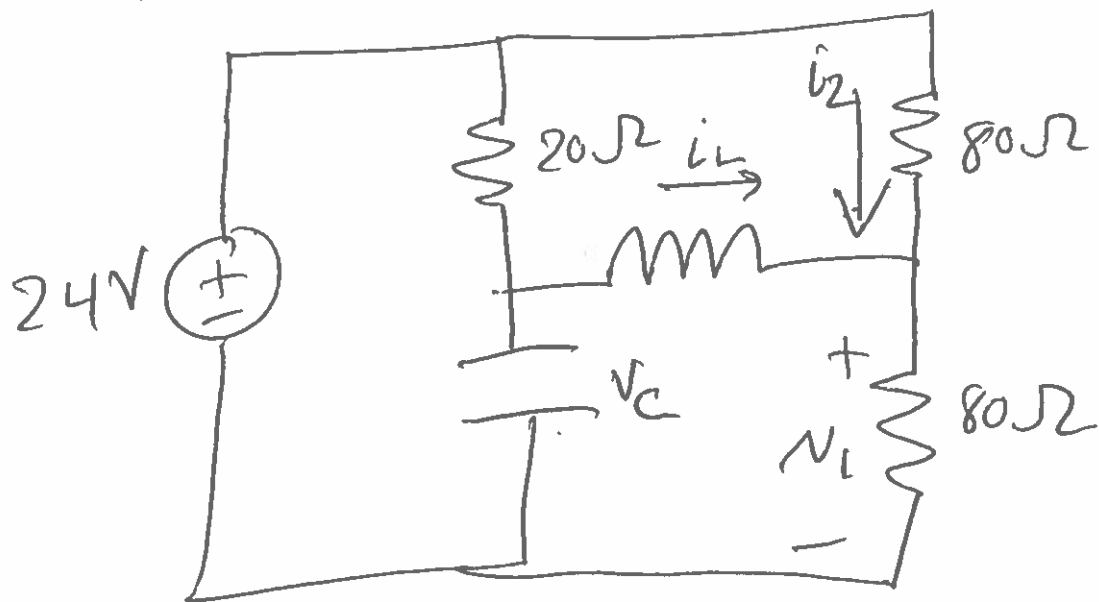

$$i_L = \cancel{0.24A} \quad V_C = 19.2V$$

$$i_2 = i_L - \frac{V_1}{80\Omega} = \cancel{0.24A}$$

Q.

$$24V = i_2 80\Omega + V_1$$

$$\cancel{i_2} = \cancel{i_L} - \frac{V_1}{\cancel{80\Omega}}$$

$$24V = i_2 80\Omega + V_1$$

$$\cancel{80\Omega i_L} = \cancel{80\Omega i_2} + V_1$$

$$i_L + i_2 = \frac{V_1}{80\Omega}$$

$$i_L = \frac{V_1}{80\Omega} - i_2$$

$$80\Omega i_L = V_1 - 80\Omega i_2$$

$$\rightarrow 24V = i_2 80\Omega + V_1$$

$$80\Omega i_L + 24V = 2V_1$$

$$80\Omega (1.24A) + 24V = 2V_1$$

$$19.2V + 24V = 43.2V = 2V_1$$

$$\rightarrow \underline{V_1 = 21.6V}$$

$$i_2 = \frac{V_1}{80\Omega} - i_L$$

$$i_2 = \frac{21.6V}{80\Omega} - 0.24A$$

$$\underbrace{0.27A}_{\text{underbrace}} - 0.24A \Rightarrow i_2 = 0.03A$$

$$i_2(0^-) = 0 \quad i_2(0^+) = 0.03A$$

$$V_1(0^-) = 19.2V \quad V_1(0^+) = 21.6V$$

$$V_L(0^-) = 0V$$


$$V_L(0^+) = 2.4V$$

$$V_L = L \frac{di}{dt}$$

$$\frac{di_L}{dt} = \frac{2.4V}{3.5H} = 0.686$$


Many
Complex
Circuits

Can be written as

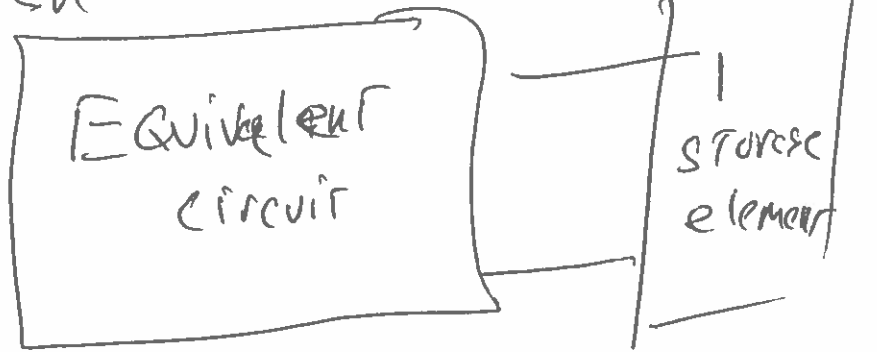


Thevenin or
Norton


When storage is a capacitor

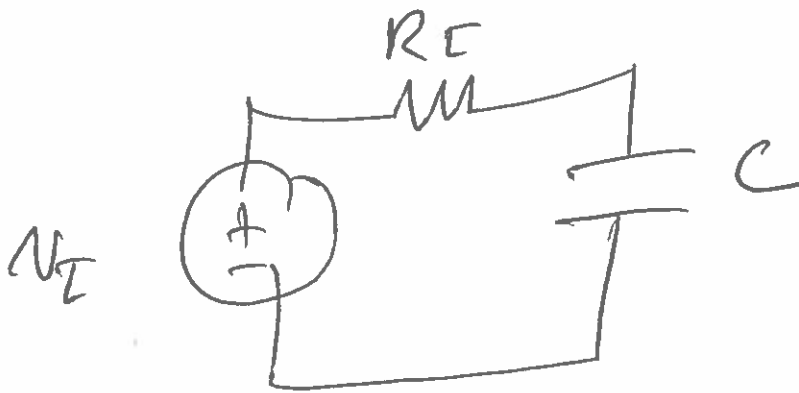

When storage is an inductor

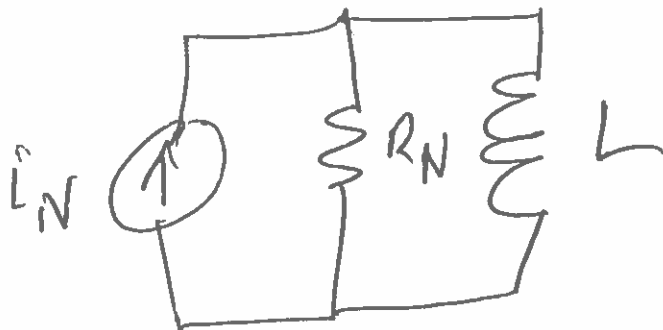

Consider Circuit

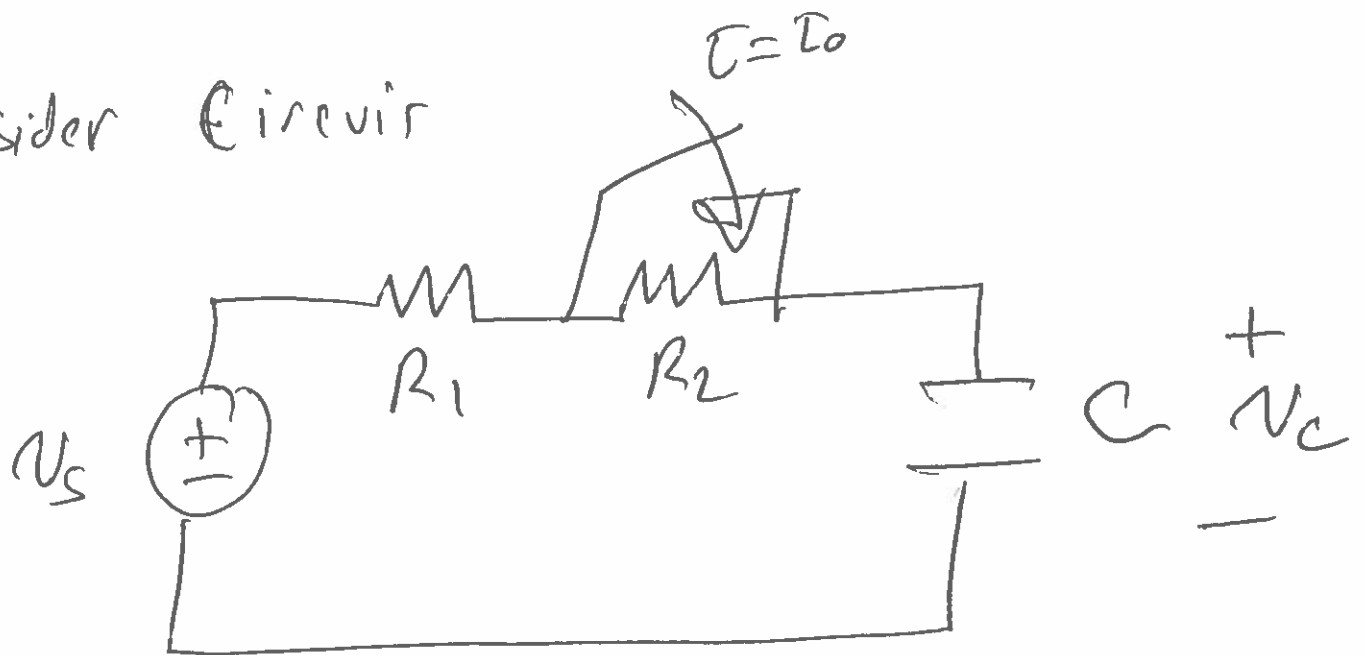

Flipping switch will change V_c

Complete Response has 2 parts

1) Steady-state after Equilibrium is reestablished

2) Transient - What happens immediately after switch is flipped

Alternatively one can consider


1) Natural response

2) Forced response


We consider 3 forcings

- 1) constant voltage - Switch flip
- 2) exponential functions
- 3) sinusoidal functions.

Consider

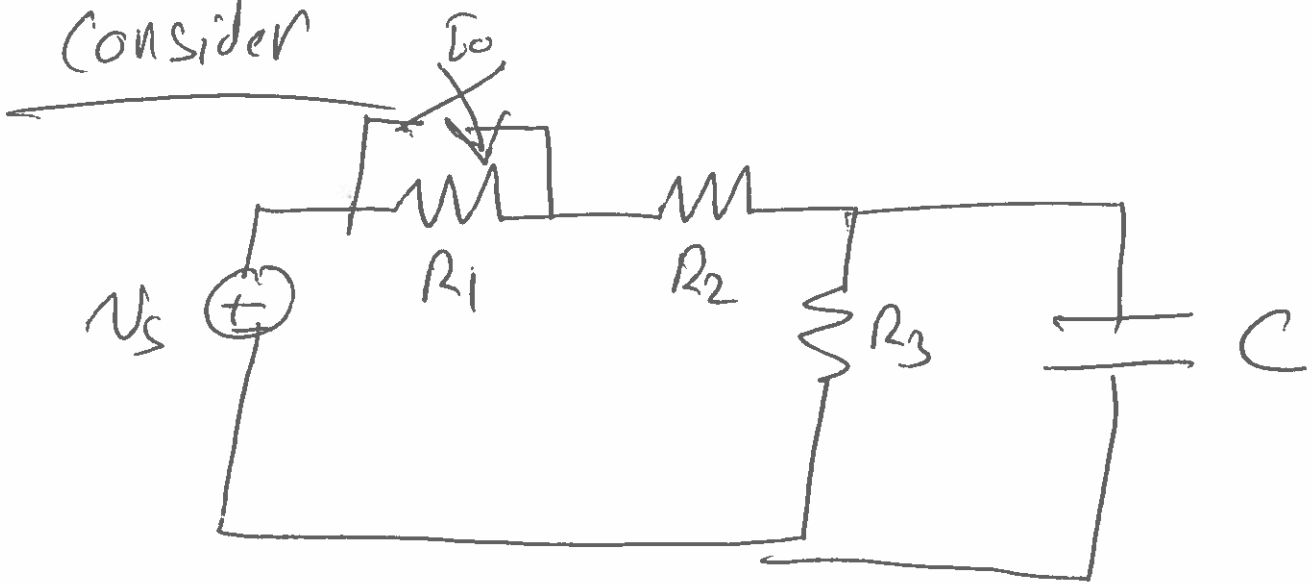

When Switch Thrown Circuit becomes

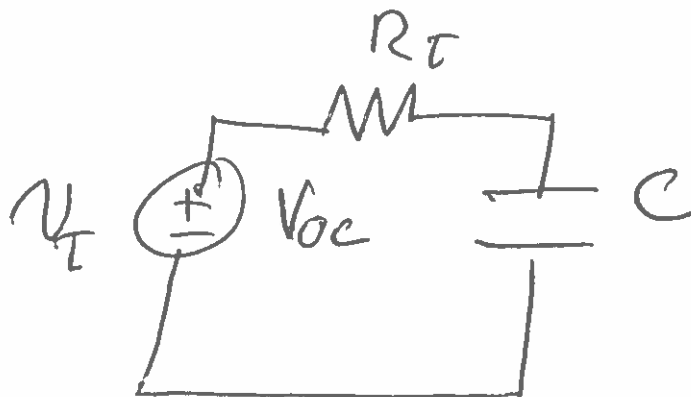

$$V_C(t_0^-) = \frac{V_S R_3}{R_1 + R_2 + R_3}$$

$$R_T = \frac{R_2 R_3}{R_2 + R_3}$$

$$V_T = V_{oc} = V_S \left(\frac{R_3}{R_2 + R_3} \right)$$

Do a voltage walk

$$V_{oc} - i R_T - V_c = 0$$


$$i = i_c = C \frac{dV_c}{dt}$$

$$\rightarrow V_{oc} - R_T C \frac{dV_c}{dt} - V_c = 0$$



$$\frac{dV_c}{dt} + \frac{1}{R_T C} V_c = \frac{V_{oc}}{R_T C}$$

$$\frac{dX(t)}{dt} + \frac{X(t)}{\tau} = K$$

Consider

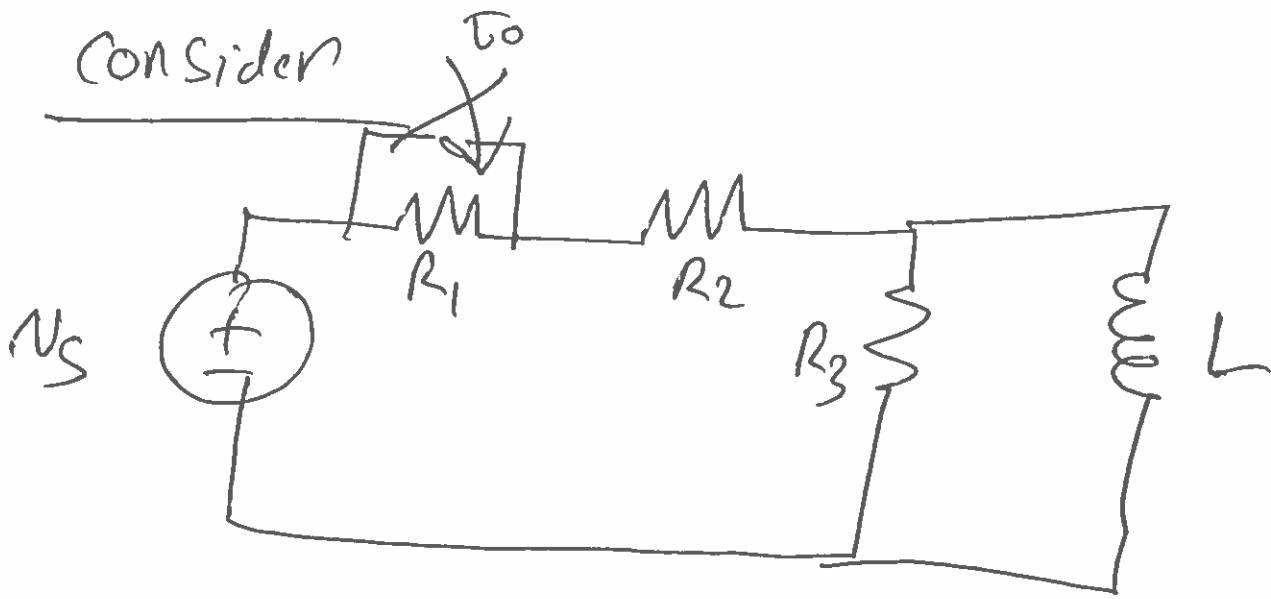

after Switch Thrown

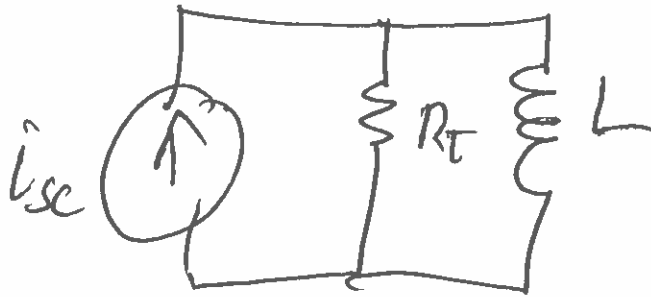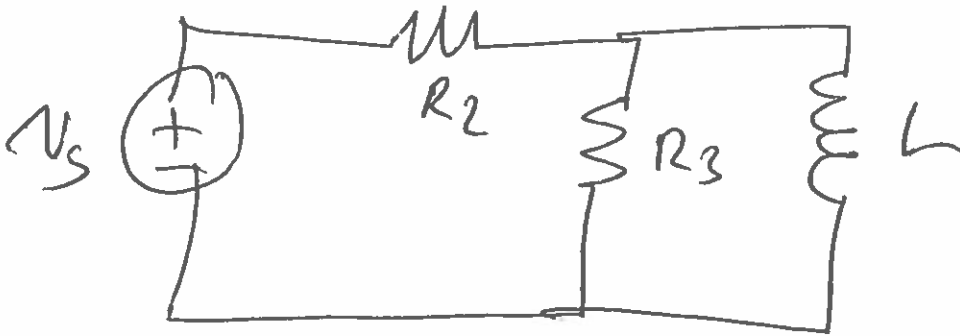

$$i_s = \frac{V_s}{R_2} \quad R_T = \frac{R_2 R_3}{R_2 + R_3}$$