
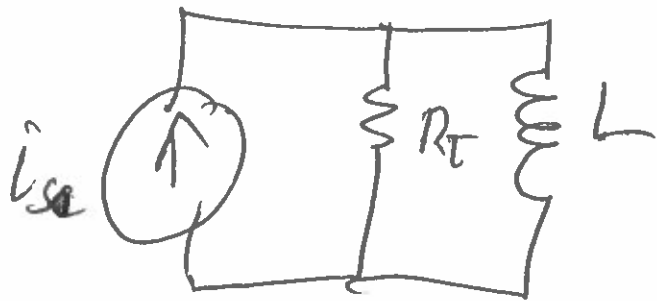


after Switch Thrown

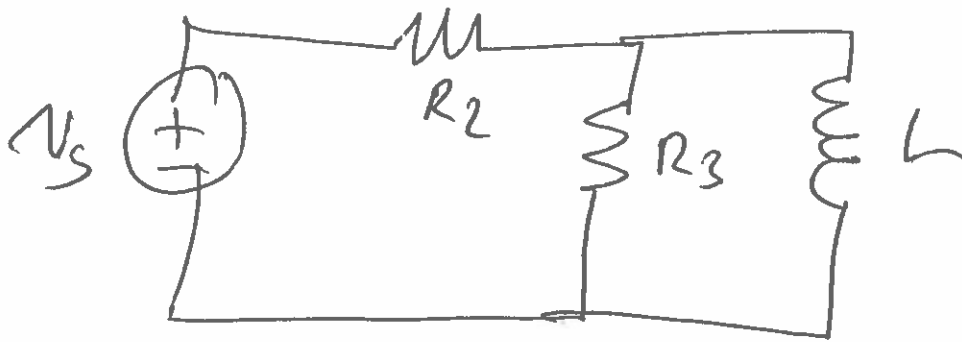

$$i_S = \frac{V_S}{R_2} \quad R_T = \frac{R_2 R_3}{R_2 + R_3}$$

$$i_S = i_R + i_L$$

$$i_R = \frac{V_L}{R_T} \quad V_L = L \frac{di}{dt}$$

$$\dot{i}_R = \frac{L}{R_T} \frac{d\dot{i}_L}{dt}$$

$$\dot{i}_S = \frac{L}{R_T} \frac{d\dot{i}_L}{dt} + \dot{i}_L$$

~~$$\frac{d\dot{i}_L}{dt} = \frac{R_T}{L} \dot{i}_S$$~~

$$\frac{d\dot{i}_L}{dt} + \frac{R_T}{L} \dot{i}_L = \frac{R_T}{L} \dot{i}_S$$

$$v_{L_L} = \frac{L}{R}$$

$$\frac{di_L}{dt} + \frac{1}{\tau} i_L = \frac{i_s}{\tau} = K$$

$$\frac{dx}{dt} + \frac{x(t)}{\tau} = K$$

- same form
as capacitor
on Monday

$$\frac{dx(t)}{dt} = K - \frac{x(t)}{\tau}$$

$$\frac{dx(t)}{dt} = \frac{K\tau - x(t)}{\tau}$$

$$\frac{dx(t)}{K\tau - x(t)} = \frac{dt}{\tau}$$

$$\int \frac{dx(t)}{x(t) - k\tau} = \int \frac{-dt}{\tau}$$

$$\ln(x - k\tau) = -\frac{t}{\tau} + D$$

\uparrow
 integration
 constant

$$e^{\ln(x - k\tau)} = e^{(-t/\tau + D)}$$

$$x - k\tau = e^D e^{-t/\tau}$$

$$x(t) = k\tau + A e^{-t/\tau}$$

initial conditions $\Rightarrow x(0)$ at $t=0$

$$x(0) = k\tau + A e^0 = k\tau + A$$

$$x(0) = k\tau + A$$

$$qT \quad t = \infty$$

$$X(\infty) = k\tau + A e^{-\infty/\tau} = k\tau$$

$$X(t) = k\tau + A e^{-t/\tau}$$

$$k\tau = X(\infty)$$


$$X(0) = k\tau + A \Rightarrow A = X(0) - X(\infty)$$

$$A = X(0) - X(\infty) \quad \cancel{k\tau} \quad k\tau = X(\infty)$$

$$X(t) = X(\infty) + (X(0) - X(\infty)) e^{-t/\tau}$$

↑
LONG TERM
STEADY STATE
SOLUTION
(FORCED)

↑
TRANSIENT
SOLUTION
(NATURAL)

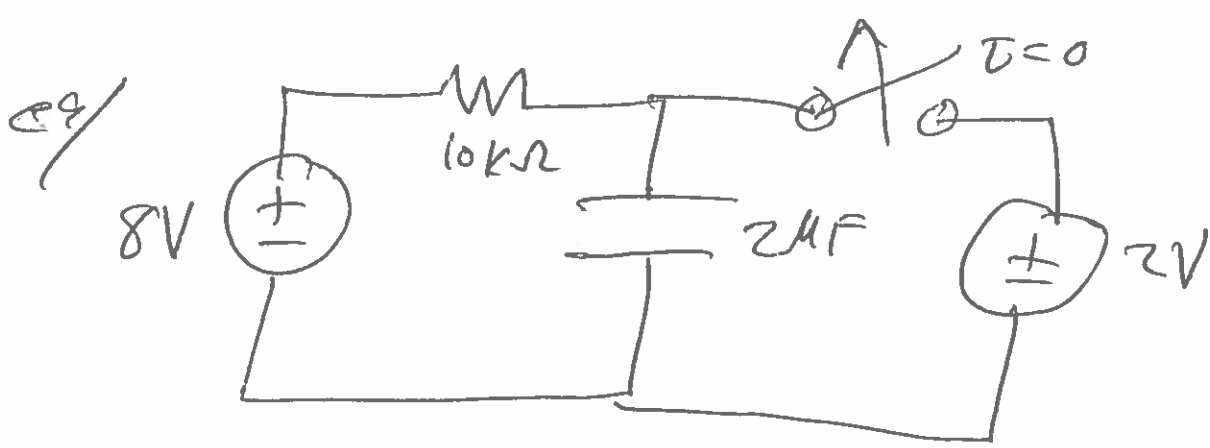

$$V_C(t) = ?$$

$$\text{at } t = 0 \quad V_C(0) = 2V$$

$$\text{at } t = \infty \quad V_C(\infty) = 8V$$

$$R_t = 10k\Omega$$

~~$$V(t) = 8V + (2V - 8V) e^{-t / (10k\Omega \cdot 2\mu F)}$$~~

$$V(t) = 8V - 6V e^{-t / 0.20s}$$

$$t = 0 \Rightarrow V(t) = 8 - 6V e^0 = 2VV$$

$$t = \infty \Rightarrow V(t) = 8V - 6V e^{-\infty} = 8VV$$

If we have non constant power sources

$$\frac{dx(t)}{dt} + ax(t) = y(t)$$

$a = \frac{1}{\tau}$ previously $y(t) = K$

Integrating factor $e^{\int a dt} = e^{at}$

$$\frac{dx(t)}{dt} e^{at} + ax e^{at} = y e^{at}$$

$$\frac{d}{dt} (x e^{at}) = y e^{at}$$

$$\int d(x e^{at}) = \int y e^{at} dt$$

$$X e^{a\tau} = \int y(t) e^{a\tau} d\tau + K$$

$$X(t) = e^{-a\tau} \int y(t) e^{a\tau} d\tau + K e^{-a\tau}$$

Check if $y(t) = M = \text{constant}$

$$X(t) = e^{-a\tau} \int M e^{a\tau} d\tau + K e^{-a\tau}$$

$\underbrace{\hspace{10em}}$
 $e^{-a\tau} \frac{M}{a} e^{a\tau}$

$$X(t) = \frac{M}{a} + K e^{-a\tau} \quad a = \frac{1}{\tau}$$

$$X(t) = M\tau + K e^{-\tau/\tau}$$

$$X(t) = X(\infty) + (X(0) - X(\infty)) e^{-\tau/\tau}$$

$y(t) \neq \text{constant}$

$$x(t) = x_F + x_n$$


$$x(t) = \underbrace{e^{-a\tau} \int y(t) e^{a\tau} dt}_{x_F} + \underbrace{K e^{-\tau/\tau_c}}_{x_n}$$

typical non constant forcing functions

are \sin , \cos , e

Use $x_F = A \cos(\omega t) + B \sin(\omega t)$

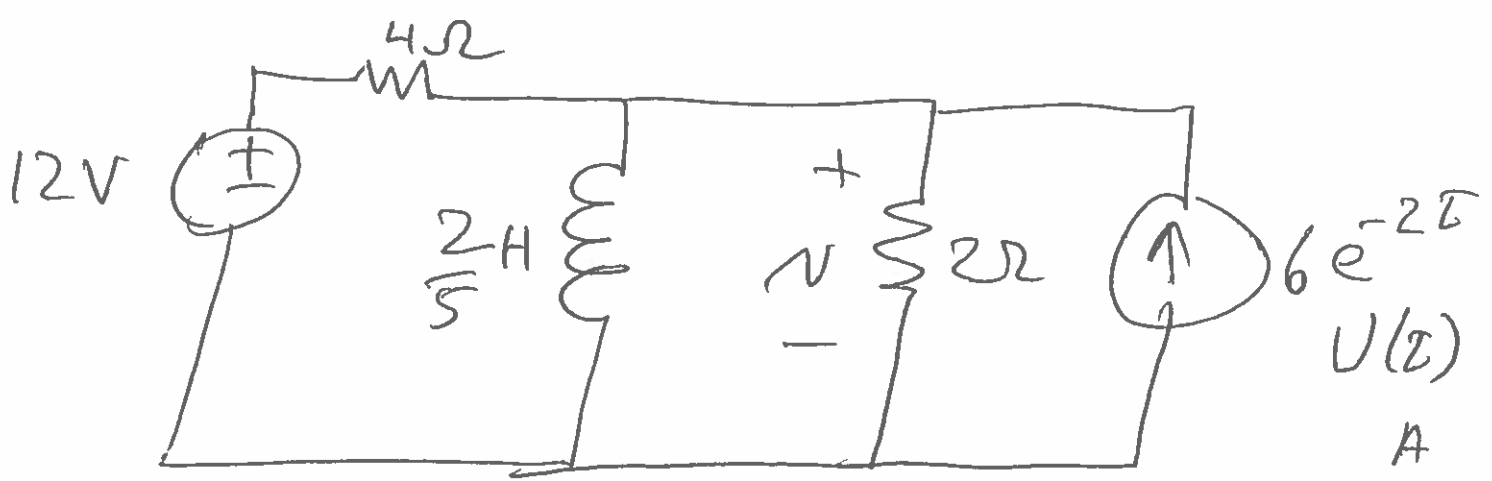
Solve diff-ee and Apply Boundary
or time conditions.



$$U(t-t_0) = 0 \quad t < t_0 = 1 \quad t \geq t_0$$

↑
STEP FUNCTION


$t < 0$ Circuit looks like

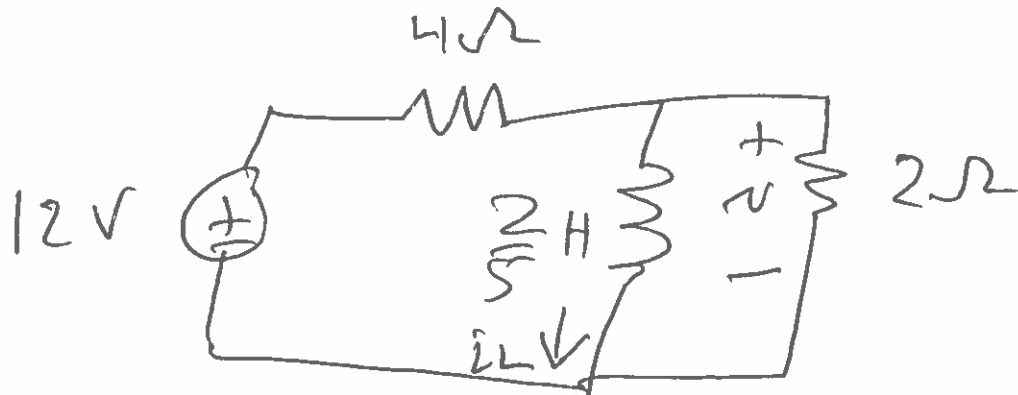

$$i_L(0^-) = \frac{12V}{4\Omega} = 3A$$

after $t = 0$

Circuit looks like

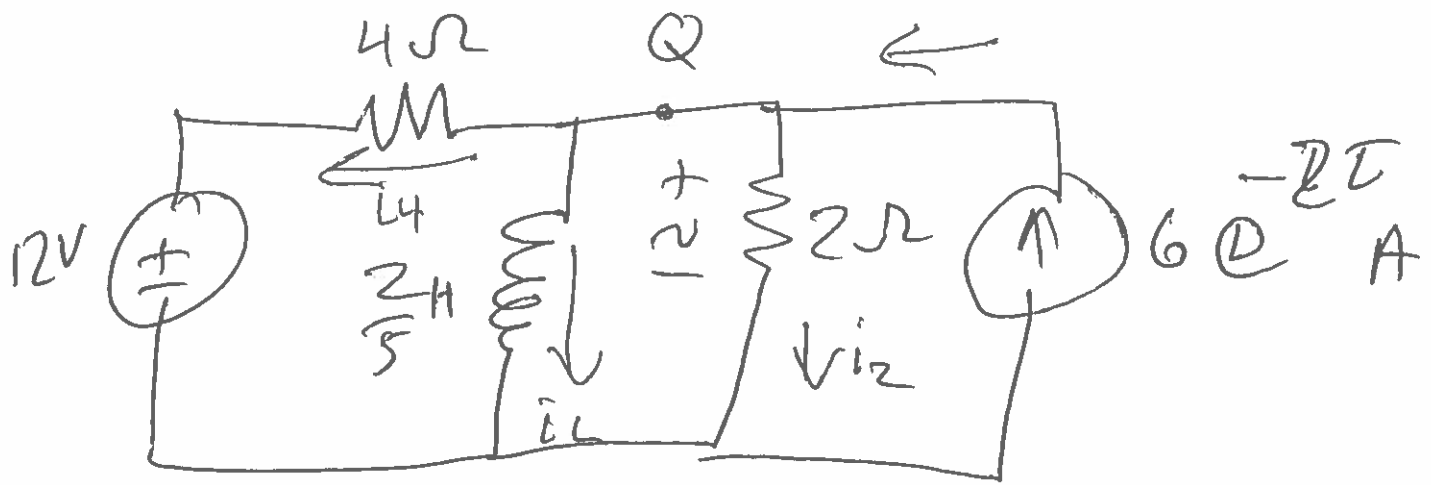

$$i_4 = \frac{V - 12V}{4\Omega} \quad i_2 = \frac{V}{2\Omega}$$

CURRENT AT
Q

$$6e^{-2t} - i_2 - i_4 - i_L = 0$$

$$6e^{-2t} - \frac{V}{2\Omega} - \frac{V - 12V}{4\Omega} - i_L = 0$$

$$V = L \frac{di_L}{dt}$$

$$6e^{-2t} - \frac{L}{2\Omega} \frac{di_L}{dt} - \frac{L}{4\Omega} \frac{di_L}{dt} + 3 - i_L = 0$$

$$6e^{-2t} - \frac{2/5}{2\Omega} \frac{di_L}{dt} - \frac{2/5}{4\Omega} \frac{di_L}{dt} + 3 - i_L = 0$$

$$\frac{2}{10} \frac{di_L}{dt} + \frac{L}{10} \frac{di_L}{dt} + i_L = 6e^{-2t} + 3$$

$$\frac{di_L}{dt} + \frac{10}{3} i_L = 20e^{-2t} + 10$$

$$i_N = A e^{-(10/3)t}$$

$$i_F = B + C e^{-2t}$$

$$i_L = A e^{-(10/3)t} + B + C e^{-2t}$$

$$\frac{di_L}{dt} = -\frac{10}{3} A e^{-(10/3)t} - 2C e^{-2t}$$

$$i(t) = -15 e^{-(10/3)t} + 3 + 15 e^{-2t}$$
