


$$V_{R_L} = ? = V_{Tcr}$$

$$i = \frac{V_{TOT}}{R_{TOT}} = \frac{10\text{V}}{10\Omega + 40\Omega} = \frac{10\text{V}}{50\Omega}$$

$$i = 0.20\text{A}$$

$$V_{Tcr} = \mathcal{E} - i r_{int} = 10\text{V} - (0.20\text{A})(10\Omega)$$
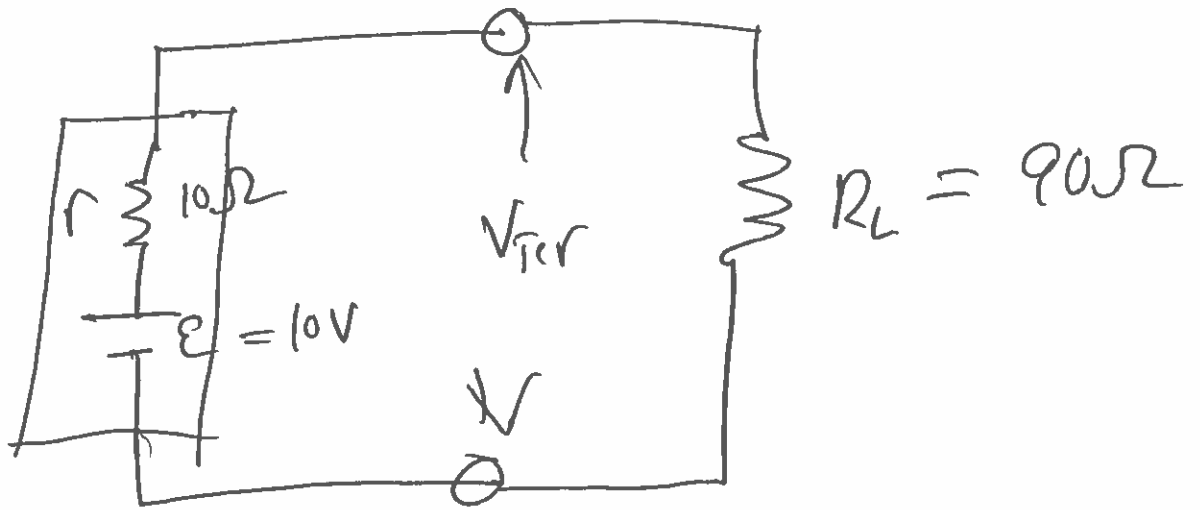
$$V_{Tcr} = 10\text{V} - 2\text{V} = \boxed{8.0\text{V}}$$




$$\hat{i} = \frac{V_{\text{for}}}{R_{\text{for}}} = \frac{10\text{V}}{10\Omega + 90\Omega} = \frac{10\text{V}}{100\Omega}$$

$$\hat{i} = 0,10\text{A}$$

$$V_{ier} = \mathcal{E} - \hat{i}r = 10\text{V} - (0,1\text{A})(10\Omega)$$


$$V_{ier} = 10\text{V} - 1\text{V}$$

$$V_{ier} = 9\text{V}$$

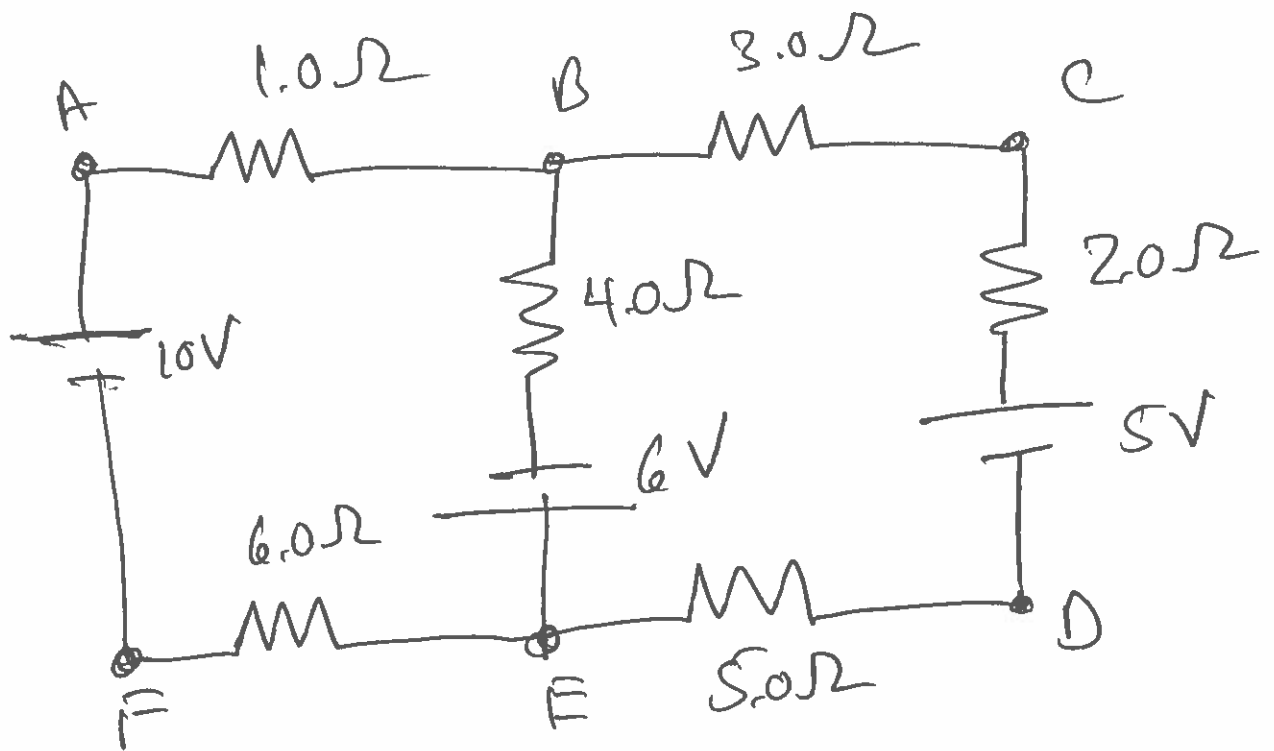

To solve this circuit use
Kirchhoff's Laws of circuits

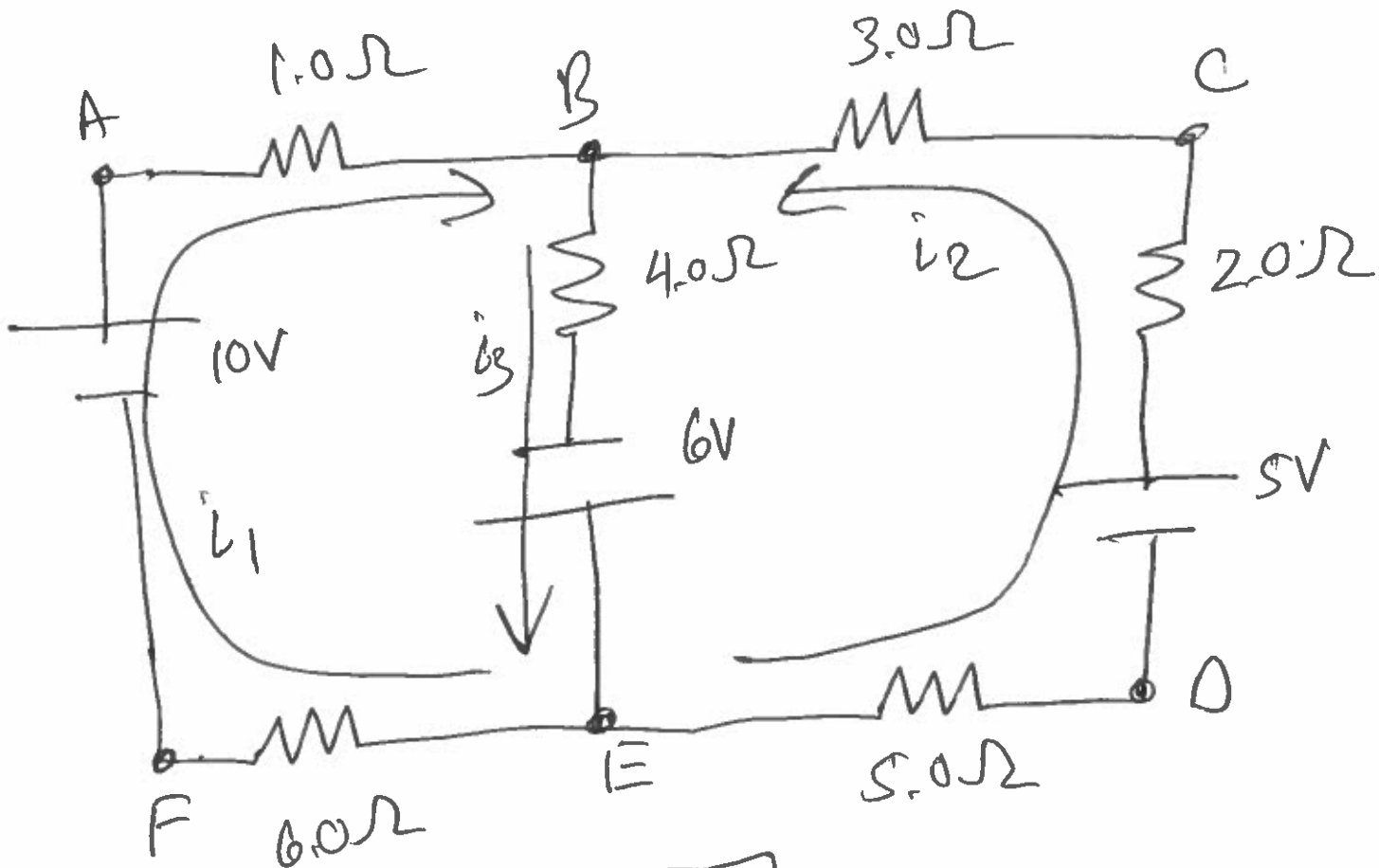- 1) Junction Rule \Rightarrow The amount of current going into a point of a circuit must equal the amount of current leaving the point. (conservation of charge).
- 2) Loop Rule \Rightarrow The sum of the voltages around a closed loop must equal zero. (conservation of energy).



Q.T (B) $i_1 + i_2 = i_3$

Current through a resistor goes from + to - potential \Rightarrow going through a resistor in same direction as current flow is a drop in potential $\Rightarrow -iR$

going through a resistor in the opposite direction as the current flow is a rise in potential $\Rightarrow +iR$

START POINT E go to left clockwise

$$-i_1(6.0\Omega) + 10V - i_1(1.0\Omega) - i_3(4.0\Omega) + 6V = 0$$

START POINT E go to right counter clockwise

$$-i_2(5.0\Omega) + 5V - i_2(2.0\Omega) - i_2(3.0\Omega) - i_3(4.0\Omega) + 6V = 0$$

3 currents i_1, i_2, i_3

3 eqns $i_1 + i_2 = i_3$

$$i_1(6\Omega + 1.0\Omega) + i_3(4\Omega) = 16V$$

$$i_2(5\Omega + 2\Omega + 3\Omega) + i_3(4\Omega) = 11V$$

$$i_1 = 1.31A$$

$$i_2 = 0.41A$$

$$i_3 = 1.72A$$

What is $\Delta V_{E \rightarrow B}$?


$$\Delta V_{E \rightarrow B} = V_B - V_E =$$

$E \rightarrow F - A \rightarrow B$

$$\begin{aligned}\Delta V_{E \rightarrow B} &= -i_1(6\Omega) + 10V - i_1(1\Omega) \\ &= 10V - i_1(7\Omega) \\ &= 10V - 1.31A(7\Omega) = +0.83V\end{aligned}$$

$E \rightarrow B$
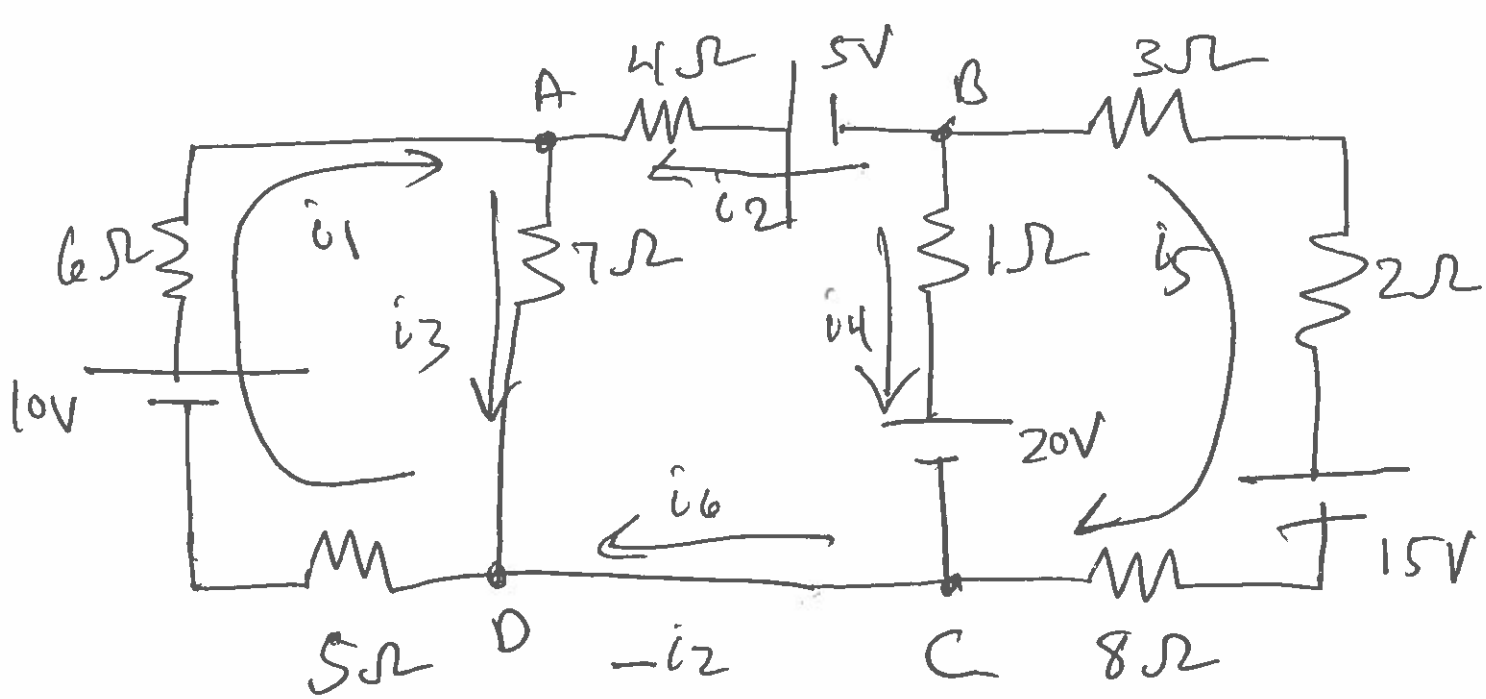
$$\begin{aligned}\Delta V_{E \rightarrow B} &= -6V + i_3(4\Omega) \\ &= -6V + (1.72A)(4\Omega) \\ &= +0.88V\end{aligned}$$



AT (A)

$$i_1 + i_2 = i_3$$

or (B)

$$0 = i_2 + i_4 + i_5$$

or (C)

$$i_2 + i_4 + i_5 = i_6$$

or (D)

$$i_3 + i_6 = i_1$$

$$i_6 = -i_2$$

Left Loop start D clockwise

$$-i_1 5\Omega + 10V - i_1 6\Omega - i_3 7\Omega = 0$$